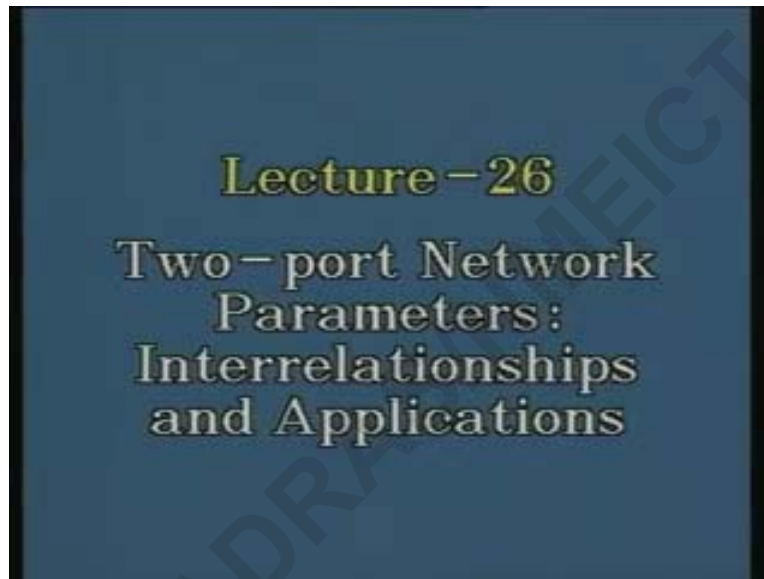


Circuit TheoryProf. S.C. Dutta RoyDepartment of Electrical EngineeringIIT DelhiLecture 26

Two-port Network Parameters: Interrelationships and Applications

(Refer Slide Time: 00:00:52 min)




this is the twenty sixth lecture and we are continuing our discussion on two port network parameters

today's topic would be interrelationships and applications of two port parameters

before i take the interrelationships we would like to work out a couple of examples on ABCD parameters and one of them is the ideal transformer

(Refer Slide Time: 00:01:25 min)

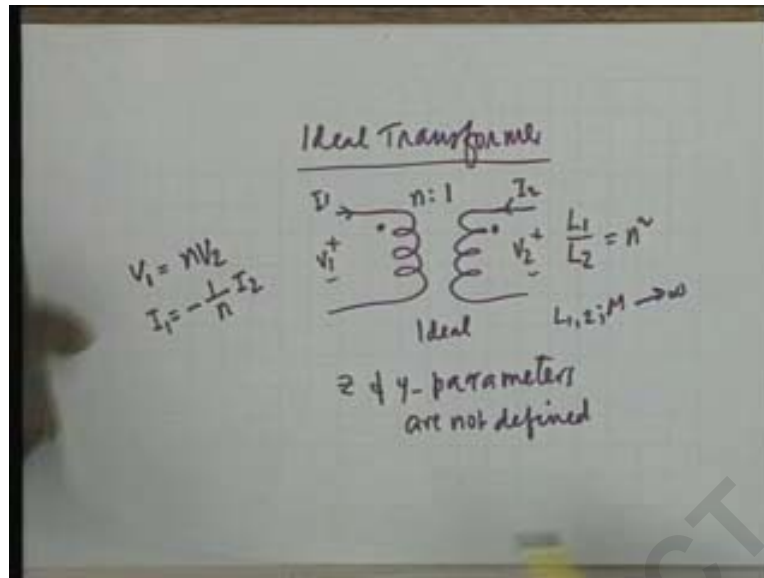

as i have already discussed an ideal transformer has primary as well as secondary inductances going to infinity

the mutual inductance also goes to infinity but the ratio of the two inductances is finite and this ratio in terms of trans ratio is equal to what L_1 by L_2

do you know the relation between inductance and number of turns inductance is proportional to

$(\)$ (00:02:07) $(\)$

square so this is equal to n^2 square of the number of turns okay

that is why the ratio is finite because the ratio the number of turns is finite

and in addition we indicate the dots and we write the word ideal here okay in addition to inductance is being infinite the coefficient of coupling has to be one exactly one

if the inductances are finite and the coefficient of coupling is one we call it a perfect transformer a perfect transformer becomes ideal if L_1 , L_2 and M all go to infinity in such a manner that the ratio of L_1 to L_2 is finite okay

now as i have already pointed out an ideal transformer does not have impedance or admittance matrices impedance and admittance matrices cannot be defined for an ideal transformer because Z_{11} is infinity so is Y_{11} okay

Z_{22} of course Z_{22} also yes correct and therefore Z and Y parameters are not defined

[Noise] are not defined

now if i take the voltage current relationships you will see that port h parameters and ABCD parameters can be defined

the voltage current relationships are that V_1 is equal to n times V_2 and I_1 is equal to minus one over n I_2 this is the relationship

(Refer Slide Time: 00:03:56 min)

Handwritten equations on a whiteboard:

$$V_1 = nV_2 = AV_2 - BI_2$$

$$I_1 = -\frac{1}{n}I_2 = CV_2 - DI_2$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} n & 0 \\ 0 & \frac{1}{n} \end{bmatrix}$$

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$[h] = \begin{bmatrix} 0 & n \\ -n & 0 \end{bmatrix}$$

now [Noise] let me write it down again V_1 equals to n V_2 and I_1 is equal to minus one over n I_2 from which the ABCD parameters are obvious

you see for ABCD V_1 is to be identified with AV_2 minus BI_2 and I_1 is to be identified with CV_2 minus DI_2 agreed

this is the definition of ABCD parameters and therefore for the ideal transformer the ABCD matrix is simply if you compare this with this you see [Noise] that A is simply equal to n B is zero C is zero and D is

<a_side> one over n <a_side>

one over n and you also notice that AB minus CD is equal to one

this has to be obeyed because the ideal transformer is a reciprocal device all right

if i want the h parameters okay the definition of h parameters are that V_1 is $h_{11}I_1$ plus $h_{12}I_2$

<a_side> V_2 <a_side>

V_2 agreed h_{12} V_2 and I_2 the other current is equal to h_{21} I_1 plus h_{22} V_2

so can you tell me what is the h matrix now h matrix if you compare these relationship with this you see V_1 h_{11} one would be zero h_{11} one is zero h_{12} would be equal to n agreed h_{21} h_{21} one

<a_side> minus n <a_side>


minus n and h_{22} would be

<a_side> zero <a_side>

zero and you notice that h_{12} is indeed equal to minus h_{21} which is the condition for reciprocity

so if you write the voltage current relationship at the port if you are able to do that a parameter should be obvious and for an ideal transformer the only way to describe it is either an h matrix or an ABCD matrix transmission matrix z and y parameters do not exist

(Refer Slide Time: 00:06:20 min)

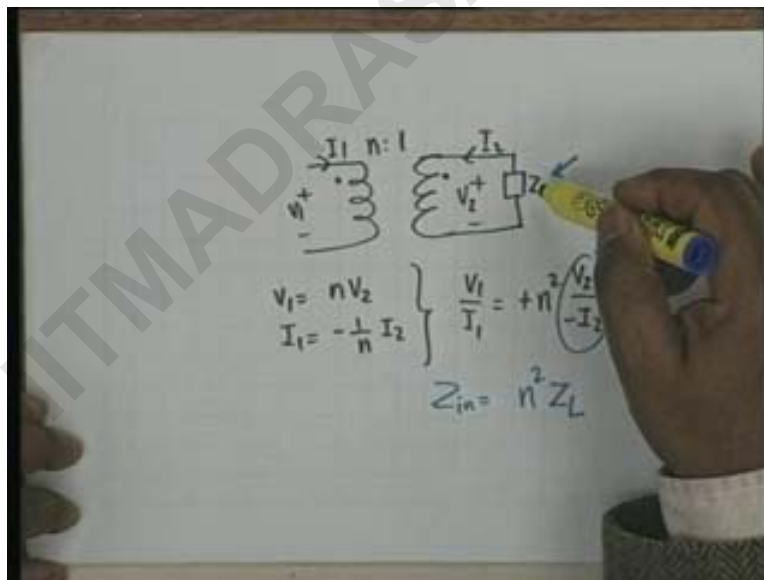

now take an ideal transformer [Noise] and understand why it is called a transformer if i have an impedance Z_L here the voltages are V_1 I_1 V_2 I_2 if it is terminated in Z_L and the ratio is n is to one these are the dots then V_1 is equal to $n V_2$ I_1 is equal to minus one over n I_2 and therefore the input impedance V_1 by I_1 is simply equal to minus n squared V_2 by I_2


now if i transfer this minus sign here then obviously V_2 by minus I_2 is equal to z_L and therefore input impedance z_{in} is equal to $n^2 z_L$ [Noise] and this is Y it is called a transformer not only transforms voltages and currents V_2 is one by n times V_1 current I_2 is equal to minus n times I_1 it transforms voltages and current it also transforms the impedance

the secondary impedance z_L is transformed into $n^2 z_L$ when referred to the primary

for example if this is an inductance then if it is the inductance L then the effective inductance looking at the primary shall be $n^2 L$

if this is a capacitance C then the effective capacitance looked at from the primary would be C divided by n^2 if it's a resistance R then it would be $n^2 R$ this is the property of a transform [Noise]

(Refer Slide Time: 00:08:14 min)

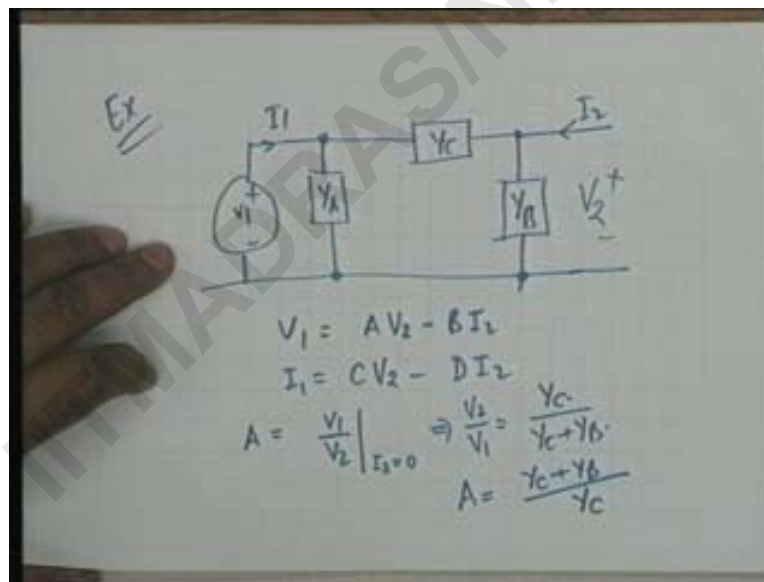

the other example that i take for ABCD parameters is i don't know if i have done this the pi network have i done this ABCD parameters or did i derive the h parameters h we derived

let's derive the ABCD parameters [Noise] V_1 I_1 V_2 I_2 we wish to derive the ABCD parameters our relationships is V_1 equal to AV_2 minus BI_2 and I_1 is equal to CV_2 minus DI_2 all right


A is equal to V_1 by V_2 under the condition I_2 equals to zero and therefore what i do is i keep this open connect a source here connect a source here this is a constraint because I_2 equal to zero i connect connect a source here all right this i have explained already

so what you have to find out is V_2 by V_1 and then find the reciprocal of this so under this condition V_2 by V_1 V_2 by V_1 would be a potential division YA is ineffective potential division between YC and YB and you can easily show that this is YC divided by YC plus YB okay

in terms of impedances it is Z_B divided by Z_B plus Z_C in terms of admittances it is YC divided by YC plus YB and therefore A is equal to YC plus YB divided by YC is that okay

this is the value of A [Noise]

(Refer Slide Time: 00:10:13 min)

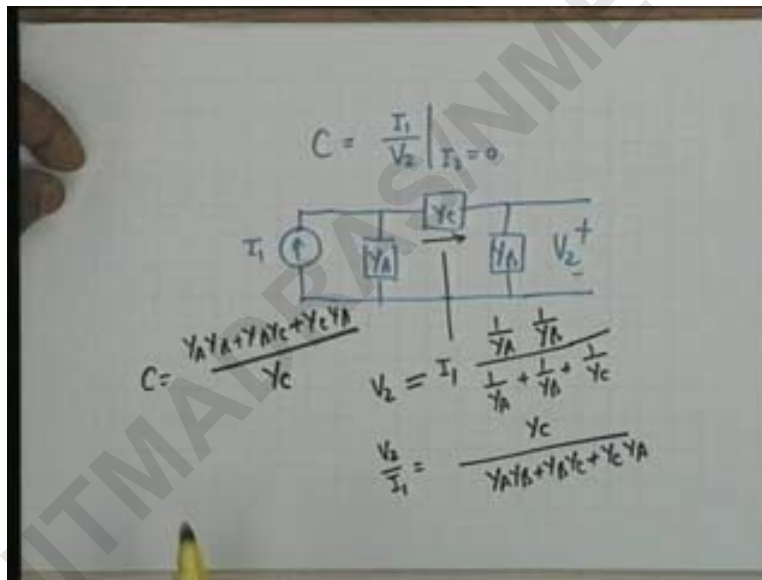

to find the parameter B well i can find another parameter from the same network you notice that C is equal to I_1 divided by V_2 with I_2 equal to zero [Noise] so i can find out C by connecting a current source I_1 to the network YA YC YB and then finding out the voltage here with I_2 equal to zero this is open circuited


now[Noise] this can be very simply solved this current this current is equal to I_1 multiplied by one by YA divided by one by YA plus one by YB plus one by YC is that okay

this is this current current division between YA and YB in series with YC and the voltage V_2 [Noise] the voltage V_2 then shall be equal to this current multiplied by one over YB and

therefore V_2 by I_1 is equal to V_2 by I_1 is equal to Y_C divided by $Y_A Y_B$ plus Y_B
 Y_C plus $Y_C Y_A$ is that okay

are the steps all right i have done it by inspection and therefore C which is the reciprocal of this
 C would be equal to $Y_A Y_B$ plus $Y_B Y_C$ plus $Y_C Y_A$ divided by Y_C this is the z parameter
 to find the B and D parameters B and D parameters we have to make V_2 equal to zero
 [Noise]

(Refer Slide Time: 00:12:16 min)

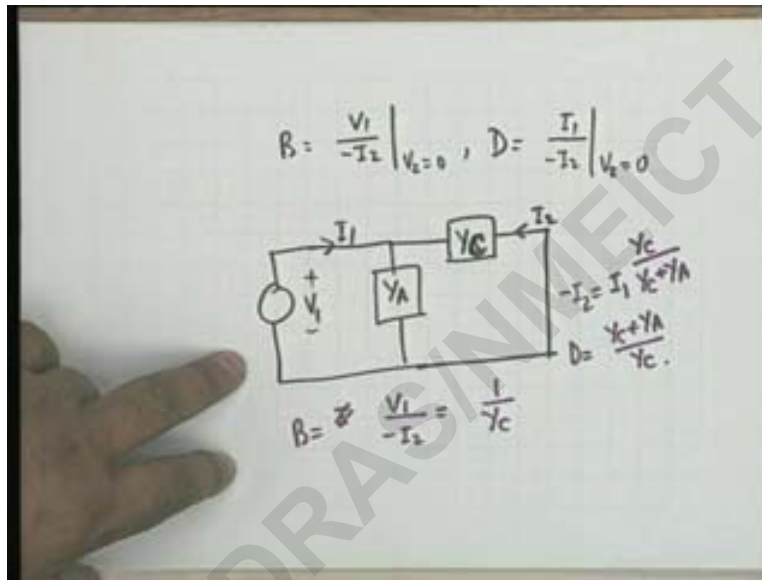

if you recall B is equal to V_1 by minus I_2 with V_2 equal to zero and D is equal to I_1
 by minus I_2 with V_2 equal to zero this is the definition [Noise] and therefore i make V_2
 equal to zero which means that Y_B goes out of the picture

so we have a Y_A i don't care what this source is obviously we require two sources we require
 voltage source and the current source or a current sources i don't care what the sources is all i
 know is this voltage is V_1 and this current is I_1

then you have an Y_B and it is short circuited Y_C short circuited so this current must be I_2 all
 right

the first thing to find out is V_1 by minus I_2 which is obviously

<a_side> that should be Y_C on the top <a_side>

on the top it is Y_C correct [Noise] this is Y_C okay

so what is ah V_1 V_1 by minus I_2 obviously this is equal to one over Y_C

are the signs all right

V one appears across YC the sign I two opposes V one and therefore the negative sign is taken care of and this must therefore be B

as far as D is concerned D is I one divided by minus I two now [Noise] minus I two is obviously equal to I one times yes YC divided by

<a_side> (()) (00:14:20) <a_side>

isn't that equal to this

<a_side> yes <a_side>

okay i just skipped one step and therefore D is equal to I one by minus I two so it is YC plus YA divided by YC all right i have found out all the parameters

let me let me write them down

(Refer Slide Time: 00:14:51 min)

Handwritten equations on a whiteboard:

$$A = \frac{Y_c + Y_B}{Y_c}$$

$$B = \frac{1}{Y_c}$$

$$C = \frac{Y_A Y_B + Y_B Y_c + Y_c Y_A}{Y_c}$$

$$D = \frac{Y_c + Y_A}{Y_c}$$

The identity $AD - BC = 1$ is circled.

A B C D D is equal to YC plus YA divided by YC [Noise] B is equal to one over YC then C is equal to YA YB plus YB YC plus YC YA divided by YC and A is equal to YC plus YB divided by YC

and you can see that AD oh i am sorry yeah AD minus BC is equal to one AD minus BC yeah it's exactly equal to one

<a_side> yes sir <a_side>

[Noise] it has to be there is no other way suppose in a problem with a reciprocal network three of the parameters are given you can find the fourth agreed because you have this relationship AD minus BC is equal to one all right [Noise] we next go to the relationships between the parameters
(Refer Slide Time: 00:16:22 min)

Interrelationships

$$z \quad \& \quad y$$

$$[Z] = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \quad [Y] = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

$$[V] = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad [I] = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[V] = [Z][I] \quad (1)$$

$$[I] = [Y][V] \quad (2)$$

interrelationships the most commonly used parameters are z and y and therefore we start with z and y and we write this matrix Z matrix as z one one [Noise] z one two z two one and z two two and the Y matrix as y one one y one two y two one y two two

the defining relations are [Noise] that the voltage vector V one V two

yeah pardon me

would you please say loud [Laughter]

<a_side> (()) (00:17:09) <a_side>

okay sure all right

the V matrix which is V one V two and the I matrix is I one I two these are vectors this is a column vector this is a column vector [Noise] and if you recall the defining relation is that V equal to $Z I$ okay

the two equations that we wrote can be expressed in this form V one equal to z one one I one plus z one two I two and V two is equals to z two one I one plus V two two I two

the other equation is that I equals to Y matrix multiplied by the V vector all right if i substitute equation two in equation one two in one okay what do i get [Noise]

(Refer Slide Time: 00:18:16 min)

The image shows a whiteboard with the following handwritten equations and annotations:

$$[V] = [Z] [Y] [V]$$

$$[V] = [Z] [I] = [Z] [Y] [V]$$

Arrows point from the $[I]$ in the second equation to the $[Y]$ in the first equation, and from the $[V]$ in the second equation to the $[V]$ in the first equation.

$$[Z][Y] = [U]$$

$$[Z] = [Y]^{-1}$$

$$[Y] = [Z]^{-1}$$

Annotations include $\Delta_Y \neq 0$ pointing to the $[Y]^{-1}$ term and $\Delta_Z \neq 0$ pointing to the $[Z]^{-1}$ term.

i get V equal to z instead of I i write YV okay this [Noise] is this clear how i wrote this would i repeat okay

what i have is V equal to Z I okay and I is Y matrix multiplied by V that's what i wrote here and therefore this matrix is the same as this matrix the pre-multiplying matrix must be an identity matrix

therefore Z Y [Noise] must be the identity matrix U of dimension two by two this is two by two this is two by two so multiplication of two by two by two by two which gives two by two what is the definition of the identity matrix

<a_side> (()) (00:19:24) <a_side>

diagonal elements are one off diagonals are zero okay and similarly Y matrix must be the inverse of the Z matrix this is the interrelationships between Z and Y matrices provided the inverse exists and the condition for that is that Δ_Y the determinant of the Y matrix must not be equal to zero and the condition for this is that the determinant of the z matrix must not be equal to zero okay and if i look at if i look at the expanded version of this inverse relationships

(Refer Slide Time: 00:20:07 min)

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}^{-1}$$

$$z_{11} = \frac{y_{22}}{\Delta_Y}, \quad z_{22} = \frac{y_{11}}{\Delta_Y}$$

$$z_{12} = \frac{-y_{12}}{\Delta_Y}, \quad z_{21} = \frac{-y_{21}}{\Delta_Y}$$

$$y_{11} = \frac{z_{22}}{\Delta_Z}, \quad y_{12} = \frac{-z_{21}}{\Delta_Z}$$

$$y_{21} = \frac{-z_{12}}{\Delta_Z}, \quad y_{22} = \frac{z_{11}}{\Delta_Z}$$

that is z one one z one two z two one z two two is equal to the inverse of y matrix if i look at this it's a two by two matrix very simple i can write down the relationships immediately z one one shall be equal to y two two divided by del y z two two shall be equal to y one one divided by del y

z one two shall be equal to

<a_side> (()) (00:20:43) <a_side>

minus y two one or one two one two there is a transposition one two by del y one must remember this one two

<a_side> (()) (00:20:58) <a_side>

now it is not two one there is a transposition after taking del one two by del there is a transposition and z two one is equal to minus y two one divided by del y

we are lucky that [Laughter] this do not interchange it's easy to remember okay all right

in a similar manner if you look at the inverse relationship obviously you can write [Noise] y one one is equal to s z two two by del z y two two is equal z one one by del z y one two is equal to z one two by del z not quite

<a_side> minus sign <a_side>

minus sign and Y two one is equal minus z two one divided by del C where del stands for the determinant of the particular matrix for example del y is equal to y one one y two two {multi} (00:22:05) minus y one two y two one okay

now what we have said about [Noise] conversion of z to y or y to z the other two matrices that is the h and the ABCD obviously they don't obey inverse relationships because the variables are different the independent set of parameters is different so one has to work out from ABCD from the from no what is it called ab initio ab initio

ab initio means going back to the roots for example i will take only one example suppose i want to convert

(Refer Slide Time: 00:22:48 min)

The image shows a whiteboard with handwritten mathematical derivations. At the top, it says 'h → ABCD'. Below this, the h-parameter equations are written: $V_1 = h_{11}I_1 + h_{12}V_2$ and $I_2 = h_{21}I_1 + h_{22}V_2$. To the right, the ABCD parameter equations are written: $V_1 = AV_2 - BI_2$ and $I_1 = CV_2 - DI_2$. A red arrow points from the h-parameter equation for V_1 to the ABCD equation for V_1 . Another red arrow points from the h-parameter equation for I_2 to the ABCD equation for I_1 . The derivation for I_1 is shown as $I_1 = \frac{I_2 - h_{22}V_2}{h_{21}}$. The values for C and D are given as $C = -\frac{h_{22}}{h_{21}}$ and $D = -\frac{1}{h_{21}}$. Finally, the expression for V_1 in terms of I_2 and V_2 is circled in red: $V_1 = \frac{h_{11}}{h_{21}}(I_2 - h_{22}V_2) + h_{12}V_2$.

the h parameters to the ABCD parameters suppose i want to convert this then what i do is i write both the relationship that is i write V one h parameter relates V one I two to V one I two to I one V two

so h one one I one plus h one two V two and I two equal to h two one I one [Noise] plus h two two V two and i also write the ABCD parameters V one I one at the dependent variables and this is AV two minus BI two one must remember this and I one equal to CV two minus D I two all right

so what we have to do is express V one in terms of V two and I two in other words i have to eliminate I one from here and this is easily found from here I one is I two minus h two two V two divided by h two one which incidentally also gives me C and D if you compare these two don't you see that I one has been expressed in terms of I two and V two

so what is C

h_{12} minus h_{22} divided by h_{21} and what is D

h_{12} minus h_{22} divided by h_{21} and what is D

h_{11} minus h_{22} by h_{21}

there is a minus sign because there is a minus sign here all right okay

now if i substitute this if i substitute this relation in the first one then i get V_1 equals to $h_{11} I_1$ plus $h_{12} V_2$ minus $h_{21} I_2$ minus $h_{22} V_2$ okay this is the first term $h_{11} I_1$ plus $h_{12} V_2$

and if i look at this relationship and this one if i compare these two then i get the following equations for A and B

(Refer Slide Time: 00:25:13 min)

The image shows a whiteboard with handwritten equations for A, B, C, and D. A large watermark 'IITMADRAS IN MEICT' is overlaid diagonally across the board.

$$A = h_{12} - \frac{h_{11}h_{22}}{h_{21}} = \frac{-\Delta h}{h_{21}}$$

$$B = -\frac{h_{11}}{h_{21}}$$

$$C = -\frac{h_{22}}{h_{21}}$$

$$D = -\frac{1}{h_{21}}$$

A is the coefficient of V_2 that is h_{12} minus $h_{11} h_{22}$ divided by h_{21} okay and B would be equal to minus h_{11} divided by h_{21}

is it a minus sign

yes (()) (00:25:44)

you don't have h_{22} this is a redundant term

is there a minus sign

yes there is

there is okay now let me write C and D also C was ah minus h two two by h two one and D was minus one over h two one okay

it appears that only this term does not come with a minus sign but if you if you simplify this the denominator is minus del h divided by h two one agreed

there is a uniformity all come with a negative sign all of them have a denominator of h two one h two one h two one h two one

the three parameters BCD have a single term in the numerator h one one h two two one whereas A has the total determinant of the h matrix okay

in a similar manner we could go back from ABCD to h or z parameters to h parameters or y parameter to ABCD parameters all them can be done and this exercise at least for some parameters you should perform

this is the table that we get ultimately

(Refer Slide Time: 00:27:07 min)

Matrix Conversion Table
 $\Delta_z = z_{11}z_{22} - z_{12}z_{21}$

	[z]	[y]	[h]	[T]
[z]	$z_{11} \quad z_{12}$ $z_{21} \quad z_{22}$	$\frac{y_{22}}{\Delta_y} \quad -\frac{y_{12}}{\Delta_y}$ $-\frac{y_{21}}{\Delta_y} \quad \frac{y_{11}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}} \quad \frac{h_{12}}{h_{22}}$ $-\frac{h_{21}}{h_{22}} \quad \frac{1}{h_{22}}$	$\frac{A}{C} \quad \frac{\Delta_T}{C}$ $\frac{1}{C} \quad \frac{D}{C}$
[y]	$\frac{z_{22}}{\Delta_z} \quad -\frac{z_{12}}{\Delta_z}$ $-\frac{z_{21}}{\Delta_z} \quad \frac{z_{11}}{\Delta_z}$	$y_{11} \quad y_{12}$ $y_{21} \quad y_{22}$	$\frac{1}{h_{11}} \quad -\frac{h_{12}}{h_{11}}$ $\frac{h_{21}}{h_{11}} \quad \frac{\Delta_h}{h_{11}}$	$\frac{D}{B} \quad -\frac{\Delta_T}{B}$ $-\frac{1}{B} \quad \frac{A}{B}$
[h]	$\frac{\Delta_z}{z_{22}} \quad \frac{z_{12}}{z_{22}}$ $-\frac{z_{21}}{z_{22}} \quad \frac{1}{z_{22}}$	$\frac{1}{y_{11}} \quad -\frac{y_{12}}{y_{11}}$ $\frac{y_{21}}{y_{11}} \quad \frac{\Delta_y}{y_{11}}$	$h_{11} \quad h_{12}$ $h_{21} \quad h_{22}$	$\frac{B}{D} \quad \frac{\Delta_T}{D}$ $-\frac{1}{D} \quad \frac{C}{D}$
[T]	$\frac{z_{11}}{z_{21}} \quad \frac{\Delta_z}{z_{21}}$ $\frac{1}{z_{21}} \quad \frac{z_{12}}{z_{21}}$	$-\frac{y_{22}}{y_{21}} \quad -\frac{1}{y_{21}}$ $-\frac{\Delta_y}{y_{21}} \quad -\frac{y_{12}}{y_{21}}$	$-\frac{\Delta_h}{h_{21}} \quad -\frac{h_{12}}{h_{21}}$ $-\frac{h_{21}}{h_{21}} \quad -\frac{1}{h_{21}}$	$A \quad B$ $C \quad D$

this is the complete table where it does not assume that the network is reciprocal it is a general table and you should keep a copy of this ready with you in working out problems on problems in network theory because you never know where you shall require a conversion this incorporates T to pi and pi to T T to pi means z parameters to y parameters and pi to T is y to z parameters you see for example the table is read like this the z matrix and the z matrix so this is this gives the matrix z matrix

is this visible on the monitor

<a_side> no <a_side>

okay no what is the problem oh okay you tell me to the shift is that okay now okay

z parameters z and z that is the one one is simply matrix {is} (00:28:10)

if you go from z if you wish to derive z from y okay the row is all z parameters and the column is in terms of those parameters if you want to find z from y parameters then you use this relation that is $z_{11} = y_{11}^{-1}$ $z_{12} = -y_{12}^{-1} y_{22}^{-1}$ as we have done already

or let's say you want to find out z parameters from ABCD parameters then $z_{11} = \frac{A}{C}$ $z_{12} = \frac{AD - BC}{C}$ which is equal to one for reciprocal network this is a general table and therefore they have used Δt


similarly $z_{21} = \frac{1}{C}$ and $z_{22} = \frac{D}{C}$ and similarly for all other entries in the table this is a [Noise] very important table and very useful table and I would advise that you keep it ready for reference all right

any question

<a_side> (()) (00:29:23) <a_side>

from the book yeah course book any network theory any respectable network theory book would have this table okay any respectable network theory book but be aware ah some of the books particularly the Indian authors have many miss prints and uh it is better that you take from course book all right [Noise]

(Refer Slide Time: 00:29:50 min)

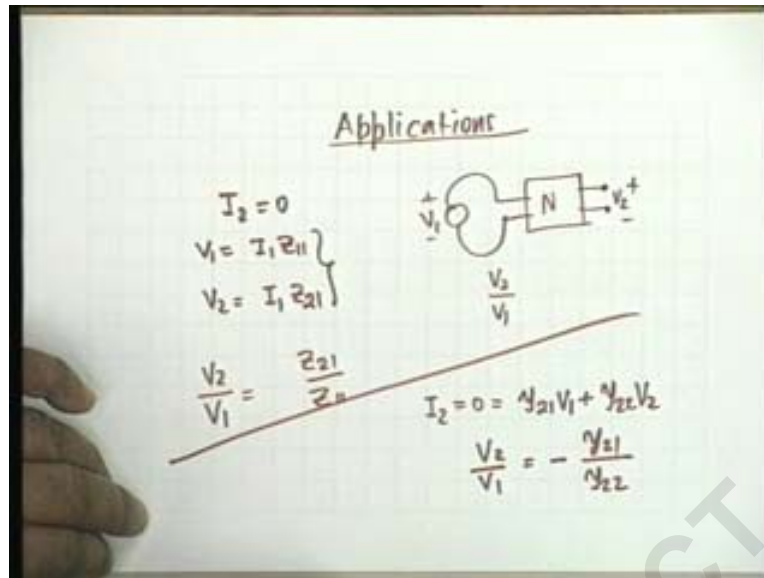

we then have a brief discussion on applications of the two port parameters application of the two port parameters in finding out network functions network functions are driving point and transfer could be impedance could be admittance or in the case of transfer it could be dimensionless

now given a network given a network N and its two port parameters any transfer function can be found out any transfer function and we shall have a graduated series of examples to illustrate the applications

the first one that i have is suppose i connect the voltage source here V one and i want to find out the voltage output voltage V two that is my transfer function is V two by V one all right

the parameters you can use any set of parameters but the condition is that I two equals to zero if I two equals to zero then you know that V one would be equal to i one z one one if i work in terms of the z parameters and V two shall be equal to I one times z two one that is correct because I two equal to zero therefore my V two by V one is simply z two one by z one one

can i explain you see my condition is this is kept open and therefore I two is zero

< a _ side > is it the implied condition < a _ side >

not implied condition there is a given condition given conditions if i connect something here then obviously I two shall not be equal to this but what i want is opens circuit voltage transfer function

if I two is zero then my z parameters give these two relations and therefore i find V two by V one

suppose one is per say i don't know the z parameter i know the y parameter and i don't want to convert fine fine


what i will do is i will write the equation for I_2 I_2 is equal to zero equal to $y_{21} V_1$ plus $y_{22} V_2$ and therefore V_2 by V_1 is equal to minus y_{21} divided by y_{22} all right is that okay

i can find out in terms of z parameters or y parameter and since i know the relationship between z and any other set of parameters what i will require is only to look at the table to be able to convert this for example in terms of A B C D parameters

all that i do is substitute for z_{21} in terms of A B C D substitute for z_{11} in terms of A B C D or else i go back to the roots that is i write the defining equations put I_2 equal to zero and then what ever V_2 by V_1 comes i accept it

is this okay all right this is the first example the simplest one

(Refer Slide Time: 00:33:07 min)

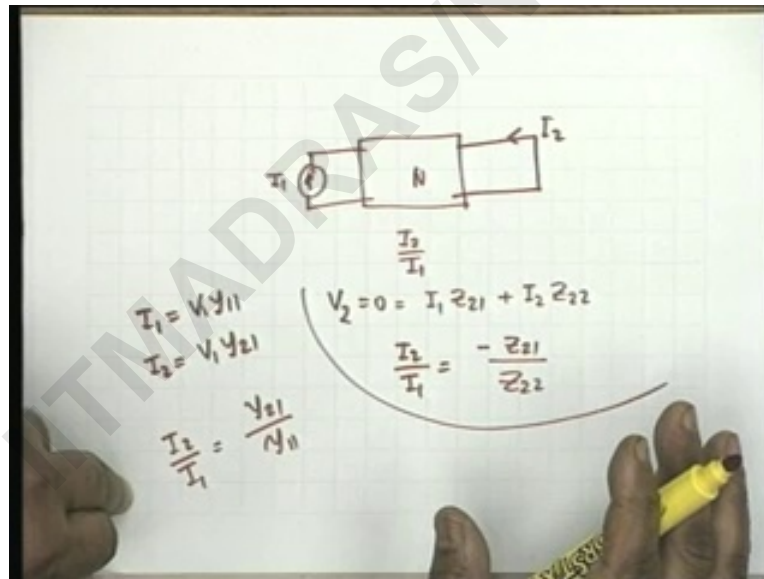


the second example well it's also very simple i have this well situation in which the network N is driven by current generator I_1 the output is short circuited I_2 and what i want to find out is I_2 by I_1 this is my transfer function okay

if i take z parameters let's say then in the second equation V_2 is equal to zero is equal to $I_1 z_{21}$ plus $I_2 z_{22}$ and therefore I_2 by I_1 would be equal to minus z_{21} divided by z_{22} agreed as simple is that from the second equation

or if i want in terms of the y parameters what i will do is i take the two equations I one shall be V_1 one Y_{11} one because V_2 is zero and I_2 is V_1 y two one all right therefore I_2 by V_1 one is equal to y_{21} one divided by y_{11} one no negative sign okay

similarly i can find out from any other set of parameters i will confine my attention to z and y other parameters you can try for your self

(Refer Slide Time: 00:34:45 min)

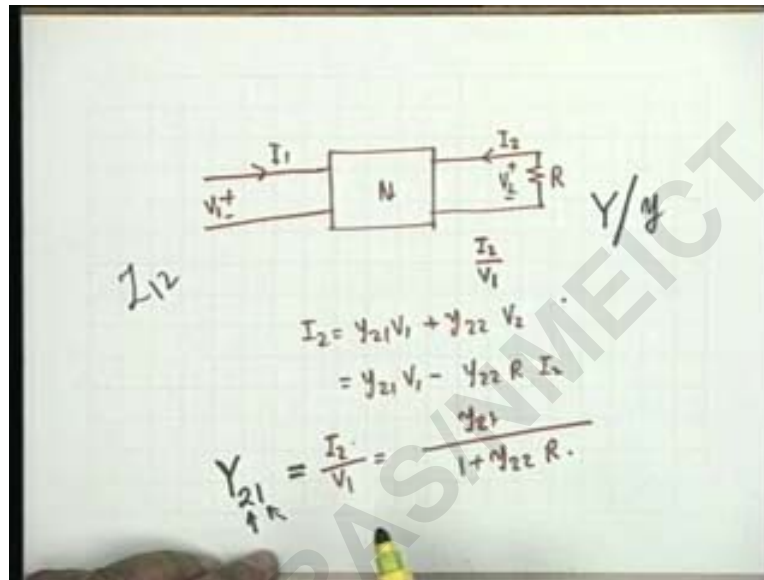

the third example that i take is slightly more involved that is a terminated network i have a network N i can connect either source here but all that matters is V_1 and I_1 and i terminate this by means of resistance let's say R the function of interest is I_2 by V_1 okay if capital R was replaced by a voltage source V_2 then what would have I_2 by V_1 become yeah

< a _ side > (()) (00:35:33) < a _ side >

ah [Noise] what would you like me to try z parameters or y parameters let's find this out then we will will will conclude let's use y parameters

are they easy to use well either of them is easy there is no problem why do i use y parameters

< a _ side > (()) (00:35:54) < a _ side >

minus V_2 by R that's perfectly all right that is what we shall use you see I_2 is $y_{21}V_1$ one i want I_2 by V_1 one I_2 is $y_{21}V_1$ one plus $y_{22}V_2$ but what is V_2

< a _ side > minus $I_2 R$ < a _ side >

so it is minus y_{22} R_{I2} therefore I_2 by V_1 is equal to i can write it down y_{21} one divided by one plus $y_{22} R_{I2}$ all right

now i {waa} (00:36:40) i want to ask you the following question if capital R is zero that is if this is short circuit then what is I_2 by V_1 it is simply small I_2 one that is the definition okay

so a [Noise] now i am introducing a notation you must be careful about this notation when i write a small y it refers to a transfer admittance of the network all right

now I_2 by V_1 is also a transfer admittance I_2 is the current in the load and V_1 is the voltage at port one so I_2 by V_1 is also a transfer admittance how do you distinguish between the two use a capital Y and use the subscripts two one

capital Y_{21} now you must be able to distinguish between capital Y and small y okay make them quite different don't make them look alike because then you might make a mistake

< a _ side > (() (00:37:44) < a _ side >

why you use this okay you see if capital R is zero if this is short circuited then I_2 by V_1 is simply y_{21} (00:37:55) small y_{21} which means the parameter of the network N it has nothing to do with terminations okay

the parameter small y is defined without termination now with termination I_2 by V_1 is still the dimension of an admittance and it is a current at one port to the voltage at the other port so it is a transfer admittance all right

small y_{21} we call it short circuit transfer admittance that is it belongs to the network N whereas under terminated condition to distinguish between small y_{21} the short circuit transfer admittance and the transfer admittance of a terminated network we use the symbol capital Y

the subscripts are still two one two the first subscript refers to the port at which the response is taken okay that is at port two and the second subscript refers to the port at which the excitation is applied this this will be our convention

y_{21} shall be that we are interested in a current at port two due to a voltage at port one similarly if i had written z_{12} this will mean that we are interested in a voltage at port one due to

< a _ side > current at port two < a _ side >

a current at port two is that okay this will be our convention all right and in the context things will be absolutely clear

now suppose suppose you are fussy and you say no i don't want to work with y parameters i want to work with z parameters well all that i have to do is to refer to the table the place y two one by by what

< a _ side > z parameter < a _ side >

what is the z [Laughter] parameter

< a _ side > z one two by del z < a _ side >


plus or minus

< a _ side > sir minus < a _ side >

minus z one two by del z and y two two i shall replace it by z one one by del z and work it out or i can go back to the rules okay i can do that

let's take the next example before taking the next example let me point out one ah [Noise] one of the interesting ah equivalent circuits you see i told you that as per as z parameter is concerned

(Refer Slide Time: 00:40:29 min)

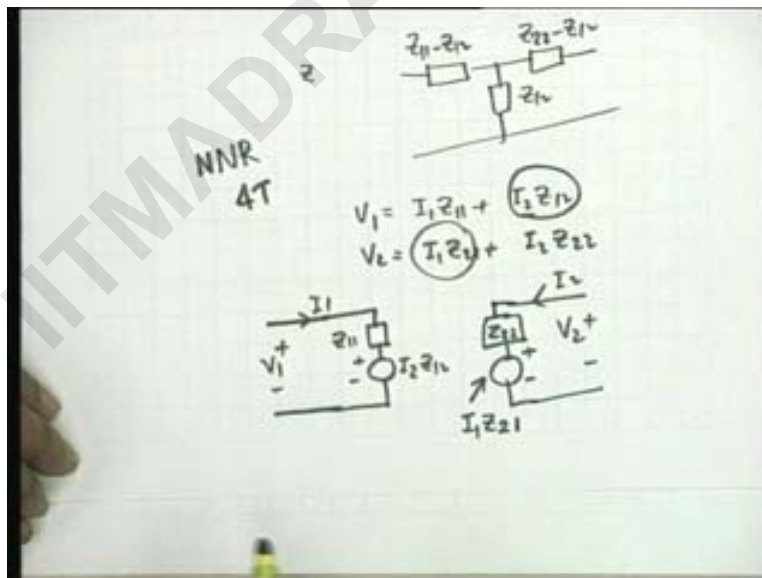

if the network is reciprocal and three terminal then you can replace the network by a T network like this where these parameters are z one one minus z one two z two two minus z one two and z one two

if the original network is reciprocal but not three terminal then this represents only a mathematical equivalent circuit all right not a physical one on the other hand if the network is reciprocal reciprocity is a must

if the network is reciprocal and the three terminal this represents the physical equivalent circuit also [Noise] suppose it's neither

suppose the network is not necessarily reciprocal not necessarily reciprocal that means it can be nonreciprocal also and it is truly four terminal can you draw an equivalent circuit well this is simplicity itself the drawing of the equivalent circuit

if i write $I_1 z_{11} + I_2 z_{12}$ and $V_2 = I_2 z_{22} + I_1 z_{21}$ then it's common sense that this equivalent circuit describes the network

that is you have a z_{11} a current I_1 V_1 so $V_1 = I_1 z_{11} + I_2 z_{21}$ plus a quantity $I_2 z_{12}$ which is the dimension of voltage so i connect a voltage generator here which is $I_2 z_{12}$ obviously is that okay it's very simple $V_1 = I_1 z_{11} + I_2 z_{21}$ plus this voltage source

now obviously this is not an independent voltage source it is a controlled source it is a dependent source the source depends on the current at port number two which is I_2 okay this current determines this voltage so it is a controlled source and by a similar by a similar argument the equivalent circuit at port number two is that we shall have a z_{22} here and another voltage source which would be plus minus and the value would be $I_1 z_{21}$ okay this is the term that we have to use

< a _ side > (()) (00:43:09) < a _ side >

small c

< a _ side > intrinsic < a _ side >


yes the network parameter no termination now is this is this clear

this is a truly four terminal truly four terminal and it does that assume either reciprocity or non reciprocity we have used z_{21} and z_{12} we have not assumed them to be equal and therefore this is a general equivalent circuit

what have we achieved through this equivalent circuit nothing much we have simply represented instead of equations we have represented this by means of a circuit

the circuit contains two controlled sources the two circuits although shown physically isolated from each other are not really isolated why because the coupling comes to the control sources you see this current control space so the two circuits are not decoupled from itself although physically there is no connection but there is a connection through the control of a voltage source by a current source similarly control of this source by the current source so {it } (00:44:24) we have not achieved much we have simply represented the equations by means of an equivalent circuit however sometimes this equivalent circuit is of great help great simplification as we shall show in one or two examples but by a similar token you can represent the y parameters

(Refer Slide Time: 00:44:42 min)

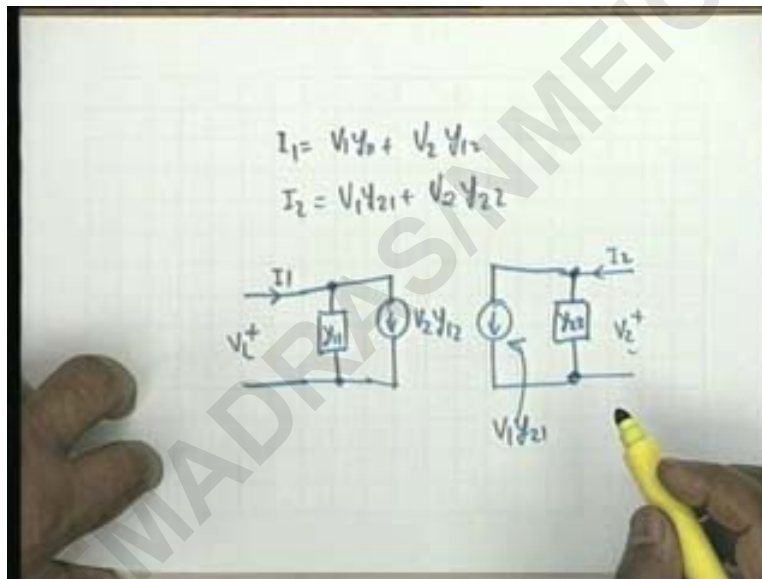

I_1 equal to $V_1 y_{11} + V_2 y_{12}$ and I_2 equal to $V_1 y_{21} + V_2 y_{22}$ you can represent this by a dual circuit that is what you do is $V_1 I_1$ is V_1 times y_{11}


so introduce an admittance y_{11} here okay plus another current and this current would be $V_2 y_{12}$ it is a current source controlled by the voltage at port two okay it's a current source controlled by voltage at port two V_2

in a similar manner for the other port V_2 and I_2 I_2 is $V_2 y_{22}$ so we have an admittance y_{22} here and another current source controlled current source whose value would be $V_1 y_{21}$ all right

this is an exact dual of the z parameter equivalent circuit in the case of z parameter there was a series connection of a voltage source and an impedance now you have a parallel connection of an admittance and a current source okay

as i said you have not achieved much you have only represented two equations by means of a circuit but a circuit a picture is a word one thousand words as we shall see in in a few examples okay

(Refer Slide Time: 00:46:33 min)

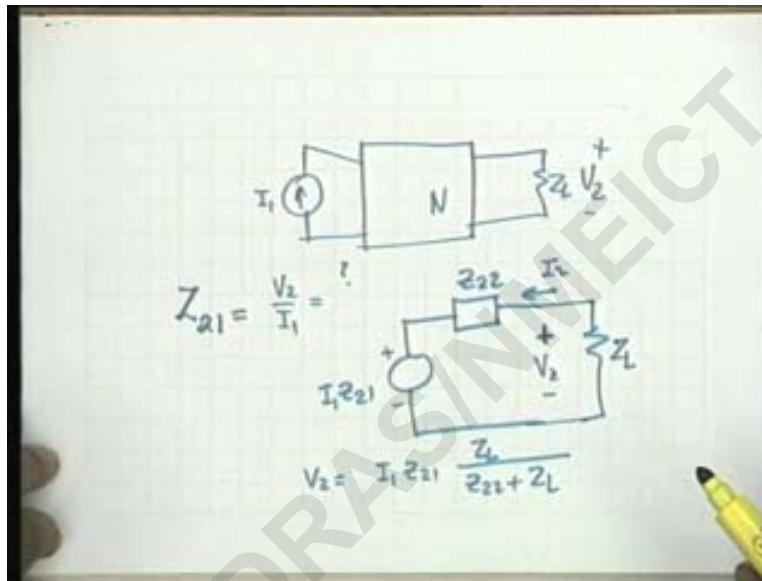

suppose we have a current source one example of application of this suppose we have a current source and network and and the termination Z_L the output voltage is V_2 and what we want is V_2 by I_1 what is it a transfer impedance okay and we should represent it by capital Z

< a _ side > two one < a _ side >

two one that is correct capital Z two one this is what you want

now instead of going into any other any other part if we simply represent if we simply take the z parameter equivalent circuit what was the output equivalent circuit you have a V_2 V_2 you have a series impedance z_{22} this is the current I_2 and a voltage source

what is the value

< a _ side > $I_1 z_{21}$ < a _ side >

$I_1 z_{21}$ agreed and what we have done here i don't have to draw the other part because i don't need it what i need is a relation between V_2 and I_1 I_1 is already here okay

so what i have here is a an impedance let's say z_L and what i have to find out is the ratio V_2 by I_1 obviously V_2 is equal to $I_1 z_{21}$ times z_L divided by $z_{22} + z_L$ is it okay simply a potential division this is the voltage source and there is a potential division between z_{22} and z_L all right and therefore in one stroke of the pen we find out

(Refer Slide Time: 00:48:35 min)

The image shows a whiteboard with handwritten mathematical derivations. The top equation is $Z_{21} = \frac{V_2}{I_1} = \frac{z_{21} z_L}{z_{22} + z_L}$. Below it is $\frac{I_2}{I_1} = -\frac{z_{21}}{z_{22} + z_L}$. At the bottom, there is a correction: $I_2 = -\frac{V_2}{z_L}$. A hand holding a yellow marker is visible at the bottom right of the whiteboard.

the transfer impedance z_{21} as V_2 by I_1 as equal to $z_{21} z_L$ divided by $z_{22} + z_L$

distinguish between small and capital i always cross the middle draw a horizontal line in the middle to indicate small z and don't do it for capital Z okay this is how i differentiate

suppose ah suppose in this example it is not V_2 well suppose the quantity of interest is I_2 that is the current current show this impedance I_2

can i find out the transfer function I_2 by I_1 very simply I_2 is related to V_2

< a _ side > (()) (00:49:28) < a _ side >

no i don't need that V_2 is equal to well I_2 is equal to V_2 divided by z_L with a negative sign agreed so all that i have to do is yeah what did you say

< a _ side > sir $z_{21} z_L$ plus z_{22} by z_L < a _ side >


there is a mistake

< a _ side > (()) (00:49:58) < a _ side >

there is a minus sign all i have to do is to divide this transfer function by minus one by z L all right so z L z L cancels the negative sign this you must not forget all right

the last example

(Refer Slide Time: 00:50:18 min)

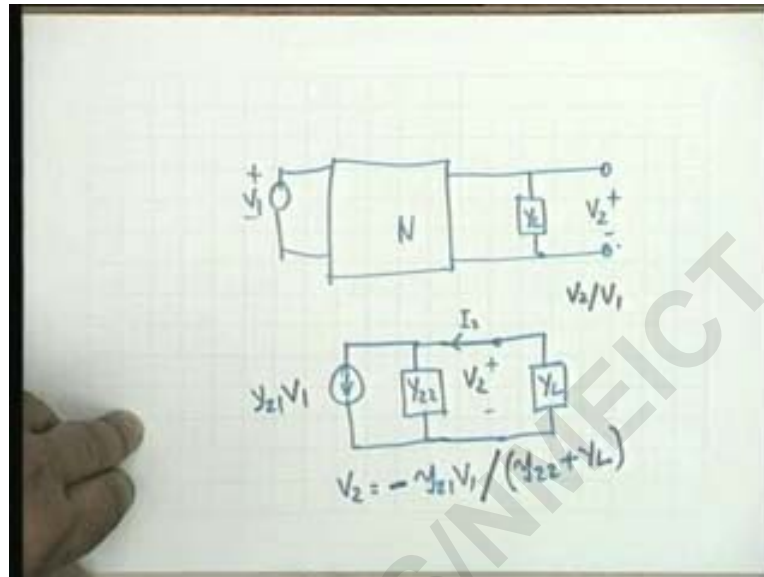

we have a voltage source V_1 one the network N and an admittance y_L our quantity of interest is V_2 and i what i want to find out is V_2 by V_1

now in this situation also the y parameter equivalent circuit the four terminal comes into help if you recall from the load end from port number two what i have is an admittance y_{22} and a current source

how much $y_{21}V_1$

<a_side> I_1 V_1 <a_side>

V_1 so i don't have to draw the other part at all all i do is connect a y_L here okay


so ah V_2 is obviously equal to V_2 is the drop due to a current $y_{21}V_1$ flowing into a parallel combination of y_{22} and y_L agreed

this is a current source which flows to this parallel combination to produce a drop of V_2 so V_2 is $y_{21}V_1$ current multiplied by impedance yeah there is a minus sign here minus sign because V_2 and y_{21} and V_1 they don't agree

therefore minus $y_{21}V_1$ divided by $y_{22} + y_L$ agreed

let me write it down again

(Refer Slide Time: 00:52:21 min)

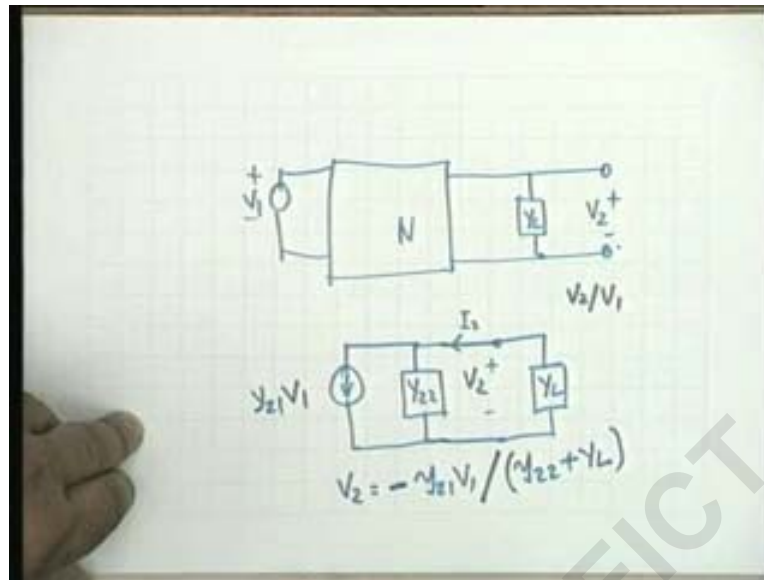

V_2 by V_1 is equal to minus y_{21} divided by $y_{22} + Y_L$ and what was the situation N there is a V_1 here and there is a Y_L here this is V_2

now I want to recall I want you to recall that if Y_L was equal to zero if Y_L was equal to zero which means that the termination is open circuit

then the transfer function open circuit voltage transfer function was precisely this was derived earlier minus y_{21} by y_{22} which checks all right it checks

the question that I leave you is that is there a preferred method of solution

given a problem is there a preferred method which parameters to use which equivalent circuit to use and so on is there a preferred method

my answer is no and yes [Laughter] what does it mean

there is a preferred method which comes there is no prescription

you can't say if this this this are to be found out and this this are given you follow z parameter no there is no prescription it comes by experience

that means you solve more and more problem then given a problem it will be obvious to you which parameter should we use all right

next occasion we shall take more examples and then go about to interrelations