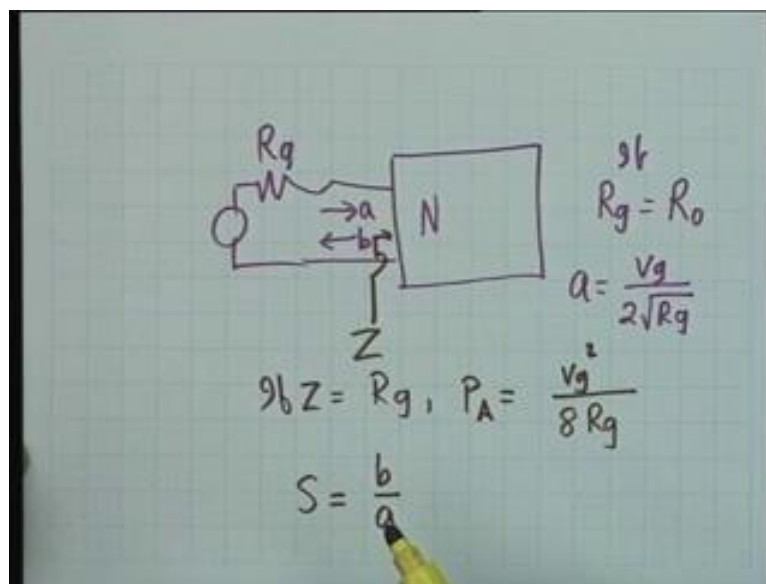


**Circuit Theory**  
**Prof. S.C. Dutta Roy**  
**Department of Electrical Engineering**  
**Indian Institute of Technology, Delhi**

**Lecture - 31**  
**Scattering Parameters of a 2-Port**

This is thirty-first lectures on Scattering Parameters of a 2 port. We first recall a few results from 1 port.

(Refer Slide Time: 00:31)



We had proved that, if you have a 1 port network  $N$  and it is driven by a source of internal impedance  $R_g$  and you choose  $R_g$  equal to the reference resistance  $R_0$ . If this is the case, then the incident wave  $a$  is simply equal to  $V_g / 2\sqrt{R_g}$ . This we proved the other day, we also proved the reflected wave is  $b$ , we also proved that if the input impedance of this network is  $Z$  and if  $Z$  equals to  $R_g$ , then the power delivered to the network is the maximum available from the source and is given by  $V_g^2 / 8 R_g$ .

This to results shall be utilized today in the discussion on 2 port, 2 ports Scattering Matrix. We also start a discussing the properties of this Scattering Parameter for a 1 port which is simply the ratio of the reflected wave to the incident wave. And we said several things mainly that, the magnitude of  $S$  also we started from this expression.

(Refer Slide Time: 02:11)

$$P = \frac{1}{2} |a|^2 (1 - |S|^2) \geq 0$$
$$|S|^2 \leq 1 \Rightarrow |S| \leq 1$$

Lossless ntk :  $|S(j\omega)| = 1.$

$S = 1$  O.C.  
 $S = -1$  S.C.

$$S = \frac{Z - R_g}{Z + R_g} = \frac{z - 1}{z + 1}$$
$$z \triangleq \frac{Z}{R_g}$$

That  $P$  is equal to half mod  $a$  squared 1 minus mod  $S$  square. And for a passive network this should be greater than or equal to 0. And therefore, for a passive network mod  $S$  squared must be less than equal to 1. That is: mod  $S$  must be less than or equal to 1 all right. That is the Scattering Parameter is upper bounded by unit. And this equality sign can be attained when the network is lossless. So, for a lossless network magnitude  $S$   $j$   $\omega$  is equal to 1.


We also showed from the definition of  $S$  another property. We said that this is reflection coefficient  $Z$  minus  $R_g$  divided by  $Z$  plus  $R_g$  and we wrote this as in the normalized form  $z$  minus 1 divided by  $z$  plus 1, where  $z$  is defined as  $Z$  divided by  $R_g$ . And we are good that, obviously for open circuit that is, if  $z$  goes to infinity  $S$  is equal to 1 for open circuit and  $S$  equal to minus 1 for short circuit. If  $z$ .

(Refer Time: 03:057)

That is correct and we have tacitly assumed here, that  $R_{naught}$  is equal to  $R_g$ . We have assumed that,  $R_{naught}$  equal to  $R_g$ . It is a good point you will see that, this is always done because it facilitates calculations. The terminating impedance is taken as the reference impedance. This is the general rule it facilitates computations; however, there are situations where this is not done there are situations, where this is not done there are situations, where this is not done. But we shall not encounter such situations in this class you might do. So, in a course on microwave circuits at a later stage in the curriculum, but up to this we did discuss in the previous class.

The further properties of the Scattering Parameter S for a 1 port network shall be obtained after we give 2 definitions.

(Refer Slide Time: 05:02)

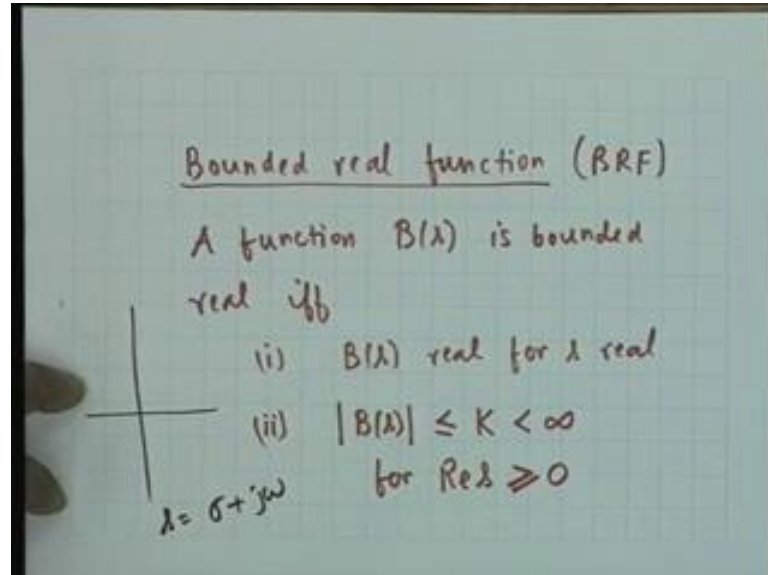


1 is that of the so, called bounded real function or which we abbreviate as BRF. And the definition is this very simple, a function B of s is bounded real is defined to be bounded real if and only if 2 conditions are satisfied, number 1 that B of s should be real for s real. That is B of s in B of s all coefficients must be real quantities; is that clear? Then if s is real, if the variable is real the function would be real this is very simple to apply it is obvious it should be obvious by instruction.

The second 1 is not obvious that is the magnitude of B of s must be bounded; that means, it should be less than or equal to some quantity K; obviously, K is positive all right which is bounded; that means, K is less than infinity for the right half of the s plane, that is for real part of s greater than equal to 0 this is the definition, you see in the s plane in the s plane, the right half is real part of s greater than or equal to 0.

If you write s equal to sigma plus j omega complex quantity then sigma is greater than equal to 0. In the right half plane the magnitude of the function must be bounded it cannot go to infinity which means: that B of s cannot have a pole in the right half plane is that clear? B of s cannot have a pole in the right. If it has a pole then the magnitude goes to infinity all right or B of s is regular there are many other kinds of expressions in the theory of complex variables to describe this but, this is, what this is what a bounded real function is. And we shall show that S the reason for bringing this definition is we

shall show that  $S$  is bounded real, but, before we do that we want to give another definition of another kind of function which are called positive real functions.

(Refer Slide Time: 07:41)

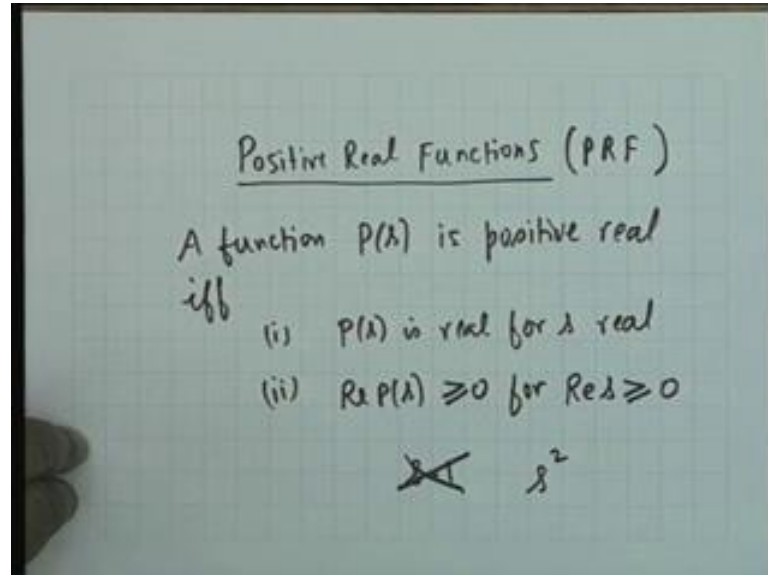

These definitions, will be useful in our further studies on network synthesis and it is a good point to give this definition. This is abbreviated as PRF and the definition is this a function  $P$  of  $s$  is positive real, if and only if 2 conditions are satisfied once again. First is that  $P$  of  $s$  is real for  $s$  real,  $P$  of  $s$  is real for  $s$  real. And the second is that the real part of  $P$  of  $s$  is non negative. It is it has nothing to do with the magnitude now, it is just the real part. Real part is non negative for the right half plane that is: for real part of  $s$  greater than or equal to 0.

In the right half of the  $s$  plane the real part of the function should be nonnegative. Now, is that point clear for example, the function  $s$  minus 1 is this positive real? No it is not positive real because its real part a sigma minus 1 can be negative in the right half plane all right. What about  $s$  squared?

(Refer Time: 09:19)

Positive real no, it is not necessarily, it is not positive real. No as far as positive realness is concerned a function is either positive real or not positive real.

(Refer Time: 09:36)

It is not all right.

(Refer Slide Time: 09:43)

$$S = \frac{z-1}{z+1}$$

Thm:  $S$  is a BRF if  $z$  is PRF.

$$z = \text{Re } z + j \text{Im } z$$
$$S = \frac{(\text{Re } z - 1) + j \text{Im } z}{(\text{Re } z + 1) + j \text{Im } z}$$

Now, the reason for bringing these 2 functions is that you saw that  $S$  for a 1 port is the normalized input impedance  $Z$  minus 1 divided by  $Z$  plus 1. And the next property can be stated in the form of a theorem that is: the Scattering Parameter  $S$  is bounded real, is a bounded real function is a BRF if  $Z$  which is the input impedance divided by a constant is PRF. If the impedance if the input impedance is a positive real function then the Scattering Parameter is a bounded real function and the proof is very simply.

Now, I can write  $z$  as equal to real part of  $z$  plus  $j$  times imaginary part of  $z$  all right. Let's call this as no let us leave it like that, then  $S$  is equal to real part of  $z$  minus 1 plus  $j$  imaginary part of  $z$ . And in the denominator I shall have real part  $z$  plus 1 plus  $j$  imaginary part of  $z$  agreed. I have just written  $z$  equal to real  $z$  plus  $j$  imaginary part of  $z$ , please recall that this is a real quantity imaginary part of  $z$  is a real quantity by multiplying by  $j$  I make it imaginary all right any question?

(Refer Slide Time: 11:34)

$$|S|^2 = \frac{(\operatorname{Re} z - 1)^2 + (\operatorname{Im} z)^2}{(\operatorname{Re} z + 1)^2 + (\operatorname{Im} z)^2}$$

$\operatorname{Re} s \geq 0 \Rightarrow \operatorname{Re} z \geq 0$   
if  $z$  is PRF

$\therefore |S|^2 \leq 1$  if  $\operatorname{Re} s \geq 0$

Also,  $S$  is real if  $z$  is real  
i.e. if  $z$  is real

Therefore magnitude  $s$  squared is equal to real  $z$  minus 1 squared plus imaginary  $z$  squared real  $z$  plus 1 squared plus imaginary part of  $z$  squared. If real part of  $s$  is greater than or equal to 0 this implies that real part of  $z$ , if  $z$  is PRF if  $z$  is PRF then this should be greater than or equal to 0 agreed, if  $z$  is PRF all right. Now, if real part of  $z$  is greater than or equal to 0 then; obviously, the numerator of this function shall be less than the denominator, is that clear? Yes or no. The numerator here.

(Refer Time: 12:42)

This is the definition of positive real function that, if  $z$  is positive real then real  $s$  greater than or equal to 0 shall imply that real  $z$  is greater than equal to 0. Therefore all right. Let I was explaining this point that under this condition under this condition which happens when real  $s$  is greater than or equal to 0 that is in the right half plane, in the right half plane real part of  $z$  is nonnegative. And therefore, the numerator of this must be less than the denominator.

The only way the numerator can exceed the denominator is, if real  $z$  can become negative all right, if real  $z$  can be become. Now, therefore, magnitude  $S$  squared is less than equal to 1, if real part of  $s$  greater than or equal to 0 all right. And obviously,  $S$  also  $S$  is real, if  $z$  is real because  $S$  is  $z$  minus 1 divided by  $z$  plus 1, if  $z$  is real then  $S$  is real that is when  $z$  real  $z$  is a positive real function and therefore, it is real when  $S$  is real if  $S$  is real.

Therefore I get 2 things about S that S is a real is real, if S is real and the magnitude of S is upper bounded by unity therefore, we have proved that is a bounded real function all right that proves the theorem agreed, I have gone very slow I have gone very slow we will come back to positive real functions in great details at a later stage, but, this is just the tip of the iceberg, if positive real functions are icebergs. They are very useful and a constant companion of electrical engineers whether they do control or circuits or whatever it is. Any question?

You see we have proved by mapping that is: real part of S greater than equal to 0 maps into real part of z greater than or equal to 0 that maps into mod S squared less than equal to 1. It is by mapping from S plane to z plane and z plane to S plane. And this mapping also many a times in your career you shall have to do yes.

(Refer Time: 15:47)


This is because z is PRF...

(Refer Time: 16:04)

s this is s equal to sigma plus j omega this is the variable, S is the Scattering Parameter all right.

(Refer Time: 16:17)

(Refer Slide Time: 16:20)

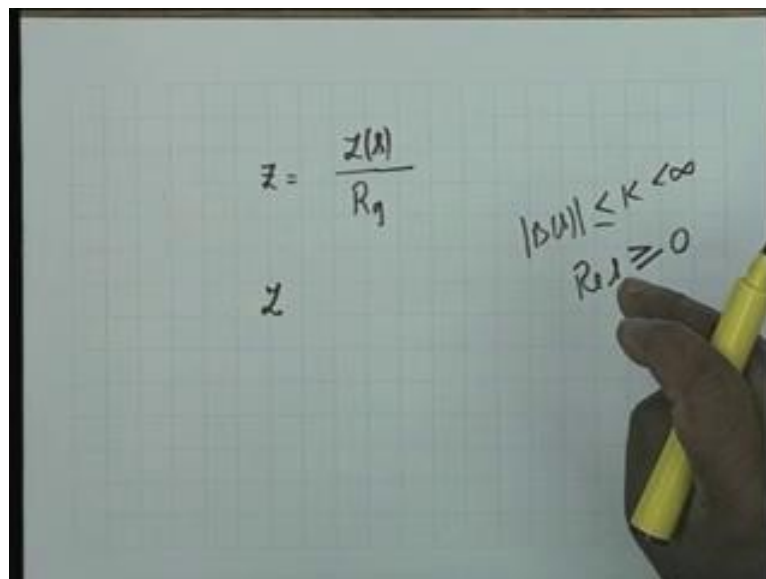

Of course, z is equal to Z divided by Rg therefore, z is a function of s I did not write it specifically z as well as z are functions of S. Yes.

(Refer Time: 16:34)

Both of them cannot have a pole in the right half plane good question.

(Refer Time: 16:46)

How do I get that  $s$  is because  $Z$  is a positive real function by hypothesis and 1 of the conditions is that it, must be real for  $s$  here.

(Refer Time: 17:02)

There is no bound in positive real functions yes.

(Refer Time: 17:10)

We will come to this, fine distinction at a later stage the difference between positive real functions and bounded real functions is in bounded real function the constraint is in magnitude only Whereas, in a positive real function the constraint is on the real part which certainly implies that, there is a bound on the magnitude also is not that right? It does imply but.


(Refer Time: 17:42)

That will come as a result of this as a result of the restriction in the real part, it will come as we will show at a later stage. A bounded real function cannot have a pole on the imaginary axis let me point out at least 1 distinction it cannot have a pole on the imaginary axis that is for a bounded real function  $B$  of  $s$  shall be less than equal to  $K$  less than infinity. For real part of  $S$  greater than equal to 0 all right it cannot have a pole on the  $j$  omega axis on the other hand a positive real function can have a pole on the  $j$  omega axis.

The 2 are not the same they have differences all right. We shall come back to positive real functions at great details after the second minor.



(Refer Slide Time: 18:59)

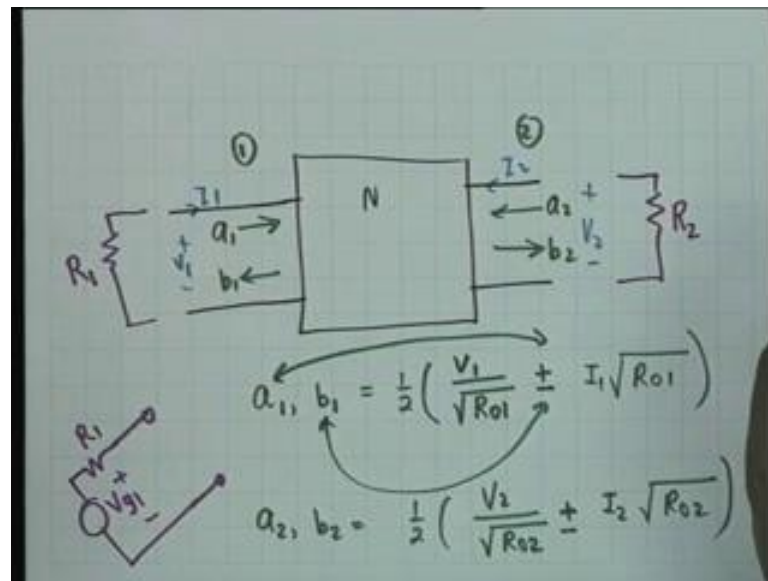

Now, we the time is appropriate for going to a description of a 2 port in terms of scattering parameters. Let us suppose that  $N$  is a 2 port, port 1 and port 2 the parameters the variables are taken as  $a_1, b_1, a_2, b_2$ .  $a_1$  is: the incident wave,  $b_1$  is: the reflected wave at port number 1. And at port number 2  $a_2$  is the incident wave and  $b_2$  is the reflected wave we require 2 incidents waves and 2 reflected waves for a 2 port description.

And the definitions of the incident and the reflected parameters are the same that is  $a_1$  and  $b_1$  would be equal to half if I call this voltage and current I require more colors  $V_1, I_1, V_2, I_2$ . If the voltage is in currents are  $V_1, I_1$  and  $V_2, I_2$  then my  $a_1, b_1$  is  $V_1$  divided by square root  $R_{01}$ , obviously we require 2 reference impedances now.

(Refer Time: 20:15)

Correct you see it is at port that we are concerned with  $a_1, b_1, V_1, I_1$  this port number 1.

(Refer Time: 20:31)

No we are considering a lumped network no it is not a lumped network the network could be distributed, but, we are considering at a specific value of  $x$  at a specific location in space we are considering the incident wave reflected wave voltage and current all right therefore, they are not functions. We are not going inside. We are not going inside the network you see all these 2 ports descriptions are external descriptions they are the descriptions of a black box.

What is inside it does not concern us at the moment all right. We will see we will take an example of a transmission line later how to find the scattering parameters. So, the definition is if you take  $a_1$  then it shall be plus, if you take  $b_1$  then it shall be minus.  $V_1$  corresponds to minus  $a_1$  corresponds to plus, plus  $I_1$  multiply by square root of  $R_{01}$  the usual definition.  $R_{01}$  is an arbitrary positive resistance which is called the reference resistance for port number 1.

Similarly,  $a_2$  and  $b_2$  is half  $V_2$  divided by square root of  $R_{02}$  plus minus  $I_2$  square root of  $R_{02}$  the usual definition. And I will be using introducing new terms 1 by 1. We introduce 2 terminating resistances that is the ports are not left open they are terminated 1 is terminated in a resistance  $R_2$  port number 2. And port number 1 is terminated in a resistance  $R_1$ . Now, where I have not shown it exactly connected the reason is the following. That if you excite the network the 2 port network at port number 1 then  $R_1$  shall be the internal resistance of the source all right.

If you excite the network at port number 2 then  $R_2$  shall be the internal resistance of the source  $V_g 2$  that is, a source connected to terminal number port number 2. So, termination can be a load termination can be the resistance connected between the terminals of the port or it can be the source resistance. Now, why do we call it a termination. Suppose  $R_1$  is the internal resistance of a source  $V_g 1$  at port 1 then actually port 1 is terminated in a source  $V_g 1$  and the resistance  $R_1$ . What is the resistance that it is terminated in total resistance; obviously,  $R_1$ .

And this is the reason why we call  $R_1$  and  $R_2$  as terminating resistances and we show them separately to indicate the fact that,  $R_1$  and  $R_2$  could as well be the internal resistances of voltage sources connected at these 2 ports is it point clear?

(Refer Slide Time: 24:23)

$$\underline{b} = \begin{bmatrix} b_1 \\ b_2 \end{bmatrix} \quad \underline{a} = \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$
$$\underline{b} = \underline{S} \underline{a}$$
$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$
$$b_1 = S_{11} a_1 + S_{12} a_2$$
$$b_2 = S_{21} a_1 + S_{22} a_2$$

Now; obviously, we have gone back to a 2 port in which there are if a is a voltage current description 2 voltages, 2 currents. Here there are 2 incident waves and 2 reflected waves and this Scattering Parameter description is in terms of the reflected variables  $b_1$   $b_2$  the matrix  $b$  in terms of the incident variables  $a_1$ ,  $a_2$ . And in terms of a matrix we write  $b$  as equal to  $S a$ .  $S$  is now, a matrix because we require 4 parameters in  $S$ .

We require a 2 by 2 matrix to relate a 2 by 1 matrix to another 2 by 1 matrix that is: if I write specifically the reflected parameters are written as a 2 by 2 matrix multiplied by the incident parameters  $a_1$ ,  $a_2$ . We call this  $S_{11}$  in the usual manner, we call this as  $S_{12}$ , this is  $S_{21}$  and  $S_{22}$  all right. Since, we have encountered this for the first time let us, expand this and look at the interpretations you see  $b_1$  is equal to  $S_{11} a_1$  plus  $S_{12} a_2$  and  $b_2$  is equal to  $S_{21} a_1$  plus  $S_{22} a_2$  all right.

This is exactly the same type, the same type of description as  $z$  parameters or  $y$  parameters or  $a b c d$  parameters or  $h$  parameters. Here instead of taking voltages and currents we have taken combinations of them to define an incident wave and a reflected wave. And what we are relating is reflected wave is being related to the incident wave variables they are not parameters, they are variables.

(Refer Slide Time: 26:19)

$$b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0}$$

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0}$$

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

Ref. coeff. at port 1

reverse transmiss. coeff.

forward  $x^n$  coeff.

If we look at this, you let me write this down again  $b_1$  equal to  $S_{11} a_1$  plus  $S_{12} a_2$   $b_2$  is equal to  $S_{21} a_1$  plus  $S_{22} a_2$ . And you notice that  $S_{11}$  from this is simply  $b_1$  by  $a_1$  under the condition  $a_2$  equal to 0. We have to find out now, what  $a_2$  equal to 0 means we will have to find out we will do that you notice,  $S_{12}$  is equal to  $b_1$  divided by  $a_2$  under the condition  $a_1$  equal to 0.  $S_{21}$  is  $b_2$  divided  $a_1$  under the condition  $a_2$  equal to 0 and similarly,  $S_{22}$  is  $b_2$  divided by  $a_2$  under the condition  $a_1$  equal to 0 of this 4 parameters

I would like you look at first the 1 1 and 2 2 parameters that is, where the 2 subscripts are equal  $S_{ii}$  parameter you see  $S_{11}$  relates the reflected wave at port 1 to the incident wave at port 1 in other words  $S_{11}$  is something like a reflection coefficient. This is how we define the S parameter the Scattering Parameter of a1 port. Now, this is a 2 port and therefore, there must be some condition on port number 2, if you wish to measure the reflection coefficient at port number 1 it depends on what conditions are there at port number 2 and  $a_2$  equal to 0 is the condition at port number 2.


We shall see, what this means in a minute excuse me therefore, I can call  $S_{11}$  as the reflection coefficient at port 1. And in a similar manner  $S_{22}$  is the reflection coefficient at port 2 with port 1 terminated in such a manner that  $a_1$  equals to 0 all right. Now, to interpret  $S_{12}$  and  $S_{21}$  we shall have to look at the figure again  $S_{12}$  all right. Let us first look at  $S_{21}$ ;  $S_{21}$  is  $b_2$  by  $a_1$  under the condition  $a_2$  equal to 0. Let's look at here  $b_2$  by  $a_1$  under the condition  $a_2$  equal to 0 all right.

Now, if  $a_2$  equal to 0 you see the only wave going out is the reflected at  $b_2$  and it agrees with the direction of  $a_1$  ar. So, it is as if due to the incident wave  $a_1$  how much wave goes out, how much is transmitted out of port 2 and therefore,  $b_2$  by  $a_1$  under the condition  $a_2$  equal to 0 is actually called the forward transmission coefficient. Forward transmission coefficient  $S_{21}$  is therefore, the forward transmission coefficient and in a similar manner  $S_{12}$  is what do you call  $S_{12}$ ? It is the...

(Refer Time: 29:59)

Reverse transmission coefficient. These are the names for the 4 parameters. Now, we shall try to see, what the interpretations are.

(Refer Slide Time: 30:17)

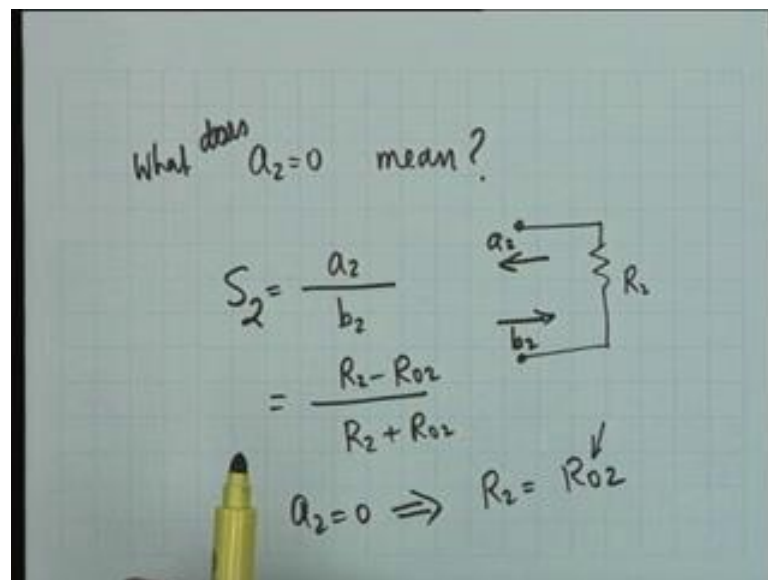

First let us consider let us find out what  $a_2$  equal to 0 means. Let's look at this terminating resistance  $R_2$  terminating resistance  $R_2$ . Now, we had an incident wave  $a_2$  and a reflected wave  $b_2$  for port number 2; if you look at  $R_2$  if you forget about port 2. As far as  $R_2$  is concerned  $b_2$  is it is incident wave, is not that right? And  $a_2$  is it is reflected wave. This is  $a_1$  port  $R_2$  is  $a_1$  port in which  $b_2$  is the incident wave and  $a_2$  is the reflected wave is the point clear? So, we can define the Scattering Parameter of  $R_2$   $S_2$  as equal to yes.

(Refer Time: 31:19)

$a_2$  by  $b_2$  and in terms of the reference resistance this is yes the Scattering Parameter input impedance minus reference So,  $R_2$  minus  $R_{02}$ ;  $R_{02}$  is the reference resistance at

port number 2 divided by  $R_2$  plus  $R_{02}$ . Now you notice, that  $a_2$  equal to 0 what does this imply? This implies that  $R_2$  equal to  $R_{02}$  is this point clear? If  $R_2$  equal to  $R_{02}$  which is the other way round that is, if the reference resistance at port number 2 is taken as the same as the terminating resistance then  $a_2$  becomes equal to 0 all right.

So,  $a_2$  equal to 0 simply means; that  $R_2$  the terminating resistance is equal to the reference resistance or it is the other way round that is: the reference resistance is chosen as the terminating resistance.

(Refer Slide Time: 32:32)

$$\begin{aligned}
 a_2=0 &\Rightarrow R_2 = R_{02} \\
 a_1=0 &\Rightarrow R_1 = R_{01} \\
 S_{11} &= \frac{b_1}{a_1} \Big|_{R_2=R_{02}}, S_{12} = \frac{b_1}{a_2} \Big|_{R_1=R_{01}} \\
 S_{21} &= \frac{b_2}{a_1} \Big|_{R_2=R_{02}}, S_{22} = \frac{b_2}{a_2} \Big|_{R_1=R_{01}}
 \end{aligned}$$

Therefore what I have is  $a_2$  equal to 0 implies that  $R_2$  equal to  $R_{02}$ . And similarly,  $a_1$  equal to 0 shall imply that  $R_1$  equal to  $R_{01}$ . And therefore, it makes sense for a 2 port to use the references resistances as the same as the terminating resistances. And under that condition our  $S_{11}$  shall be redefined as  $b_1$  by  $a_1$  under the condition that  $R_2$  is equal to  $R_{02}$   $S_{12}$  will come in a minute  $V_1$  by  $a_2$  under the condition.

(Refer Time: 33:20)

$R_1$  equal to  $R_{01}$   $S_{21}$  is equal to  $b_2$  by  $a_1$  under the condition  $a_2$   $R_2$  equal to  $R_{02}$  and  $S_{22}$ , shall be equal to  $b_2$  by  $a_2$  under the condition  $R_1$  equal to  $R_{01}$  all right. And this is the logic of the rationale behind choosing the reference resistances to be equal to the terminating resistances then the definition becomes absolutely clear.

(Refer Time: 34:00)

This is unmatched termination yes, yes.

It is not necessarily matched matching will occur when  $R_1$  is equal to the input impedance that is  $V_1$  by a  $I_1$  all right others not otherwise.

(Refer Time: 34:20)

Shall I explain reference resistance once again; reference resistance is an arbitrary positive constant having the dimension of impedance all right. Now, reference resistance is left arbitrary as long as possible then at a certain point of time when you are going to calculate this Scattering Parameter you have to fix the reference resistance we have to choose them. And this choice for a 2 port is to be equal to the terminating resistances the terminating resistances, are not under your control.


It is fixed some 1 gives you a source, whose power is to be transferred to a given load some1 gives you a source for example, a microphone. The power of the microphone is to be transmitted to a loud speaker then in between you design a network all right. So, the terminating resistances here are the microphone resistances and the loud speaker resistances. And in order to calculate the scattering parameters you fix  $R_{01}$  equal to  $R_1$  and  $R_{02}$  equal to  $R_2$ .

So, long as you have the flexibility you keep them flexible you keep them arbitrary, but, when actually required to calculate and make use of the network, then you choose the scattering you choose the reference resistances.

(Refer Time: 35:50)

No, we are not matching right away matching should occur only, if we should transfer maximum power.

(Refer Slide Time: 36:03)

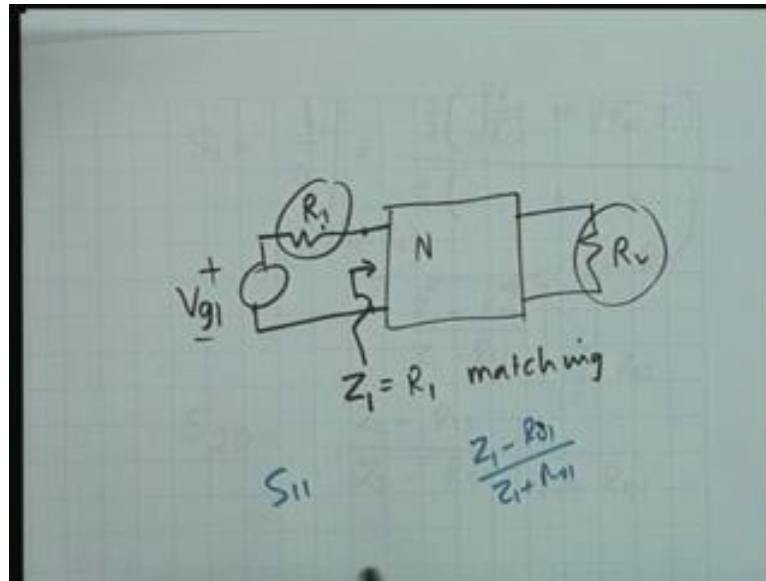

Matching shall occur suppose  $R_2$  is fixed suppose  $R_2$  is this is a loud speaker. We want to transfer maximum power from the source  $V_{g1}$  from the source  $V_{g1}$   $2R_2$ . Then you must design  $N$  in such a manner that  $Z_1$  which is equal to  $V_1$  by  $I_1$  is equal to  $R_1$  this is the condition for matching, that means; maximum available power shall be transferred we have not brought this into consideration here. All we have done so, far is in the definition; we have fixed the terminating we have fixed the reference impedances to be equal to the terminating resistances.

We will see what happens, when matching occurs at a later stage, but before that.

(Refer Time: 36:55)

Well it is not necessarily matched because  $R_1$  and  $R_2$  may not be under our control. And all that is under our control is  $N$  you may able to design  $N$ . In fact, that should be your aim your aim should be design  $N$  in such manner that the input impedance is as close to  $R_1$  as possible all right then  $N$  shall be called a matching network, any other question?



(Refer Slide Time: 37:34)

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \frac{\frac{1}{2} \left( \frac{V_1}{\sqrt{R_{01}}} - \sqrt{R_{01}} I_1 \right)}{\frac{1}{2} \left( \frac{V_1}{\sqrt{R_{01}}} + \sqrt{R_{01}} I_1 \right)}$$

$$= \frac{Z_1 - R_{01}}{Z_1 + R_{01}} \quad \left. \begin{array}{l} R_2 = R_{02} \\ R_1 = R_{01} \end{array} \right\}$$

$$S_{22} = \left. \frac{Z_2 - R_{02}}{Z_2 + R_{02}} \right|_{R_1 = R_{01}}$$

Let us look at the interpretation of these parameters  $S_{11}$  and  $S_{22}$  to start with  $S_{11}$  is equal to  $b_1/a_1$  under the condition  $a_2$  equal to 0 that is  $R_2$  is equal to  $R_{02}$ . And if you take the if you recall the definition this is half  $V_1$  divided by square root of  $R_{01}$  plus square root of  $R_{01}$   $I_1$  divided by half this quantity minus this is minus and this is plus. And this is minus and this is plus and you notice that this is simply equal to  $Z_1$  minus  $R_{01}$  divided by  $Z_1$  plus  $R_{01}$  under the condition that  $R_2$  is equal to  $R_{02}$ .

It is indeed a reflection coefficient that is: the input impedance minus reference resistance which you have chosen to be equal to  $R_1$  all right divided by  $Z_1$  plus  $R_{01}$ . And you notice what happens when the terminals when the resistances are matched. That is if the input impedance  $Z_1$  is equal to  $R_{01}$  which is equal to  $R_1$  then; obviously, maximum possible power shall be transferred to the network agreed.

(Refer Time: 39:07)

We had, we have put  $R_1$  equal to  $R_{01}$ , if I want to match not otherwise. Similarly,  $S_{22}$  is equal to  $S_{22}$  is equal to  $Z_2$  minus  $R_{02}$  without going into this derivation divided by  $Z_2$  plus  $R_{02}$  under the condition that  $R_1$  equals to  $R_{01}$ . And once again you can see that;  $S_{22}$  shall be equal to 0 that is, there have been no reflection then the absolute there will be all absorption of power in the resistance  $R_2$  if  $Z_2$  is equal to  $R_{02}$  that is, if the port number 2 is matched.

(Refer Time: 39:59)

This is under the condition  $R_2$  equal to  $R_{02}$  that is a 2 equal to 0.

(Refer Time: 40:09)

How does it affect? This has to be measured you see you have to measure the input impedance  $Z_1$  with the output terminals terminated in  $R_2$   $Z_1$  is affected by  $R_2$ . Is that clear? The input impedance depends on  $R_2$  therefore, you must specify the terminating condition.

(Refer Time: 40:38)

Well this is the general expression.

(Refer Time: 40:48)

Yeah, but, then you have to fixed what is your  $R_{01}$  because  $R_{01}$ .

(Refer Time: 40:58)

It does not mean anything  $R_{01}$  has to be related now, to the terminating impedance you see as soon as you say that  $S_{11}$  is the reflection coefficient at port number 1. Now, reflection coefficient you define as  $Z_1$  minus  $R_{01}$  divided by  $Z_1$  plus  $R_{01}$  as long as  $R_{01}$  is arbitrary  $Z_1$  equal to  $R_{01}$  it does not mean anything. It does not indicate how much power is actually being transmitted from  $V_g$   $R_1$  to the network. Therefore, to get a quantitative estimate of that; you must relate  $R_1$  to  $R_{01}$ .

If  $R_1$  is equal to  $R_{01}$  then maximum available power from the source  $V_g$   $R_1$  is being transmitted to N all right.


(Refer Time: 41:52)

Well in the a practical situation when you are calculating  $S_{11}$ ,  $S_{11}$  you require a choice of  $R_{01}$  you require a choice of  $R_{02}$  as I said  $R_{02}$  is chosen to be equal to  $R_2$ , but,  $R_{01}$  must also be chosen otherwise how do you get a quantity? How do you calculate  $S_{11}$ . So,  $R_{01}$  under that condition is taken to be equal to  $R_1$ .

(Refer Time: 42:29)

And this would be more clear.

(Refer Slide Time: 42:36)

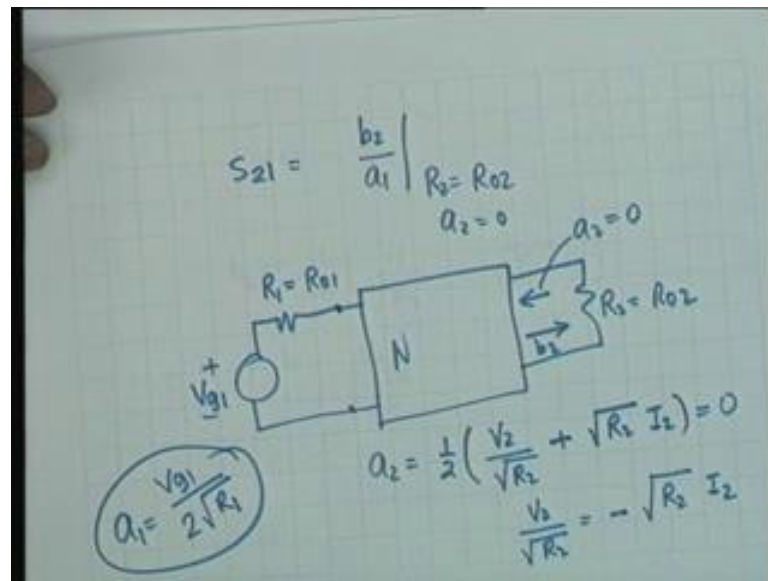

If we calculate  $S_{21}$ ,  $b_2$  upon  $a_1$  under the condition  $R_2$  equal to  $R_{02}$ . Now,  $b_2$  upon  $a_1$  which means  $a_2$  equals to 0. And our situations, for calculation of this please do follow this carefully. The situation is that we have  $R_1$  which is now chosen equal to  $R_{01}$  a  $V_g 1$  and network  $N$  and a resistance  $R_2$  which is equal to  $R_{02}$ . And do you want  $a_2$  we want only  $b_2$  we want  $a_2$  to be equal to 0. If you look at  $a_2$ , if you look at  $a_2$  the definition it is half  $V_2$  by square root  $R_2$  plus square root  $R_2$  times  $I_2$ .

If this is equal to 0 what does this mean? It means that:  $V_2$  by square root  $R_2$  should be equal to minus square root  $R_2$  multiplied by  $I_2$ .

(Refer Time: 44:13)

That is right  $Z_2$  equal to minus  $R_2$  yes not quite, does this mean  $Z_2$  equal to minus  $R_2$ .

(Refer Time: 44:29)

This is a constraint on  $V_2$  and  $I_2$   $V_2$  by  $I_2$  is equal to minus  $R_2$  because of the termination it is nothing to do with the impedance.


(Refer Slide Time: 44:47)

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \quad a_1 = \frac{V_{g1}}{2\sqrt{R_1}}$$
$$b_2 = \frac{1}{2} \left( \frac{V_2}{\sqrt{R_2}} - \sqrt{R_2} I_2 \right)$$
$$= \frac{V_2}{\sqrt{R_2}}$$
$$S_{21} = \frac{V_2}{\sqrt{R_2}} \cdot \frac{2\sqrt{R_1}}{V_{g1}}$$

Now, I want you to follow this carefully  $S_{21}$  is  $b_2$  by  $a_1$  under the condition  $a_2$  equal to 0 and what is  $b_2$ . If you go back to the definition half  $V_2$  by square root  $R_2$  minus square root  $R_2 I_2$ , but, we have already proved that this is equal to minus this therefore, this is simply equal to  $V_2$  by square root  $R_2$  agreed. Now I go back to the to the 1 port result you recall you recall that, if consider this now as 1 port. If the internal resistance is chosen as the reference resistance then what is  $a_1$ ;  $a_1$  is  $V_{g1}$  divided by twice square root  $R_1$  all right.

I shall utilize this result here and therefore, I get  $S_{21}$  as equal to  $V_2$  divided by square root  $R_2$  multiplied by twice square root  $R_1$  divided by  $V_{g1}$  is it. I have substituted for a 1,  $a_1$  is  $V_{g1}$  divided by 2 square root  $R_1$  I have substituted this.

(Refer Slide Time: 46:28)

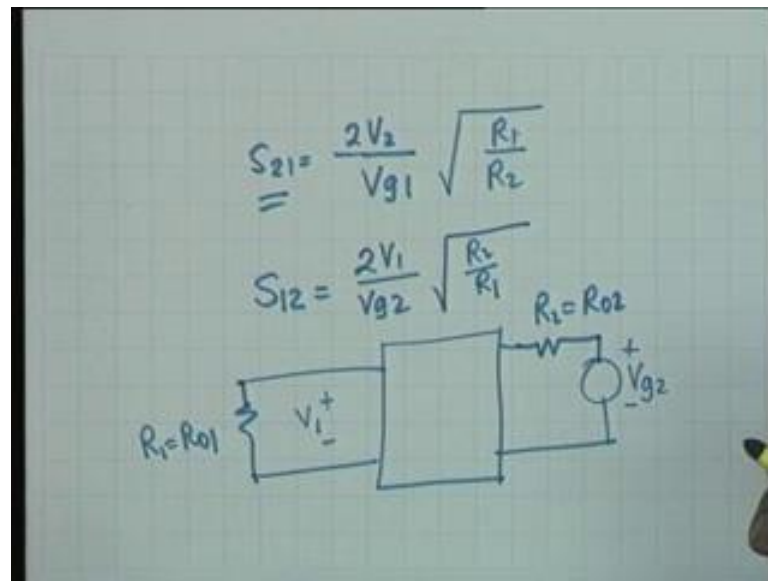

And the end result that I get is  $S_{21}$  equal to  $V_2$  by  $V_{g1}$  multiplied by twice multiplied by square root  $R_1$  divided by  $R_2$ . And this gives you a physical interpretation of  $S_{21}$  voltage transfer function multiplied by a constant. And if  $R_1$  and  $R_2$  are equal, if it is a network with equal termination then it is simply twice a voltage transfer functions. So, to calculate  $S_{21}$  all that you have to calculate is a voltage transfer function. And in the problem session today we shall, take examples of such calculations.

In a similar manner for calculating  $S_{12}$  what shall you do you will terminate port number 2 in a source in series with a resistance  $R_2$ ,  $R_2$  and measure the voltage across port number 1  $V_1$  with a termination of  $R_1$  which is equal to  $R_{01}$ . And under this condition  $S_{12}$  shall be twice  $V_1$  divided by  $V_{g2}$  multiplied by square root of yes.  $R_2$  by  $R_1$  let us close, this class with a simple example. Is there any question?

(Refer Time: 48:10)

Why did we put  $R_2$  because this shows our choice of reference impedance.

(Refer Time: 48:20)


No  $S_{21}$  had, the condition  $a_2$  equal to 0  $S_{12}$  request 1 equal to 0  $R$  naught 1.

(Refer Time: 48:33)

We can have any other value or  $R_{02}$ , but, we calculate with  $R_{02}$  equal to  $R_2$  with the specific value and this is how it is done. That is you see once, a network is chosen once a network is there, if you want to calculate the 4 parameters; obviously, you shall have to

fix your R01 and R02. It is not that S12 only shall be useful you want to characterized the network completely, and therefore it is the what is done is we first fixed R01 fixed R02 equal to R1 and R2 and then calculate the parameters.

(Refer Slide Time: 49:27)

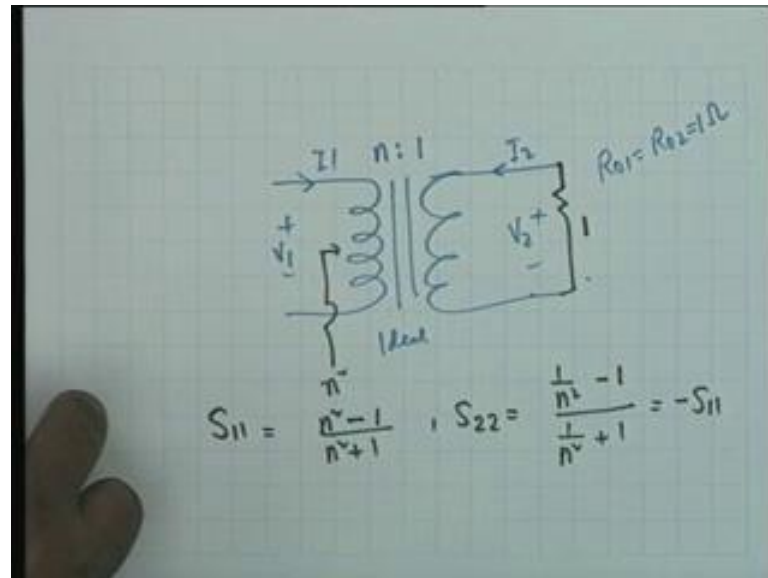

Now, I want to conclude this class with an example, which I can do by inspection an ideal transformer.

(Refer Time: 49:33)

It is not maximum power. R2 equal to R02 is not the condition for maximum power, it only makes a2 equal to 0 under which condition you have to measure S11 and S21 all right. This is an ideal transformer V1 I1 V2 I2. And it is given that R01 equal to R02 equal to 1 Ohm for simplicity all right. And you are required to calculate the four parameters. To calculate S11 I am going very slow to calculate S11 you have to terminate this in 1 Ohm.

If you terminate this in 1 Ohm then what is the impedance here? N squared. Therefore S11 shall be equal to n squared minus the reference impedance 1 divided by n squared plus 1. Can you tell me what would be S22? If you call if you terminate this.


(Refer Time: 50:53)

This will be 1 by n squared.

(Refer Time: 50:58)

Don't you see that this is exactly minus S11 is not right? This is minus S11.

(Refer Slide Time: 51:11)

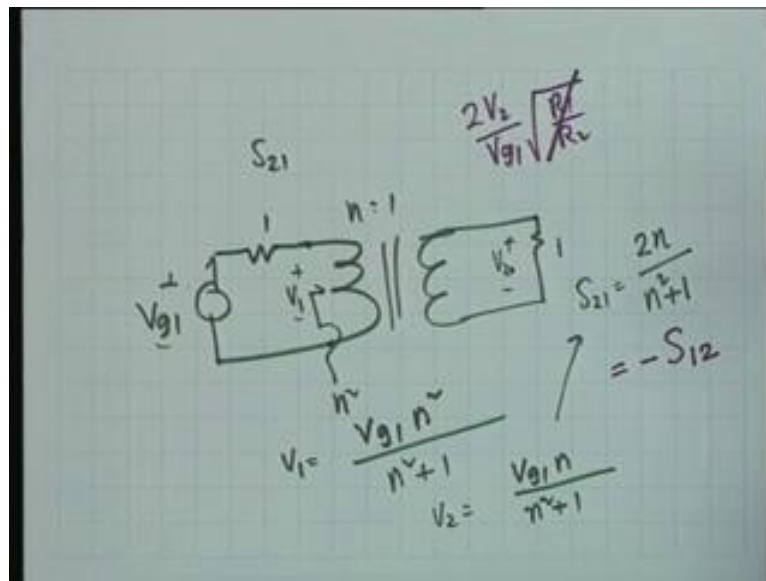

Now, calculation of S21 requires. Now, you have to terminate this have a  $V_{g1} n$  is to 1. And then terminate this in 1 Ohm and this is  $V_2$  all right. So, what you have to calculate is  $V_2$  by  $V_{g1}$  actually twice  $V_2$  by  $V_{g1}$ .  $R_1$  and  $R_2$  are equal. So, the ratio is equal to 1. Now, to calculate this; what is this impedance here? This is  $n$  squared therefore,  $V_1$  this a style of calculation by you can do it by inspection  $V_1$  is therefore, the potential division of  $V_{g1}$  into 1 Ohm and  $n$  squared Ohms therefore,  $V_1$  is  $V_{g1} n$  squared divided by  $n$  squared plus 1 agreed yes or no.

(Refer Time: 52:17)

Not  $n$  times divided by  $n$ . So, it is  $V_{g1} n$  divided by  $n$  square plus 1 therefore,  $S_{21}$  would be simply equal to twice  $n$ , you understand why this factor 2 come? because, it is  $2 V_2$  by  $V_{g1}$ . So, twice  $n$  by  $n$  squared plus 1 And I leave it to you to show that; this is equal to minus  $S_{12}$ .

(Refer Time: 52:52)

$S_{21}$  by definition is twice  $V_2$  by  $V_{g1}$  squared root  $R_1$  by  $R_2$ .  $R_1$  and  $R_2$  are equal. So, we have calculated  $2 V_2$  by  $V_{g1}$ . One can show that  $S_{21}$  is not too sure about this whether the minus sign is there or not, we will clarify this in the next class.

Thank you.