

**Microwave Engineering**  
**Professor Ratnajit Bhattacharjee**  
**Department of Electronics & Electrical Engineering**  
**Indian Institute of Technology Guwahati**  
**Lecture 14**  
**Series and Parallel RLC Resonators**

(Refer Slide Time: 00:28)

## Microwave Resonators

We start a new module Microwave Resonators.

(Refer Slide Time: 00:38)


### Contents

- Series and Parallel Resonant Circuits
- Q-factor (unloaded and loaded)
- Bandwidth
- Transmission Line Resonators
- Waveguide resonators

In this module, we cover the following contents. First, we discuss series and parallel resonant circuits, conventional circuits, then we discuss Q-factor both unloaded and loaded Q-factor.

We discuss the bandwidth of such circuits then we also cover transmission line resonators, and finally we discuss waveguide resonators.

(Refer Slide Time: 01:04)

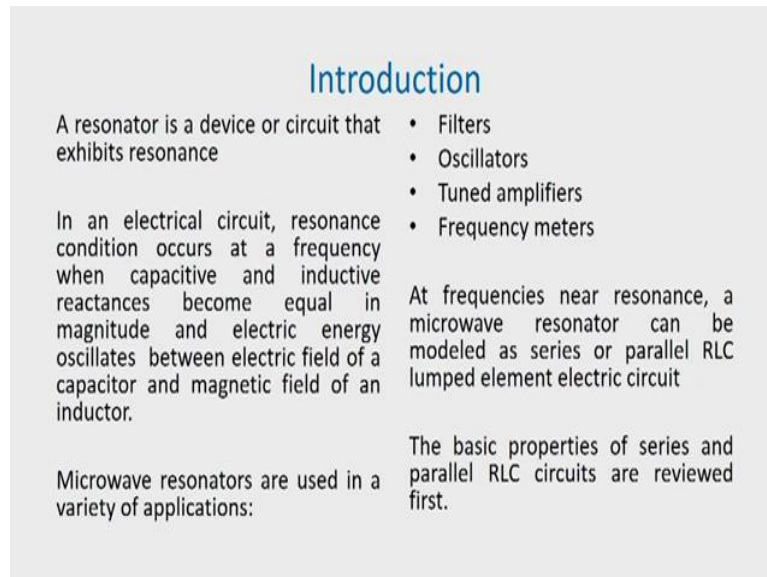

**Introduction**

A resonator is a device or circuit that exhibits resonance

In an electrical circuit, resonance condition occurs at a frequency when capacitive and inductive reactances become equal in magnitude and electric energy oscillates between electric field of a capacitor and magnetic field of an inductor.

Microwave resonators are used in a variety of applications:

- Filters
- Oscillators
- Tuned amplifiers
- Frequency meters

At frequencies near resonance, a microwave resonator can be modeled as series or parallel RLC lumped element electric circuit

The basic properties of series and parallel RLC circuits are reviewed first.

So, a resonator is a device or circuit that exhibits resonance. An electrical circuit resonance condition occurs at a frequency when the capacitive and inductive reactances become equal in magnitude, and electrical energy oscillates between electric field of a capacitor and magnetic field of an inductor. Microwave resonators are used in a variety of applications, for example, filters, oscillators, tuned amplifiers, frequency meters, these are some of the examples where microwave frequency resonators are used.

Now, at frequencies near resonance, a microwave resonator can be modeled as series or parallel RLC lumped-element circuit. Therefore, the basic properties of series and parallel RLC circuits are reviewed first.


(Refer Slide Time: 02:35)

For the series RLC circuit shown in the figure:

$$Z_{in} = R + j\omega L - j\frac{1}{\omega C} = R + j\omega L \left(1 - \frac{1}{\omega^2 LC}\right)$$

$$Z_{in} = R + j\omega L \left(1 - \frac{\omega_0^2}{\omega^2}\right)$$

where  $\omega_0 = \frac{1}{\sqrt{LC}}$

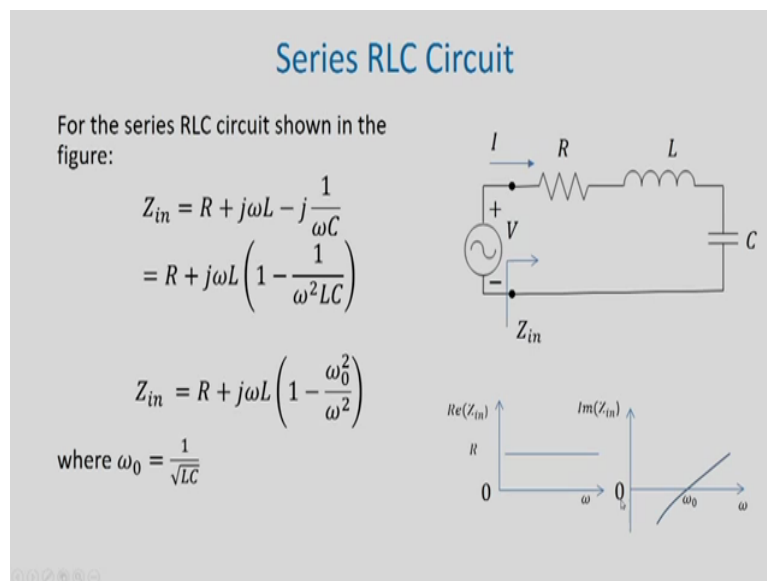

So, we consider series RLC circuit, and for the series, RLC circuit shown in the figure we can write  $Z_{in}$  is equal to  $R$  plus  $j\omega L$  minus  $j\frac{1}{\omega C}$ , and then we can write  $Z_{in}$  equal to  $R$  plus  $j\omega L$  into  $1 - \frac{1}{\omega^2 LC}$ . Now, writing  $\omega_0$  square is equal to  $\frac{1}{LC}$ . We find that  $Z_{in}$  can be written as  $R$  plus  $j\omega L$   $1 - \frac{\omega_0^2}{\omega^2}$  square divided by  $\omega^2$ .

So,  $\omega_0$  is the resonant frequency because whenever  $\omega$  is equal to  $\omega_0$  the imaginary part of the input impedance become zero, and  $Z_{in}$  becomes purely ( $R$ )(04:04). We should note that for a series RLC circuit, the real part of  $Z_{in}$ , this is constant  $R$  and the imaginary part of  $Z_{in}$  below resonant frequency  $\omega_0$ , this is capacitive and above resonant frequency  $\omega_0$  it becomes inductive. So, if we plot the imaginary part of  $Z_{in}$  and here at  $\omega$  equal to  $\omega_0$  the resonant frequency the imaginary part of  $Z_{in}$  becomes zero.

(Refer Slide Time: 04:58)


$$|Z_{in}(\omega)| = \sqrt{R^2 + \omega^2 L^2 (1 - \omega_0^2 / \omega^2)^2}$$

An important parameter of the resonant circuit is its  $Q$  which is defined as:

$$Q = \omega \frac{\text{average energy stored}}{\text{average power dissipated}}$$

$$Q = \omega \frac{W_m + W_e}{P_{loss}}$$

At resonance,  $W_m = W_e$

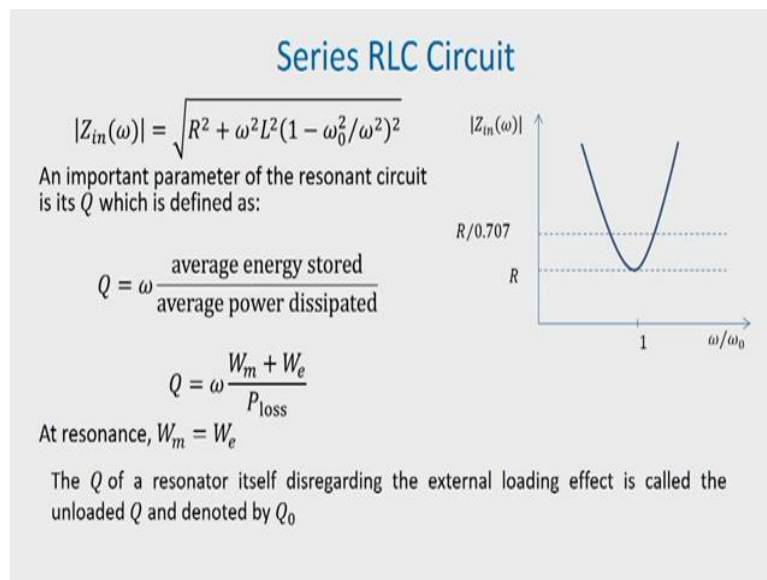

We can write magnitude of  $Z_{in}$  as a function of  $\omega$  as under  $\sqrt{R^2 + \omega^2 L^2 (1 - \omega_0^2 / \omega^2)^2}$  and if we plot magnitude of  $Z_{in}$  versus  $\omega$  then we find that from this expression at  $\omega = \omega_0$ , magnitude of  $Z_{in}$  becomes minimum and equal to  $R$  for other values of  $\omega$  magnitude of  $Z_{in}$  is greater than  $R$ , and we have marked this horizontal line where it becomes  $R/0.707$  that means root to  $R$ .

These particular points see we will relate it to half-power bandwidth of the resonator. An important parameter of resonant circuit is it is  $Q$  which is defined as  $Q$  is equal to  $\omega$  average energy stored divided by average power dissipated, this parameter  $Q$  is called the equality factor and therefore, we can write  $Q$  is equal to  $\omega (W_m + W_e) / P_{loss}$ , this is the energy stored in the inductor  $W_m$ .

So, sum of these two energies it gives the total energy divided by P loss, the loss happens at the resistance R. Now, at resonance that means when omega is equal to omega naught W m becomes equal to W e and therefore we can write Q it can be written as either omega naught 2W m by P loss or omega naught 2W e by P loss we will see and the Q of a resonator itself this regarding external loading.

That means we are assuming that no external load is connected to this resonator whatever Q that we are getting that is within the resonator itself that is because of the losses within the resonator itself and this is called unloaded Q and denoted by Q naught.

(Refer Slide Time: 08:09)

Therefore,  $Q_0 = \omega_0 \frac{2W_m}{P_{\text{loss}}}$

$$Q_0 = \omega_0 \frac{|I|^2 L}{|I|^2 R} = \omega_0 \frac{L}{R}$$

Since  $\omega_0^2 = \frac{1}{LC}$

$$Q_0 = \frac{1}{\omega_0 RC}$$

Let us now study the behavior of the input impedance of a series RLC resonator near its resonance

$$Z_{in} = R + j\omega L \left( \frac{\omega^2 - \omega_0^2}{\omega^2} \right)$$

In the vicinity of resonance,

$$\omega^2 - \omega_0^2 = (\omega - \omega_0)(\omega + \omega_0) \cong 2\omega\Delta\omega$$

For small  $\Delta\omega$ ,

$$Z_{in} \cong R + j\omega L \frac{2\omega\Delta\omega}{\omega^2} \cong R + j2\Delta\omega L$$

$$Z_{in} \cong R + \frac{j2\Delta\omega R Q_0}{\omega_0}$$

## Series RLC Circuit

Therefore,  $Q_0 = \omega_0 \frac{2W_m}{P_{\text{loss}}}$

$$Q_0 = \omega_0 \frac{|I|^2 L}{|I|^2 R} = \omega_0 \frac{L}{R}$$

Since  $\omega_0^2 = \frac{1}{LC}$

$$Q_0 = \frac{1}{\omega_0 RC}$$

Let us now study the behavior of the input impedance of a series RLC resonator near its resonance

$$Z_{in} = R + j\omega L \left( \frac{\omega^2 - \omega_0^2}{\omega^2} \right)$$

In the vicinity of resonance,

$$\omega^2 - \omega_0^2 =$$

$$(\omega - \omega_0)(\omega + \omega_0) \approx 2\omega\Delta\omega$$

For small  $\Delta\omega$ ,

$$Z_{in} \approx R + j\omega L \frac{2\omega\Delta\omega}{\omega^2} \approx R + j2\Delta\omega L$$

$$Z_{in} \approx R + \frac{j2\Delta\omega R Q_0}{\omega_0}$$

So, therefore  $Q$  naught is  $\omega$  naught  $2W_m$  divided by  $P_{\text{loss}}$ , and when we substitute the term related to the energy stored in the inductor and the power loss or dissipation in the resistor then we get  $Q$  naught equal to  $\omega$  naught  $L$  by  $R$  and since  $\omega$  naught square is equal to  $1$  by  $LC$  we can also write  $Q$  naught is equal to  $1$  by  $\omega$  naught  $RC$  we can substitute  $L$  to be equal to  $1$  by  $\omega$  naught square  $C$  and then we will get this term.

Now, let us study the behavior of the input impedance of a series RLC circuit or a series RLC resonator near it is resonance frequency. So, this expression  $Z_{in}$  is equal to  $R$  plus  $j$   $\omega$   $L$   $\omega$  square minus  $\omega$  naught square divided by  $\omega$  square that we have already seen. So, what do we can do in the vicinity of the resonance? We can expand this term  $\omega$  square minus  $\omega$  naught square is equal to  $\omega$  minus  $\omega$  naught into  $\omega$  plus  $\omega$  naught.

Now, we write  $\omega$  minus  $\omega$  naught as  $\Delta\omega$  and when we are close to the resonance  $\omega$  plus  $\omega$  naught can be written as  $2\omega$  and therefore small  $\Delta\omega$  we can write  $Z_{in}$  is equal to  $R$  plus  $j$   $\omega$   $L$  into  $2\omega$   $\Delta\omega$  by  $\omega$  square which becomes approximately equal to  $R$  plus  $j2\Delta\omega L$  and if we substitute from here  $L$  equal to  $R Q$  naught by  $\omega$  naught then we get approximate expression for  $Z_{in}$  which is given by  $R$  plus  $j2\Delta\omega R Q$  naught by  $\omega$  naught.

Now, this form of representation of the input impedance near it is resonant frequency this expression is a very useful expression, and we will make use of this expression in our later analysis of transmission line resonators.

(Refer Slide Time: 11:38)

Let us now consider half power fractional bandwidth of the resonator

We have  $P_{in} = \frac{1}{2}VI^* = \frac{1}{2}Z_{in} \left| \frac{V}{Z_{in}} \right|^2$  Therefore,  $Re(P_{in}) = \frac{1}{2}R \left| \frac{V}{Z_{in}} \right|^2$

When  $\omega = \omega_0$ ,  $Z_{in} = R$  and  $Re(P_{in})|_{\omega=\omega_0} = \frac{|V|^2}{2R}$

When  $|Z_{in}|^2 = 2R^2$  that is  $|Z_{in}| = \frac{R}{0.707}$   $Re(P_{in}) = \frac{1}{2}Re(P_{in})|_{\omega=\omega_0}$

From  $Z_{in} \cong R + \frac{j2\Delta\omega RQ_0}{\omega_0}$ ,  $|Z_{in}|^2 = R^2 + \frac{4\Delta\omega^2 R^2 Q_0^2}{\omega_0^2} = 2R^2$

$\Rightarrow \left(\frac{2\Delta\omega}{\omega_0}\right)^2 = \frac{1}{Q_0^2}$  Therefore, fractional bandwidth  $\frac{2\Delta\omega}{\omega_0} = \frac{1}{Q_0}$

### Series RLC Circuit

Let us now consider half power fractional bandwidth of the resonator

We have  $P_{in} = \frac{1}{2}VI^* = \frac{1}{2}Z_{in} \left| \frac{V}{Z_{in}} \right|^2$  Therefore,  $Re(P_{in}) = \frac{1}{2}R \left| \frac{V}{Z_{in}} \right|^2$

When  $\omega = \omega_0$ ,  $Z_{in} = R$  and  $Re(P_{in})|_{\omega=\omega_0} = \frac{|V|^2}{2R}$

When  $|Z_{in}|^2 = 2R^2$  that is  $|Z_{in}| = \frac{R}{0.707}$   $Re(P_{in}) = \frac{1}{2}Re(P_{in})|_{\omega=\omega_0}$

From  $Z_{in} \approx R + \frac{j2\Delta\omega RQ_0}{\omega_0}$ ,  $|Z_{in}|^2 = R^2 + \frac{4\Delta\omega^2 R^2 Q_0^2}{\omega_0^2} = 2R^2$

$\Rightarrow \left(\frac{2\Delta\omega}{\omega_0}\right)^2 = \frac{1}{Q_0^2}$  Therefore, fractional bandwidth  $\frac{2\Delta\omega}{\omega_0} = \frac{1}{Q_0}$

### Series RLC Circuit

Therefore,  $Q_0 = \omega_0 \frac{2W_m}{P_{loss}}$   
 $Q_0 = \omega_0 \frac{|I|^2 L}{|I|^2 R} = \omega_0 \frac{L}{R}$

Since  $\omega_0^2 = \frac{1}{LC}$   
 $Q_0 = \frac{1}{\omega_0 RC}$

Let us now study the behavior of the input impedance of a series RLC resonator near its resonance

$$Z_{in} = R + j\omega L \left( \frac{\omega^2 - \omega_0^2}{\omega^2} \right)$$

In the vicinity of resonance,

$$\omega^2 - \omega_0^2 = (\omega - \omega_0)(\omega + \omega_0) \approx 2\omega\Delta\omega$$

For small  $\Delta\omega$ ,

$$Z_{in} \approx R + j\omega L \frac{2\omega\Delta\omega}{\omega^2} \approx R + j2\Delta\omega L$$

$$Z_{in} \approx R + \frac{j2\Delta\omega RQ_0}{\omega_0}$$

Let us now consider half-power fractional bandwidth of the resonator. Now, we have  $P_{in}$  is equal to half VI conjugates which can be written as  $\frac{1}{2} Z_{in} V$  by  $Z_{in}$  mod whole square and therefore the real part of  $P_{in}$  becomes real part of  $Z_{in}$  is R. So,  $\frac{1}{2} R V$  by  $Z_{in}$  mod square and when  $\omega$  is equal to  $\omega_0$  we have seen that  $Z_{in}$  is equal to R and therefore real part of  $P_{in}$  at  $\omega$  equal to  $\omega_0$  this becomes equal to  $\frac{1}{2} V^2$  by  $2R$ .

And if you remember we have seen that mod  $Z_{in}$ , we mark the line when mod  $Z_{in}$  becomes equal to R by 0.707 that means  $\sqrt{2}R$ . So, mod  $Z_{in}$  square at those frequencies become  $2R^2$  square and when mod  $Z_{in}$  square becomes equal to  $2R^2$  square, the real part of  $P_{in}$  becomes half of real part of  $P_{in}$  at  $\omega$  equal to  $\omega_0$ .

So, that is why this frequency points are called half-power points, and in the plot shown we see that we have two such points, one below  $\omega_0$  and one is above  $\omega_0$  and from this expression  $Z_{in}$  is equal to  $R + j 2 \Delta \omega R Q$  by  $\omega_0$  we can find the modulus of  $Z_{in}$  square and this becomes  $R^2 + 4 \Delta \omega^2 R^2 Q^2$  by  $\omega_0^2$  and we can equate this to  $2R^2$  square.

So, once we do that we will get if you can take out  $R^2$  common from here then  $R^2$  will get cancel from both side, will be left with 1 here and when it is subtracted from here then we will get  $4 \Delta \omega^2 Q^2$  by  $\omega_0^2$  is equal to 1, and therefore we can write  $2 \Delta \omega$  by  $\omega_0$  whole square is equal to  $1$  by  $Q^2$  and this quantity  $2 \Delta \omega$  by  $\omega_0$  this quantity we defined as fractional bandwidth, and therefore we see that the fractional bandwidth is given by  $1$  by  $Q$ .

So, higher the value of Q the fractional bandwidth will be narrower and we have seen that  $Q$  is given by  $\omega_0 L$  by R. So, if R increases, the power loss in the circuit increases Q will decrease and we will have larger fractional bandwidth whereas if R is very small then Q will be large and fractional bandwidth will be very small.

(Refer Slide Time: 16:01)



## Series RLC Circuit

Let us now consider half power fractional bandwidth of the resonator

$$\text{We have } P_{in} = \frac{1}{2} V I^* = \frac{1}{2} Z_{in} \left| \frac{V}{Z_{in}} \right|^2 \quad \text{Therefore, } Re(P_{in}) = \frac{1}{2} R \left| \frac{V}{Z_{in}} \right|^2$$

$$\text{When } \omega = \omega_0, Z_{in} = R \text{ and } Re(P_{in})|_{\omega=\omega_0} = \frac{|V|^2}{2R}$$

$$\text{When } |Z_{in}|^2 = 2R^2 \text{ that is } |Z_{in}| = \frac{R}{0.707} \quad Re(P_{in}) = \frac{1}{2} Re(P_{in})|_{\omega=\omega_0}$$

$$\text{From } Z_{in} \approx R + \frac{j2\Delta\omega R Q_0}{\omega_0}, \quad |Z_{in}|^2 = R^2 + \frac{4\Delta\omega^2 R^2 Q_0^2}{\omega_0^2} = 2R^2$$

$$\Rightarrow \left( \frac{2\Delta\omega}{\omega_0} \right)^2 = \frac{1}{Q_0^2} \quad \text{Therefore, fractional bandwidth } \frac{2\Delta\omega}{\omega_0} = \frac{1}{Q_0}$$

So, for a highly tune circuit or a very narrow band resonator, we will have large value of  $Q$  naught, and for that we will have  $R$  to be very small.

(Refer Slide Time: 16:21)


For the parallel RLC circuit shown in the figure:

$$Z_{in} = \frac{1}{\left(\frac{1}{R} + \frac{1}{j\omega L} + j\omega C\right)} = \frac{1}{\left(\frac{1}{R} - \frac{j}{\omega L}(1 - \omega^2 LC)\right)}$$

$$Z_{in} = \frac{\frac{1}{R} + j\left(\frac{1 - \omega^2 LC}{\omega L}\right)}{\left(\frac{1}{R}\right)^2 + \left(\frac{1 - \omega^2 LC}{\omega L}\right)^2}$$

$Re(Z_{in})$  attains its maximum value  $R$  at the resonance frequency

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

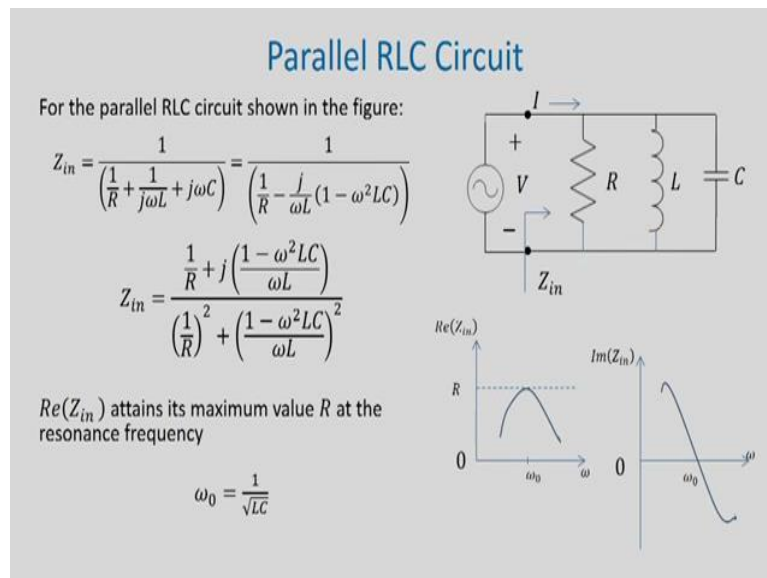

Let us now consider the properties of parallel RLC circuit near its resonance. So, the parallel RLC circuit is shown in the figure. For this type of a circuit we can write  $Z_{in}$  is equal to  $1$  by  $1$  by  $R$  plus  $1$  by  $j\omega L$  plus  $j\omega C$  and this can be written as  $1$  by  $1$  by  $R$  minus  $j$  by  $\omega L$   $1$  minus  $\omega^2 LC$ . Now, we can find out the real and imaginary parts of  $Z_{in}$  if we multiply the numerator and the denominator by the complex conjugate of this term.

Now, real  $Z_{in}$  will attend it is maximum value  $R$  at the resonant frequency, and at the resonant frequency the imaginary  $Z_{in}$  will be zero and this resonant frequency is given by  $\omega_0$  which is equal to  $1$  by root  $LC$ . Now this plot show the roughly the nature of variation of real part of  $Z_{in}$  and imaginary part of  $Z_{in}$  with frequency.

And we see that for a parallel RLC circuit below the resonant frequency  $\omega_0$  it will be inductive in nature and above  $\omega_0$  it will be capacitive in nature. In a series RLC circuit, we saw that below resonant frequency  $\omega_0$  the circuit behaves like a capacitive circuit while above resonant frequency it is an inductive circuit.

(Refer Slide Time: 19:00)

For such parallel RLC circuit

$$Q_0 = \omega_0 RC = \frac{R}{\omega_0 L}$$

Near resonance  $\omega = \omega_0 + \Delta\omega$

$$Z_{in} = \left( \frac{1}{R} + j\omega C + \frac{1}{j\omega L} \right)^{-1} = \left( \frac{1}{R} + j\omega_0 C + j\Delta\omega C + \frac{1}{j(\omega_0 + \Delta\omega)L} \right)^{-1}$$

$$Z_{in} = \left( \frac{1}{R} + j\omega_0 C + j\Delta\omega C + \frac{1}{j\omega_0 L(1 + \Delta\omega/\omega_0)} \right)^{-1}$$

When  $\Delta\omega/\omega_0 \ll 1$  we can use the approximation  $1/(1 + \Delta\omega/\omega_0) \cong 1 - \Delta\omega/\omega_0$

$$Z_{in} \cong \left( \frac{1}{R} + j\omega_0 C + j\Delta\omega C + \frac{1}{j\omega_0 L} - \frac{\Delta\omega}{j\omega_0^2 L} \right)^{-1}$$

**Parallel RLC Circuit**

For such parallel RLC circuit

$$Q_0 = \omega_0 RC = \frac{R}{\omega_0 L}$$


Near resonance  $\omega = \omega_0 + \Delta\omega$

$$Z_{in} = \left( \frac{1}{R} + j\omega C + \frac{1}{j\omega L} \right)^{-1}$$

$$= \left( \frac{1}{R} + j\omega_0 C + j\Delta\omega C + \frac{1}{j(\omega_0 + \Delta\omega)L} \right)^{-1}$$

$$Z_{in} = \left( \frac{1}{R} + j\omega_0 C + j\Delta\omega C + \frac{1}{j\omega_0 L(1 + \Delta\omega/\omega_0)} \right)^{-1}$$

When  $\Delta\omega/\omega_0 \ll 1$  we can use the approximation  $1/(1 + \Delta\omega/\omega_0) \approx 1 - \Delta\omega/\omega_0$
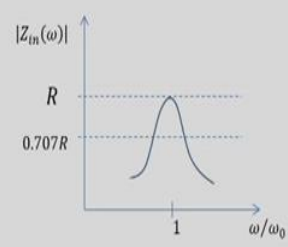
$$Z_{in} \approx \left( \frac{1}{R} + j\omega_0 C + j\Delta\omega C + \frac{1}{j\omega_0 L} - \frac{\Delta\omega}{j\omega_0^2 L} \right)^{-1}$$


Now,  $Q$  is the unloaded  $Q$  factor for such resonant circuit can be found out and  $Q$  will be equal to  $\omega_0 RC$  and which is also  $R$  by  $\omega_0 L$ . Near it is resonance the frequency angular frequency  $\omega$  can be written as  $\omega_0 + \Delta\omega$  and  $Z_{in}$  once we substitute  $\omega$  is equal to  $\omega_0 + \Delta\omega$  can be expressed in this form.

And if we plot the variation of magnitude of  $Z_{in}$  with respect to  $\omega$  by  $\omega_0$  then we will have the maximum value of the magnitude of  $Z_{in}$  at  $\omega$  equal to  $\omega_0$  that means when this ratio is 1, and we will see that half-power points will be for magnitude of  $Z_{in}$   $\omega$  to be equal to 0.707 of its maximum value that is  $R$ . Now, this term we can do some approximation particularly because of the fact that  $\Delta\omega$  by  $\omega_0$  is very, very less as compared to 1 when we are operating the circuit near the resonant frequency  $\omega_0$ .

So, what we can do? This term  $1 + \Delta\omega$  by  $\omega_0$ , this can be approximated as  $1 - \Delta\omega$  by  $\omega_0$ . So, once we substitute this approximation then we get  $Z_{in}$  to be equal to  $1/R + j\omega_0 C + j\Delta\omega C + \frac{1}{j\omega_0 L} - \frac{\Delta\omega}{j\omega_0^2 L}$  entire thing raised to the power minus 1.

(Refer Slide Time: 22:44)

$$Z_{in} = \left( \frac{1}{R} + j\omega_0 C + j\Delta\omega C + \frac{1}{j\omega_0 L} - \frac{\Delta\omega}{j\omega_0^2 L} \right)^{-1}$$

$$Z_{in} = \left( \frac{1}{R} + j\Delta\omega C + \frac{j\Delta\omega}{\omega_0^2 L} \right)^{-1}$$

$$Z_{in} = \left( \frac{1}{R} + j\Delta\omega C + j\Delta\omega C \right)^{-1} = \frac{R}{1 + j2\Delta\omega RC}$$

Since  $Q_0 = \omega_0 RC$ ,

$$Z_{in} = \frac{R}{1 + j2\Delta\omega Q_0/\omega_0}$$

## Parallel RLC Circuit

$$Z_{in} \approx \left( \frac{1}{R} + j\omega_0 C + j\Delta\omega C + \frac{1}{j\omega_0 L} - \frac{\Delta\omega}{j\omega_0^2 L} \right)^{-1}$$

$$Z_{in} = \left( \frac{1}{R} + j\Delta\omega C + \frac{j\Delta\omega}{\omega_0^2 L} \right)^{-1}$$

$$Z_{in} = \left( \frac{1}{R} + j\Delta\omega C + j\Delta\omega C \right)^{-1} = \frac{R}{1 + j2\Delta\omega RC}$$

Since  $Q_0 = \omega_0 RC$ ,

$$Z_{in} = \frac{R}{1 + j2\Delta\omega Q_0/\omega_0}$$

Now, this is the form of  $Z_{in}$  we have seen, and these two terms  $j\omega_0 C$  plus  $1/j\omega_0 L$  when combined will give  $1 - \omega_0^2 LC$  and therefore these two terms will cancel out. So, we find that this  $j\omega_0 C$  and  $1/j\omega_0 L$  when combining they will give a term like  $1 - \omega_0^2 LC$  and therefore it will become the sum of these two terms will become 0 and we will be left with  $Z_{in}$  equal to  $1/R$  plus  $j\Delta\omega C$  plus  $j\Delta\omega$  by  $\omega_0^2 L$  whole raised to the power minus 1.

Now, once we substitute  $\omega_0^2 LC = 1$  here we will see that this term  $j\Delta\omega$  by  $\omega_0^2 L$  will be reduced to  $j\Delta\omega C$  and therefore  $Z_{in}$  can be written as  $1/R$  plus  $j\Delta\omega C$  from here and another  $j\Delta\omega C$  from here whole raised to the power minus 1 and therefore it can be written as  $R$  divided by  $1 + j2\Delta\omega RC$ .

Since we have  $Q_0$  is equal to  $\omega_0 RC$ , therefore, we can now write  $Z_{in}$  equal to  $R$  divided by  $1 + j2\Delta\omega Q_0/\omega_0$ . So, this expression of input impedance gives the input impedance of the parallel resonant circuit near its resonance, and you can see that this expression also includes  $Q_0$  the unloaded Q factor and also  $\omega_0$  the angular resonant frequency.

(Refer Slide Time: 26:10)

$$Re(P_{in}) = \frac{1}{2} V \left( \frac{V}{R} \right)^* = \frac{1}{2} \frac{|V|^2}{R} = \frac{1}{2} |I|^2 |Z_{in}|^2 \frac{1}{R}$$

At resonance  $Re(P_{in})|_{\omega=\omega_0} = \frac{1}{2} |I|^2 R$

Therefore,  $\frac{Re(P_{in})}{Re(P_{in})|_{\omega=\omega_0}} = \frac{|Z_{in}|^2}{R^2}$

For  $\frac{Re(P_{in})}{Re(P_{in})|_{\omega=\omega_0}}$  to become  $\frac{1}{2}$ ,  $\frac{R^2}{2} = |Z_{in}|^2$

From  $Z_{in} = \frac{R}{1+j2\Delta\omega Q_0/\omega_0}$ ,  $2\Delta\omega Q_0/\omega_0 = 1$

Therefore, fractional bandwidth  $2\Delta\omega/\omega_0 = 1/Q_0$

### Parallel RLC Circuit

$$Re(P_{in}) = \frac{1}{2} V \left( \frac{V}{R} \right)^* = \frac{1}{2} \frac{|V|^2}{R} = \frac{1}{2} |I|^2 |Z_{in}|^2 \frac{1}{R}$$

At resonance  $Re(P_{in})|_{\omega=\omega_0} = \frac{1}{2} |I|^2 R$

Therefore,  $\frac{Re(P_{in})}{Re(P_{in})|_{\omega=\omega_0}} = \frac{|Z_{in}|^2}{R^2}$

For  $\frac{Re(P_{in})}{Re(P_{in})|_{\omega=\omega_0}}$  to become  $\frac{1}{2}$ ,  $\frac{R^2}{2} = |Z_{in}|^2$

From  $Z_{in} = \frac{R}{1+j2\Delta\omega Q_0/\omega_0}$ ,  $2\Delta\omega Q_0/\omega_0 = 1$

Therefore, fractional bandwidth  $2\Delta\omega/\omega_0 = 1/Q_0$

Now, let us develop the expression for the fractional bandwidth. From the parallel RLC circuit, we see that real part of P in input power is equal to half V the voltage it is a parallel RLC circuit so the voltage will be same across all the elements. So, it is half V, V by R conjugate and V by R is essentially the current through the resistance and therefore we can write it half mod V square by R and which is equal to half I square mod of Z<sub>in</sub> square divided by R because V is written as I into Z<sub>in</sub>.

Now, at resonance that means when omega equal to omega naught real part of P<sub>in</sub> becomes equal to half mod of I square R because we have seen that at omega equal to omega naught mod Z<sub>in</sub> become equal to R and therefore we can now write real part of P<sub>in</sub> divided by real part of P<sub>in</sub> at omega equal to omega naught this can be written as mod of Z<sub>in</sub> square divided by R

square and for this quantity to become half because we are talking of half-power bandwidth we must have  $R$  square by 2 equal to mod of  $Z_{in}$  square.

Now, we already have an expression for the approximate input impedance of the parallel RLC circuit near it is resonant frequency and therefore we can write from  $Z_{in}$  is equal to  $R$  divided by  $1 + j 2 \Delta \omega Q$  naught by  $\omega$  naught from this expression we can see that mod  $Z_{in}$  square will become  $R$  square by 2 when we have  $2 \Delta \omega Q$  naught by  $\omega$  naught is equal to 1.

And the fractional bandwidth is given by  $2 \Delta \omega$  by  $\omega$  naught, and therefore once again, we find that just as the case of series RLC circuit the fractional bandwidth  $2 \Delta \omega$  by  $\omega$  naught is equal to  $1$  by  $Q$  naught. That means for higher  $Q$  the fractional bandwidth will be very less and for lower  $Q$  we will have larger fractional bandwidth.

(Refer Slide Time: 29:58)

Let the loading of the external circuit be represented by a load resistance  $R_L$  and the  $Q$  of the external circuit by  $Q_e$ .

Let  $Q_L$  be the  $Q$  of the loaded circuit.

For series RLC circuit  $Q_L = \omega_0 \frac{L}{R+R_L}$  Therefore,  $\frac{1}{Q_L} = \frac{R+R_L}{\omega_0 L} = \frac{1}{Q_0} + \frac{1}{Q_e}$

Similarly, for a parallel RLC circuit  $R$  and  $R_L$  are in parallel and

$Q_L = \frac{RR_L}{\omega_0(R+R_L)L}$  Therefore,  $\frac{1}{Q_L} = \frac{\omega_0(R+R_L)L}{RR_L} = \frac{1}{Q_e} + \frac{1}{Q_0}$

### Loaded Q

The unloaded  $Q$  of a circuit  $Q_0$  is the quality factor of the circuit without any external loading

In practice, external circuitry connected to the resonator will produce loading effect.

Let the loading of the external circuit be represented by a load resistance  $R_L$  and the  $Q$  of the external circuit by  $Q_e$ .

Let  $Q_L$  be the  $Q$  of the loaded circuit.

For series RLC circuit  $Q_L = \omega_0 \frac{L}{R+R_L}$  Therefore,  $\frac{1}{Q_L} = \frac{R+R_L}{\omega_0 L} = \frac{1}{Q_0} + \frac{1}{Q_e}$

Similarly, for a parallel RLC circuit  $R$  and  $R_L$  are in parallel and

$Q_L = \frac{RR_L}{\omega_0(R+R_L)L}$  Therefore,  $\frac{1}{Q_L} = \frac{\omega_0(R+R_L)L}{RR_L} = \frac{1}{Q_e} + \frac{1}{Q_0}$

Now, so far we were discussing  $Q$  naught the unloaded  $Q$ . Let us now consider another form of quality factor, which is called the Loaded  $Q$ . The unloaded  $Q$  of a circuit  $Q$  naught is the quality factor of the circuit without any external loading. In practice, external circuitry that will be connected to the resonator will produce loading effect and let us see how we can take this loading effect into account.

Let us represent the loading of the external circuit by a load resistance  $R_L$  and  $Q$  of the external circuit by  $Q_e$  and  $Q_L$  with a  $Q$  of the loaded circuit. Now, when we consider series RLC circuit our external resistance  $R_L$  will come in series with the resistance of the RLC circuit  $R$  and therefore the effective resistance will be  $R$  plus  $R_L$  and therefore by definition of  $Q$  we can write  $Q_L$  that of the loaded circuit is equal to  $\omega$  naught  $L$  divided by  $R$  plus  $R_L$ .

If you write  $1$  by  $Q_L$  then it becomes  $R$  plus  $R_L$  divided by  $\omega$  naught  $L$ , and this term  $R$  divided by  $\omega$  naught  $L$  can be written as  $1$  by  $Q$  naught and  $R_L$  divided by  $\omega$  naught  $L$  can be written as  $1$  by  $Q_e$ . So, the  $Q$  of the loaded RLC series RLC circuit  $1$  by  $Q_L$  is  $1$  by  $Q$  naught the unloaded  $Q$  plus  $1$  by  $Q_e$  the  $Q$  of the external circuit. Let us now consider the parallel RLC circuit.

In case of parallel RLC circuit, the external resistance  $R_L$  will come in parallel with  $R$  and the effective resistance will now be  $R$  into  $R_L$  divided by  $R$  plus  $R_L$  and therefore for a parallel circuit  $Q_L$  can be written as  $RR$   $L$  divided by  $\omega$  naught  $R$  plus  $R_L$  into  $L$  and if we write  $1$  by  $Q_L$  can be written as  $\omega$  naught  $R$  plus  $R_L$  into  $L$  divided by  $RR$   $L$  and when this is separated then we will get  $\omega$  naught  $L$  by  $R_L$  which is  $1$  by  $Q_e$  plus  $\omega$  naught  $L$  by  $R$  which is  $1$  by  $Q$  naught.

So, once again we find that for a parallel RLC circuit also  $1$  by  $Q_L$  is equal to  $1$  by  $Q_e$  plus  $1$  by  $Q$  naught. So, once we know the unloaded  $Q$  of the series or parallel RLC circuit and we know the external loading that means  $R_L$  we can find out the  $Q$  of the loaded circuit. So, we have studied series RLC and parallel RLC circuits and particularly how such circuits behave near their resonant frequency.

Next we will see how transmission line sections either short or open can act as resonators and also near the resonant frequency of how we can model this type of transmission line resonators by equivalent RLC circuit.