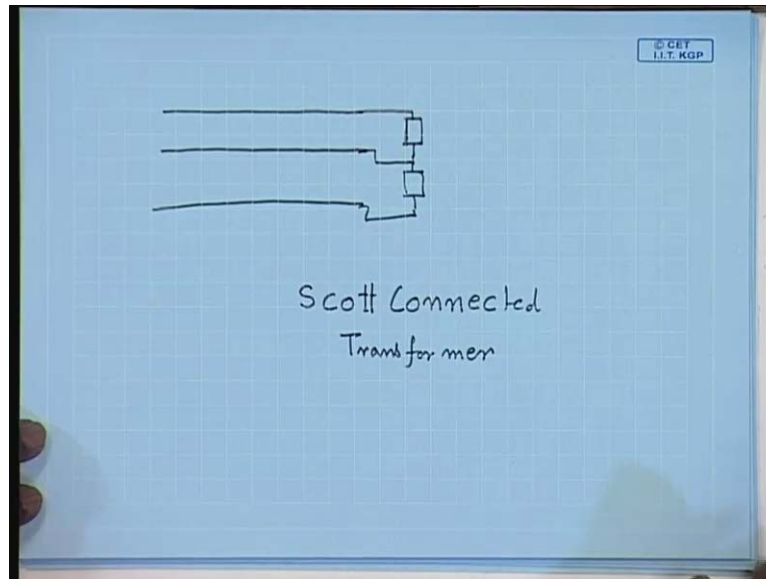


Electrical Machines - I
Prof. D. Kastha
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture - 19
Scott Connected Transformers


(Refer Slide Time: 00:39)



In many situations it becomes necessary to supply a balanced or unbalanced two phase or three single phase load on a balanced three phase supply. One way to do, let us say for a two phase load to connect the two phases between two lines, this is one possibility; however, even when these phases are balanced impedances are balanced, they will draw unbalanced current from the supply. Not only that many two phase loads will require a balanced two phase supply as well.

Some of this two phase loads are large art furnaces or induction melting furnaces. The power can range in megawatts. So, care should be taken to make sure that the loading of the three phase system is balanced to the extent possible. This can be done by what is called a Scott connected transformer. This Scott connected transformer can convert a balanced three phase supply to a balanced two phase supply. If the load on the two phase supply is balanced, then the line current drawn from the three phase will also be balanced, we will see how?

(Refer Slide Time: 02:32)

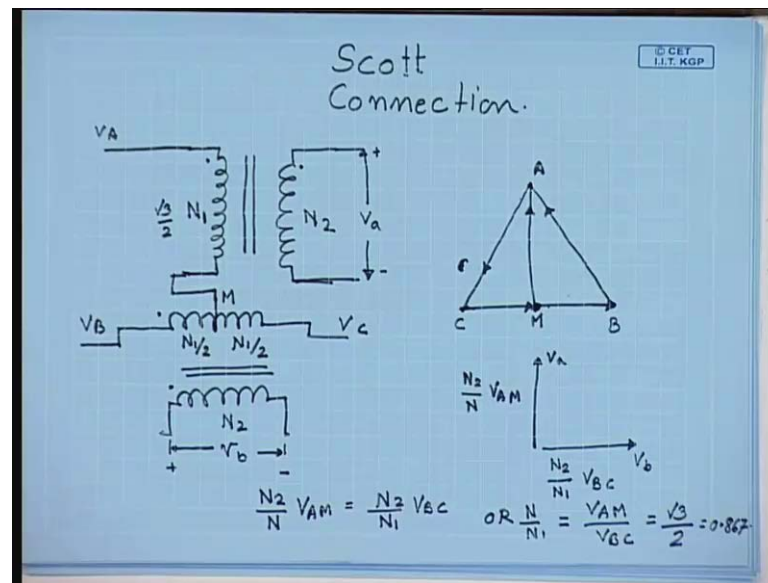


For Scott connection, we take two single phase transformers; let us say here the turns is N . This turn is N_2 , this is the dot polarity; another transformer with a 50 percent tapping, so that this number of turns is N_1 by 2 and this is N_1 by 2, and the corresponding secondary have the same number of turns N_2 . Now let us connect this end of one of the transformers to the 50 percent tapping point and keep balanced three phase supply to this side; that is V_A , V_B and V_C . And let us see what happens to the induced voltages here. This is the instantaneous polarity here; here this is the instantaneous polarity.

So, the three phase supply is balanced. So, let this point be M . So, let us say this is the phasor V_{bC} and this is the phasor A , so that this is the phasor V_{aB} ; this is the phasor V_{cA} . Now the voltage phasor V_{mC} , V_{mC} will be half of V_{bC} . This is the point M V_{mC} , and what will be the voltage phasor V_{aM} ? V_{aM} will be V_{aC} minus V_{mC} , V_{aC} minus V_{mC} ; V_{aC} is in this direction, this is V_{mC} . So, the voltage phasor V_{aM} will be this. It shows that the voltage phasor V_{aM} is at right angle to the voltage phasor V_{bC} . Hence, the induced voltage V_a will be in phase with the voltage V_{aM} .

So, this will be the voltage V_a , and its magnitude will be N_2 by N into V_{aM} , whereas the voltage phasor V_b will be in phase with the voltage V_{bC} . So, this will be the voltage phasor V_b , and its magnitude will be N_2 by N_1 into V_{bC} . Now if we want the voltages V_{aB} and V_{bC} to be balanced two phase that is they are already 90 degree,

and if we want their magnitudes also to be same, then it is imperative that we should have N_2 by N_1 into V_a should be equal to N_2 by N_1 into V_b . Or we want N_1 should be equal to V_a by V_b . Now from this phasor diagram V_a by V_b equal to $\sqrt{3}$ by 2 or equal to 0.867. Hence, number of turns should be here $\sqrt{3}$ by 2 into N_1 .

(Refer Slide Time: 09:03)

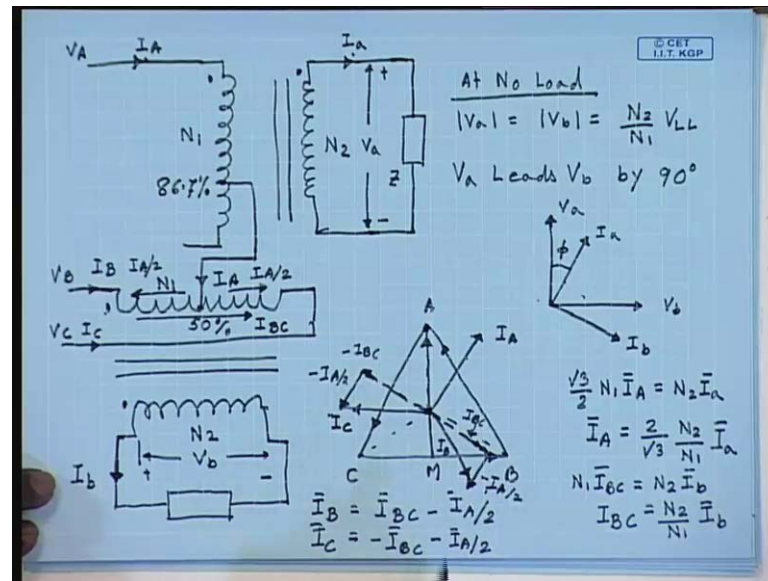

So, a Scott connected transformer can be obtained by two single phase transformers with turns N_1 and N_2 . The first term any suitable turns ratio N_1 by N_2 with one transformer having a tapping at 86.7 percent, the other transformer having a tapping at 50 percent. Now we connect the 86.7 percent tapping to the 50 percent tapping, and then give three phase balanced supply in this manner V_A , V_B , V_C in which case we have just seen that the induced voltages V_a and V_b . This instantaneous polarity we have seen at no load mod of V_a equal to mod of V_b equal to N_2 by N_1 into V_{LL} of the primary, and V_a leads V_b by 90 degree. So, this is at no load.

Now let us see what happens. So, at no load we have got a balanced two phase system. Now let us see what happens if we connect a balanced load of some arbitrarily power factor; that is we connect two impedances Z to this transformer. Once we connect impedance Z there will be a current I_a flowing in this and I_b flowing in this. Now this is V_a ; this is V_b . If these are balanced impedances, then this will be I_a and this will be I_b . The currents will also be balanced with a power factor angle of ϕ .

What will happen to the primary currents? Let us see that. Let us say the primary currents are I_A here, I_B here and I_C here. If we neglect the magnetization current of the transformers which are very small in any case, then I_A $I_{\text{capital A}}$ will be the reflection of $I_{\text{small a}}$. Hence, $I_{\text{capital A}}$ and I_a will be in phase. So, the voltage phasor diagram on the primary side is somewhat like this. This is C, this is B, this is A, this is voltage V_{bc} , this is A_B , this is C_A , this is voltage A_M . So, the current capital I_A , this is the neutral point of the supply voltage. The current capital I_A will be in phase with I_a .

So, we can draw the current capital I_A represented by this line I_A , and the ratio will be $\sqrt{3} \text{ by } 2 N_1 I_A$ should be equal to $N_2 I_{\text{small a}}$ or I_A equal to $2 \text{ by } \sqrt{3} N_2 \text{ by } N_1$ into I_a . Similarly, please note that in the secondary the current is going out of the dot terminal; hence, in the primary the current must enter into the dot terminal. Similarly, for the other transformer the current I_B is flowing out of the transformer. Hence, the reflection current I_{bc} should be in this direction; reflection current I_{bc} flows through the entire winding. So, $N_1 I_{bc}$ should be equal to $N_2 I_b$ or I_{bc} equal to $N_2 \text{ by } N_1 I_B$, but the line currents are not just I_{bc} . The current I_A is coming here, and then it divides in two equal parts.

This current is $I_A \text{ by } 2$, and this current is $I_A \text{ by } 2$; the phase current I_B then equal to $I_{bc} \text{ minus } I_A \text{ by } 2$. Now I_{bc} will be in phase with I_B . This is the current I_{bc} . This is $\text{minus } I_{bc}$; this is I_{bc} . So, phase current I_B will be $I_{bc} \text{ minus } I_A \text{ by } 2$. So, this will be the phase current I_B . Similarly, the phase current I_C will be $\text{minus } I_{bc} \text{ minus } I_A \text{ by } 2$. So, this is $\text{minus } I_{bc} \text{ minus } I_A \text{ by } 2$. So, this will be the current I_C . It can be easily shown that I_A, I_B, I_C is balanced. The reason is very simple. Since, I_A and I_B are orthogonal to each other so are I_A and I_{bc} . In other words I_{bc} is at ninety degree with I_a . So, the angle between I_{bc} and $\text{minus } I_A \text{ by } 2$ is 90 degree.


(Refer Slide Time: 19:34)

$$\begin{aligned}
 |I_B| &= [|I_{Bc}|^2 + |I_{A/2}|^2]^{1/2} \\
 &= [\left(\frac{N_2}{N_1} \right)^2 |I_b|^2 + \left(\frac{N_2}{N_1} \right)^2 \left(\frac{1}{2} \frac{2}{\sqrt{3}} |I_A| \right)^2]^{1/2} \\
 &= \frac{N_2}{N_1} |I_A| \left[1 + \frac{1}{3} \right]^{1/2} = \frac{N_2}{N_1} \frac{2}{\sqrt{3}} |I_A| = |I_A| \\
 |I_C| &= |I_B| = |I_A|
 \end{aligned}$$

Therefore, the phase current I B magnitude will equal to mod I b C square plus mod I A by 2 square to the power half, but I b C we have seen it to be N 2 by N1 square mod I b square and I A by 2 plus I A by 2 is N 2 by N 1 square into half into 2 by root 3 mod I a square to the power half. This is equal to N 2 by N 1 into; now in a balanced two phase system mod I B is same as mod I A. So, I can say this is equal to I a, 1 plus one-third to the power half. This is equal to N 2 by N 1 2 by root 3 mod of I a. This is same as the mod of I capital A. Similarly, it can be shown that mod of I C equal to mod of I B equal to mod of I A.

The angle between them is also 120 degree. This can be seen very easily. This is the phasor I A; this is the phasor I B, and this is the phasor I A by 2, but mod of I B we have just shown to be equal to I A. So, this length is half of this length. Hence, this angle is 30 degree, but this angle is 90 degree. Hence, this angle is 120 degrees. Similarly, this angle is also 120 degrees. So, we see when we put a balanced two phase load on the Scott connected transformer secondary of arbitrary power factor, it does not necessarily have to be unity power factor, then the three phase side currents are also balanced. What happens when we connect an unbalanced load?

(Refer Slide Time: 24:01)

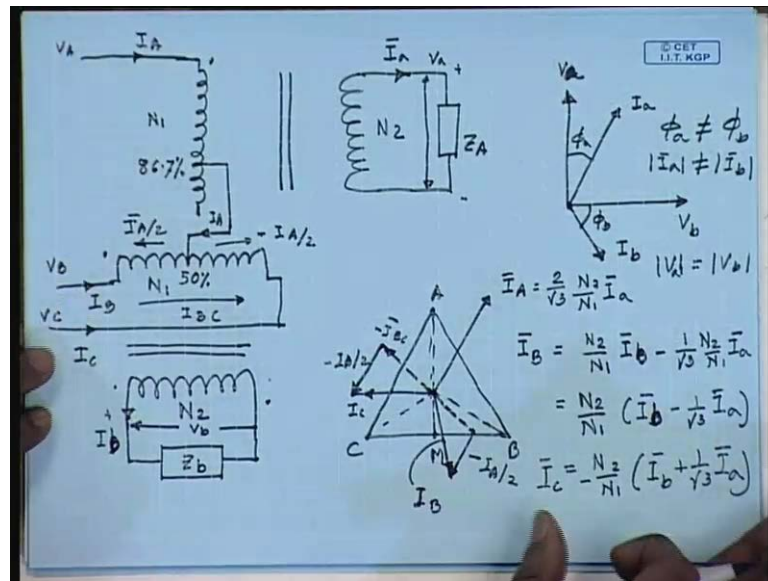


Let us draw the same circuit diagram. Now we have connected an unbalanced load Z_A to the voltage V_a , the current is again I_A and another load Z_B the source V_b . The currents drawn here is I_A, I_B, I_C . We can draw the phasor diagram in a similar manner. On the secondary side, the voltages are still balanced though, because the supplied three phase voltage is balanced. So, this is V_a , this is V_b . Now let us say this is I_a , and this is I_b . They are unbalanced both in magnitude and in phase angle. This is ϕ_a , this is ϕ_b , unbalanced; hence, ϕ_a is not equal to ϕ_b and $\text{mod } I_a$ is not equal to $\text{mod } I_b$, but nevertheless $\text{mod } V_a$ is still equal to $\text{mod } V_b$.

So, let us see on the three phase side, what will happen? This is the three phase voltage phasor line voltage phasors A, B, C. This is M, this is, say, N. So, as in the previous case the line current will be I_A , if this will be still be $\frac{2}{\sqrt{3}} \frac{N_2}{N_1} I_a$. This will still be I_B, I_C . This is $-I_B, I_C$ and I_B is I_B, I_C minus I_A by 2. This will be the current I_B and I_C will be minus I_B, I_C minus I_A by 2; obviously, the three phase currents are no longer balanced, but still they will be given by the same formula.

I_B will be I_B, I_C which is $\frac{N_2}{N_1} I_b$ minus $\frac{1}{\sqrt{3}} I_a$ minus $\frac{1}{\sqrt{3}} I_a$ by 2. This is I_A ; this is minus I_A by 2; this is I_A by 2. This current is I_B, I_C ; this current is I_b . I_a by 2, hence it is $\frac{1}{\sqrt{3}} \frac{N_2}{N_1} I_a$; that is equal to $\frac{N_2}{N_1} I_b$ minus $\frac{1}{\sqrt{3}} I_a$. Similarly, I_C will be minus of $\frac{N_2}{N_1} I_b$ plus $\frac{1}{\sqrt{3}} I_a$. How much this magnitudes will be, let us try to see with an example.


(Refer Slide Time: 31:27)

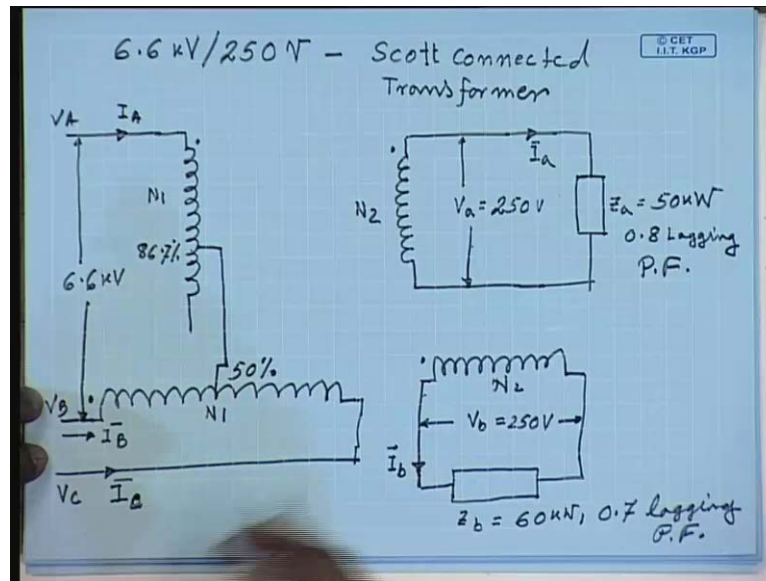

Say, we have a 6.6 kV by 250 volts Scott connected transformer the leading phase that is this is the 6.6 kV. This is N_1 ; this is N_1 at 50 percent tapping, at 86.7 percent tapping. The line voltage and this is V_A , V_B , V_C . The line voltage here is 6.6 kV, and this is the two phase side. This is V_{small} a nominally this is 250 volts. Similarly, this number of turns is N_2 here. Here this is also N_2 ; this is also V_B equal to 250 volts nominally.

Now the load on this transformer on the leading phase that is on phase A, I have connected a load Z_a which is equal to nominally 50 kilowatt; that is when the voltage is 250 volts, it is 50 kilowatt at 0.8 lagging power factor. And I have connected another load Z_b to the lagging phase. This current is I_a ; this current is I_b equal to this is 60 kilowatt at 0.7 lagging power factor; that is the load is unbalanced. So, neglecting no load current we are expected to find out what will be the three phase input currents I_A , I_B and I_C .

(Refer Slide Time: 35:40)

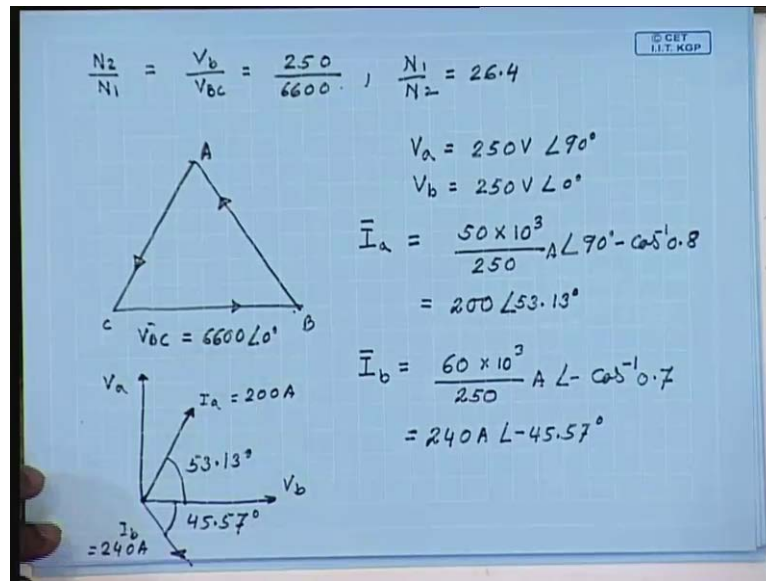

Obviously, the turns ratio N_2 by N_1 equal to V_b by V_{bc} equal to 250 divided by 6600 or N_1 by N_2 equal to 26.4. Now if we choose V_{bc} to be the reference phasor, this is 6600 angle 0 degree. This is V_{bc} ; this is V_{ab} ; this is V_{ca} . V_{bc} is the reference phasor, then we know V_a equal to 250 volts angle 90 degree and V_b equal to 250 volts angle 0 degree. Therefore, the load current I_a equal to 50 kilowatt divided by this is 50 KVA and by mistake this is 50 KVA at 0.8, and this is 60 KVA at 0.7.

So, the load current I_a is 50 KVA divided by 250 at an angle of 90 minus cos inverse 0.8 or I_a equal to 200 amperes at an angle of 53.13 degrees. Similarly, phasor I_b equal to 60 KVA divided by 250 amperes at an angle of minus cos inverse 0.7; that is I_b equal to 240 amperes at an angle of minus 45.57 degrees. So, this is V_a ; this is V_b . This is I_a equal to 200 amperes, and this angle is 53.13 degrees. This is I_b equal to 240 amperes, and this angle is 45.57 degrees. So, what will be the line current capital I_A ?

(Refer Slide Time: 40:37)


The image shows handwritten mathematical derivations for currents in a three-phase system. The equations are as follows:

$$\bar{I}_A = \frac{2}{\sqrt{3}} \cdot \frac{N_2}{N_1} \cdot \bar{I}_a = \frac{2}{\sqrt{3}} \cdot \frac{1}{26.4} \cdot 200 \angle 53.13^\circ$$
$$= 8.75 \text{ A} \angle 53.13^\circ$$
$$\bar{I}_{BC} = \frac{N_2}{N_1} \cdot \bar{I}_b = \frac{1}{26.4} \cdot 240 \angle -45.57^\circ = 9.091 \angle -45.57^\circ$$
$$\bar{I}_B = \bar{I}_{BC} - \frac{\bar{I}_A}{2} = 9.091 \text{ A} \angle -45.57^\circ - \frac{8.75}{2} \text{ A} \angle 53.13^\circ$$
$$= 10.67 \text{ A} \angle -69.48^\circ$$
$$\bar{I}_C = -\bar{I}_{BC} - \frac{\bar{I}_A}{2} = -9.091 \text{ A} \angle -45.57^\circ - \frac{8.75}{2} \text{ A} \angle 53.13^\circ$$
$$= 9.47 \text{ A} \angle 161.6^\circ$$

Capital I A we have seen is given by 2 by root 3 into N 2 by N 1 into I a. Hence, this comes to 2 by root 3 into 1 by 26.4 into 200 angle 53.13 degrees. This comes to 8.75 ampere at an angle of 53.13 degrees. Now I b C will be equal to N 2 by N 1 into I B. Hence, this will be 1 by 26.4 into 240 angle minus 45.57 degrees. This comes to 9.091 angle minus 45.57 degrees.

Therefore, the current I B will be equal to I b C minus I A by 2; that is 9.091 ampere angle minus 45.57 degrees minus 8.75 by 2 amperes angle 53.13 degrees. Once we do the calculation it comes to 10.67 ampere angle of minus 69.48 degrees. The phasor I C will be minus I b C minus I a by 2; that is minus 9.091 ampere angle minus 45.57 degrees minus 8.75 by 2 amperes angle. This comes to 9.47 amperes angle 161.6 degrees.


(Refer Slide Time: 44:42)

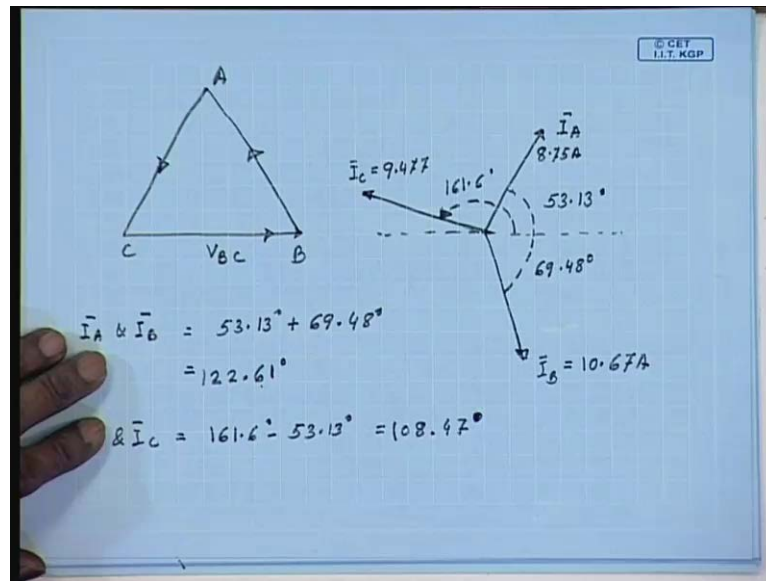

So, if we draw the phasor diagram we have taken V_{bc} to be the reference phasor, the current I_a is 8.75 amperes at an angle of 53.13 degrees. This is the reference direction. So, this is let us say current I_A . This angle is 53.13 degrees. The current I_B is 10.67 ampere at an angle of almost minus 70 degrees. So, this is I_B . This angle is 69.48 degrees; the magnitude is 10.67 amperes. On the other hand, I_C is somewhere here; magnitude is 9.47 amperes, and this angle with respect to reference is 161.6 degrees. So, what is the angle between different? For example, between I_A and I_B the angle is 53.13 degrees plus 69.48 degrees. This comes to between I_A and I_B this angle is 122.61 degrees.


Similarly, what is the angle between I_C and I_A ? This angle is 161.6 degrees minus 53.13 degrees; this angle is 108.47 degrees. So, we see that when the load current is unbalanced, the current supplied by the three phase side in a Scott connected transformer is also unbalanced. Now one extreme case of unbalance is of course, a single phase load; a Scott connected transformer can be used to supply a single phase load.

(Refer Slide Time: 48:40)

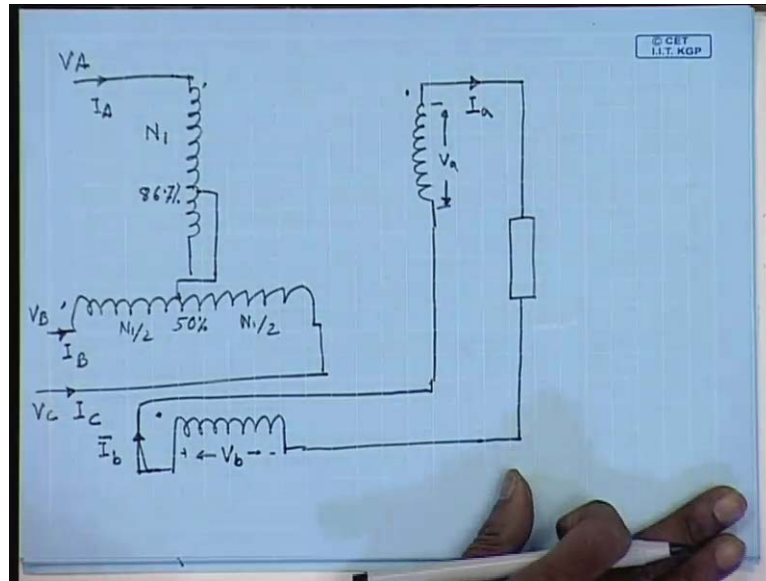

Same connection, this is 50 percent tapping; this is 86.7 percent tapping. For single supplying single phase load, we connect these two points. We connect the windings in series, and this is how the single phase load is connected. So, the current here is I_A ; this is the current I_b . If we look at the phasors this is the voltage V_b ; this is the voltage V_a .

(Refer Slide Time: 51:42)

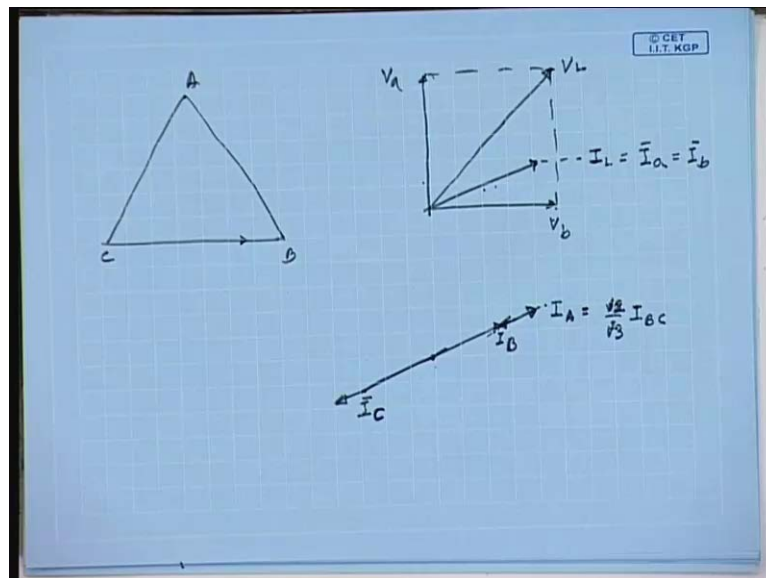

If we look at the phasor diagram this is the input side phasor; this is V_b ; this is V_a . The load voltage is V_L , I_a equal to I_B equal to I_l here. This is V_b ; this is V_a . Hence, the load voltage is the vector sum of V_a plus V_b which is here this is the load voltage V_L ,

and let us say this is the load current I_L equal to I_A equal to I_B . Hence, we see that this is a special case of unbalanced loading where the magnitudes of the two phase currents are same, but their phase angles are not same.

So, what will happen here? The current I_A will still be in the direction of I_L , but now I_B which is, this will also be the direction of I_C . This will actually be $\sqrt{3}$ by 2 times I_B , 2 by $\sqrt{3}$ times. So, I_B will be I_C minus I_A by 2. So, I_B will be somewhere here, and I_C will be minus I_B minus I_A by 2; I_C will be somewhere here. So, even in the three phase side the line currents will be all in phase; that is what happens when a Scott connected transformer secondary's are connected in series to supply a single phase load.

Thank you.