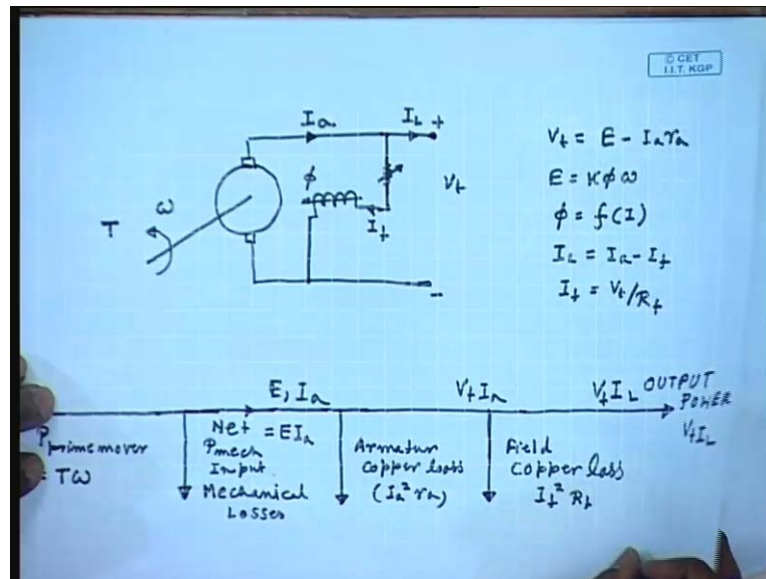


Electrical Machines - I
Prof. Dr. Debaprasad Kastha
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture - 30
Characteristics of DC Shunt Motors

(Refer Slide Time: 00:24)



In the last few classes, we have seen that a DC machine can work as a generator when its armature is rotated with a prime mover, and when excitation is provided to the field winding which produces the flux. However, when we have seen that we can connect a load, so that current will flow into it. However, it is not essential that a load is connected. Just a resistance is connected. It can as well be connected to a constant DC supply of voltage V_t . Even then it will work as a generator provided the prime mover can run the armature at a speed, such that the generated voltage E is larger than the terminal voltage V_t .


So, the armature current will flow in this direction. Since, the terminal of the generator I have already connected to a constant voltage source, we can as well connect the field winding across the armature. Now, it will not behave really as a shunt generator, but it will behave like a separately excited generator with a constant voltage applied across the field in order to vary field flux. It is possible to provide a resistance which can be controlled to control the field current. Now, for this generator, we can write V_t equal to E minus $I_a R_a$, where E equal to $k\phi\omega$. ϕ is given by the saturation

characteristics as function of I_f and I_L equal to I_a minus I_f , where I_f equal to V_t by R_f .

If we look at the power distribution, then you find that let the rotational speed of the shaft be ω and the torque provided by the prime mover be T , then the power input power output by the prime mover is P , mechanical P prime mover equal to $T \omega$. Now, the part of the power provided by the prime mover will be lost into mechanical loss that is frictional and windage losses. So, this is a part goes out as mechanical losses. So, this is the mechanical power provided to the net mechanical power input to the generator. This is equal to also $E I_a$.

Next power loss component is the armature copper loss $I_a^2 R_a$. Next loss is the field copper loss which is $I_f^2 R_f$. Finally, the rest is the output power which is $V_t I_L$. So, the current here is, this is voltage induced is E_a I_a . Here, the voltage is V_t I_a , and here the voltage and current is V_t I_L . So, this is how the power flow picture will look like in this is operating as a generator. Obviously, in order for this system to work as a generator, the prime mover should be rotated. It should rotate the armature at a speed, such that with the given field excitation, the generated E_m f across the armature is larger than the supplied terminal voltage and then only, it will work as a generator. Now, what will happen if the rotational speed is less such that E is less than V_t ? In that case, the direction of current through the same generator will reverse and now, the machine will work as a motor.

(Refer Slide Time: 07:21)

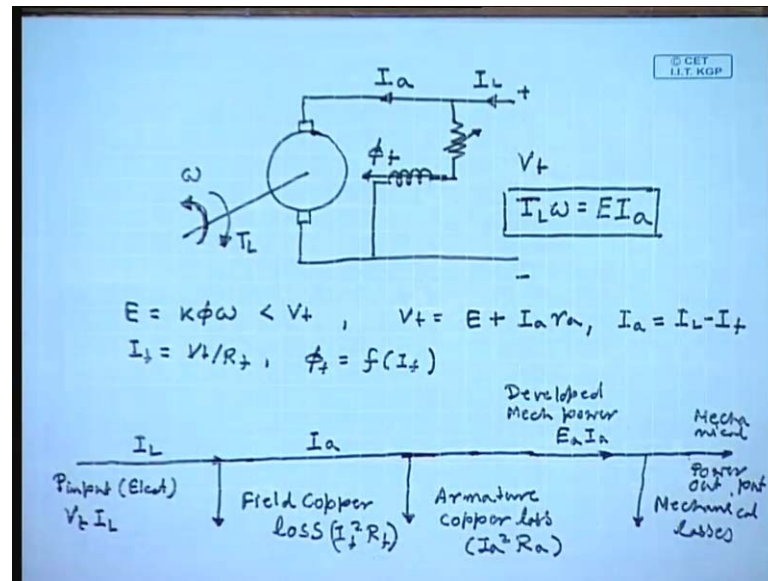


We see that in a generator mode of operation, the power input is the mechanical power input from the shaft and the output power is the electrical power which may be consumed by a resistive load, or can be fed back to the supply. So, it is not essential in order to operate this machine as a generator to have a DC supply available. This can work very easily as a self excited shunt generator supplying an insulated resistive load, but the situation is different for a motor mode of operation. Here, also the armature is connected to a DC supply of terminal voltage V_t a field winding connected across the same supply.

Hence, you can call it a shunt gen motor or a separately excited motor because they are connected at the same supply voltage. Normally, an additional resistance R_f will be connected in the field in order to control the field current. This will produce a flux of ϕ_f . Now, let us say at any prime, it is rotating at a speed of ω . In that case, the induced voltage E equal to $k\phi\omega$ as in the previous case and we are assuming that this is less than V_t . So, for this case, the current will flow into the armature and we can write V_t equal to E plus $I_a R_a$ I_a equal to I_L minus I_f I_f equal to V_t by R_f , and ϕ_f is a non-linear function of I_f given by the magnetization characteristics a power flow in this case. Now, here the input power is electrical power. That is why it is essential that a DC source be present for motor mode of operation.

1 by R_{a1} , but E_1 equal to $k\phi_1\omega$, so I_{a1} equal to $\frac{V_{t1} - k\phi_1\omega}{R_{a1}}$. Similarly, for machine 2, E_2 equal to $V_{t2} - I_{a2}R_{a2}$ equal to $V_{t2} - E_2$ by R_{a2} E_2 equal to $k\phi_2\omega$ and I_{a2} equal to $\frac{V_{t2} - k\phi_2\omega}{R_{a2}}$.


(Refer Slide Time: 18:22)

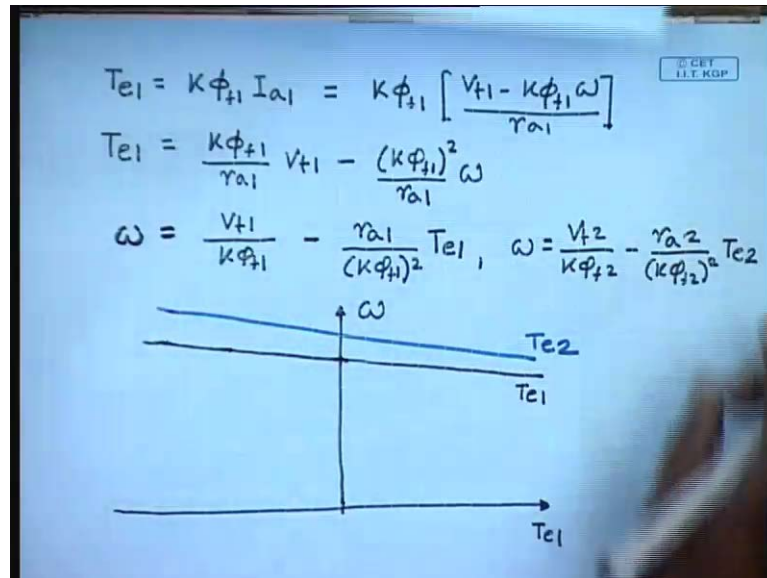

Now, what are the talks? T_{e1} and T_{e2} . T_{e1} equals $k\phi_1 I_{a1}$. This is equal to $k\phi_1 I_{a1}$ and I_{a1} is given by $\frac{V_{t1} - k\phi_1\omega}{R_{a1}}$. This can also be written as $T_{e1} = \frac{k\phi_1}{R_{a1}} V_{t1} - \frac{(k\phi_1)^2}{R_{a1}} \omega$ or in other words, we can write ω as $\frac{k\phi_1}{R_{a1}} V_{t1} - \frac{T_{e1}}{k\phi_1}$. So, this is the equation of straight line and if we plot it, this is ω at $T_{e1} = 0$. This is the no load operation. It looks like a straight line like this. Similarly, for the second machine, we can write $\omega = \frac{V_{t2}}{k\phi_2} - \frac{R_{a2}}{(k\phi_2)^2} T_{e2}$, and if I plot that may be looking somewhat like this. This is T_{e1} , this is T_{e2} .

Now, let us go back to the original arrangement. You see that the two motors are mechanically coupled. So, in steady state, there should be no made set of, that is it is necessary that $T_{e1} + T_{e2} = 0$, that is the machine will operate at such a speed such that $T_{e1} + T_{e2} = 0$ or in other words, T_{e2} should be equal to minus T_{e1} or $T_{e1} = -T_{e2}$, so instead of plotting T_{e2} , if we plot minus T_{e2} . So, this is T_{e1} and then I plot minus T_{e2} . It will be something like this. We find that this is minus T_{e2} .

(Refer Slide Time: 23:50)

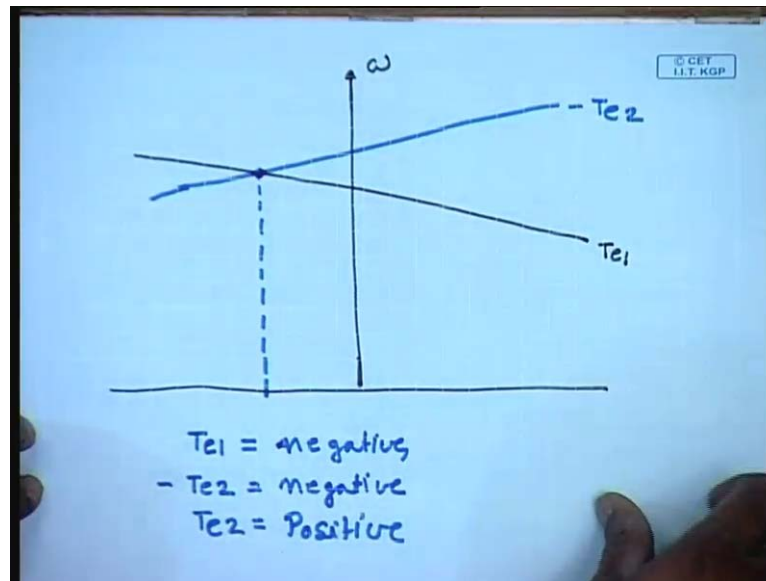


We find that the operating point is, actually in this case, we will have T_{e1} will be negative and minus T_{e2} is negative. That means T_{e2} is positive. What does positive and negative mean? In this sense from the diagram we see that any talk that assist the mechanical motion, that is in the direction of motion is assumed to be positive and any talk that is in direction opposite to the motion, that is which tries to slow down the motion is negative.

So, from the mechanical power point input point of view, any talk, the generated talk, if it is assisting the mechanical motion, then mechanical power is input to the machine. That means that machine is operating as a motor. The developed mechanical power assists motion. That means, electrical power is getting converted to mechanical power and causing motion. So, that is a motor and if the developed electrical torque opposes motion, then the mechanical power that is the machine is driven against the opposing torque. Then the mechanical power is input to that machine and that machine operates as a generator. Hence, we find that in this case T_{e1} is negative. That means, the talk generated by machine 1 is opposing motion. Hence, it is operating as a generator while talk generated by machine 2 is positive. It is assisting motion. This is operating as a motor.

So, we find that if the torque speed characteristics of a machine is above the other, then that works as a motor naturally, because then it will try to drive the other machine at a

higher speed and hence, the other machines backing it will be larger than terminal voltage and it will operate as a generator, we could have reversed the roles particularly if we find that the torque speed characteristics depends on several parameters.


(Refer Slide Time: 27:56)

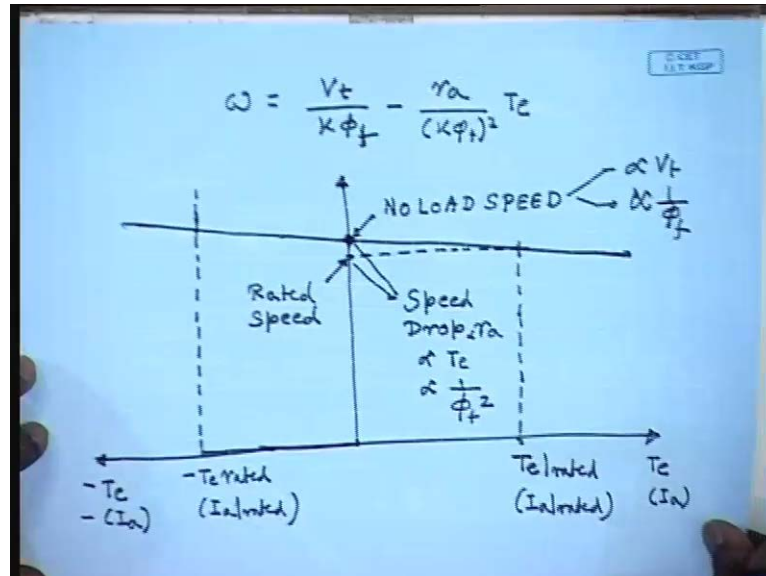

The expression for the torque speed characteristic is speed equal to V_t by $k\phi_f$ minus R_a by $k\phi_f^2$ to T_e , and without assume positive direction of current flowing into the machine, the motoring mode torque is positive and the generating mode torque is negative. Since, in a DC machine with constant field flux, torque is proportional to armature current. So, this x axis also to scale represents the armature current. This is the speed at which torque is 0 indicating the machine is operating at no load if we neglect mechanical losses. So, this is the no load speed. We see that this no load speed with T_e equal to 0, this is proportional to the terminal voltage and inversely proportional to the field flux. This is slope and let us say, this is the rated armature current and hence, the corresponding T_e rated. Hence, corresponding to I_a rated in the generating side, also there will be a minus T_e rated by...


So, although we see that if this is the no load speed, this will be the rated speed which is somewhat lower than the no load speed. Hence, there is a load, there is a speed drop at load which is proportional for, speed drop is proportional to R_a proportional to T_e and inversely proportional to ϕ_f^2 . So, if we change these parameters, how do you think the characteristics is going to change?

(Refer Slide Time: 32:15)

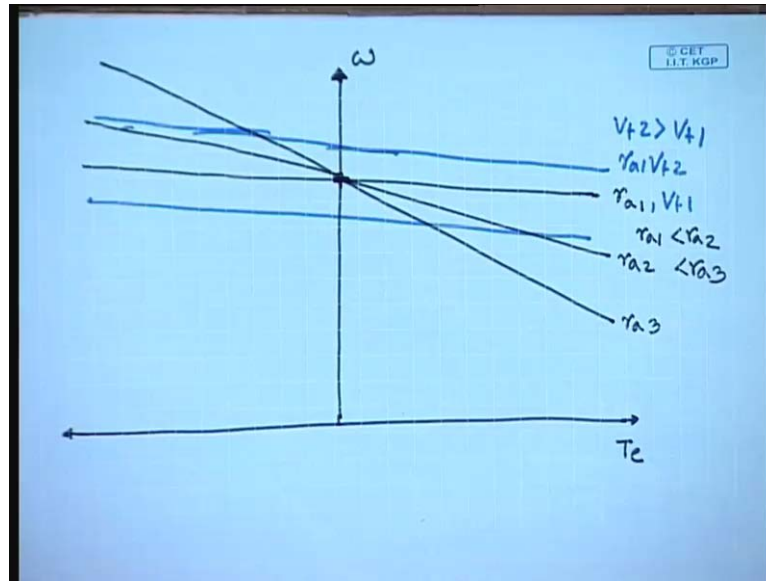

So, let us say at any terminal voltage, this is the torque speed characteristics. Simplest thing keeping everything else same. If additional resistance is included in the armature winding, then this is $R_a 1$, this is $R_a 2$. $R_a 1$ is less than $R_a 2$. So, the slope of the torque speed characteristics can be changed. Similarly, keeping the armature resistance constant $R_a 1$, if we increase the armature voltage in the torque speed characteristics sits parallel upward, its slope remains same. This is $R_a 1 V_t 1$, this is $R_a 1 V_t 2$ and $V_t 2$ is larger than $V_t 1$, but if we reduce, then torque speed characteristics also moves down.

(Refer Slide Time: 34:34)

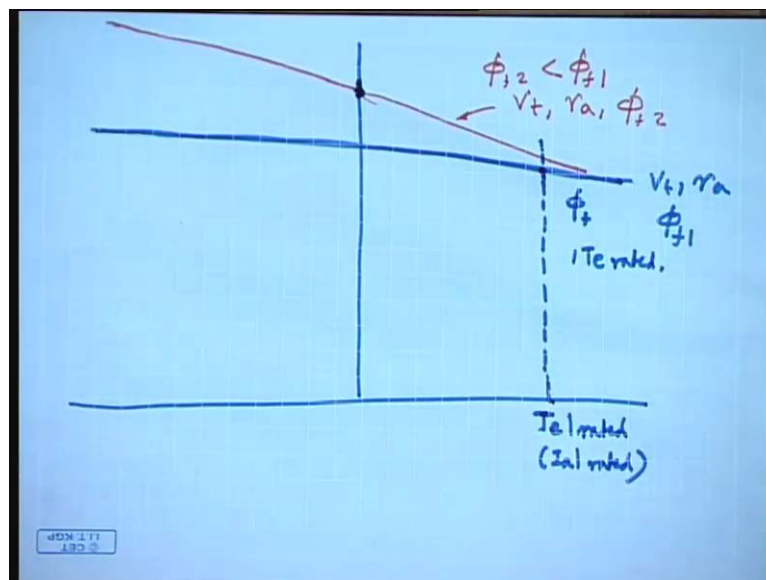

What happens? If we change the field flux by changing the field resistance? This was say for terminal voltage V_t resistance R_a , and field flux ϕ_f . Suppose, I reduce the field flux to a value ϕ_f , then naturally the no load speed will increase, but the slope will also increase. This is $V_t - R_a \phi_f$ with ϕ_f less than ϕ_f . It will be interesting to find out how far we can reduce this field flux. In fact, we cannot increase the field flux very much because of saturation. The machines are almost always works at rated flux. We can reduce it, but cannot increase it very much. So, we will consider only decrease of field flux and not increase. It will be interesting to find out how far we can reduce this field flux.

Now, we have seen that we cannot operate the machine anywhere on these characteristics because of limitation of the armature current. So, only that much torque can be generated which corresponds to rated armature current. So, with rated flux ϕ_f , this is the T_e rated that we can generate if I reduce the flux.

(Refer Slide Time: 37:21)

$$T_e = k \phi_f I_a.$$

$$T_e|_{max} = k \phi_f I_{a,max}, \quad I_{a,max} = I_{a,rated}$$

$$T_e|_{max} = k I_{a,max} \phi_f$$

$$I_a = \frac{V_t - E}{r_a} = \frac{V_t - k \phi_f \omega}{r_a}$$


$$I_{a,max} = \frac{V_t - k \phi_f \omega_{max}}{r_a}$$

$$\phi_f = \frac{V_t - I_{a,max} r_a}{k \omega_{max}}$$

Let us say to ϕ_f , what will happen? The armature current will still remain same. So, the torque generated T_e is $k \phi_f I_a$. The maximum torque that can be generated irrespective of the value of ϕ_f is at any given flux. So, at any reduced flux, the maximum power that can be generated since $I_{a,max}$ is constant which is equal to $I_{a,rated}$. Then T_e max is equal to $k I_{a,max} \phi_f$. What is the corresponding machine speed at a current of $I_{a,max}$? We know I_a equal to V_t minus E by R_a equal to V_t minus k

$\phi \omega$ by R_a . So, $I_a \max$ equal to V_t which is constant minus $k \phi f$ corresponding $\omega \max$ by R_a . So, what is ϕf ? If for a constant value of I_a , what is the relationship between I_a , and ϕ , and $\omega \phi f$ equal to V_t minus $I_a \max R_a$ by $k \omega \max$.


(Refer Slide Time: 40:23)

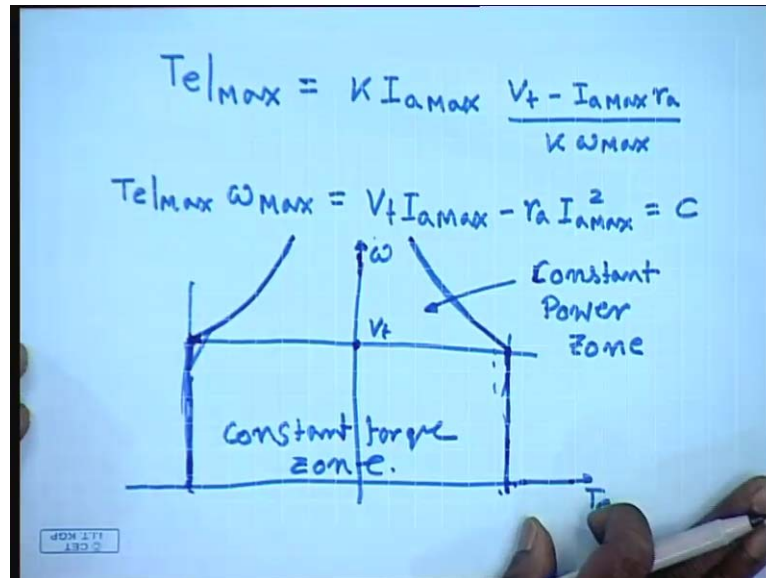

So, substituting this, we get $T_e \max$. We find that everything on the right hand side is constant. That means, $T_e \max \omega \max$ equal to constant. So, when you reduce field flux, it turns out that within the given armature current limit, the maximum mechanical power that you can develop either in the motoring or in the generating mode is constant. So, the operating point the machine must be operated bounded by these two vertical lines which indicate the armature current limit, and this rectangular hyperbola which are indicated, which are restricted again by armature current limit, but when the field flux is reduced below its rated value. So, this is called the maximum power, the constant power operating zone, constant power zone.

Now, below this corresponds to rated armature voltage. We are by some means if we can reduce the armature voltage below the rated value, then the limits corresponding to rated armature current become straight line. So, this and you can generate constant maximum rated torque. This is called the constant torque zone. A DC shunt machine must. The operating point of the DC shunt machine must be within this region, so that the armature current limit is not exceeded whatever way we may achieve that.

(Refer Slide Time: 44:10)

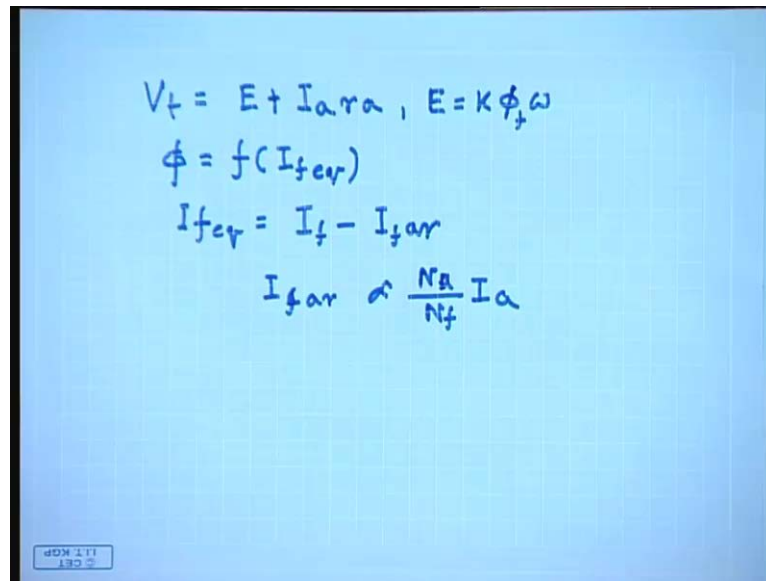


The image shows a blue grid background with handwritten mathematical equations in black ink. The equations are:

$$V_t = E + I_a r_a, \quad E = k \phi_f \omega$$
$$\phi = f(I_{fe})$$
$$I_{fe} = I_f - I_{far}$$
$$I_{far} \propto \frac{N_a}{N_f} I_a$$

In the bottom left corner of the grid, there is a small, faint logo that reads "IIT KGP".

Now, so far we have neglected armature reaction. We have written V_t equal to E minus $I_a R_a$ and E plus $I_a R_a$ and E equal to $k \phi_f \omega$, where ϕ_f equal to function of I_f , but when you consider armature reaction, this should be ϕ_{fe} equivalent. Now, I_{fe} equivalent equal to I_f minus I_{far} corresponding to armature reaction. Now, I_{far} armature reaction in means most cases is proportional to armature current. Therefore, physically what happens is that as the motor is loaded, the armature current increases. As the armature current increases, armature reaction becomes more prominent and hence, the effective field flux reduces and hence, the generated voltage reduces. So, more current flows and the torque increases.

(Refer Slide Time: 45:56)

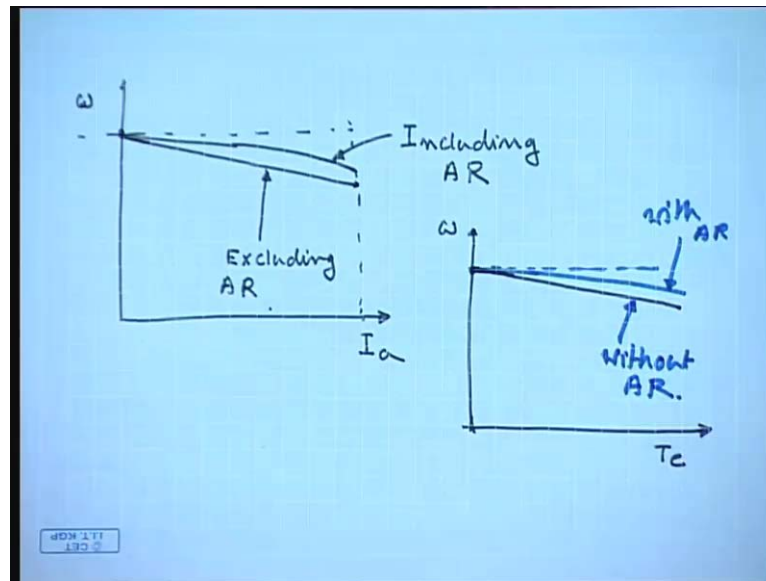

Therefore, if the effect on the torque speed or current speed characteristics is somewhat like this, suppose if I draw the current I_a versus speed at no load current is 0. If we neglect armature resistance, then armature reaction, then as the speed decreases, the current increases linearly, but if we include armature reaction, then what happens is that for a given current, the speed does not drop as much it is above this and somewhat non-linear. This is excluding armature reaction, this is including armature reaction.

Since, torque is proportional to armature; the torque speed characteristics will also look similar. This is the no load torque 0. Ideally, if no armature reaction was there, it would have dropped linearly, but when one takes into account the effect of armature reaction, the actual torque speed characteristics lies somewhat above this. So, this is with armature reaction, this is without armature reaction. We will see how it effects quantitatively through few examples.

(Refer Slide Time: 48:55)

8 kW, 230V, 1200 RPM
 $r_a = 0.7 \Omega$, $E_{\text{no load}} = 250V$
 $N_{\text{no load}} = 1250 \text{ RPM}$,
 $I_a_{\text{no load}} = 1.6 \text{ A}$
 $I_a_{\text{load}} = 40$, $N_{\text{load}} = 1150 \text{ RPM}$
 $\Delta \phi / \Delta R$.
$$N = \frac{E}{k\phi} = \frac{V - I_a R_a}{k\phi}$$

$$\phi = \frac{V - I_a R_a}{kN}$$

Let us say, we have a DC machine 8 kilowatts, 230 volts, 1200 RPM. The armature resistance r_a equal to 0.7 ohm and no load voltage, the field current is tested the no load voltage set at E at no load and set at 250 volts. The motor runs at no load is 1250 RPM and draws armature current 1.6 amperes. Now, under this condition, you apply a load such that under loaded condition, I_a , becomes equal to 40 ampere and N at load becomes equal to 1150 RPM. Find out how much reduction in flux per pole happens? $\Delta \phi / \Delta R$ due to armature reaction.

Now, we know the speed N equal to E divided by $k\phi$ equal to V minus $I_a R_a$ by $k\phi$ or ϕ equal to $I_a R_a$ by kN . So, ϕ at no load was, at no load V was equal to 250 volts, I_a was 1.6 amperes into R_a was 0.7 and the speed was 1250 RPM.

(Refer Slide Time: 52:15)

$$\begin{aligned}\phi(\text{No Load}) &= \frac{250 - 1.6 \times 0.7}{1250 \text{ k}} = \frac{0.2}{\text{k}} \\ \phi(\text{Load}) &= \frac{250 - 40 \times 0.7}{1150 \text{ k}} = \frac{0.193}{\text{k}} \\ \frac{\Delta\phi}{\phi(\text{No Load})} &= \frac{\frac{0.2}{\text{k}} - \frac{0.193}{\text{k}}}{\frac{0.2}{\text{k}}} \\ &= 3.5\%\end{aligned}$$

So, this was equal to 0.2 by k and phi on load becomes 250 minus 40 into 0.7 by 1150 k. So, this is equal to 0.193 by k. So, delta phi by phi no load, this is equal to 0.2 by k minus 0.193 by k divided by 0.2 by k. This comes to 3.5 percent. So, from actual measured data, we can find out the effect of armature reaction on the field flux.

Thank you.