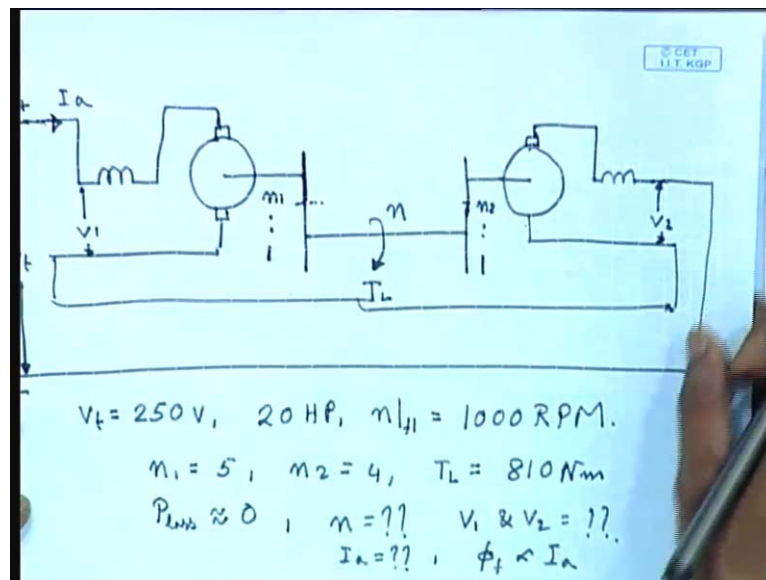


Electrical Machines - I
Prof. Dr. Debaprasad Kastha
Department of Electrical Engineering
Indian Institute of Technology Kharagpur

Lecture - 40
Characteristics of Compound DC Series Motors

In one of our previous lectures we have seen how dc shunt generators can be connected in parallel to supply a common load. A similar arrangement is sometimes possible with motors also particularly with series motors.

(Refer Slide Time: 00:35)



It is possible to connect mechanically coupled 2 series motors to drive a common shaft usually through a gear reduction. You can drive the same shaft whereas, the load torque is applied on the common shaft, this is N 1 is to 1 and this is N 2 is to 1, normally for series motor it is 2 machine are also electrically connected in series and connected across a supply voltage V t it is possible to adjust the loading of the motor by properly selecting the gear ratio.

Let us try to see how this is done through an example. Let us consider 2 identical dc series motors for which this V t equal to 250 volts both of them are rated at twenty hertz power and N full load that is full load equal to 1000 rpm. The gear ratio are N 1 equal to 5 and N 2 equal to 4 the total load torque t l equal to 810 newton meter if the losses are neglected p loss in both the motors are almost negligible. So, we have to find out what is

the speed of this common shaft N what will be the voltage across individual motors V 1 and V 2 and what will be the common armature current I a in such an arrangement. we will also assume that phi f is proportional to I a that is the machines are unsaturated .

(Refer Slide Time: 04:11)

Handwritten mathematical derivation on a whiteboard:

$$\frac{n_1}{n} = 5, \quad \frac{n_2}{n} = 4$$

$$\frac{n_1}{n_2} = 5/4, \quad I_{a1} = I_{a2} = I_a, \quad \phi_f \propto I_a$$

$$\phi_{f1} = \phi_{f2} = \phi_f$$

$$\frac{E_1}{E_2} = \frac{\phi_{f1} n_1}{\phi_{f2} n_2} = \frac{n_1}{n_2} = 5/4$$

$$r_a + r_s \approx 0, \quad E_1 + E_2 = V_t = 250V$$

$$E_2 \left[1 + \frac{E_1}{E_2} \right] = 250V, \quad \frac{E_1}{E_2} = 5/4$$

$$V_2 = E_2 = 111V$$

$$V_1 = E_1 = 139V$$

Now, for this particular case N 1 by N equal to 5 and N 2 by N equal to 4, therefore N 1 by N 2 equal to 5 by 4. Since, I a 1 equal to I a 2 equal to I a and phi f is proportional to I a, we have phi f 1 equal to phi f 2 equal to phi f, therefore E 1 by E 2 the induced voltages equal to phi f 1 N 1 divided by phi f 2 N 2 where these are same as phi f. So, this is equal to N 1 by N 2 equal to 5 by 4, but since r a plus r E plus r s E is approximately 0 then E 1 plus E 2 equal to V t equal to 250 volts. therefore, E 2 into 1 plus E 1 by E 2 equal to 250 volts, but we already have E 1 by E 2 equal to 5 by 4 this gives you the value of E 2 equal to 111 volts and E 1 equal to 139 volts. The voltage it is V 2 equal to V 1 equal to E 1 because the resistance drop is negligible.

(Refer Slide Time: 06:29)

Handwritten mathematical derivations on a light blue background:

$$T_{e1} = K_1 \phi_{f1} I_{a1} \quad T_{e2} = K_2 \phi_{f2} I_{a2}$$

$$K_1 = K_2, \quad \phi_f \propto I_a.$$

$$I_{a1} = I_{a2}, \quad \phi_{f1} = \phi_{f2}.$$

$$T_{e1} = T_{e2}$$

$$5T_{e1} + 4T_{e2} = 9T_e = T_i = 810 \text{ Nm.}$$

$$T_{e1} = T_{e2} = T_e = 90 \text{ Nm.}$$

$$T_{e|_{\text{rated}}} = \frac{20 \times 746}{\frac{1000}{60} \times 2\pi} = 142.47 \text{ Nm}$$

$$I_{a|_{\text{rated}}} = \frac{20 \times 746}{250} = 59.68 \text{ A}$$

Now, let us look at the torque generated T_{e1} is equal to $K \phi_1 f_1 I_{a1}$ and T_{e2} is equal to $K_2 \phi_2 f_2 I_{a2}$, but these are identical machines. So, $K_1 = K_2$ also $\phi_1 f_1$ is proportional to I_a and $I_{a1} = I_{a2}$, and since $\phi_1 f_1 = \phi_2 f_2$ therefore, $T_{e1} = T_{e2}$. So, both the machines they share the torque equally. Now, let us look at the mechanical arrangement [nosie] the gear ratio is N is to n . So, 5 is to 1, so if the generated torque by the motor is T_{e1} then the shaft torque contribution by motor 1 is 5 times T_{e1} plus 4 times T_{e2} , which is equal to 9 times T_e this is the total shaft torque which is given as 810 Newton meter. So, $T_{e1} = T_{e2} = T_e$ this comes to 90 Newton meter.

Now, what about the rated torque of the machines T_e rated can be found out from the rating of the machines, which are given as 20 hertz power. So, many watts divided by their rated speed 1000 rpm by 60 is the rated rps into 2π the rated omega this comes to 142.47 Newton meter what about I_a rated again losses are negligible. So, this is the output power of the motors by the input voltage this comes to 59.68 amperes. Now, we know in unsaturated dc machine T_e is proportional to I_a^2 , therefore I_a in this case will be square root 90 divided by 142.47 into rated current this comes to 47.43 amperes.

(Refer Slide Time: 09:21)

Handwritten mathematical derivation on a light blue background:

$$T_e \propto I_a^2 \quad I_a = \frac{\sqrt{90}}{142.47} \times 59.68A$$

$$= 47.43A$$


$$(E_1 + E_2) I_a = T_L \omega_L$$

$$\omega_L = \frac{250 \times 47.43}{810}$$

$$n_L = 60 \times \frac{\omega_L}{2\pi} \approx 140 \text{ RPM}$$

Now, coming to the shaft speed the in since losses are negligible. E 1 plus E 2 into I a this should be equal to T l omega l. So, omega l equal to E 1 250 into 47.43 p by 810 and N l equal to 60 into 2 pi this comes to approximately equal to 140 rpm.


(Refer Slide Time: 11:03)

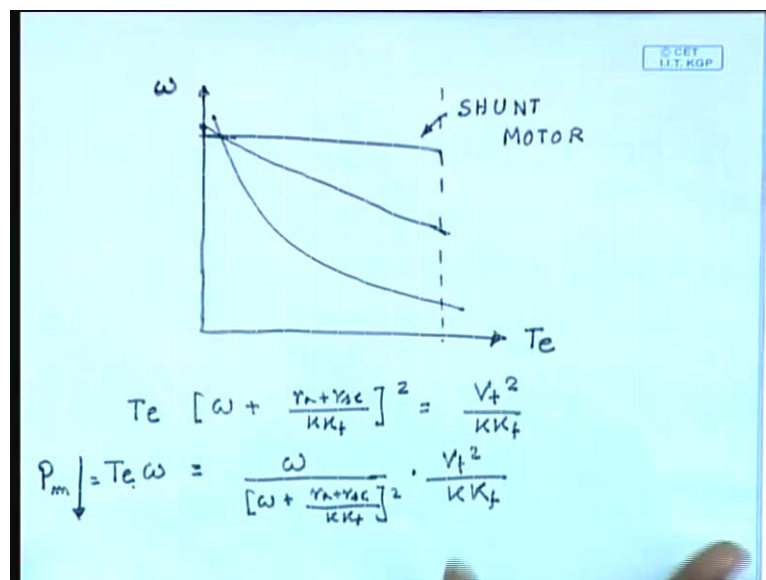

So far, we have seen 2 types of dc series motor 1is the shunt motor whose torque speed characteristics is a straight line with a little, this is the shunt motor. And, the series motor in which case the power drops very fast as the speed increases. In fact, for the series motor we know T e into omega plus r a plus r s E divided by K K f whole square equal to

V_t square by $K K f$ therefore, $T_e \omega$ equal to ω by plus r_a plus $r_s E$ by $K K f$ whole square into V_t square by $K K f$. So, as the speed increases in the power output this drops in on the other hand for the shunt motor as the torque increases power output also increases, it may be desirable to get a characteristic which is somewhat in between the 2. The 1 disadvantage of dc series motor is that it is no load, it does not have a finite no load speed as the load reduces the load torque reduces thus speed can become dangerously high, which is a undesirable feature, but 1 desirable feature of this is that the as the load on the motor is increased its speed drastically falls thereby sharing a lot of power, a limiting is more or less power limited. So, in order to combine these 2 features that is in order have a definite no load speed, but a more grouping characteristics than the shunt motor I can use a compound dc motor by adding a shunt field to a series machine.

(Refer Slide Time: 14:05)

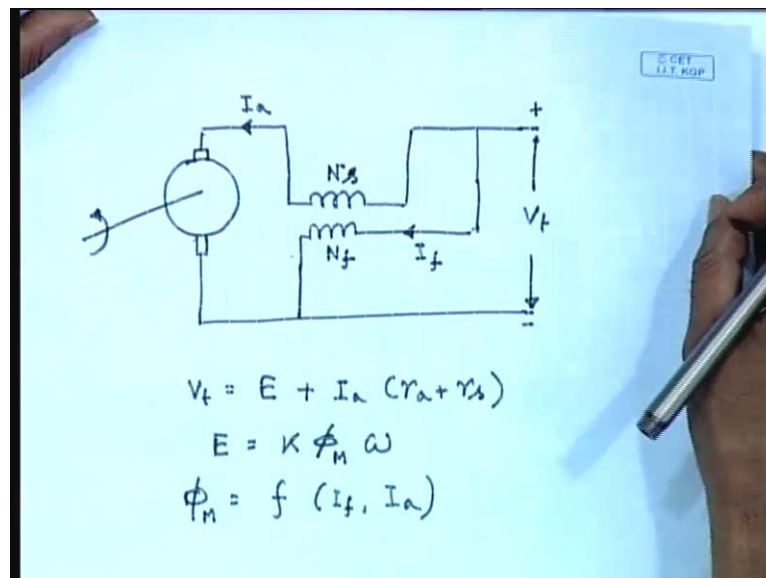

As shown below normally a long shunt cumulative connection is used that is this is a series motor to which a shunt field is also added, of course I can also see it as a shunt motor to which a series field has been added, but this can give interesting torque speed and all other characteristics. So, let us say this is the armature current I_a or this machine we would write V_t equal to the back emf E plus I_a into r_a plus r_s , where E equal to $K \phi_M \omega$ normally this ϕ_M will be some non-linear function of the shunt field current and the series field current, but if we assume the motor magnetic circuit to be unsaturated.

(Refer Slide Time: 16:11)

$$\phi_M = K_f \left(I_f + \frac{N_s I_a}{N_f} \right)$$

$$E = K K_f \left[I_f + \frac{N_s}{N_f} I_a \right] \omega$$

$$\omega = \frac{E}{K K_f} = \frac{1}{I_f + \frac{N_s}{N_f} I_a}$$

$$= \frac{V_t - (r_a + r_s) I_a}{K K_f \left[I_f + \frac{N_s}{N_f} I_a \right]}$$

$$\omega \left[I_f + \frac{N_s}{N_f} I_a \right] = \frac{V_t}{K K_f} - \frac{(r_a + r_s)}{K K_f} I_a$$

We can write this ϕ_M to be some K_f into I_f plus the equivalent field amperes of the armature current which is $N_s I_a$ by N_f . $N_s I_a$ is the ampere turns due to the series field and a equivalent field current is that divided by equivalent field ampere turns is that divided by N_f . If we replace this then we get E equal to some $K K_f$ into I_f plus N_s by $N_f I_a$ into ω . In other words we can write ω equal to E divided by, where E itself is V_t minus r_a plus r_s into I_a divided by $K K_f$ I_f plus N_s by $N_f I_a$ from where we can find out the current speed characteristics of the machine as follows, so this can be written as ω into I_f plus N_s by $N_f I_a$ equal to V_t by $K K_f$ minus r_a plus r_s by $K K_f I_a$.

(Refer Slide Time: 19:18)

$$\omega I_f + \frac{N_s}{N_f} \omega I_a = \frac{V_t}{K K_f} - \frac{(r_a + r_s)}{K K_f} I_a$$


$$\omega I_a + \frac{N_f I_f}{N_s} \omega + \frac{N_f}{N_s} \cdot \frac{(r_a + r_s)}{K K_f} I_a = \frac{N_f}{N_s} \cdot \frac{V_t}{K K_f}$$

$$\left(\omega + \frac{N_f}{N_s} \cdot \frac{r_a + r_s}{K K_f} \right) \left(I_a + \frac{N_f I_f}{N_s} \right) = \frac{N_f}{N_s} \cdot \frac{V_t}{K K_f} + \left(\frac{N_f}{N_s} \right)^2 \frac{(r_a + r_s)}{K K_f} I_f$$

$$= \frac{N_f}{N_s} \cdot \frac{1}{K K_f} \left[V_t + (r_a + r_s) \frac{N_f I_f}{N_s} \right]$$

In other words $\omega I_f + \frac{N_s}{N_f} \omega I_a = \frac{V_t}{K K_f} - \frac{r_a + r_s}{K K_f} I_a$ we can write $\omega I_a + \frac{N_f I_f}{N_s} \omega + \frac{N_f}{N_s} \cdot \frac{(r_a + r_s)}{K K_f} I_a = \frac{N_f}{N_s} \cdot \frac{V_t}{K K_f}$ this can further be written as $\omega + \frac{N_f}{N_s} \cdot \frac{r_a + r_s}{K K_f} \left(I_a + \frac{N_f I_f}{N_s} \right) = \frac{N_f}{N_s} \cdot \frac{V_t}{K K_f} + \left(\frac{N_f}{N_s} \right)^2 \frac{(r_a + r_s)}{K K_f} I_f$ divided by $K K_f I_f$ is equal to $\frac{N_f}{N_s} \cdot \frac{1}{K K_f} \left[V_t + (r_a + r_s) \frac{N_f I_f}{N_s} \right]$ by N_s . So, this is the current speed characteristics of the compound cumulatively compound long shunt d c series motor please note that on the right hand side for constant terminal voltage and constant values of I_f the right hand side is constant. So, this is again the equation of a rectangular hyperbola, but not with ω or I axis as the asymptotes, now the asymptotes are slightly different.

(Refer Slide Time: 23:19)

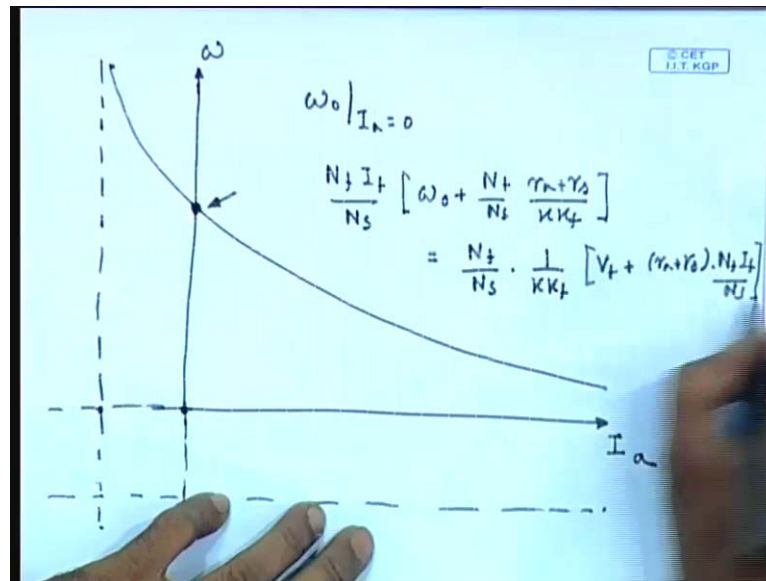

So, this is omega this is I a these asymptotes are somewhat different the interesting point to note is that at no load that is at armature current equivalent to 0 the omega does not become infinity here. In fact, we can find out what will be this no load speed that is omega 0 at I a equal to 0 from the given torque speed equation by setting I a equal to 0. In this equation we get N f I f by N s into omega 0 plus N f by N s r a plus r s divided by K K f this should be equal to N f by N s into 1 by K K f V t plus r a plus r s into N f I f by N s or in other words we can write omega 0 plus.

(Refer Slide Time: 26:01)

$$\omega_0 + \frac{N_f}{N_s} \frac{r_a + r_s}{K K_f} = \left[\frac{V_t}{K K_f I_f} + \frac{(r_a + r_s) N_f I_f}{N_s K K_f I_f} \right]$$

$$= \frac{V_t}{K K_f I_f} + \frac{N_f}{N_s} \cdot \frac{r_a + r_s}{K K_f}$$


$$\omega_0 = \frac{V_t}{K K_f I_f} = \frac{V_t}{K \phi_f}$$

$$T_e = K \phi_m I_a$$

$$\phi_m = K_f \left[I_f + \frac{N_s I_a}{N_f} \right]$$

N_f by N_s into r_a plus r_s divided by $K K_f$ equal to V_t by $K K_f I_f$ plus r_a plus r_s $N_f I_f$ divided by N_s into $K K_f I_f$ this comes to V_t by $K K_f I_f$ plus N_f by N_s into r_a plus r_s divided by $K K_f$ or ω_0 comes to V_t divided by $K K_f I_f$ equal to V_t divided by $K \phi$ just as the shunt motor with just the shunt motor field winding this is expected. Now, let us look at the torque speed characteristics or torque current characteristics first for this machine. The torque of this machine is given by just as any other dc machine it would be $K \phi M I_a$, but ϕM itself equal to K_f into I_f plus $N_s I_a$ by N_f , therefore T_e equal to $K K_f$ into I_f plus $N_s I_a$ by N_f into I_a .

(Refer Slide Time: 29:20)

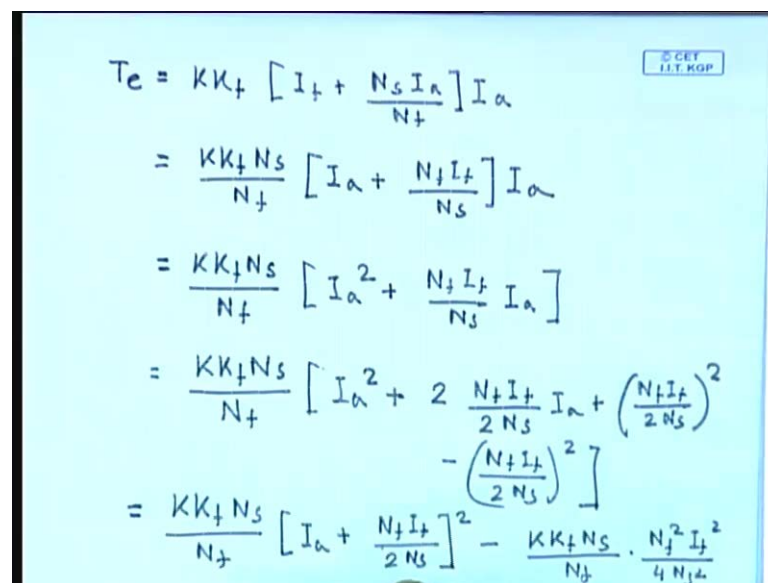

$$T_e = K K_f \left[I_f + \frac{N_s I_a}{N_f} \right] I_a$$

$$= \frac{K K_f N_s}{N_f} \left[I_a + \frac{N_f I_f}{N_s} \right] I_a$$


$$= \frac{K K_f N_s}{N_f} \left[I_a^2 + \frac{N_f I_f}{N_s} I_a \right]$$

$$= \frac{K K_f N_s}{N_f} \left[I_a^2 + 2 \frac{N_f I_f}{2 N_s} I_a + \left(\frac{N_f I_f}{2 N_s} \right)^2 - \left(\frac{N_f I_f}{2 N_s} \right)^2 \right]$$

$$= \frac{K K_f N_s}{N_f} \left[I_a + \frac{N_f I_f}{2 N_s} \right]^2 - \frac{K K_f N_s}{N_f} \cdot \frac{N_f^2 I_f^2}{4 N_s^2}$$


In other words, this can be written as $K K_f N_s$ by N_f into I_a plus $N_f I_f$ by N_s into I_a , but we have seen that, so this is equal to $K K_f N_s$ by N_f into I_a square plus $N_f I_f$ by N_s I_a . This can be written as $N_f I_f$ by $2 N_s$ whole square minus $N_f I_f$ by $2 N_s$ whole square equal to $K K_f N_s$ by N_f into I_a plus $N_f I_f$ by $2 N_s$ whole square minus $K K_f N_s$ by N_f into N_f square.

(Refer Slide Time: 32:50)

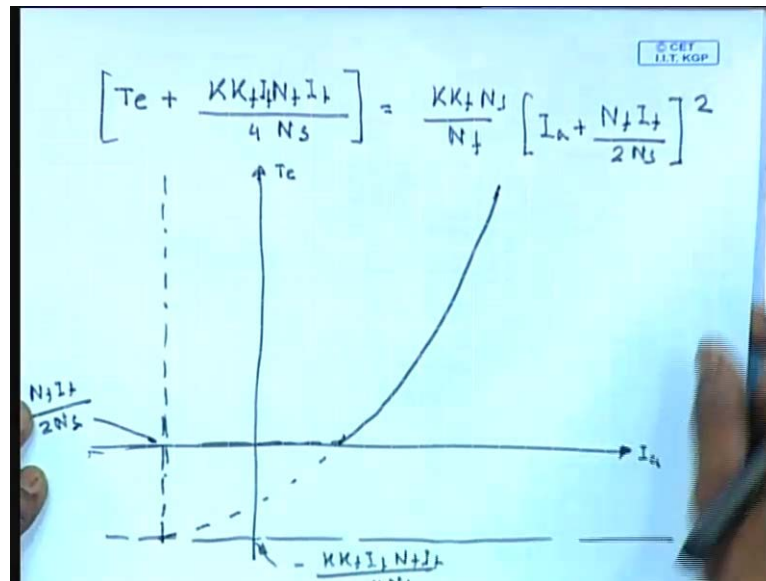


If square by $4 N_s^2$ or $T_e + \frac{K_f N_f I_f^2}{4 N_s} = \frac{K_f N_s}{N_f} \left[I_a + \frac{N_f I_f}{2 N_s} \right]^2$. This is also an equation of a parabola, but not with the normal axis of T_e and I_a . Rather, here also the torque-current characteristics are followed given by this equation. I am sorry $T_e + \frac{K_f N_f I_f^2}{4 N_s}$, you can write this as $\frac{K_f I_f N_f I_f^2}{4 N_s}$. This is equal to $\frac{K_f N_s}{N_f} \left[I_a + \frac{N_f I_f}{2 N_s} \right]^2$. So, this gives you a torque-speed characteristic somewhat like this point is $-\frac{K_f I_f N_f I_f^2}{4 N_s}$, and this point is $\frac{N_f I_f}{2 N_s}$ looks somewhat like this. We can also find out the torque-speed characteristics by simply substituting the value of current.

(Refer Slide Time: 38:19)

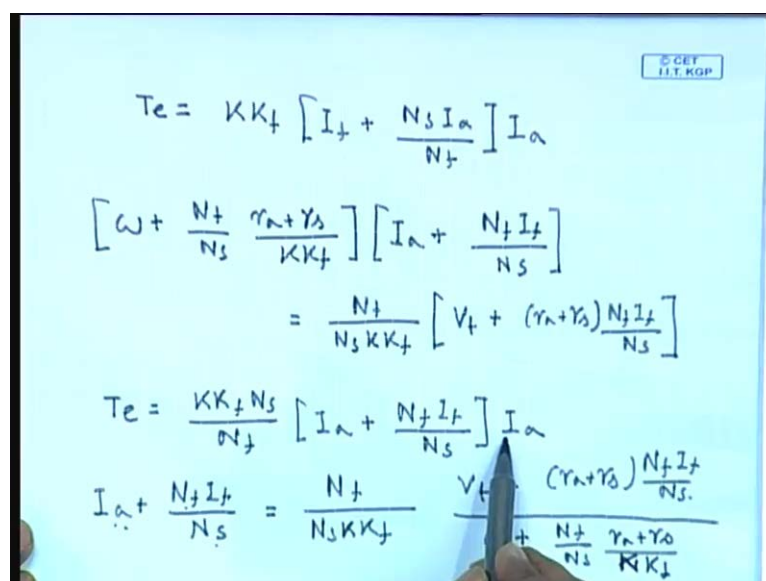


We have seen T_e to be equal to $K K_f I_f$ plus $N_s I_a$ by N_f into I_a , and we have also seen from the current speed characteristics $\omega + N_f$ by $N_s r_a$ plus r_s divided by $K K_f$ into I_a plus $N_f I_f$ by N_s equal to N_f by $N_s K K_f$ into V_t plus r_a plus $r_s N_f I_f$ by N_s from this we can write T_e equal to $K K_f N_s$ by $N_f I_a$ plus $N_f I_f$ by N_s into I_a from here, we can find out I_a plus $N_f I_f$ by N_s to be equal to N_f divided by $N_s K K_f$ into V_t plus r_a plus $r_s N_f I_f$ by N_s divided by $\omega + N_f$ by $N_s r_a$ plus r_s by $K K_f$. Now, this value of I_a plus $N_f I_f$ by N_s can be substituted in the torque equation as well as the value of I to get the torque speed characteristics.

(Refer Slide Time: 41:13)

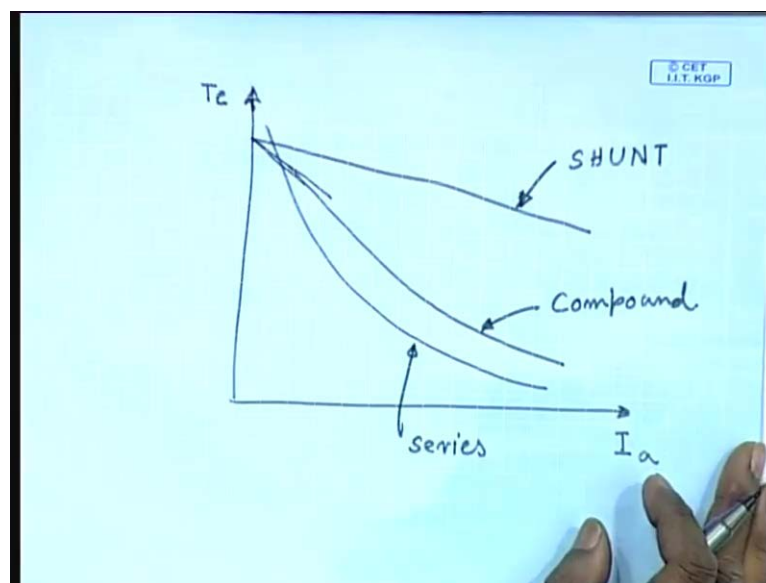


And the torque speed characteristics for this machine comes somewhat like this looks somewhat in between the dc shunt and the dc series motor whereas, for this series motor the torque speed characteristics would have been somewhat like this and for the shunt motor, it would have been this is shunt, this is series and this is compound similarly we can find out the other characteristics for example, the speed current characteristics rpm.

(Refer Slide Time: 42:25)

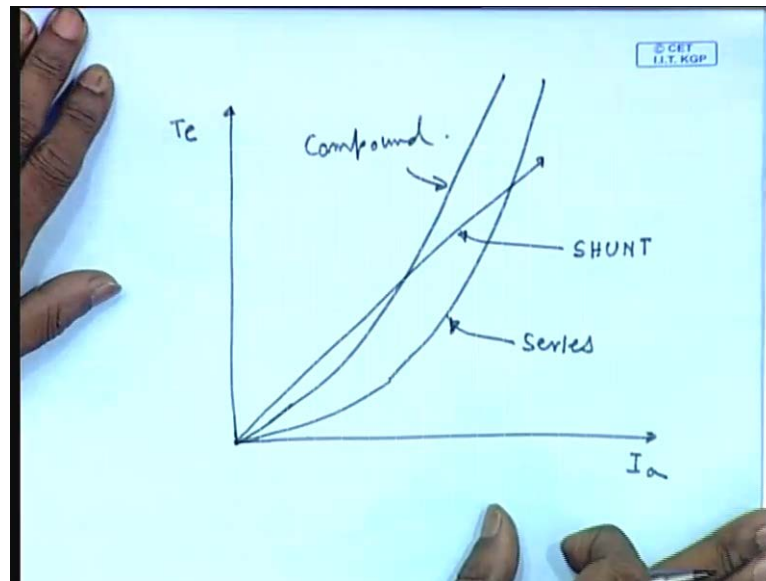


Whereas for the shunt it is again straight line and for the series, this is rectangular hyperbola for compound it is also a rectangular hyperbola, but not with these 2 as asymptotes. So, this looks somewhat like this, so this is shunt this is series, and this is compound it should be understood that we are talking about cumulatively compound motors the torque speed characteristics for shunt. We know it is a straight line for series this is the series for cumulatively compound. We will get something in between this will be shunt this is series this is compound the interesting thing is these characteristics of shunt and series machines. The compound machine can be controlled by controlling the proportion of the series or shunt field ampere turns as a percentage of the total ampere turns of the machine.

(Refer Slide Time: 45:04)

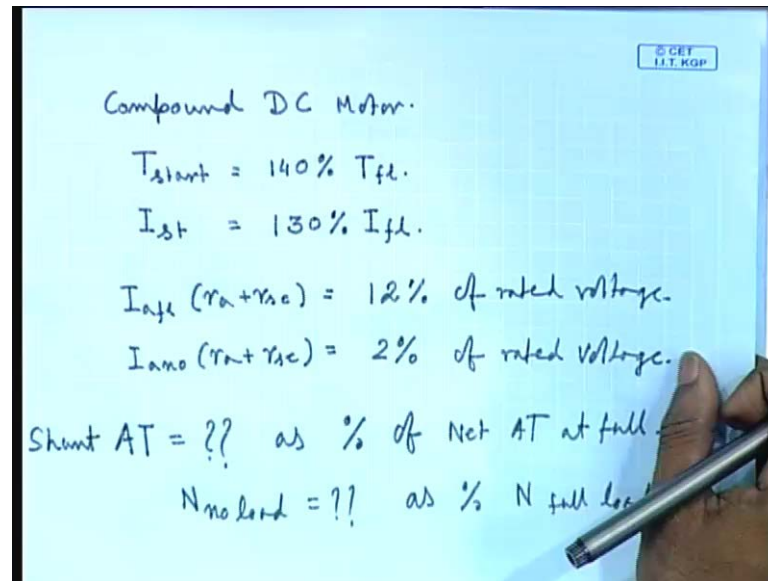

Let us look at it through an example let us consider a cumulatively compound dc motor the characteristics is its starting torque equal to 150 percent of the full load torque while the starting current is 130 percent of the full load current the full load armature drop is 12 percent of the rated voltage whereas, no load armature drop is just 2 percent of the rated voltage for this we have to find out what is the shunt ampere turns as percentage of net ampere turns at full load, we have to find out what is the percentage of shunt ampere turns as the percentage of the total ampere turns at full load and also what is the no load as percentage of full load for these characteristics, we have to find out how much shunt ampere turns will be necessary and what no load speed would it give as percentage of the full load speed.

(Refer Slide Time: 47:41)

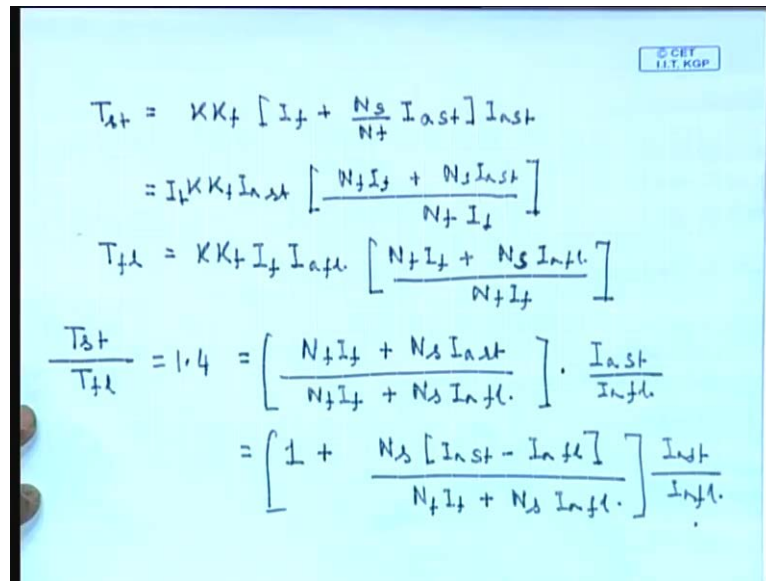

$$T_{st} = K K_f \left[I_f + \frac{N_s}{N_f} I_{ast} \right] I_{nst}$$

$$= I_f K K_f I_{nst} \left[\frac{N_f I_f + N_s I_{ast}}{N_f I_f} \right]$$


$$T_{fl} = K K_f I_f I_{afl} \left[\frac{N_f I_f + N_s I_{afl}}{N_f I_f} \right]$$

$$\frac{T_{st}}{T_{fl}} = 1.4 = \left[\frac{N_f I_f + N_s I_{ast}}{N_f I_f + N_s I_{afl}} \right] \cdot \frac{I_{ast}}{I_{afl}}$$

$$= \left[1 + \frac{N_s [I_{ast} - I_{afl}]}{N_f I_f + N_s I_{afl}} \right] \frac{I_{ast}}{I_{afl}}$$

To solve this problem, we note that T_{st} equal to $K K_f$ into I_f plus N_s by N_f I_{ast} into I_{nst} this can be written as $K K_f I_{nst}$ into $N_f I_f$ plus $N_s I_{ast}$ divided by N_f similarly full load equal to $K K_f I_f I_{afl}$ into $N_f I_f$ plus $N_s I_{afl}$ divided by N_f now if we divide then T_{st} starting by T_{fl} which is 1 point four this comes to $N_f I_f$ plus $N_s I_{ast}$ at starting divided by $N_f I_f$ plus $N_s I_{afl}$ at full load this is equal to 1 plus $N_s I_{ast}$ minus I_{afl} divided by $N_f I_f$ plus $N_s I_{afl}$ at full load this into I_{ast} divided by I_{afl} into I_{ast} divided by I_{afl} . Now, this again is 1.3.

(Refer Slide Time: 50:41)

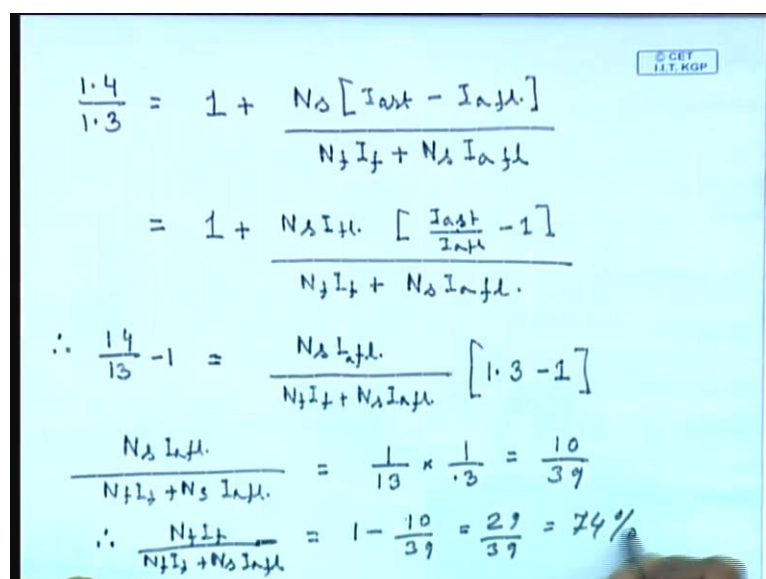

$$\frac{1.4}{1.3} = 1 + \frac{N_s [I_{ast} - I_{afl}]}{N_f I_f + N_s I_{afl}}$$

$$= 1 + \frac{N_s I_{afl} \left[\frac{I_{ast}}{I_{afl}} - 1 \right]}{N_f I_f + N_s I_{afl}}$$

$$\therefore \frac{1.4}{1.3} - 1 = \frac{N_s I_{afl}}{N_f I_f + N_s I_{afl}} [1.3 - 1]$$

$$\frac{N_s I_{afl}}{N_f I_f + N_s I_{afl}} = \frac{1}{13} \times \frac{1}{3} = \frac{10}{39}$$

$$\therefore \frac{N_f I_f}{N_f I_f + N_s I_{afl}} = 1 - \frac{10}{39} = \frac{29}{39} = 74\%$$

Therefore, we have 1.4 divided by 1.3 equal to 1 plus $N_s I_a$ start minus I_a full load divided by $N_f I_f$ plus $N_s I_a$ full load equal to 1 plus $N_s I_a$ full load into I_a start by I_a full load minus 1 divided by $N_f I_f$ plus $N_s I_a$ full load. Therefore, 14 by 13 minus 1 equal to $N_s I_f$ I_a full load divided by $N_f I_f$ plus $N_s I_a$ full load into this thing is known as 1.3 minus 1. Therefore $N_s I_a$ full load divided by $N_f I_f$ plus $N_s I_a$ full load equal to 1 by 13 into 1 by .3 equal to 10 by 39, therefore the field ampere turns $N_f I_f$ divided by $N_f I_f$ plus $N_s I_a$ full load as a percentage of net ampere turns equal to 1 minus 10 divided by 39 comes to 29 by 39 which is 74 percent.

(Refer Slide Time: 53:23)

$$\begin{aligned}
 I_a(r_a + r_{sc})|_{fl} &= 0.12 \text{ pu} \\
 I_a(r_a + r_{sc})|_{nl} &= 0.02 \text{ pu} \\
 E|_{fl} &= 0.88 \text{ pu} \\
 E|_{nl} &= 0.98 \text{ pu} \\
 \frac{\phi_{nl}}{\phi_{fl}} &= \frac{N_f I_f + N_a I_{a, nl}}{N_f I_f + N_a I_{a, fl}} \\
 &= 0.74 + \frac{N_a I_{a, fl}}{N_f I_f + N_a I_{a, fl}} \cdot \frac{I_{a, nl}}{I_{a, fl}} \\
 &= 0.7833
 \end{aligned}$$

And, to find out no load speed we note that $I_a r_a$ plus $r_s E$ at full load equal to 0.12 pu $I_a r_a$ plus $r_s E$ at no load equal to 0.02 pu. So, E at full load equal to 0.88 pu E at no load equal to 0.98 pu ϕ at no load divided by ϕ at full load equal to $N_f I_f$ plus $N_s I_a$ no load divided by I_f plus $N_a I_a$ full load this is equal to 0.74 plus $N_a I_a$ full load divided by $N_a I_f$ plus $N_a I_a$ full load into I_a no load divided by I_a full load this comes to .7833.

(Refer Slide Time: 55:06)

© CET
IIT KGP

$$\frac{E_{nl}}{E_{fl}} = \frac{\phi_{nl} \times N_{nl}}{\phi_{fl} \times N_{fl}}$$
$$\therefore \frac{N_{nl}}{N_{fl}} = \frac{\phi_{fl}}{\phi_{nl}} \cdot \frac{E_{nl}}{E_{fl}}$$
$$= \frac{1}{0.7833} \times \frac{0.98}{0.88}$$
$$= 142\%$$

And, E_{nl} / E_{fl} equal to ϕ_{nl} / ϕ_{fl} into N_{nl} / N_{fl} therefore, N_{nl} / N_{fl} equal to ϕ_{fl} / ϕ_{nl} into E_{nl} / E_{fl} . This comes to $1 / 0.7833$ into $0.98 / 0.88$ this is 142 percent.

Thank you.