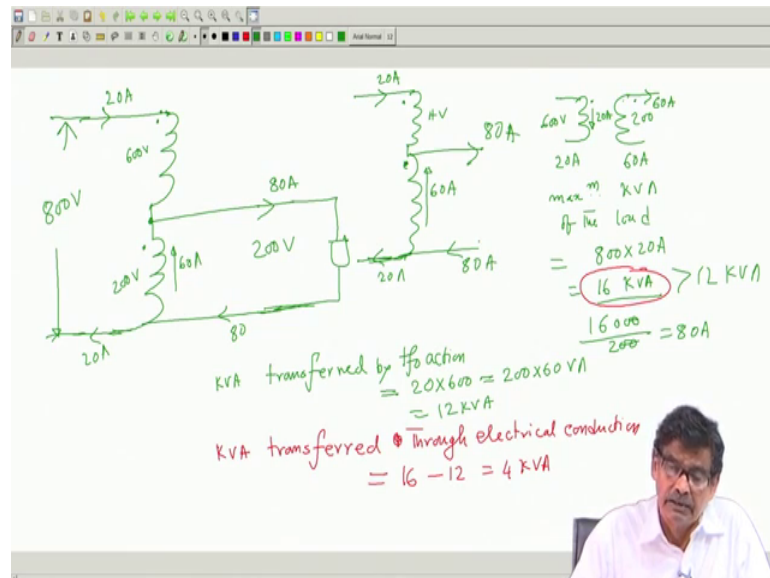


Electrical Machines - I
Prof. Tapas Kumar Bhattacharya
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture - 31
Practical Auto Transformer

(Refer Slide Time: 00:22)



Welcome to 31st lecture on Electrical Machines I. In our last class as you know, we were discussing about how a two winding transformer can be also connected as an auto transformer and for some two connections, interesting connections. We how to calculate the distribution of current in several windings? See, a two winding transformer when you connect in auto transformer form it really this primary and secondary winding is really unaware of the fact that you have connected in this manner or like a two winding transformer; it only knows this much that if it has to deliver 60 ampere. The moment it delivers through the dots here 20 ampere must come in; that is what duties.


Voltages are rated voltages; based on that everything all the calculations go, And as and we have also seen another interesting feature that a two winding transformer whose rating is suppose for the numerical example we have considered 12 KVA. It can be; apparently it looks something very surprising that the KVA handled by this connection is much more than the KVA rating of the two winding transformer and we also told that this is possible in this mode of connection because of the fact that power will be transferred

from source to the load side either by two actions. One is just by transformer action another is by electrical conduction.

It is very easy to calculate how much is transferred by transformer action that I will calculate. And from the total KVA I will subtract that to figure out how much is conducted by conduction that way you just think. And you can do; and of course, these are the only two connections I have discussed; you try on your own how differently you can connect this two coils in, apply voltage appropriate voltage mind you to the windings to get how much KVA? How much current? The interesting thing is whichever winding is left out alone sort of thing you first fix up that current I should not allow more than. And the moment you decide that current the other part of the winding which is which has its own identities separate no common portion of this and this.

Therefore this current can be fixed up and then, the total current. Anyway this you please try solve many problems. Now, in today's lecture I; my plan is to tell you something what is going to happen if it is a practical auto transformer.

(Refer Slide Time: 03:57)

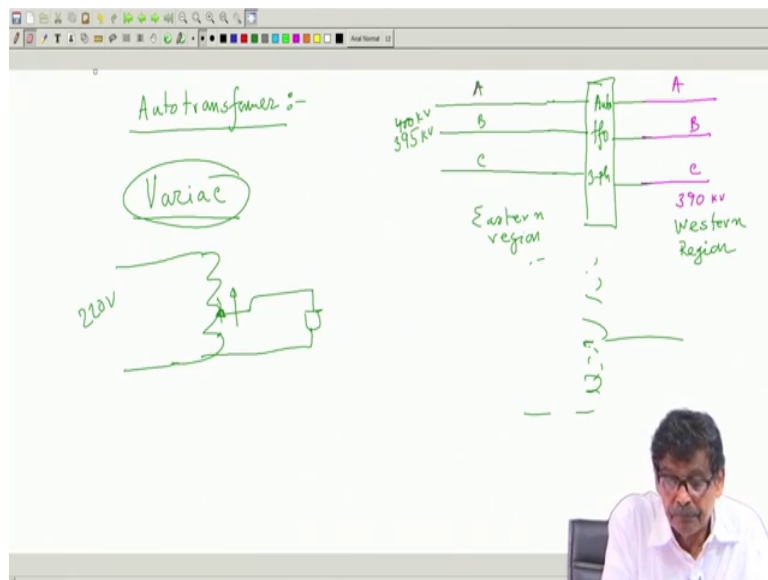

I will discuss that, but before that one point I must tell you; see, auto transformer is the thing. What will be its useful applications auto transformer? It is useful applications will be you must have heard that starting of three phase induction motor; is not? You use an auto transformer start it at a tapings of x then the current drawn from this supply is

reduced. Torque is also of course, reduced by a factor of x square current drawn from the supply is reduced by x square and so on.

Another interesting application of auto transformer will be to connect two power systems. You must understand this point that we have in our country or in all other countries also there common power grid ok; you have several level of voltages ok. Suppose, the 400 KVA is the one line 400 KVA system ok; see, eastern region grid; suppose, there is a grid eastern region 400 KVA. Now, the western region grid also should be supposed to be 400 KVA ok, another grid with different colors I will draw; try to understand. This is supposed to be also 400 KVA.

And you know this power lines will be ultimately connected in parallel that is this is suppose a phase b phase c phase a phase b phase c phase, coming from western region grid; this is coming from eastern region grid and loads are connected in both the system, but I want to make them common member; that is power may go when, there is deficiency in power generation in western grid. Perhaps, this grid will supply power or there and vice versa.

So, grids, common grids if you want to make all over the country; all the grids are to be connected in parallel. Suppose, this level of voltage should be also 400 KVA then, only this two can be; suppose this is A phase; this is B phase; this is C phase and these are corresponding phases here ABC. This is supposed eastern region, eastern region grid; this is western region. Who have kept this lines a live? Several generators. They are connected in parallel you get the voltage. Here also several generators connected in parallel as generated this grid. Now suppose, you want to make it more flexible that I will connect them also in parallel and if due to some reason Western Region some generators fail. So, the eastern region can help to pump power into this side or vice versa that is what I am telling.

Now, what happens is this? This is 400 when you connect this to in; if you want to short this you cannot just do just like that because of the fact the level of the voltage must be same. It may so happen; it is absolutely this side voltage is suppose not 400 KV because of some practical reason or otherwise, it is suppose 390 KV; are you getting? Because loads here also it is not 400 KV; may be 402 KV or say 395 KV because you will be loading. These systems are loaded; this volt bus voltage may not exactly match. Suppose

it is 395 KV, but I want to connect them in parallel. So that flexibility increases this side can fit power; this side can fit power and what not.

So, in such situations these two systems can be connected. If you connect an auto transformer in between, three phase auto transformer I will tell what this auto transformer. Three phase through an auto transformer you will be able to parallel; two winding transformer can be also used to parallel them, but I will not do that why? Because I see that the ratio of the voltage is so small; 395 to 390 KV I have to connect. This side is 395 KV; this side 395 KV, nothing better than auto transformer you should think about because trans ratio or the voltage ratio is close to 1.

You will be saving more or very large amount of copper; size of the auto transformer will be less. So, this is one very practical use of an auto transformer, three phase auto transformer. Now, what is a three phase auto transformer? I will just this I will take up when I will take three phase transformer; right now you just try to understand. Here is a case, where the voltage ratios will be close to 1 and I have to connect these two.

So that I can parallel them not directly because if I connect them directly without transformer 5 KV difference will cause large current to flow almost like short circuit. So, this is one case or maybe you can start connect an auto transformer to start an induction, three phase induction motor. Of course, I must add one remark. Now to start an induction motor using a bulky auto transformer that to I mean is not a good solution; there are very good solutions because of the use of invertors power electronics there, but earlier it was very much used.

So, auto transformer is an natural choice when, the voltage of the two sides you require voltage levels are of this same order ok you really save money copper that is there. Now, another thing you have used in the laboratory which is called variac sorry variac. In the laboratory you must have used to carry out experiments and I also was telling that is it is drawn like this and this stepping point you can move you can adjust to anywhere you like and you can supply your load at various level of voltage.

Suppose, there is 220 volt you want to do some experiments to find out the characteristics of the load starting from 0 voltages up to 220 volt. So, there is a pointer there which you can vary by rotating a shaft through a carbon brass this is connected.


You touch different segments of the turns and gradually you can increase voltage to the load.

But it is called variac. It will be same the current distribution etcetera we have to find out from the whatever analysis we have done like that you have to do no doubt about it, but here while doing this, while making this variac do you think the cross sectional area of this portion is less than the cross sectional area of this portion no because you do not know where he will be operating; so, this must be understood.

Variac is strictly not an auto transformer in this sense we design the auto transformer get some economic advantage. Well, here nothing like that you should be prepared. So, the gauge of the wire here throughout is fixed; you must understand this distinction in a variac laboratory equipment that is why you will find variac is too heavy mean there is no savings this side. Its KVA rating is known; maximum current it can draw and so on. This point I must bring out to you. So that you distinguish between an auto transformer dedicated auto transformer like this where it will be used; it will have a fixed tapping; is not?

This is thinner wire. I drew with different colors, fixed tapping over. Nothing like that this can be moved this way that way. If you do it between taking lot of risk you do not know what is the current rating, mixed up current rating of the turns? I hope you have got the point. So, this must be kept in mind.

(Refer Slide Time: 15:23)

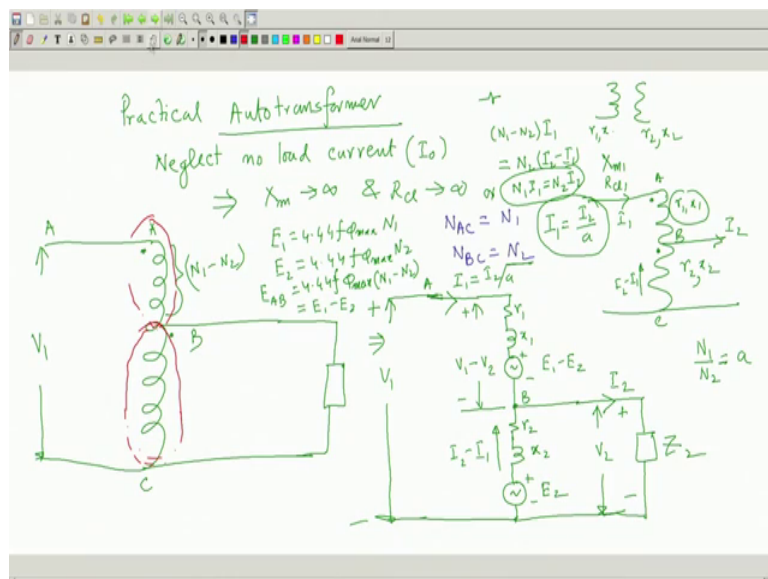

Now, I will discuss what to do if the auto transformer; how to analyze a circuit involving an auto transformer, but which is not ideal, non ideal auto transformer, a practical auto transformer; what should I do? Practical auto transformer not variac; a practical two winding transformer we; you have to take then r_1, x_1 ; r_2, x_2 and then, magnetizing reactance X_m ; R_{cl} core loss component of resistance; all these things we have to bring here.

So, similarly in the auto transformer since there is a core; there is time varying field therefore, there will be core losses and not only that there will be this is the auto transformer thing where a fixed tapping is taken. So, this portion of the winding will have r_1, x_1 ; this portion of the winding will have r_2, x_2 and so on. Similarly, the magnetizing branch and no load current; first what will do is this I will assume that windings will have some resistance and leakage reactance because leakage flux will be there and this portion and this portion of the windings have their own electrical identity no mixed up between them.

So, I will say the resistance of this portion of the winding is r_2 and leakage reactance is x_2 and this portion of the winding is r_1 and x_1 ; I can very well define that ok. So long when there was this things were and magnetizing and no load current first neglect. I will tell you how to take no load current, neglect no load current; that means, I naught which implies that I am telling that X_m is tending to infinity and R_{cl} is tending to infinity it means that we shall see [FL]. Now, and I will first draw as usual; this is my transformer and I use this nomenclature A C and this is B C. And I will say that N_{AC} is equal to N_1 and N_{BC} is equal to N_2 and this two are my output where, I will connect load; is not? This is the thing.

Now, I am saying that this portion A B has a resistance r_1, x_1 and this portion BC is having a resistance r_2 and leakage reactance x_2 and here I am applying a voltage V_1 . Earlier, when this things were not present B 1 is equal to the induced voltage here; V_2 was equal to induced voltage here. Therefore, we can easily see that if I want to show this resistance and leakage reactance I must draw it like this. A point I will draw it slightly higher place. So, I will draw it in this way. A; I start from a point; V_1 is the supply voltage A. Then, there will be just like two winding transformer r_1, x_1 ; it will only cause extra voltage drop and then, we will come your v_1 and this two were dots, E 1; I am not sure whether it will be E 1. I will write what it will begin.

Now, I reach up to point B. So, it will be; this is the point B and then, I will draw r_2 ; I will draw I mean $j \times 2$ I am not writing you understand it is $j \times 2 r_2 \times 2$ and then, there will be another induced emf in this portion. This induced emf, I can write it has E_2 no problem why? Because this is the voltage you have applied; flux is same. So, voltage induced N BC is N_2 . So, $4.44 \phi_{max} N_2$. So, this is the induced voltage correctly I have drawn and voltage per turn is fixed; how much it is? It is approximately B_1 by N_1 , total number of turns

Number of turns here is N_1 minus N_2 . So, what will be the induced voltage here? It will be E_1 minus E_2 . Are you with me? Because induced voltage in N_1 turns; if I call it as E_1 induced voltage in N_1 minus N_2 turns will be N_1 minus N_2 . So, I let me write E_1 is equal to $4.44 f \phi_{max}$ into N_1 whatever it is total; between these two terms E_2 is equal to $4.44 f \phi_{max} N_2$ and if I say what is the induced voltage between A and B; here, what will be the induced voltage? It will be equal to $4.44 f \phi_{max}$ into number of turns between these two points which is nothing, but N_1 minus N_2 and which will give me E_1 minus E_2 got the point.

So, this is the thing and here will be one load. So, immediately we see that there will be; it is not as simple as that of a two winding transformer where, the equivalent circuit was $r_1 \times 1$ and. so on $E_1 E_2$. Here this, this is what it should look like and there will be a distinction between V_1 and see, if you start from this to this in so far as induced voltage is concerned it is fine; $E_2 E_2$ will cancel and E_1 induced voltage, but there is a mix up now.

I will tell that this current is I_2 first thing is; first thing first I_2 and suppose, I say that this current is I_1 . I do not know what are the relationships that I will find out, but I am sure about one point that is if this is I_2 ; if this is I_1 no matter whether $r_1 \times 2$ or $r_2 \times 2$ is present; the current here has to be I_2 minus I_1 and this current has to be I_1 it does not debar me or does not confuse me that $r_1 \times 1$ is there; can I write these? Yes; k c l I have simply applied.

But only argument is interesting argument; see, the portion AB and portion BC they are two individual coils as if and these voltage I will call V_2 terminal voltage which is not same as E_2 because $r_2 \times 2$ is there, but $r_2 \times 2$ is not carrying same current as the load it is different. So, this current is I_2 minus I_1 ; is not? So, therefore, the moment load is


connected some I_2 is flowing it will draw some current I_2 and this time $r_1 \times I_1 = r_2 \times I_2$ is present I cannot easily say how much current it will draw by balancing output power and input power because there will be power loss in this element; in this element as well; is not? It is slightly complicated, but one thing is clear, the mmf balance that rule must prevent. If this portion carries winding, this portion cannot remain silent.

Therefore, I will say and this two are dots. So, $N_1 I_1 - N_2 I_2$ must be balanced of this current through the dot this current is $I_2 - I_1$; it must be equal to $N_2 I_2 - N_1 I_1$ that remains there is no doubt about that and odd this means $N_2 I_1$ cancels off from both sides; is not? This is I_2 . So, this also means $N_1 I_1$ is equal to $N_2 I_2$. See, the point is I should not start from this I must establish it. So, happens that like a two winding transformer I mean $N_1 I_1$ is equal to $N_2 I_2$. I have derived that I will define N_1 by N_2 as a I will define that.

Then, I will say that I_1 is equal to I_2 by a ; this much I am I can confidently say. If this current you record it so much ampere $N_1 \times$ total turns N_2 this turn. Then, this current will be I_2 by a . This I am sure off; got the point; this is the thing [FL]. Now, this voltage is V_2 and this voltage is V_1 , applied voltage; terminal voltage, induced voltage they are not now same there will be a little drop here, but this tells me that the voltage here across so called across A B portion of the winding, this must be $V_1 - V_2$ it has to be this voltage minus this voltage is $V_1 - V_2$ with this side plus this side minus.

Now, look at this; today, I will only tell this much look at this portion this coil and this coil. These two coils are separate; is not magnetically coupled? Therefore, I can say that I mean what I am trying to tell in the next page I will draw.

(Refer Slide Time: 29:30)

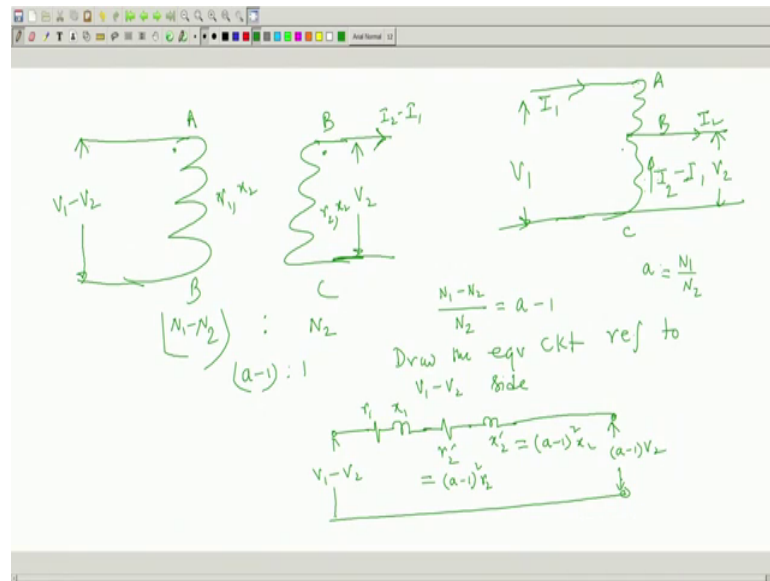

What I am telling is A B is a coil and I will write B C is another coil; this two coils and I find that A B has been supplied with a voltage of $V_1 - V_2$ terminal voltage; is not? $V_1 - V_2$ and this fellow across V_2 it is V_2 I am not showing the load yet because the problem here is this coil current and load current as different, but can say this much. See, this winding is delivering a current $I_2 - I_1$; this much I am certain.

What things is to be connected to achieve this? Let us not bother right now, but this is what I can think of ok. So, I will draw once again here. So that we can easily refer to A B and C. What I am telling this current is $I_2 - I_1$ and this current is I_1 and this voltage is V_1 and this terminal voltage is V_2 ; these are all fine V_2 ; this current is I_2 that is there, but if you look at this two separate coils it is telling me as if I can draw this diagram and say that it is a at least these two portions are a two winding transformer across the primary of which I have applied $V_1 - V_2$ and secondary is loaded such that it delivers a current of $I_2 - I_1$ this much I can say.

And then, I will say; so for as this transformer is concerned what is the number of turns of this A B $N_1 - N_2$ is not very interesting, $N_1 - N_2$ is the number of turns and what is the number of turns of this N_2 ? I will say that this is a transformer whose trans ratio is $N_1 - N_2$ by N_2 .

I will say whose trans ratio is this $N_1 - N_2$ by N_2 and this one is equal to then, a minus 1 because I have defined a to be N_1 by N_2 . Now, please be with me, what I have

done; this to be separate windings. This fellow is carrying a current I_2 minus I_1 ; this portion is carrying a current I_1 . So, it is just like a two winding transformer having applied voltage to this coil $A B$ V_1 minus V_2 and this as V_2 , but delivering a current of I_2 minus I_1 ; not I_2 then, you will be doing mistake because as I told you this coils are really unaware of the fact that is whether it is connected like an auto transformer or like a two winding transformer.

So, this is the thing and if that be the case then, I will say that this is a transformer of ratio a minus 1 is to 1 . Then I will go another step ahead and today, I will stop it here. Then draw the equivalent circuit; equivalent circuit of this thing circuit refer to source; refer to I will not say source to V_1 minus V_2 side because this winding will see it across it has been applied a voltage of V_1 minus V_2 and what will be the equivalent circuit? V_1 minus V_2 is the applied voltage; is not? Then there is r_1 ; there is x_1 will be there, it is winding; this winding $r_1 \times 1$. This winding $B C$ I have assumed that to x_2 ; so, this will be $r_1 \times 1$ and this will be your what? R_2 dashed and x_2 dashed.

Now, the big question is what is this r_2 dashed in terms of r_2 ? Trans ratio is this. So, a ; this must be a minus 1 whole square into r_2 , not s square into r_2 . Similarly, this x_2 dashed should be equal to a minus 1 square into x_2 ; is not? What voltage should I write? Here, this V_2 a times V_2 . So, I must write it here a minus 1 into V_2 , actual voltage V_2 a times this. See, what I have drawn; I have this two windings I have drawn separately, they are doing this.

So that I can invoke whatever I have learned from two winding transformer those simple, but important principles I will straightaway apply and say this is the thing. We will continue with this in the next class; it will take some time, but up to this point be absolutely clear ok; try to understand it is very logical and interesting. In autotransformer the equivalent circuit drawing is slightly; I will not say the word tricky, but rather I will say you have to apply your own minds correctly. So that correct equivalent circuit you can draw refer to a particular side.

Thank you.