

Network Analysis
Prof. Tapas Kumar Bhattacharya
Department of Electrical Engineering
Indian Institute of Technology-Kharagpur

Lecture # 27
Circuit Analysis with Phasor – II

(Refer Slide Time: 00:15)

dec-27

Phasor Analysis of Electrical Circuit when excitation or forcing fⁿ is sinusoidal.

$v_s(t) = V_m \sin \omega t$
 $i_{ss}(t) = \frac{V_m}{Z} \sin(\omega t - \theta)$

$Z = R + j\omega L$
 $\tan \theta = \frac{\omega L}{R}$

$\cos \theta = \frac{R}{Z}$
 $\sin \theta = \frac{\omega L}{Z}$

$R = Z \cos \theta$
 $\omega L = Z \sin \theta$

$\bar{V}_s = V_s + j0 = V_s e^{j0} = V_m \angle 0^\circ$
 $\bar{I}_s = I_m \cos \theta - j I_m \sin \theta = I_m \angle -\theta$

$i(t) \rightarrow \bar{I} = \frac{\bar{V}_s}{Z} = \frac{V_m \angle 0^\circ}{Z \angle \theta} = \frac{V_m}{Z} \angle -\theta$

$= \frac{V_m}{Z} e^{j\theta} = Z \cos \theta + j Z \sin \theta = (R + j\omega L) = \frac{V_s}{I_s} = \text{constant}$
 $= \bar{Z}$

out of curiosity $\frac{V_m}{I_m} = Z$

So, we have been discussing with phasor analysis of electrical circuit essentially, any circuit with energy storing elements will have a natural response and solution due to forcing function if the solution due to natural response will decay down to 0 very quickly and people are mostly interested to find out the solution due to steady state currents. If that be the case then we have found for an RL circuit the supply voltage is equal to $V_{max} \sin \omega t$ and the current of the RL circuit we have seen it is equal to $\frac{V_m}{Z} \sin(\omega t - \theta)$ and this is steady state current.

We are interested in steady state current only then what I am telling is this that this voltage if it is, but they must be were in sinusoidal otherwise not phase phasor analysis of electrical circuit, when excitation is sinusoidal away in excitation or forcing function excitation or forcing function, then only you can do it forcing function is sinusoidal. So, V_s is this then I told that then this V_s can be represented as a phasor moving with the speed, ω and your current phasors will be can be represented as \bar{I} and it will lag this by the angle θ .

And suppose this is the reference for that you have drawn then in general at this plane and both of them are moving with ω so, that is fine. So, at any arbitrary position if they move that is, this is that $t = 0$, I have drawn the position of the phasors, but related positions of the phasor the is independent of time that is at ωt , the situation will be like this position of the voltage phasors will advance V_s and your current will come here, but the angle between them is θ and this is ωt . This angle is ωt because v_s at $t = 0$ it was horizontal.

So, it has moved by ωt , I is also moved by ωt . That is why the angle between them is constant from these 2 ω . So, earlier I was there when v were there, I was there. So, this has also moved by ωt and it is there. But anyway So, I will always draw the phasor diagram in this way that is at $\omega = 0$ V_s t is occupying the reference and then I can say if I think that it is a complex plane. So, I will say V as a bar the angle this is suppose the real axis and this is imaginary axis, then I will say V_s bar is only having real part.

So, $V_s + j 0$ is not you draw it in this way also you can relate V_s bar will be I mean $\theta + \omega t$ whatever you do you do, but in this way I will just write V_s bar and then I will say that I_s bar we will have that is no imaginary component present in V_s bar I bar on the other end as got a real part whose magnitude will be this length into cosine θ . And if you break it up into 2 components $I \cos \theta - j I \sin \theta$ sine θ . So, in polar form at this will be V_s into e the power $j 0$. And this current in polar form will be e to the power $- j \theta$ at $\omega t = 0$ am writing.

So, this is the voltage and current phasor this 1 instead of writing e to the power $j 0$ always people write it like this angle 0 it means that it is V_s into e to the power $j 0$ but similarly this 1 people right $i - \theta$ like that got the point therefore, your supply voltage see everything is real here, but now I am some body suggested not somebody I should say is Steinmetz for the first time told that to get the solution due to forcing function, you do not have even to write the differential equation do it like this, because excitation is sinusoidal.

So, forcing function solution in this steady state will be also sinusoidal of same frequency. If that be the case, then you can represent them in this fashion. Of course, this tool is also adopted classically then e is suggesting something very interesting. So, e tells that to represent V_{st} in terms of phasors, the current in terms of phasors like this now, the argument is like this, just out of curiosity what do you do? You divide this 2 phasors V_s bar by i , I must draw the circuits.

So, that you do not be misunderstanding this is the supply voltage time V_{sd} and this is the current i . So, y as is it current I it is not it is a current in the circuit i . Now, this I will just divide what is the value of this V_s it is the magnitude V_m , what is the value of this current i , it is this i and this is I am writing as the magnitude of the magnitude of the weather so, the prequels V_m by i . Now, therefore, what I will do is this this can be written as easily magnitude and angle 0 divided by magnitude of the current that is i . This is suppose I_m with maximum value in.

So, I_m divided by $- \theta$ and the $\sin 0$ is nothing but $V_m e^{j 0}$ divided by $I_m e^{j \theta}$ the power $- j \theta$. If you divide this to 8 will come out to be the M by M magnitude divided and the angle gets subtracted into the power $j - \theta$, it will be just like this. $- , + 0 - \theta +$. Now, what is the V_m by I_m ? $I_m = V_m / z$ therefore, $V_m / I_m = z$. So, this quantity is z into $e^{j \theta}$ the power $j \theta$, this is the thing, record recall that, this j I will write it with different color this j we established it is nothing but $R^2 + \omega^2 L^2$ and what is $\tan \theta$ can take $\tan \theta$ was $R / \omega L$ is not.

This weak inside then you get this j into the $e^{j \theta}$ power θ which is $z \cos \theta + j z \sin \theta$ and then this $z \cos \theta$ you see this temp tides $R / \omega L$. So, if you consider a right angle triangle, $z \cos \theta$ $\tan \theta$ is known so $\cos \theta$ is known, how much it will be it will be $z \cos \theta$ I am so this a road wrongly $\omega L / R \tan \theta$ is $\omega L / R$ so what will be $\cos \theta$ is $R / \sqrt{R^2 + \omega^2 L^2}$ which is equal to R / z and $\sin \theta = \omega L / \sqrt{R^2 + \omega^2 L^2}$, which is equal to $\omega L / z$, this will be the thing.

Therefore $j \cos \theta$ is nothing but R and $z \sin \theta = \omega L$ so, these 2 things gives you $R = z \cos \theta$ and all my guys to get $\sin \theta$ so, I just put $j \omega L$. So, what I told you yesterday,

I represented sinusoidal quantities in phasors the angle between phasors do not change that is comes out to be theta and then I could represent the supply voltage as a phasor as $V_m \angle 0^\circ$ peak value 0° current value I_m it will lag this supply voltage in case of this - theta, you divide these 2 and you get this thing ratio of V_s by I_s phasors.

And this is what this is the ratio of V_s further by I_s further and this thing constant to be a constant of the circuit for a it depends on supply frequency that is there but no supply voltage is that So, this ratio is constant. and how did you did e established that I did all the hard work to get the solve the differential equations got this steady state voltage and steady state current then I am told that only steady state currents we are interested in and then I thought both are of same frequency and sinusoidal varying therefore, they can be expressed as some lengths whose values are peak values.

V_m and I_m and this is the I_s and then I represented at complex plane as $V_s \angle 0^\circ$ and $V_m \angle -\theta$ then I_m telling let us see whether these 2 phasors have some relations see in case of inductor are these B by $i = R$ that is what we are always applying. Now, when it comes to a capacitor efficiently then I find that the ratio of the phasors not of the instantaneous quantities not V_{st} by I_{st} it cannot proceed part that because $\sin \omega t$ by $\sin \omega t - \theta$ that will be also a function of time it has got no meaning, I mean no meaning means it does not help me in any way.

But we find that if you represent them in phasors then take the ratio of the phasors voltage phasors divided by current phasors. If you do, then a surprise thing happens, we discovered that the ratio is a constant complex number whose value depends on the circuit parameters are and then of course not tail alone supply frequency which is ω it is to be multiplied by ω that I can always do and this ratio is constant. So, the thing is, the current phasors in the circuit will be equal to V as bar by get complex number, this is called \bar{z} having real and imaginary part. So, to summarize this Point is important.

(Refer Slide Time: 17:00)

$i(t) = I_m \sin(\omega t - \theta)$
 $v_s(t) = V_m \sin(\omega t)$
 $Z = R + j\omega L$
 $\bar{V}_s = \bar{I} \bar{Z}$
 $\bar{I} = \frac{\bar{V}_s}{\bar{Z}}$
 $\bar{I} = \frac{V_m \angle 0^\circ}{Z \angle \theta}$
 $i(t) = \frac{V_m}{Z} \sin(\omega t - \theta)$

Phasor diagram: \bar{V}_s at 0° , \bar{I} at $-\theta$.
 $\bar{Z} = Z \angle \theta = R + j\omega L = R + jX_L$
 write \bar{Z}
 then get \bar{I}
 then $i(t)$

That here is a circuit R L here is your supply voltage V_{st} in time domain This is this archaic $V_{st} = \text{some } V_m, \sin \omega t$ and the current will be also real why things will be imaginary no imaginary thing in real life situations applied sinusoidal voltage you will get some current the value of this current is $I_m \sin \omega t - \theta$ and this was shown to be V_m by Z , Z what is j to do over $R^2 + \omega^2 L^2 \sin \omega t - \theta$. This is all done, but now I am telling that this circuit imagine it is like this R and here you write some $j \omega L$ and represent the variables as phasors.

So, supply voltage is the angle 0 degree and then the current \bar{I} you show it like this then we showed that $\bar{V}_s = \bar{I} \bar{Z}$ therefore, if I knew this earlier that forcing function maintain such a beautiful relationship similar to that of a disease or it vesical to I guess Nothing is better than that. What do you will simply do is the supply will descend a certain time wearing term remove that time terms represented by L and m V_s then the result in current 2 will be a feather \bar{I} and it will lag the supply this is ω , this is also ω moving.

So, currently lag by this and if you know the supply voltage then R problem is to find out the current After establishing these I will tell henceforward I will represent the supply voltage as $V_m \angle 0$, I will find out \bar{Z} like this, I will find out and say that my current in the circuit will be \bar{V}_s bar by j bar What is \bar{V}_s bar the am angry theater degree, what is \bar{Z} bar will be $Z \angle \theta$ Z into

the power $j\theta$ treatments and if you divide these 2 you will get V_m by $z - \theta$. So, I have solved for phasor current. Of course, I will be interested to know how current varies with time.


Then I will say if this is the phasor representation, $i(t)$ will be V_m by z sine of $\omega t - \theta$. Got the point that is you do your calculation in phasor point get the current feather find out the impedance of the circuit $\bar{z} = r + j\omega L$ it is a complex number, this is not a phasor it is neither rotating nothing like that, but the ratio of the voltage and current phasor comes out to be a complex number and so, \bar{z} I will be always using bar over it magnitude these z and angle is θ and we have shown in my last slide.

This is nothing but $z \sin \theta$ $z \cos \theta$ is $R + j\omega L$ is often called lead across of this arcade and written like excel inductive reactance. So, this is a very important and crucial step that is there is another alternative way of getting the solution due to force in function. You do not have to write down the differential equation anymore, it is those days are over after knowing these the voltage phasor and current phasor this ratio is a constant complex number decided by the circuit parameters if that be the case.

If I knew this, I would if I knew this relationship I should know do like this supply voltage is known \bar{z} is known, get \bar{I} and I will get this Current in further form but switching from feather to time domain does not take any time just looking at the title right side $\omega t - \theta$ but deployed therefore circuits with a cetacean excitation excitations. And if you are only interested in phasor sort, I mean steady state corrects then nothing is better than this phasor analysis.

Supply voltages they are represented in phasor form circuit parameters unknown, right \bar{z} your steps will be supply voltage weather, then write \bar{z} then get \bar{I} Then $i(t)$ time domain expression that is the thing. See it has got a tremendous now I am going to make a very big statement.

(Refer Slide Time: 24:21)

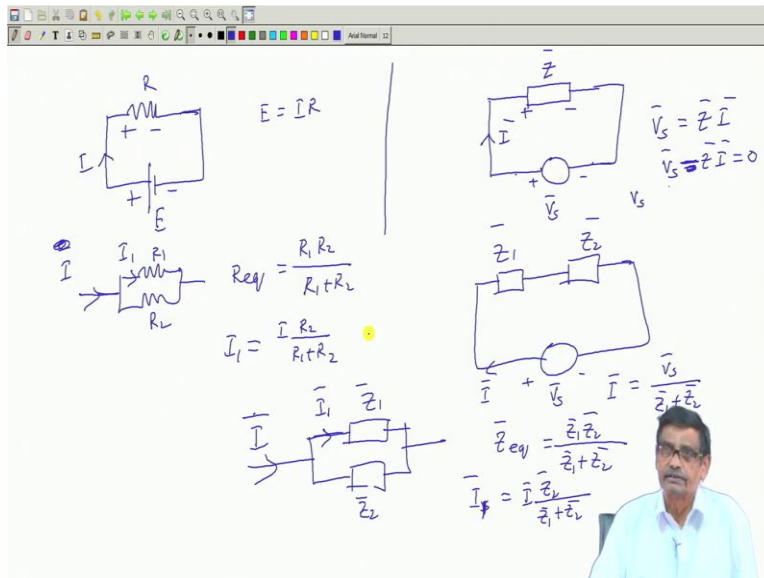

Now, in case of DC Circuit I told you this is the battery and this is the current and this is R and we know that $E = IR$ we have seen that now in AC circuit, there will be some impedance, z bar and here is some supply voltage, which is feather I will put a bar always to indicate phasors and this current i it is saying just like this no differential equation writing, no $+ -$. If that was the case, then I can invoke all the things I have learned with the AC circuits DC circuits that it is to resistances are connected in parallel if you volatize this $R_1 R_2$ by $R_1 + R_2$ how did I derive this based on this only wrote some KVL KCL equations here got discouraged.

For example, if the total current is I bar I what is the current I_1 will be I into R_2 by $R_1 + R_2$ all these things happen because $E = I R$ similarly here only thing is these are not some real numbers you have to deal with complex numbers. But nonetheless $V_s = z$ bar into I bar means that if 2 impedances are connected in 3 these is z_1 bar This is z_2 bar This is V_s bar current in this arcade will be I bar = V_s bar divided by $z_1 + z_2$, this will be the current, if the impedances are in parallel.

But this time you have to show with a bar in phasor domain will calculate everything here also z if you valet will be equal to z_1 bar z_2 bar same relationships had 1 world $+$. Similarly current in this branch, I_1 bar, all are phasor will be equal to total current I bar into z_2 bar divided by $z_1 + z_2$ bar see the power of the phasors notations lies here that immediately you get $V_s = z$ into I

hear is there any time terms no only complex numbers once you get that then all the rules of impedance manipulation resistance manipulations current divisions.

Similarly KVL here \bar{V}_s as you can see $-2 + \bar{V}_s + -i \bar{z}$ that is what $\bar{V}_s = -z \bar{I} = 0$. So, KVL equation KCL equations at the junctions in terms of phasors will all be valid. Anyway, we will continue with this in the next class but you see try to understand the flow of logic that brings us to phasor notations whether a relationship $V_s = IR$ in DC a DC Circuit It was so, obvious and everything is constant here.

Similarly, there exists similar relationship in SSL, but the only thing these are not time domain equations, these are all expressed in phasors and if you know further the presentation of any of the quantities voltage or current writing down the time domain expression should not take any time at all provided you know where do your difference where there is anyway, we will continue with this in the next class. Thank you.