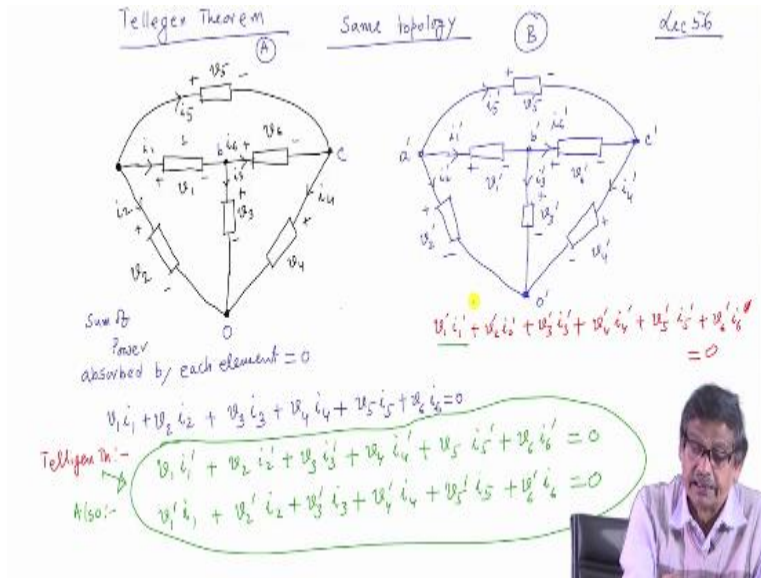


Network Analysis
Prof. Tapas Kumar Bhattacharya
Department of Electrical Engineering
Indian Institute of Technology –Kharagpur

Lecture - 56
Tellegen's Theorem

(Refer Slide Time: 00:12)



Welcome to lecture number 56 and we have been discussing with Tellegen's Theorem very interesting theorem Tellegen's Theorem. And in my last class I told it is applicable only to different networks, but having same topology, same topology and in this network 6 elements, in this network 6 elements, elements are different it is like that then about one thing I am certain.

Suppose I forget about the second network which are the this is suppose network A and this is network B where all the quantities I have marked with primes. Now in the network at least this thing I know if I calculate total absorbed total power absorbed by each element and sum them up that must be = 0. Now what is the power absorbed power absorbed sum of power absorbed by each element must be 0.

What is that power absorbed by element 1 $v_1 i_1$ so the plus current is entering (()) (02:02) element to absorbing power based on the voltage polarity and the current reduction yes it absorbs so $+ v_2 i_2$. What the element 3 is doing it is also absorbing power so it will be $v_3 i_3$. What is element 4 doing absorbing $+ v_4 i_4$. Element 5 absorbing $+ v_5 i_5$ and element 6 okay it is also absorbing $v_6 i_6$.

And this must be = 0 that is what we have learned. Similarly, in this network separately only thing this numbers have been replaced by prime therefore if you say I will use for network B it will be similar equation will be $v_1 i_1$ dash absorbing power all the elements are that is how I have assigned the introduction + $v_2 i_2$ dash + $v_2 i_3$ dash + $v_4 i_4$ dash v_3 dash v_2 dash v_4 dash + v_5 dash i_5 dash + v_6 dash i_6 dash that will be also 0 why not separate network.

So this is the power balance equation for each of the networks and nothing surprising about this, but now Tellegen's Theorem states that if you multiply voltages of network A with corresponding currents in those elements in network B that is what I will do Tellegen's Theorem this is not Tellegen's Theorem it is known total power absorbed will be 0. Tellegen's Theorem tells that you take voltage of this network let us use different color say you take this color voltage of this network across element 1.

Multiply with current i_1 dash same element, element number 1 of the second network + voltage of this network across element 2 that is v_2 I will not multiply with i_2 , but we will multiply with i_2 dash and so on $v_3 i_3$ dash + $v_4 i_4$ dash + $v_5 i_5$ dash + $v_6 i_6$ dash and Tellegen's Theorem tells that this two will be = 0. Alternatively, you take the voltage of this network and multiply with the current of network A then also it will be 0.

What does this mean. Also v_1 dash into i_1 that is voltage across each element of network B multiplied by the corresponding currents of network A and (\cdot) (06:01). So v_1 dash into i_1 + v_2 dash into i_2 + v_3 dash into i_3 + v_4 dash into i_4 + v_5 dash into i_5 + v_6 dash into i_6 that will be also equal to 0 that is the new thing the above 2 equations are okay individually we know for each network it is it looks surprising voltage of one circuit multiplied with current of another circuit this 2 has got no coupling etcetera how this happens.

But that is what Tellegen's propose that this has to happen and we will try to prove it. Proof is very simple and elementary nothing complex, but the statement of the theorem you have understood. Therefore 2 networks having same topology has to individually satisfy their own power balance equation that was known, but in addition to that this 2 lines this 2 equations are also true this is the Tellegen's Theorem.


Now we will try to see how this can be proved, why such a thing which is not so apparent

why voltage of this circuit and current in some other circuit even if their topologies are same why you multiply and sum them up we will give you 0 how do you say that. It must be told that this v_1 and i_1 dash for example v_1 into i_1 .

I know specifically it has got a physical meaning. What it is amount of power absorbed by the load, but so far as v_1 into i_1 dash is concerned we cannot assign any physical significance to that because voltage of across element one of this network and current of network B you are multiplying what does it physically signify we do not know. It is not possible to signify anything to this product.

Although $v_1 i_1$ and v_1 dash i_1 dash I know pretty well what this signify, but let us come to this result why it will be like that.

(Refer Slide Time: 08:53)

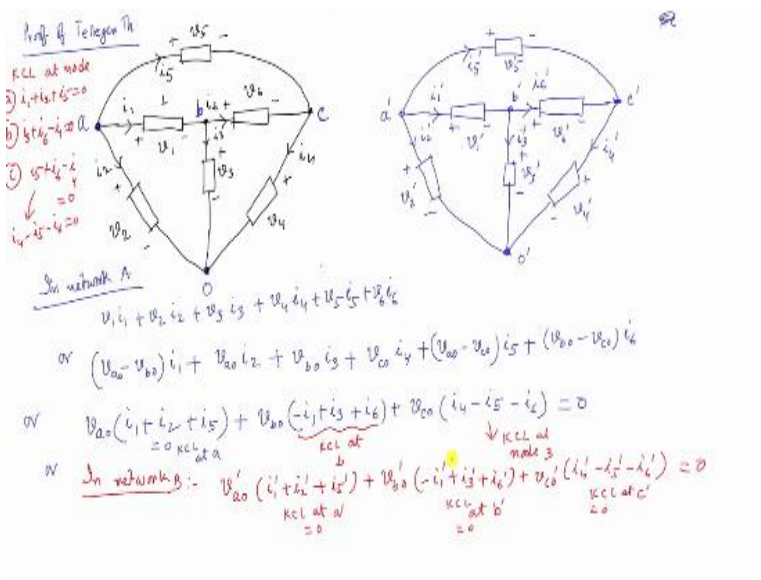

So I go to next page and paste it once again so this is the thing. So proof of this network I am trying to do. So this is so this is this network okay only thing this has not been copied this number was node a this is node b this is node c and this is node a all things have come correctly. Now from whatever network so this is Proof of Tellegen's Theorem. Now it is done like this suppose I calculate the power here that is I calculate $v_1 i_1$ of this network.

$v_1 i_1$ all are absorbed $v_2 i_2 + v_3 i_3 + v_4 i_4 + v_5 i_5 + v_6 i_6$. Now this v_1 or v_1 can be written as $v_{a0} - v_{b0}$ potential this v_1 is $v_{a0} - v_{b0}$ $v_{a0} - v_{b0}$ into i_1 this I can write + v_2 voltage across this element 2 is v_{a0} itself $v_{a0} - v_{00}$ that is 0. So $v_{a0} i_2$ for element 3 it will be simply $v_{b0} = v_{30}$. So v_{b0} into i_3 for element 4 it is + v_{c0} into i_4 and for element 5 it will be v_{a0}

direction of current I have assumed like this.

So $v_a - v_c$ is the voltage which will make this side + this side - into i_5 and finally the voltage across this element 6 is $v_b - v_c$ into i_6 this will be the thing and this I know is certain to be 0 because power observed by all the elements in this network, network A in network A this is the thing. Now what I will do is this I will collect the terms of v_a , v_b , v_c separately.

So I can say that v_a into from this term it will come $i_1 + i_2$ this term v_a no v_a here, here also there + i_5 and no other v_a this will be the thing I can write + v_b similarly I will calculate v_b . v_b is $-i_1$ this will give $-i_1$ this will give + i_3 v_b , v_b is here once again + i_6 this will be v_b then what is v_c all the terms v_c I am collecting no v_c here v_c no v_c it is i_4 .

Here $-i_5 - i_5$ and oh sorry then another term is there $-i_6$ and that must be equal to 0 that is what I am telling. You see I have calculated the power across each element and express the same quantity in terms of node voltages and some of the currents. Now you see or $i_1 + i_2 + i_5$ $i_1 + i_2 + i_5$ (()) (14:20) must be 0. This is KCL at a similarly $i_3 + i_6 - i_1$ at node b you see $i_3 + i_6 = -i_1$.

So here I write KCL this side only from this KCL at node a what it will be i_1 all currents are coming out from the node $i_1 + i_2 + i_5$ this must be equal to 0. KCL at node b node b what is there node b $i_3 + i_6$ going out so $i_3 + i_6$ and i_1 is coming in so $-i_1$ this must be 0 that is $i_3 + i_6 = i_1$ so $i_3 + i_6 - i_1$ must be 0 and at node c at node c it will be i_5 is converging at c i_3 . So $i_5 + i_6$ and another $-i_4$ is also coming $-i_4$ that = 0.

Which of course mean this is if you take two other side $i_4 - i_5 - i_6 = 0$ same thing. Therefore, you see this KCL at a similarly this term is KCL at node b and this term is nothing but KCL at node 3. So what I am telling is suppose you have not this is another way of proving that power balance. Suppose I am just calculating how much total power absorbed no = 0 I have put.

I know it has to be 0 this is one way of proving okay. In terms of node voltage you express and then you say v_a into 0 + v_b into 0 + v_c into 0 and this must be equal to 0 that is what

the power balance equation is. So the total power absorbed by all the elements has to be 0 and it has come out to be 0 and this only thing I have expressed in terms of node voltages that is all. Now come to this network, in this network everything is like this.

Therefore I have no point in going on writing v_1 dash i_1 dash + v_2 dash, i_2 dash what I am telling in network B. In network B which is totally a separate network B only thing all the quantities here has been replaced by primes. So same thing you will get if you apply only thing they will become prime that is i_1 dash + i_2 dash + i_5 dash then + v_{b0} dash into $-i_1$ dash + i_3 dash + i_6 dash and + v_{c0} dash into i_4 dash - i_5 dash - i_6 dash.

And once again i_1 dash + i_2 dash + i_5 dash will be KCL at a dash at node a dash. This is KCL at b dash and this is KCL this must be at c dash node number c dash. So this will be once again 0 v_{a0} into 0 so these are all 0 this term bracketed terms are 0 so this will be also = 0 that is separately the power balance will take place (()) (19:26) that is the whole idea. Now we are just the last line of proving this. What is that now I am telling that.

(Refer Slide Time: 19:47)

$$\rightarrow v_1 i_1' + v_2 i_2' + v_3 i_3' + v_4 i_4' + v_5 i_5' + v_6 i_6'$$

$$= (v_{a0} - v_{b0}) i_1' + v_{a0} i_2' + v_{b0} i_3' + v_{c0} i_4' + (v_{a0} - v_{c1}) i_5' + (v_{b1} - v_{c0}) i_6'$$

$$= v_{a0} (i_1' + i_2' + i_5') + v_{b0} (-i_1' + i_3' + i_6') + v_{c0} (i_4' - i_5' - i_6')$$

$$= v_{a0} \times 0 + v_{b0} \times 0 + v_{c0} \times 0 = 0$$

Okay let me do elaborately go to the next page and paste this one move it. Okay now come to this circuit once again. Now what I will be doing is this as suggested by Tellegen that now let us try to calculate v_1 and then i_1 dash voltage across this element and current in this element + power absorbed all the things + v_2 voltage across this and current in second element of network B this is network A this is network B + v_3 into i_3 dash + v_4 into i_4 dash + v_5 into i_5 dash and + v_6 into i_6 dash this is the thing.

Here on once again I will do the same thing that is v_1 this voltage is of course $= v_{a0}$ let me write that okay $- v_{b0}$ into i_1 dash v_2 , v_2 is nothing but v this is a mind you $v_{a0} + v_{a0}$ into i_2 dash what is v_3 v_{b0} into i_3 dash $+$ what is v_4 voltage across element 4 it is nothing but v_{c0} into i_4 dash. What is v_5 $v_{a0} - v_{c0}$ i_5 and finally across this element 6 v_6 is $v_{b0} - v_{c0}$ $v_{b0} - v_{c0}$.

This will be the thing into i_6 and once again I collect the terms of v_{a0} so just out of curiosity I have multiplied without knowing really what does it physically imply I have taken the voltage across element 1 and multiplied it with i_1 dash (i_1) (22:50) and so on just out of curiosity I am doing and then I collect the term of v_{a0} what I will be left with i_1 dash this is $+$ i_2 dash this i_2 dash will come.

And v_{a0} where else $+$ i_5 dash then for $v_{b0} + v_{b0}$ if you collect it is $- i_1$ dash from this then $+$ i_3 dash from this term and $+$ i_6 dash and finally v_{c0} into all the terms of v_{c0} that is i_4 dash from this place $- i_5$ dash from this and $- i_6$ dash this one. Now what is KCL at a KCL in network B at a dash is how much i_1 dash $+$ i_2 dash $+$ i_5 dash is 0. KCL at node b dash is i_3 dash $+$ i_6 dash $- i_1$ dash and that $= 0$.

And KCL at node c dash will be how much i_4 dash $- i_5$ dash $- i_6$ dash $= 0$. Therefore with this sum $a = v_{a0}$ into $0 + v_{b0}$ into $0 + v_{c0}$ into 0 and this has to be 0. This is the most interesting part see this v_{a0} a into now KCL of node see no matter this 2 circuits are independent $i_1, i_2, i_3, i_4, i_5, i_6$ will be totally different from i_1 dash, i_2 dash, i_3 dash, i_4 dash, i_5 dash and i_6 dash.

But i_1 dash, i_2 dash and i_5 dash when added must be 0 because it is the compulsion of this network to satisfy KCL at all the points at all the nodes a dash, b dash and c dash. So V_{a0} is multiplied with a term which is KCL at node a dash, b dash, c dash and they are 0 that is why we say that and we started with this and then came to this to establish that this indeed is 0. I am not going to elaborate it.

But you can easily see similarly v_1 dash if you wish to calculate you can calculate and i_1 I will do okay. So understood this, this is Tellegen's Theorem voltage across this element current in other sum them up then also it is 0.

(Refer Slide Time: 26:57)

Also note

$$v_1' i_1 + v_2' i_2 + v_3' i_3 + v_4' i_4 + v_5' i_5 + v_6' i_6$$

$$= (v_{a'o'} - v_{b'o'}) i_1 + v_{a'o'} i_2 + v_{b'o'} i_3 + v_{c'o'} i_4 + (v_{a'o'} - v_{c'o'}) i_5 + (v_{a'o'} - v_{b'o'}) i_6$$

$$= v_{a'o'} \underbrace{(i_1 + i_2 + i_5)}_{\text{KCL at } a = 0} + v_{b'o'} \underbrace{(-i_1 + i_3 + i_4)}_{\text{KCL at } b \text{ net } A} + v_{c'o'} (i_4 - i_5)$$

Similarly I could do which is just few lines I will write because it is necessary also this is network B this is network A also node that v1 dash into i1 (()) (27:25) + v20 dash voltages of this networks multiplied by the respective current in the first network that is network A actual current i2 + v3 dash + i3 + v4 dash i4 + v5 dash i5 + v6 dash i6 what this comes out to be. Okay same procedure v1 dash is what voltage across this element in terms of the node voltages v dash a0 – v dash b0.

I am sorry I should write it much more correctly va dash 0 dash this is this dash will come a dash 0 – b dash a dash 0 dash into i1 + v2 dash is nothing but v2 dash is this one v a dash 0 dash into i2 this is i1 + element 3 v element 1, element 2 is va dash 0 i2 element 3 is v b dash 0 into i3 b dash 0 dash + element 4 it is v c dash 0 dash into i4 element 5 v dash I mean b a dash 0 dash I am always making a mistake ba dash 0 dash – element 5 vc dash 0 dash.

And that will be into i5 current of this circuit and finally the last term that will be + that is element 6 which is vb dash 0 dash – b c dash 0 dash into i6 dash i6 and once again you collect the terms that is v a dash 0 dash it = i1 from this i1 will come then + i5 from this it will come and + i2 sorry i+ i2 also. So let me put this two comes first i2 + i5 similarly v b dash o dash will be equal to – i1 from this + i3 from this and + i6.

And finally v c dash 0 dash will come as v dash 0 dash c. C is not there here it is i4 – i5 and – i6, but what is this thing i1 + i2 + i5 is KCL of network at node a this is a b c and this must be 0. This one i1 + i3 is nothing but KCL at node b of network a not b dash but this must be 0 this network whatever it is separate, but it is satisfying KCL at around all the node i1 + i3 +

it hopefully it is coming correctly.

And finally this one is nothing but KCL at node c of network A these are all of network A. So this in general is your Tellegen's Theorem okay. One interesting point is that see okay it is nothing, but because KCL is satisfied that is why you get this. We will see its application next class, but another interesting thing is the voltage across each element of this network that is v_1 i_1 dash suppose this two circuits are having current bedding voltages and currents suppose time dependent thing.

It is also to be noted that you can take the voltages of this network I would set some time say T_1 all the voltages I have taken and the current values of this network I will take at some different times say T_2 still this will hold simply because KCL is satisfied of all the times no matter that it is satisfying now and then it is not satisfying not like that in fact we have pointed this out many a times while going.

KVL and KCL will be satisfied at all times in a circuit be it linear circuit, non linear circuit whatever it is KCL has to satisfy KVL has to satisfy. There are many applications in communication signal processing of this particular theorem, but we will apply here this theorem in our next class to establish another interesting circuit theorems called reciprocity theorem.

Thank you I stop here today, but go through this carefully it is very interesting otherwise two totally different circuit, but only a point is they must be of same topology then you cannot do you cannot have a circuit like this with triangular topology, with a circuit like that this circuit is different topology. I mean perhaps another element you bring in. You must see structurally there same time. Thank you.