

**Network Analysis**  
**Prof. Tapas Kumar Bhattacharya**  
**Department of Electrical Engineering**  
**Indian Institute of Technology-Kharagpur**

**Lecture # 06**  
**Nodal Analysis-I**

Welcome to lecture number 6 and we have been discussing 2 very popular method of solving a network problem. Of course, as I told you earlier that I will be considering to begin with.

**(Refer Slide Time: 00:28)**

Mesh Analysis / Node Analysis

Sources → constant DC values  
 Only resistances

KVL mesh 3  
 $-R_1 I_1 + R_3 I_2 + (R_1 + R_4 + R_3) I_3 = 0 \dots (3)$

KVL in mesh 1  
 $E_1 - R_1 (I_1 - I_3) - R_2 (E_1 - I_2) = 0$   
 or  $(R_1 + R_2) I_1 - R_1 I_3 - R_2 I_2 = +E_1 \dots (1)$

KVL eqn in mesh 2  
 $-R_2 I_1 + (R_2 + R_3 + R_5) I_2 - R_3 I_3 = -E_2 \dots (2)$

**(Refer Slide Time: 00:35)**

Mesh-1 KVL  
 $10I_1 - 7I_2 + 0I_3 + 0I_4 = 22 \dots (1)$

Mesh 2  
 $-7I_1 + 29I_2 - 18I_3 - 4I_4 = -12 \dots (2)$

Mesh 3  
 $0I_1 - 18I_2 + 30I_3 + 0I_4 = -7 \dots (3)$

Mesh 4  
 $-0I_1 - 4I_2 - 0I_3 + 5I_4 = -4 \dots (4)$

DC sources to be present only and all the resistances are there of course, that I will remove soon, that restriction just to get an idea how we applied this method to solve this network. Main thing is that in mesh analysis identify the number of meshes. In general number of equations to be solved is equal to the number of meshes algebraic equation, and if you are lucky in mesh analysis. If can reduce the number of equations to be solved, provided there exists some current sources in the outer meshes.

If you can identify some mesh where after this nothing is present then that mesh current is known that is there were only for example 2 meshes are there we have to solve only 1 question, this mesh current being known.

**(Refer Slide Time: 01:39)**

Mesh Analysis:

dec-6

$I_2 - I_1 = 2$  (1)

KVL in mesh 1:

$$6I_1 - 0I_2 = 4 - x$$

$$6I_1 = 4 - x \quad (2)$$

KVL mesh 2:

$$0I_1 + 6I_2 = -6 + x \quad (3)$$

assumed voltage across current source

✓

**(Refer Slide Time: 01:05)**

$P = 3 \times 2 \times 2$   
 Current source =  $6 \times 4 \text{ W}$  (absorbing)

$1.5 + 1.7 = 1.7 \times 4 + 3 \times 6 + 6 \times 4$

$I_2 = 2 \text{ A}$

$P_{\text{battery}} = 1.7 \times 10 = 17 \text{ W}$  (delivering)

$P_{\text{battery}} = 5 \times 3 = 15 \text{ W}$  (delivering)

$6 \times 3 = 1.8 \text{ V}$

$10I_1 - 6I_2 = 10 - 5 = 5$

$10I_1 - 12 = 5 \therefore I_1 = \frac{17}{10} = 1.7 \text{ A}$

$I_1 - I_2 = 1.7 - 2 = -0.3 \text{ A}$

$V_{AB} = 6 \times 3 - 5 = 1.8 - 5 = -3.2$

$\therefore V_{BA} = -V_{AB} = 3.2$

Now, what happens when I consider a circuit like this for example, you have a network like that, suppose this current is 2 ampere and this is there and here is another resistance maybe another battery is present and let us put some numbers to highlight this method because with numbers it becomes easier otherwise lengthy expressions, suppose it is 4 volt it is 6 volt with this polarity is important and this is 2 ampere ideal current source and this is supposed to 2 ohm.

This is suppose 4 ohm this is suppose 6 ohm and have to find out the current in various branches and solve this network. Now and I have decided I will apply Mesh analysis. So, first thing I identify the meshes, independent meshes are this too early. So, I will assign a current  $I_1$  here and  $I_2$  there this is  $I_2$  to Mesh Karts unfortunately here I cannot say  $I_2$  is 2 ampere. 2 ampere in this branch but about 1 thing I am here.

Current in this branch because of these assumptions of this mesh current this is true  $I_2 - I_1 = 2$ , this is definitely true has to be, because in this branch current is fixed a current source is present. So, what do I do then, if I want to apply mesh analysis, as I told you that suppose I attend to write down the KVL equation in mesh 1 KVL in mesh 1 it will be as we have learned, the sum of all the voltages in this loop has to be 0.

So, coefficient of  $I_1$  will be 6 into  $I_1$  is not coefficient of  $I_1$ . Now, here comes coefficient of  $I_2$ , there is no resistance here so, it is expected coefficient of  $I_2$  will be zero I mean  $-0 \times I_2$  let me

write that  $-0 \cdot I_2$  and on the right hand side I will write about the sources what are the sources for volt is present. So, on the right hand side and deduction of  $I_1$  is in consonant with this polarity of these 4 volt, so, +4 volt will come there.

Now, there is that another source which is 2 ampere current source, but as I told you, when the current source is there it is true the current in this branch has to be 2 ampere, but voltage I do not know got the point. So, that becomes an additional unknown therefore, the rule is same  $6I_1 - 0 \cdot I_2$  is this is equal to and only 2 meshes are there is equal to the source terms will appear. So, it is +4 volt it is over.

Now, here you have to then assume this thing I do not know these voltage is x volt because in an ideal current source current is fixed but voltage is decided by what are the things connected across it, so, many things are connected some voltage will definitely appear across x. So, this can be taken into account by rating like this, but here is the important thing, this is voltage across current source assumed voltage have assumed both.

The polarity and magnitude of the voltage x as I have shown assumed voltage across current source. So, this is the question so, what will be the thing then  $6I_1$  will be equal  $4-x$ . So, it looks like there are now 3 unknowns to mesh current and this x fellow. So, this is in mesh 1 in mesh 2 KVL in mesh 2 will be coefficient of  $I_1$  nothing there is no common resistance so  $0 \cdot I_1$ . Then coefficient of  $I_2$  is sum of all the resistances 6 only +  $6I_2$ .

That will be there and they should be equal to the sources on the right hand side. Sources should appear that is the logic we develop circuit from the basics so, this must be -6 volt because direction of this  $I_2$  and plus or opposite so, -6 and then there is another source whose voltage is not known, but I have assumed it to be x here should I write +6 or -6, +6 because this is the direction of  $I_2$  and here is the source. Whose voltage is + and -. So, +6 volt.

So, this equation was equation 1, this equation was equation 2 and this is equation 3 and nothing is to be any double. So, 3 unknowns 3 equations. Therefore, the point I want to stress if a current source appears in the common branch between 2 adjacent meshes then the number of equations

are to be solved is not equal to the number of meshes, but one more for in this problem more 3 equations.

This is 1 this is 2 this is 3 is not, but if this current source appears in the outer loop then you really get advantage got the point? In any case, normal thing we say generally in mesh analysis number of equations to be solved is equal to number of meshes. And in some particular cases when the current sources present in the outer meshes in some outer meshes of this circuit, then you get some advantage because those mesh currents are known but number of variables increases.

When there will be current sources present in the common branch. As in this simple example, we see  $I_1$   $I_2$ , they are of course, related by this current so, simple equation  $I_2 - I_1$  has to be 2 and then voltage of this current source is unknown. So, while writing down KVL equations, you follow the single coefficient of  $I_1$  some of resistances and so on, coefficient of  $I_2$  if there is no resistance in this branch it is  $0 \cdot I_2$ . But on the right hand side, this  $X$  will have to appear.

Do not be under the impression, this voltage is 0. You do not write anything here. It is not short circuit often students make mistake here understood. Therefore, if at all you choose mesh analysis, you should be careful about this points try to take advantage of the fact that current sources in many of the outer loops are present. Do not immediately go to mesh analysis because outer loop current sources means those mesh currents unknown.

Number of equations will be to be solved these will be less than the number of meshes. If current sources appear in the common wall between the 2 adjacent meshes, then actually number of equations to be solved becomes more understood, this point must be highlighted. Once again 1 can apply after you have solved as I told you solved it get the values if  $I_1$  comes out to be negative.

Then it is a good practice at least when you beginning to learn this course, regard the circuit. So, the actual current direction if  $I_1$  becomes negative put it negative see that case KCL really satisfied then you can do power balance of the network as usual. So that I am not doing so, I am

also not solving this network. So, 3 equations 3 unknown except than other nodes, now I will tell you about

(Refer Slide Time: 13:43)

Nodal Method for solving network problem.

no. of nodes  $n = 4$   
 choose a ref mode  $\rightarrow O$

$V_{A0}, V_{B0}, V_{C0}$   
 suppose these are

$I_4 = \frac{V_{BY}}{R_4}$   
 $= \frac{V_{B0} - V_{Y0}}{R_4}$   
 $= \frac{V_{B0} - E_2}{R_4}$

$I_2 = \frac{V_{AX}}{R_2} = \frac{V_{A0} - V_{X0}}{R_2}$   
 $= \frac{V_{A0} - (V_{B0} - E_2)}{R_2} = \frac{V_{A0} - V_{B0} + E_2}{R_2}$

$I_3 = \frac{V_{A0} - (V_{C0} - E_4)}{R_3}$

$I_6 = \frac{V_{C0} - E_3}{R_6}$

$I = \frac{V_{XY}}{R}$

The nodal method that is also very interesting and see, the point is, there are several techniques. If major techniques, then for a given network you try to adopt a method which will reduce your labor to solve the network that is the whole idea efficiently you try to solve that. So nodal method of solving network for solving network problem very good. Now in this problem once again let us take A an example suppose, and first I will write down in terms of variables, I mean symbols E1.

This is R1 this is R2 let there be another voltage source, it does not matter E2 there is voltage a voltage there and there is resistance here and another resistance there and also there is something like here. So, E1 let this be E2 let this be E3 and this is R1 R2 so this be R3 and this be R4 R5 and R6 in nodal analysis what they say is this that first identify how many nodes are there as in case of mesh analysis we identify how many meshes are there.

Now, junction between 2 elements in general can be called a node in general. But here what I will tell is this a no disappoint were more than 2 elements inside join. For example, this I will

call it a node got the point. For example, this I am not going to call a node elements of R2. And this element source is A, N has had been joined this I am not going to call. So at least so nodes are these things, at least more than 2 elements ends had been joined.

That I am going to call node. So here you see this, becomes 1 node. 1 to 3 ends of 3 elements have been joined this I am not going to call him node, although it can be called loosely, but this is how and this is another node. And this is another nodes and of course, this becomes another nodes and name the nodes. For example, call it a B C and let us call this to be O the essence of the nodal method for solving electrical circuit centers around this path.

I have told you that given a network the potential between any 2 points, what does it mean and how to calculate that, I know for example, if you have a resistance first, let us try to understand this is R, this is pointing, suppose, not in context with this A B. A general then the current through this if you say from A to B current is flowing, that is what you are assume, then I must right  $I = \text{potential of A with respect to B divided by R}$ .

The same thing I can write that a same R same AB points and if you assume the current to be in this direction he will write x ampere he should write the BA by x R you must understand this point. So, depending upon the direction of the current that is your choice potential of a potential difference across R is  $V_{AB}$ . We know that now, if this current in this R gate there is some other point to and if you have calculated  $V_{AB}$  can be written as  $V_{AO} - V_{BO}$  with respect to same point.

If you know the potential of point A with respect to the same point if you know the potential of point B, then  $V_{AB}$  will be nothing but the difference of these 2. Why? Because you see the AO. For example, in this example  $V_{AO}$  I know what I mean I have to start from O try to reach point B. So, I start from O suppose I decide I will go by had this path. So, put in shall appoint a can be written as from this to this whatever voltage will be there.

That is also potential difference between these 2 points  $V_{BO}$  start from O.  $V_{BO}$  he will get that is this draw and this draw we do regard to their + - sign you calculate this we have reached this

point is not  $V_{AO} = V_{BO}$ . Then from this to this you have to go and that voltage is what  $V_{AB}$  whatever it will be potential of A with respect to B you go. Therefore  $V_{AB}$  is always  $V_{AO} - V_{BO}$  it is an important thing.

That is with respect to but the point of reference should be same for both the ends, so, this you must understand and then I will say that forget about this we have understood this and this point so, that is the thing. So, what is done in nodal method is that first you identify how many nodes are there in this particular problem number of nodes, is equal to which I will denoted by  $n$  and in this case.

It is 4 it is that then what we will be doing is this will be and then I say that choose a reference Choose a reference node I have identified the nodes I have chosen a difference node and that reference node I have named it as O at this point you must understand that any of this I could choose as reference not necessarily this I got the point I could choose C as my reference. Now, what is a reference node with respect to this node, I will calculate the potential of further nodes.

That is, I am going to find out  $V_{AO}$ ,  $V_{BO}$  and  $V_{CO}$  got the point. If you have had chosen C as your reference then we will say I will calculate all the potentials of the circuit with respect to this point BAC, BOC, BBC. So in this case, I have just arbitrarily chosen O as a reference node generally one observation is this people choose that point as a reference node, where many aims of have been joined more than 3, 4, 5 bends are join that part will come to this.

So, I have chosen O as a reference node. Then I know what the, what is the meaning of  $V_{AO}$  means potential of A with respect to O, potential of B with respect to O potential of C with respect to O so, this is  $E_1$ ,  $E_2$ ,  $E_3$  and  $E_4$  now, I make 1 statement that in a network my final thing I have to calculate what will be the currents in various branches. For example in this branch what will be the currents.

Now, as I told you current in a resistance, if you have X and Y as it is 2 terminals, and if you want to find out current in this direction I, then you must write I as potential of X with respect to

Y by R this is crucial. There you do not fumble, this is the thing. Now, I am saying that if by some means, by hook or by crook, if you can somehow know this voltages this 3 voltages somehow you have been able to calculate doing what that to be discuss, but if I say that in this network node that VAO is known.

VBO is known say it is 10 volt VBO is 5 volt VCO is 12 volt. Suppose I say that, then I will say the calculation of branch currents will be just very simple now, why suppose, these are known, these are known, then I am saying that all the branch currents can be calculated using those 3 information alone how let us see for example, to calculate the current in this branch say I say I want to calculate this current this branch.

Although this is not named let me given him X this point let me call next, then what is this current I2 say this branch current I2 will be VAX potential of A with respect to X divided by R2 grab the resistance in that branch find out voltage across that resistance divided by R2 and no one can contest me this is absolutely correct. Now, this VAX this is the crucial step. I will write it as  $VA0 - VX0$  divided by R2, this will be this current title.

Now then I will say that look here VX0. Now, this point is crucial VX0, potential of X with respect to O because these are the things I know VA0 VB0 VC0 somehow I know so VX0 will be how much you know VB0 that means, you have already reached point B, then point B you cry to go to X. So, what it will be it will VB0 then + to - so  $-E2$  that will be the thing VX0 therefore, you see I2 then becomes I2.

VA0 then  $- VX0$  is nothing but this quantity  $- VB0 - E2$  it is not and that divided by R2 it will be  $= VA0 - VB0 - + E2$  divided by R2 this will be the current. So, can I not calculate I2 because I have told you that VA0 VB0 VC0 I am supplying you the values I2 can be expressed in terms of that it is after all a constant EMF value. So, these things are known I2 can be calculated take this current these branch currents say this current is I4 grab the resistance R4.

So I for, will be equal to, at this point no name is given. Let us call it Y. So to be consistent to this, expression here, I can write I4 will be nothing but VBY potential of B with respect to Y

divided by  $R_4$  this will be the current. Then what do I do  $V_{BY}$  can be written as  $V_{B0} - V_{Y0}$  with respect to same point divided by  $R_4$  this will be the current. Now, the big question is what is  $V_{Y0}$  from 0 you try to go to Y it is  $+E_2$  to nothing else. So, this =  $V_{B0} - E_2$  divided by  $R_4$   $I_4$  can be calculated.

Because  $V_{A0}$ ,  $V_{B0}$ ,  $V_{C0}$  are known very simple. Similarly,  $I_6$  can be calculated one can go on adding and I am now telling it will be simply you try on your own it will be  $V_{C0}$  and from these to these minus potential of this point if you call it Z,  $BZ_0$  is  $-C_3 +$  to  $-$  so,  $-C_3$  divided by  $R_6$  and so on similarly this branch current I am very quickly writing it will be this branch current say  $I_3$  if I say  $I_3$ , it will be called to  $V_{A0}$ . Will be there - potential of this point with respect to this.

And that can be translated into  $BC_0 - E_4$  and divided by  $R_3$  is not. So, in fact for a new branch you can do it therefore, first the point to be noted these days, identify the number of nodes and I just told you today that  $E$  this node voltage is unknown with respect to a difference node voltages say here  $n$  equal to 4. So, 3 node voltages 1 of them you will choose as reference and there is no condition that O is to be chosen as a reference.

Any 1 of them can be chosen as a reference I have chosen O. So, the other 3 node voltages with respect to that reference node. If these potentials are known, I am telling you, you have almost solved the socket. Because the branch currents, any branch current in this type of network can be expressed in terms of those node voltages. As example  $I_4$  is  $V_{B0}$ . And so on  $I_2$  is this one  $V_{A0} - V_{B0} + E_2$  by  $R_2$ .

Therefore calculations what is the essence of the thing in any branch grab the resistance. Whatever is present and apply this route these the fundamental ohms law voltage across this resistance is the current  $V_X$  by  $R_2$  is current from left to right. And  $V_{AX}$  can be written as  $V_{A0} - V_{X0}$  so, from O right to the reach X and you will find that can be expressed in terms of other node voltages and some sources present. Anyway we will continue with this in the next class. Thank you.