

Network Analysis
Prof. Tapas Kumar Bhattacharya
Department of Electrical Engineering
Indian Institute of Technology – Kharagpur

Lecture – 75
Two Port Network – V

We are discussing about reciprocity condition of 2 port network and we have found out for a given 2 port network conditions which must be satisfied if it is Z represented if it is y represented in terms of admittance matrix or if it is h parameter weight is represented and of diagonal elements some conditions are there Z_{12} should be equal to Z_{21} . Similarly, Y_{12} should be equal to Y_{21} but for h parameters there is a slight difference which should be once again h_{12} h_{21} but h_{12} should be equal to negative of h_{21} .

(Refer Slide Time: 01:02)

Condition of Reciprocity of a two-port network when represented as (A, B, C, D) parameters transmission line parameters. $[T] = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$ Lec-75

$\det \begin{bmatrix} A & B \\ C & D \end{bmatrix} = 1$

Find $\frac{V_1}{I_2}$ with $V_2=0$

$V_1 = AV_2 + BI_2$
 $I_1 = CV_2 + DI_2$

$V_1 = BI_2$
 $\frac{V_1}{I_2} = B$

$B = -\frac{B}{(BC-AD)} = \frac{B}{(AD-BC)}$
 $AD-BC=1$

Reciprocity condition

$\frac{V_1}{I_2} = \frac{V_2}{(-I_1)} = -\frac{V_2}{I_1}$ or $\frac{V_2}{I_1} = \frac{B}{(BC-AD)}$

Now today I will discuss condition for reciprocity of a 2 port network when represented as A, B, C, D parameter or transmission line parameters as A, B, C, D parameters what relation A, B, C, D parameters looks like that is A, B, C, D parameters you know this is A, B, C, D from the other two you may be tempted to say maybe something to do with the off diagonal element B should be C we will see that what it is really.

In fact, it is not $B = C$ let us see that so first of all draw the 2 port network and write down the general equations fundamental equations that is if you apply a voltage V_1 here this current is I_1

and here the voltage polarity is V_2 . But as I told you in case of A, B, C, D parameters which is also called T parameters transmission line parameters A, B, C, D parameters are also called transmission line parameter and usually written as T that is T is equal to this is T okay.

Anyway so this is the general thing I have drawn but while drawing this I should be careful about this I_2 fellow it is assumed always positive when it is going out like that and then the input quantities basic equations are V_1 and I_1 sending a voltage and sending a current of a transmission line is represented in terms of receiving end voltage and receiving end current that is $AV_2 + BI_2$ and $CV_2 + DI_2$ this is the thing this is a fundamental equations good.

But once again I have to find out V_1 / I_2 relation therefore first what we do is this find V_1 / I_2 with $V_2 = 0$ that is for this from which circuit this is to be found out that was the general circuit that is V_2 must be made 0. So, I will short-circuit it V_2 is 0 I_2 mind you this way and this is you have applied the voltage here V_1 . So, from this network I have to find out V_1 / I_2 this ratio and how can I find it out so V_1 / I_2 I find out okay and this ratio if I want to find out V_1 / I_2 so from the first equation I will say that look here V_1 / I_2 okay it is right.

So this first equation will then become how much V_1 is there from the first equation this $V_1 = AV_2$ that is $0 + BI_2$ that is very nice because I want to find out V_1 / I_2 and I have got it so I will keep this V_1 / I_2 that is the transfer impedance I have to calculate whatever it is V_1 / I_2 and this will become equal to B and keep this, this is an important result. Then what I will be doing is I will excite this output port with a voltage V_2 and keep this side short it.

And I_1 current direction of current as I have told you it is specified in this way; I should not play with this but anyway you excite this with V_2 short circuit this $V_1 = 0$ clear. Now I calculate V_2 / I_1 , but do you think that V_2 / I_1 should be equated to V_1 / I_2 no because you have energized V_1 and shown this current to be coming out I_2 . Therefore, you have applied V_2 here current in the other side in this direction is $-I_1$ I should take this ratio that is what important.

So anyway first calculate V_2 / I_1 that is V_1 / I_2 in this case because of this thing see the direction of I_2 in this case and the direction of I_1 should be consistent that is the ratio that is what

reciprocity theorem tells us. So V_1 / I_2 I have calculated I will keep it in which mode this is $V_1 +$
- and current is coming out from this output. Similarly, I have energized this with V_2 and but I_1 ,
 I_2 is specified like this.

So I must look forward for $V_2 / -I_1$ and this should be equated with V_1 / I_2 anyway let us see
what happens. So that is the thing with this thing if you come to the from the so $V_1 = 0$. So first
equation will give you 0 this is the second experiment we have put a horizontal line here first
experiment is over. Second experiment but this equation is fundamental $V_1 = 0$ should be equal
to A into V_2 is not $0 + BI_2$ this will be there.

And the second big equation is I_1 is there which is equal to $CV_2 + DI_2$ nothing is 0 here but you
want to find out V_2 / I_1 . So first divide by I_1 both sides any mistake point out. So I_1 you divide
so if you divide I_1 it will be $1 = C$ into $V_2 / I_1 + D$ I_2 , I_2 goes is it correct DI_2 / I_1 because I
have divided this to this or. Now who will give me this I_2 / I_1 business V_2 / I_1 , I have to do so if
you divide V_2 this is 1 that is what I have to do.

So what I will do is this instead of dividing first this I_2 I will represent it first step let us see, see
in this equation V_2 / I_1 is necessary. So from this equation I will find out I_2 as $-A / B$ into V_2 . So
that this equation $I_1 = CV_2$ was there plus D into I_2 and for I_2 I will put $-DA / B$ into V_2 is it
not this is the thing, and this will be equal to $BC - AD$ divided by B into V_2 or I will say V_2 / I_1
 $= B / BC - AD$ that is what I will get.


But the question is here because this I_2 I have a defined in a different way for one experiment
you have found out you have excited this side got the current this way. So to have the networks
satisfying reciprocity same polarity of voltage I have applied on this side, but I should take the
current in the same way is it not. So I should not equate $V_1 / I_2 = V_2 / I_1$ what it will be equated
to for the; this quantity for the reciprocity condition we must demand that V_1 / I_2 should be
equal to $V_2 / -I_1$ that is what I require which is $= -V_2 / I_1$.

This is very important to note because what happens A, B, C, D parameters are defined like that
all people are following this that is the convention because of this thing happens. Therefore, I

will say then V_1 / I_2 is B. B should be equal to $-V_2 / I_1$ that is $-B / BC - AD$ which means that $B / AD - BC$. B, B goes and I will say $AD - BC$ should be equal to 1 that is the condition therefore if a network two port network is represented in terms of A, B, C, D parameters B and C alone does not decide whether it is a of diagonal elements same or no.

The condition is totally different it says that determinant of this matrix A, B, C, D determinant this must be equal to 1 that is the condition got the point therefore if it is represented in terms of impedance matrix Z_{12} is Z_{21} if it is in terms of admittance matrix Y_{12} should be equal to Y_{21} if it is h parameters then also h_{12} and h_{21} but h_{12} should be negative of h_{21} and if it is represented in terms of A, B, C, D parameters this is the condition final condition got the idea. So this is how it is to be found out see reciprocity property you must as I was telling if somebody says that one should not be have any doubt about the step one that is why I am telling.

(Refer Slide Time: 15:50)

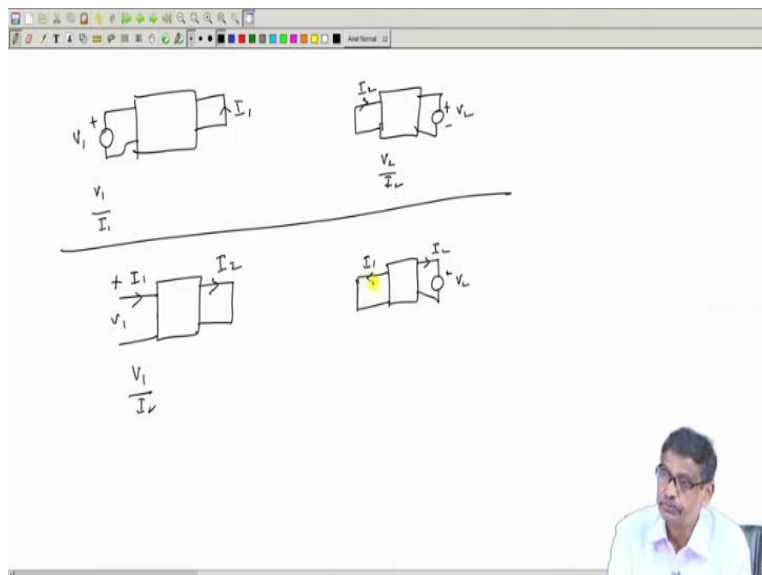

If somebody says here is a network and you apply a voltage here V_1 forget about these Two port network V_1 you have applied and you record this current in this direction I_1 calculate this ratio V_1 / I_1 now what I am telling if the same network if you excite keeping the voltage polarity same with V_2 and short it and tell this current to be also I_2 like this then there is no conflict everything is then V_1 / I_2 should be equal to V_2 / I_2 . Here current is coming in here also current is coming in case of A, B, C, D parameters what has happened if somebody says that this is V_1 this is I_1 and somebody says that I_2 I will take like this calculate V_1 / I_2 of this.

But then in the second case this is V_2 this remains I_2 , but this current is of interest transfer this voltage and divided by this current. If somebody says this current is I_1 when you short it because deduction of current is my prerogative I will choose the way I like then this impedance V_2 / I_1 if you calculate and equate it to V_1 / I_2 that is not fair that is not correct that is what I want to tell what you should do V_1 / I_1 that is fine so V_2 / I_1 in this way if you assume that is okay. So i think you have got the point any doubt hopefully okay that is fine okay.

(Refer Slide Time: 18:27)

Suppose a Two port network is Reciprocal $\Rightarrow Z_{12} = Z_{21}$
 If represented in terms of Z-parameters

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$V_1 = Z_{11} I_1 + Z_{12} I_2$
 $V_1 = Z_{11} I_1 - Z_{12} I_1 + Z_{12} I_1 + Z_{12} I_2$
 $V_1 = (Z_{11} - Z_{12}) I_1 + Z_{12} (I_1 + I_2)$ — (1)

$V_2 = Z_{21} I_1 - Z_{12} I_1 + Z_{12} I_1 + Z_{22} I_2$
 $V_2 = (Z_{22} - Z_{12}) I_2 + Z_{12} (I_1 + I_2)$ — (2)

The diagram shows a two-port network with input voltage V_1 and current I_1 , and output voltage V_2 and current I_2 . It illustrates the process of short-circuiting the output to find Z_{12} and Z_{21} .

After I have done this now the question is you will be able to solve several problems okay today I will tell you an interesting thing that is suppose a Two port network is reciprocal okay we know what it means therefore if represented in terms of Z parameters I have represented in terms of Z parameters then these equations are true. So reciprocal so I know that then $Z_{12} = Z_{21}$ that is what. So $V_1 = Z_{11} I_1 + Z_{12} I_2$ and $V_2 = Z_{21} I_1 + Z_{22} I_2$ is it not.

But in that case, $Z_{12} = Z_{21}$ okay so this equation then by writing metrics way it is okay so I can replace it this one sorry by Z_{12} itself of diagonal elements will be same that is what we have found. Let us look at the first equation V_1 can written as $Z_{11} I_1 + Z_{12} I_2$ that is fine then I will just manipulate this equation a bit this way I write Z_{11} . I will go step by step so I will write it is equal to $Z_{11} I_1$ was there then what I do I subtract this term $Z_{12} I_1$ and add the same terms like this I can do that everything remains same.

Now this V_1 then will become $Z_{11} - Z_{12}$ into I_1 and this one will be sorry this one will be Z_{12} into $I_1 + I_2$ is it not like this so keep this the equation 1. Similarly, you play with the second equation what do you do that second equation $V_2 = Z_{22} I_2$. So, you write $Z_{22} I_2$ then subtract $Z_{12} I_2$ then add $Z_{12} I_2$ so that it remains same as it was and finally the first term is always there $Z_{12} I_2$.

Therefore, it can be written like this that $Z_{22} - Z_{12}$ into I_2 these two terms and this one will be $+Z_{12}$ into $I_1 + I_2$ let this equation be 2. Now if it is like this then this 2 port network can be because see in these 2 port network what I told I do not know how the impedances are connected actual networks we have shown with some example earlier that $+ - V_1$ these are the terminal voltage current I am only measuring and trying to model in my own way whether Z parameters, h parameters or things like that that is fine $V_1 I_1 V_2 I_2$ now and I find out the parameters and I am told that it is a reciprocal networks.

So in that case Z_{12} must be equal to Z_{21} therefore this basic equation can be written like this that is highlight these two equations this equation and this equation looking at this equation I will say that inside this network I can presume that the network is a T connected network $Z_{11} - Z_{12}$ and this one these are impedances $Z_{21} Z_{22}$ and Z_{12} and here Z_{12} these are very interesting desserts and see earlier it was unknown how these impedances are there.

But what I am telling it was a black box I found out these and also concluded it is a reciprocal network during the course of experiment Z_{12} came out to be same as Z_{21} I concluded it is a reciprocal network if it is then I am telling manipulate these 2 equations in this way then you see the this is your V_1 you are applying plus minus this is your V_2 you are applying this is also plus minus.

Now this current I_1 is like this so what is this current I can think it is I_1 goes in. Similarly, this current V_2 I always assume in this way so this current is going like this that is this $I_1 I_2$ be thought up to be a look current of this state work of this T network it is called it looks like a T


where the elements impedance values of this one is $Z_{11} - Z_{12}$ it is $Z_{22} - Z_{12}$ and Z_{12} you see this what is the loop equation here the first equation look at $V_1 = Z_{12} I_1 + Z_{12} I_2$.

What is the current flowing through this branch $I_1 + I_2$ into Z_{12} ? And these 2 voltages must balance V_1 that is what exactly I am getting. Similarly, in the second loop applied voltage is V_2 it will be $= Z_{22} - Z_{12} I_2$ but what is the current flowing through this Z_{12} it is $I_1 + I_2$ and $I_1 + I_2$ into Z_{12} . So this then tells me that okay you may not be knowing the internal structure of the impedances how they are connected.

But if it is a reciprocal network you can always think this network is nothing but a T network with these parameter values are you with me that is I am now telling something more inside this I can now think of it is a network like this got the point which was hidden to not known to me and once you do this let me be in this page only once you do this see the interesting part is these are the ports these are available to me and inside.

Now I can think okay it is a T network or this one if it is like that these 3 impedances that connected in star I could also if I wish this star, I will represented by some delta impedance because I now know the parameter values here, there, there. So I can also represent it by an equivalent let me go to next page.

(Refer Slide Time: 29:22)

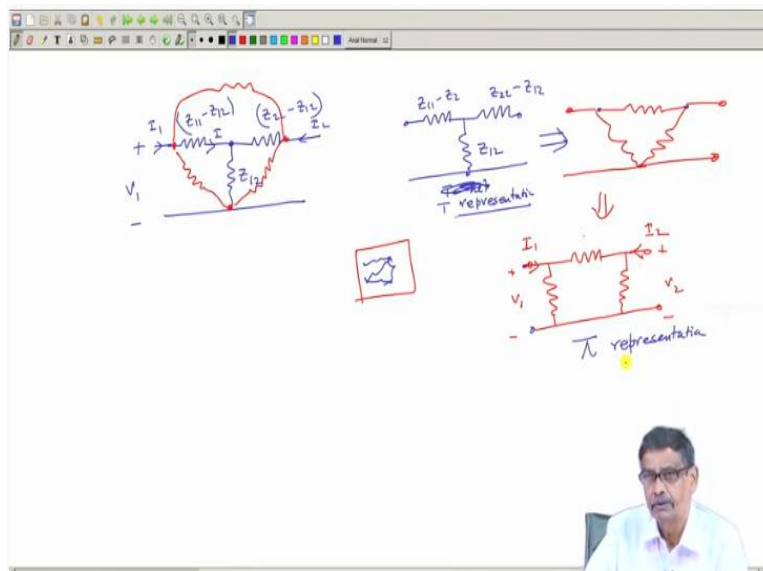

So I have got this thing I do not bother what or how complex the network was but ultimately I have shown that if this is a supply voltage this is the current I_1 you can represent it as a this, this is Z_{12} know and this is $Z_{22} - Z_{12}$ this is I_2 this is I_1 and this current is $I_1 + I_2$ and so on we have seen that let me now put too many things here and all the parameter values are known this, this and this now what I am telling these three impedances are connected in star.

Therefore, I can replace this by some equivalent delta these are the key points about which I can do the star delta transformation and I will put it like this, and it is the blue terms. So this this star connected networks that is this 3 that is a good thing $Z_{11} - Z_{12}$ $Z_{22} - Z_{12}$ and this is Z_{12} with respect to these 3 points this can be these 3 points are I cannot touch their 3 terminal 2 port network, this can be drawn as a circuit like this. Is it not, that is what I told you.

This is my input port, and this is my output port input port remains same or with respect to input and output port you can write like this. So I_1 V_1 this is V_2 and this is I_2 what will be the value of this impedance star connected rule I will apply this plus this plus this into this divided by this. So I can always find out these values also therefore I am telling that in a sense generally all the networks will be bilateral and linear networks.

And no matter how in the complex way the impedances are connected inside this black box. If you tell me the value I will always tell that okay this network can be represented as a T network if it is like this, this is the T representation T network T representation T this is not the way to A, B, C, D parameters T representation or you can say it is a pi representation do I know the values of these impedances yes I know because I know and vice versa.

Therefore, remember how or whatever complex way the impedances are connected inside eventually you can with respect to the input and output ports you can consider to be some lumped parameters connected in T fashion and delta fashion pi fashion and this is widely used in power system sort of representation and we will continue further with our discussion what do I mean by series parallel connection of 2 port networks in my next class. Thank you