

Network Analysis
Prof. Tapas Kumar Bhattacharya
Department of Electrical Engineering
Indian Institute of Technology – Kharagpur

Lecture – 76
Two Port Network – VI

So in this lecture we are going to tell you about the symmetry property of a Two port network under what condition we call this 2 port network to be symmetric and will be followed by the series parallel and cascade connection of 2 port network. So let us see what does that symmetry means.

(Refer Slide Time: 00:41)

The handwritten notes on the whiteboard show the following derivations:

- Circuit Diagram:** A two-port network with input voltage V_1 and current I_1 entering, and output voltage V_2 and current I_2 leaving.
- Z-Parameters:**

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$
- Reciprocity Condition:**

$$Z_{12} = Z_{21} \text{ for Reciprocity}$$
- Symmetry Condition:**

$$Z_{11} = Z_{22} \rightarrow \text{symmetric}$$
- Y-Parameters:**

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$
- Derivation of $Y_{11} = Y_{22}$:**

$$\left. \begin{aligned} I_1 &= Y_{11} V_1 + Y_{12} V_2 \\ I_2 &= Y_{21} V_1 + Y_{22} V_2 \end{aligned} \right\} \begin{aligned} \text{At } I_2 = 0: & 0 = Y_{21} V_1 + Y_{22} V_2 \Rightarrow V_2 = -\frac{Y_{21}}{Y_{22}} V_1 \\ \text{Substituting in } I_1: & I_1 = Y_{11} V_1 + Y_{12} \left(-\frac{Y_{21}}{Y_{22}} V_1\right) \\ &= \left(Y_{11} - \frac{Y_{12} Y_{21}}{Y_{22}}\right) V_1 \\ \therefore \frac{V_1}{I_1} \Big|_{I_2=0} &= \frac{Y_{22}}{Y_{11} Y_{22} - Y_{12} Y_{21}} \end{aligned}$$
- Final Result:**

$$Y_{11} = Y_{22}$$

You recall that in a 2 port network we have drawn these figures several times but this is V_1 this is I_1 and this is V_2 this is I_2 and we are writing sometimes capital sometimes these one because they may be in time domain they may in Laplace domain they maybe in frequency domain it does not matter but the point is we have seen that the if these 2 port networks is expressed in terms of z matrix it will be and that is the input voltage and output voltage can be written as we did not ask they the $Z_{11} I_1$ okay we are writing capital letters let me write that.

So these are I_2 and this is I_1 and we have seen that V_1 is so $V_1 = Z_{11} I_1 + Z_{12} I_2$ is it not and $V_2 = Z_{21} I_1 + Z_{22} I_2$ we have seen that if this a network 2 port network is when this 2 port

network will be which property that is reciprocal if these 2 port network is reciprocal you have seen that Z_{12} should be equal to Z_{21} that we have established earlier for reciprocity.

Similarly, whether there exists any condition under which these metrics will be symmetrical. These 2 port network will be symmetrical okay. A 2 port network is said to be symmetrical if these 2 elements are same for an impedance case if Z_{11} is it not is equal to Z_{12} then it is a; to be symmetrical Z_{22} symmetric now. What is Z_{11} , $Z_{11} = V_1 / I_1$ with I_2 equal to 0 that is the driving point impedance of the network looking for port 1 and driving point importance of these 2 port network looking from a port 2 that is V_2 / I_2 with $I_1 = 0$.

If these two are same if these two ratios are same under the condition that $I_2 = 0$ here and I_1 is equal to that is secondary is opens circuit driving point impedance are same, then it is this one. So naturally this is the condition for reciprocity that is no matter in which form you describe the Two port network that is in short circuit admittance matrix or A, B, C, D parameters or h parameters whatever you do this is the thing driving V_1 / I_1 with $I_2 = 0$ you have find out and V_2 / I_2 with $I_1 = 0$ you find out and for impedance metrics this one it happens to be $Z_{11} = Z_{22}$.

So the thing is this thing I have to calculate that is V / I_1 with $I_2 = 0$ should be equated to V_2 / I_2 with $I_1 = 0$. So let us see what happens if it is admittance parameters if we describe the function so for y matrix so it will be called I_1 and I_2 it will be equal to $Y_{11} V_1 + Y_{12} V_2$ and this will be $= Y_{21} V_1 + Y_{22} V_2$ is it not therefore to find out V_1/I_1 with $I_2 = 0$ I have to calculate this under this condition that is if we want to find out V_1/I_1 with $I_2 = 0$ first I will find out this.

So this equation then will give me for this condition I_2 being 0 the second equation will give you $0 = Y_{21} V_1 + Y_{22} V_2$ this is the second equation will give me this because $I_2 = 0$ and the first equation will give you is $I_1 = Y_{11} V_1 + Y_{12} V_2$ my objective is to calculate V_1 / I_1 so V_1 is there I_1 is there but here is a V_2 and this V_2 I will calculate from this first equation as $Y_{21} = -Y_{22} / Y_{12}$ into V_1 and this I will substitute here or I will say $I_1 = Y_{11} V_1$ and then for V_2 you substitute this and this will become $- Y_{21} Y_{12} / Y_{22}$ into V_1 and this will be $= Y_{11} Y_{22} - Y_{21} Y_{12} / Y_{22}$ into V_1 .

Therefore, you can easily say that V_1/I_1 with the condition $I_2=0$ will be $=Y_{22}$ divided by Y_{11} $Y_{22} - Y_{21} Y_{12}$ this will give then I calculate V_2/I_2 this of course is obvious hopefully I will get $Y_{22} = Y_{11}$ why not driving point admittance should be same. So anyway I will do this very quickly, so V_2/I_2 I want to find out with the condition $I_1 = 0$.

So from the first equation I will get $0 = Y_{11} V_1 + Y_{12} V_2$ this is the first equation and second equation is $I_2 = Y_{21} V_1 + Y_{22} V_2$ this is the second equation and I want to find out V_2 / I_2 so V_1 I will substitute from the first equation so it will be V_1 will be equal to minus Y_{12}/Y_{11} is it not into V_1 into V_2 and plus $Y_{22} V_2$. So this will be the once again $Y_{22} - Y_{21} Y_{12} / Y_{11}$ into V_2 . So V_2 / I_2 this is what I have to find out with $I_1 = 0$ will be simply Y_{11} divided by the same thing $Y_{11} Y_{22} - Y_{21} Y_{12}$ this and these.

If you equate these two, the conclusion is Y_{11} should also be equal to Y_{22} that is driving point admittance should be also same. So this is the condition for a 2 port network which represented in the form of admittance matrix this condition should be satisfied.

(Refer Slide Time: 11:21)

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$

$$\left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}}$$

$$\left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{1}{h_{22}}$$

$$\therefore \frac{1}{h_{22}} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}}$$

$$\text{or } h_{11} h_{22} - h_{12} h_{21} = 1$$

$$\text{or } \det \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = 1$$

Now let us do it for h metrics what condition it will satisfy in order that it becomes a symmetric matrix. Therefore, you recall that this h matrix equation is V_1 I_2 is equal to is it not $h_{11} I_1 + h_{12} V_2$ and this is $h_{21} I_1 + h_{22} V_2$. So this is the 2 port network plus minus these are the conventions which we should not break to find out anything. So this is V_2 , this is I_2 suppose this

relationships are expressed in terms of the h parameters then we know to test the symmetry we have to calculate this V_1 / I_1 with $I_2 = 0$ and V_2 / I_2 with $I_1 = 0$ and I will equate them to get the desired condition.

That is what I have to do so in this case the first one if you take that is, I want to calculate V_1 / I_1 with $I_2 = 0$ means that I will keep the secondary open circuit I will apply some voltage here. Therefore, from the first equation we will get $V_1 = h_{11} I_1 + h_{12} V_2$ that you will get is it not and from the second equation you will get $0 = h_{21} I_1 + h_{22} V_2$ this is from this equation you will get this, and I want to calculate V_1 / I_1 .


So this V_2 I will express in terms of I_1 therefore here I will write V_2 nothing but $-h_{21} / h_{22}$ into I_1 and this I will put it here then it will be $V_1 = h_{11} I_1 + h_{12} (-h_{21} / h_{22} I_1)$ that means $-h_{12} h_{21} / h_{22}$ and this into I_1 it will be like this. Therefore, we get V_1 / I_1 with the condition that $I_2 = 0$ output port open circuit you will get $h_{11} - h_{12} h_{21} / h_{22}$ divided by h_{22} this is what you will get I will all this is equation 1.

Similarly I will calculate a now calculate V_2 / I_2 with the condition $I_1 = 0$ that is primary side there is input side is open circuited so that $I_1 = 0$ you excite with the voltage V_2 and record this quantities then you will get from the first equation since $I_1 = 0$ V_1 will be equal to $h_{12} V_2$ this is simply $h_{12} V_2$ I will get the from the first equation and from the second equation you will get I_2 is equal to this equation I am writing now $I_2 = h_{21} (0) + h_{22} V_2$ this is what I will get and this is $h_{22} V_2$ I have to calculate V_2 / I_2 is it not V_2 / I_2 I have to calculate everything is fine here.

So V_2 / I_2 from the second equation itself I get that V_2 / I_2 from this equation is $1 / h_{22}$ therefore the condition this is with $I_1 = 0$ and I know that for these Two port network to be symmetric this one and this one this ratio this and this they must be equal therefore the condition is $1 / h_{22} = h_{11} - h_{12} h_{21} / h_{22}$ or I will say this h_{22} cancels out provided it is not equal to 0, h_{22} cannot be 0.

Therefore, the condition is $h_{11} h_{22} - h_{12} h_{21}$ this must be equal to 1 or I will simply say the determinant of this matrix $h_{11} h_{12} h_{21} h_{22}$ this must be equal to 1. Determinant this determinant if it is 1, I am sure it is a symmetric 2 port network is that clear? now we will see what about A, B, C, D parameters how it will what are what is the condition when a 2 port network same Two port network is expressed in terms of A, B, C, D parameters then if that network is to be symmetric what is the condition? So let us do it once again.

(Refer Slide Time: 18:47)

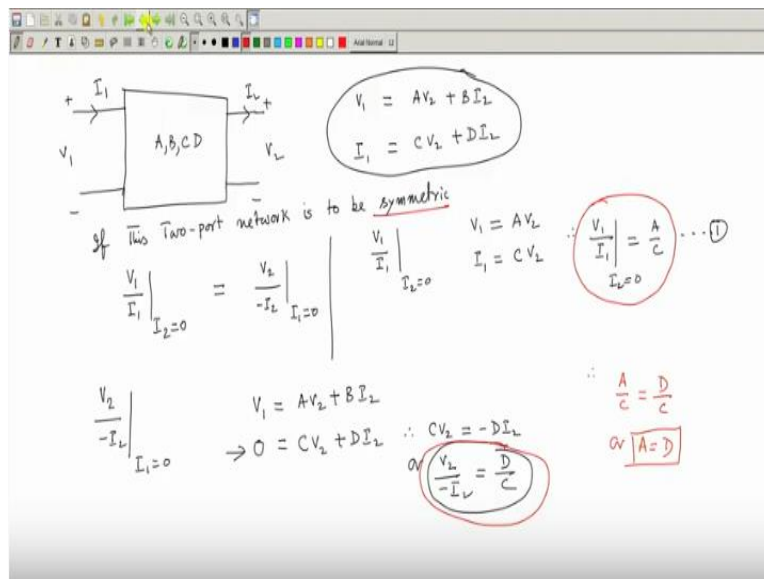

So a network is like this suppose a this network is expressed in terms of T parameters or A, B, C, D parameters this is this thing plus minus V_1 and this is I_1 is it not and for A, B, C, D parameters what I have assumed earlier that is will keep it, it is like this this is the convention for A, B, C, D parameters or transmission line parameters and then we know there is input voltage and current you know it is expressed in terms of $AV_2 + BI_2$ and this is equal to $CV_2 + DI_2$ these are the conditions.

But what if this network is to be symmetric if this 2 port network is to be symmetric I will demand that V_1/I_1 with $I_2 = 0$ is with $I_2 = 0$ this is open circuited V_1/I_1 driving point impedance of this network they should be equal to $V_2/I_2 = 0$ is it not but what should I write here I should write minus I_2 driving point admittance is this. This you must understand very clearly so in this case because of this surprise change in the direction of I_2 while describing an A, B, C, D parameters this is I have to do.

But so far as driving point admittance that is the impedance is concerned Z_{22} . So the current is to be reversed because for Z parameter it enters you have got the point. Now this is the thing therefore let us first calculate first do this V_1 / I_1 with $I_2 = 0$ this thing so what we get? With $I_2 = 0$, V_1 from the first equation these are the fundamental equation for general case okay. So $V_1 = AV_2 + 0$. I am not writing that from this first equation $I_2 = 0$ from the second equation for the same condition you will get $I_1 = CV_2$ is it not that is what you will get.


Therefore, the ratio V_1 / I_1 you just divide these 2 and you get your desired result that is I wanted to calculate V_1 / I_1 with $I_2 = 0$ then I will get it as this by this which will be equal to A/C I keep this result with me. Now I have to calculate $V_2 / -I_2$ okay for the second now I have to calculate V_2 divided by $-I_2$ with $I_1 = 0$ I have to calculate. Now to calculate that first let us see from these equations what we get we get that $I_1 = 0$ and so the first equation is $V_1 = AV_2 + BI_2$ that is there and from the second equation I will get this equation $I_1 = 0 = CV_2 + DI_2$.

But I have to calculate V_2 / I_2 and V_2 / I_2 can be calculated from this itself is it not first equation is not necessary if wrong tell me so this is fine. Therefore, I will say that $CV_2 = -DI_2$ or I will say that $V_2 / -I_2 = D / C$ this is the thing I will get and so these two should be equated this and this should be equated? So what will be the result? therefore to be symmetric these two should be same that is $A / C = D / C$ or $A = D$ is the condition is that clear $A = D$ is the condition.

Therefore, for A, B, C, D parameters just looking at the values of A, B and C and D we can conclude whether this we can say about these Two port network whether it is symmetric or not that is the thing. So for a 2 port network to be symmetric if it is expressed in terms of impedance matrix Z_{11} should be equal to Z_{22} , Y_{11} should be equal to Y_{22} and if it is expressed in terms of h parameters then the determinant of h matrix should be equal to 1 and if it is expressed in terms of A, B, C, D or T parameters then A and D should be equal.

So this is about the symmetry in the same way we have found out the conditions for a network to be reciprocal like that several conditions we have found out. Now what I will do is this so this is the thing okay understood.

(Refer Slide Time: 26:21)

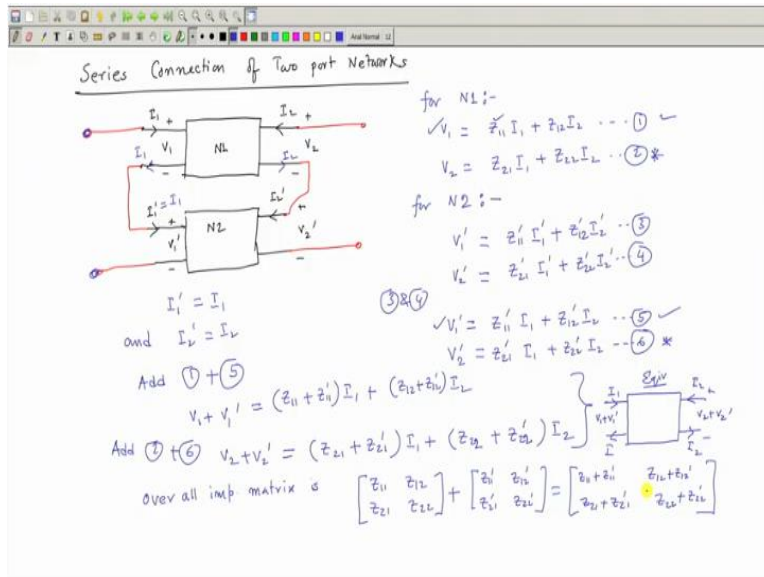

Therefore, we will know say something about series parallel connection of various Two ports network okay series connection these are very simple stuff not tough at all series connection of Two ports networks. Now suppose we have got two 2 port networks it can be extended to three 2 port networks as well only for 2 if we understand we know what to do with others, so this is 1 plus minus this is V1 this is I1 and this is the network plus minus V2 and this is I2.

Now so this is network 1 take another network so N1 Two port network another network N2 it will also have a pair of terminals here in the input port and also in the output port. Let this be called I1 dash and its input voltage be called V1 dash and this voltage is plus minus V2 dash and this is I2 dash. First of all, what do I mean by serious connection when we say that these two 2 port networks are in series it means that the input ports will be in series connected that is this connection, I will show with a red color it is connected like this and these 2 are the total input of this.

Similarly, on the output side you connect them in series and treat these 2 as output terminals. Now obviously you can easily see that suppose I am expressing this network N1 and N2 in terms of impedance parameters suppose so what we are what we will be getting? So far as network N1 network 1, I will get $V_1 V_2 = Z_{11} I_1 + Z_{12} I_2$ that is what I will get is $Z_{21} I_1 + Z_{22} I_2$ this

is for network. For network 2 what I will get. So far as this one is concerned, I will say all the parameters will be replaced by dash here.

So V_1 dash is the input voltage for N2 input port voltage and V_2 dash these are the input voltages and they are expressed in terms of Z_{11} dash I_1 for this network parameter value maybe different we do not know I_2 so I_1 dash I_2 dash. Similarly, Z_{21} dash I_1 dash + Z_{22} dash I_2 dash this will be the thing. Now this if you so this is equation 1 this is equation 2, 3, 4 okay this is how I have written it but now you see that because these 2 ports are series connected this I_1 dash is nothing but I_1 itself this I_1 and I_1 dash they are same.

Therefore, these 2 equations can be similarly so important thing to note is I_1 dash = I_1 and I_2 dash = I_2 so these 2 currents were the same if that be the case then V_1 dash is equal to this 3 and 4 I am rewriting after knowing this I will say it is nothing but Z_{11} dash I_1 + Z_{12} dash into I_2 dash and the fourth equation that is this one will then be Z_{21} dash I_1 + Z_{22} dash into I_2 I am sorry this dash goes because I am using this equation.

So this is 5 and 6 same 3 and 4 equation with this 5 and 6 here. Now what do you do you add that is equation 1 and 5 you add, if you add equation 1 and 5 you will get left hand side you will get $V_1 + V_2$ dash this equation and this equation I am adding so $V_1 + V_2$ dash it will be simply $Z_{11} + Z_{11}$ dash into I_1 this term and this term added up similarly this term and this term added up so plus of $Z_{12} + Z_{12}$ dash into I_2 that is what I get is it not have I written something wrong yeah I believe.

So this is $V_1 + V_1$ dash so $V_1 + V_1$ dash similarly you add 1 + 5 I have added now I will add 2 + 6, add 2 + 6. If you add 2 + 6, you will get $V_2 + V_2$ dash to be equal to $Z_{21} + Z_{21}$ dash into I_1 + $Z_{22} + Z_{22}$ dash into I_2 $Z_{22} + Z_{22}$ dash is it not, this is what I will get. Now this whole network this 2 series network can be thought of as single 2 port network after knowing these 2 equations I will say that this is the equivalent 2 port network is this.

These 2 are series connected where the input voltage you see what is the potential of this? These are the input ports can be considered to be the series connected 2 port networks and these two are

output ports of these two series connected networks. Therefore, between these two points the voltage is how much $V_1 + V_1$ that is the input voltage $V_1 + V_1$ what is the current I_1 and this side it can be thought of $V_2 + V_2$ is the voltage between this output port so $V_2 + V_2$ and what is this current I_2 so equivalent.

So therefore if 2 or several Two port networks are connected in series and then the overall equivalent Two port network representation will be input port voltages will be sum of all the voltages their input current same I_1 it is I_2 but the interesting thing is the impedance matrix of these 2 port network will be sum of the impedance values of this network and this network. That is the overall impedance matrix is nothing but Z_{11} Z_{12} , Z_{21} $Z_{22} + Z_{11}$ dash Z_{12} dash, Z_{21} dash Z_{22} dash, is it not?

Then only you will get term by term addition these elements will be $Z_{11} + Z_{11}$ dash this element will be $Z_{12} + Z_{12}$ dash this will be $Z_{21} + Z_{21}$ dash and this will be $Z_{22} + Z_{22}$ dash got the point. Obviously you can easily you know feel any Two port network can be represented in several ways either in terms of Z parameters A, B, C, D parameters, Y parameters like that but if they are series connected I can find out the overall I can replace this series connected to port network by a single 2 port network whose parameters values if you know the impedance matrix separately here and there you can just add them and get it very simple.

Perhaps in series connected to port networks it will be easier if you represented it in the form of Z matrix. What it will turn out to be if it is an admittance or h parameter we can find it out but it will be complicated after all after you have found out this one you always know how to translate this parameter value in terms of A, B, C, D or Y parameters or so on or h parameters because each one this representation is related with others provided determinant is not equal to all these things. We will continue our discussion with this in the next class. Thank you.