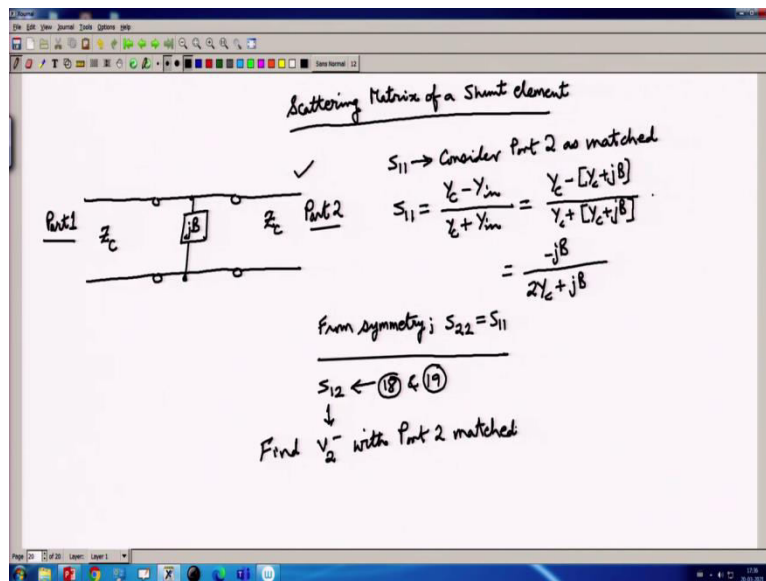


Advanced Microwave Guided – Structures and Analysis
Professor Bratin Ghosh
Department of Electronics and Electrical Communication Engineering
Indian Institute of Technology, Kharagpur
Lecture 4

Scattering Matrix Concepts (Contd.)

So, welcome back to the Scattering Matrix Concepts. In this session we will investigate the scattering matrix parameters for elements like the shunt element and the series elements.

(Refer Slide Time: 00:29)



So, let us begin for the shunt element, we will write the scattering matrix of a shunt element. So, in this case I have a transmission line. So, let us have a shunt element connected on either sides to transmission line. So, the input transmission line has a characteristic impedance Z_c , the output transmission line has a characteristic impedance of Z_c

So, to find S_{11} of this network we consider port 2 to be matched. So, S_{11} because this is a shunt element, we will discuss this in terms of the admittance. Looking at towards the right side from port 1.

$$\begin{aligned}
 S_{11} &\rightarrow \text{Consider Port 2 as matched} \\
 S_{11} &= \frac{Y_c - Y_{in}}{Y_c + Y_{in}} = \frac{Y_c - [Y_c + jB]}{Y_c + [Y_c + jB]} \\
 &= \frac{-jB}{2Y_c + jB}
 \end{aligned}$$

Now, from symmetry, we can see S_{22} will be equal to S_{11} . You can easily see that this network is symmetrical from the port 1 and port 2. So, from symmetry we can write S_{22} equal

to S_{11} . So, S_{12} can be evaluated by using 18 and 19. So, that can be obtained from 18 and 19 or S_{12} can be found also from the network by finding V_2^- with port 2 matched.

From symmetry; $S_{22} = S_{11}$

$S_{12} \leftarrow (18) \& (19)$
 \downarrow
 Find V_2^- with Port 2.

(Refer Slide Time: 06:14)

Scattering Matrix of a shunt element

Port 1 Z_c jB Z_c Port 2 ✓

$S_{11} \rightarrow$ Consider Port 2 as matched

$$S_{11} = \frac{Z_c - Y_{sm}}{Z_c + Y_{sm}} = \frac{Z_c - [Y_c + jB]}{Z_c + [Y_c + jB]}$$

$$= \frac{-jB}{2Y_c + jB}$$

From symmetry; $S_{22} = S_{11}$

$S_{12} \leftarrow (18) \& (19)$
 \downarrow
 Find V_2^- with Port 2 matched

Now, for a pure shunt element, we must have the total input voltage will be equal to V_2^- because port 2 is matched. So, there is no reflected wave from port 2. Now, as $V_1^- = S_{11}V_1^+$ we can write

For a pure shunt element:

$$V_1^+ + V_1^- = V_2^-$$

As $V_1^- = S_{11} V_1^+$

$$V_1^+ + S_{11} V_1^+ = V_2^-$$

$$V_1^+ (1 + S_{11}) = V_2^-$$

Now, since,

Since $V_2^- = S_{21} V_1^+$, we get


$$V_1^+ (1 + S_{11}) = S_{21} V_1^+$$

$$\therefore S_{21} = 1 + S_{11} = S_{12}$$


$$1 + S_{11} = 1 - \frac{jB}{2Y_c + jB} = \frac{2Y_c}{2Y_c + jB} = S_{12}$$

So, this is for the pure shunt element.

(Refer Slide Time: 10:41)

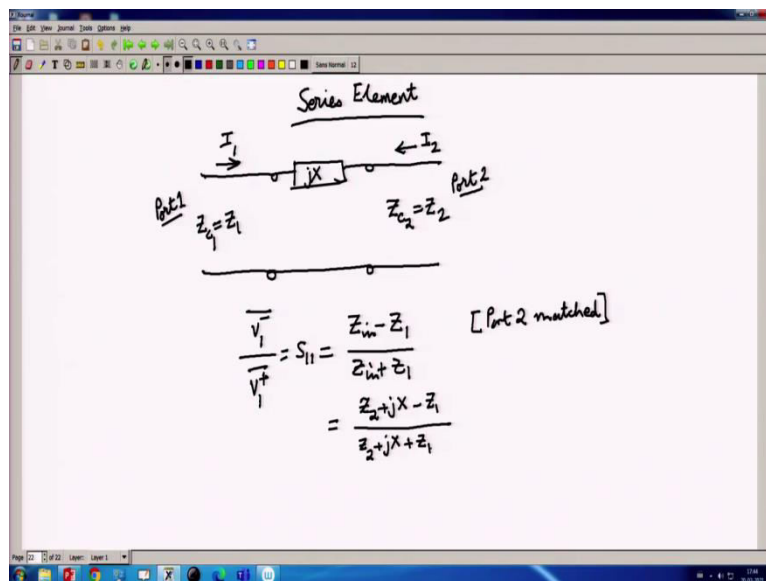

Next we take the case of a series element, and in this case we have this kind of a network. So, the two characteristic impedances of the transmission line on the two sides, they are different. Z_{c1} is the characteristic impedance of the transmission line on the left hand side it is Z_1 and Z_{c2} is the characteristic impedance of the transmission on the right hand side and that is Z_2 . The left is port 1 and the right is port 2.

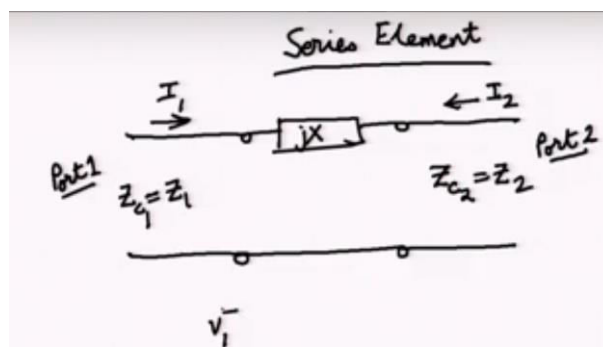

So, we can write that

$$\frac{\overline{V}_1}{V_1^+} = S_{11} = \frac{Z_{in} - Z_1}{Z_{in} + Z_1} \quad [\text{Port 2 matched}]$$

$$= \frac{Z_2 + jX - Z_1}{Z_2 + jX + Z_1}$$

(Refer Slide Time: 14:44)

If Port 1 is matched:

$$\frac{\overline{V}_2}{V_2^+} = S_{22} = \frac{Z_1 + jX - Z_2}{Z_1 + jX + Z_2}$$

$S_{21} = ?$ (Port 2 is matched)

On Port 1, we have:

$$V_1 = V_1^+ + V_1^- = V_1^+ + S_{11} V_1^+ = V_1^+ (1 + S_{11})$$

$$I_1 = Y_1 (V_1^+ - V_1^-) = Y_1 V_1^+ - Y_1 S_{11} V_1^+ = Y_1 V_1^+ (1 - S_{11})$$

Series Element

Port 1 $Z_1 = Z_1$ Port 2 $Z_2 = Z_2$

$$\frac{\overline{V}_1}{V_1^+} = S_{11} = \frac{Z_{in} - Z_1}{Z_{in} + Z_1} \quad [\text{Port 2 matched}]$$

$$= \frac{Z_2 + jX - Z_1}{Z_2 + jX + Z_1}$$

Similarly, if port 1 is matched, we can write

If Port 1 is matched:

$$\frac{\overline{V_2^-}}{\overline{V_2^+}} = S_{22} = \frac{Z_1 + jX - Z_2}{Z_1 + jX + Z_2} \checkmark$$

In order to find S_{21} , we again consider port 2 is matched. So, on port 1, what do we have? It is

$S_{21} = ?$ (Port 2 is matched)

on Port 1, we have:

$$V_1 = V_1^+ + V_1^- = V_1^+ + S_{11} V_1^+ = V_1^+ (1 + S_{11})$$

$$I_1 = Y_1 (V_1^+ - V_1^-) = Y_1 V_1^+ - Y_1 S_{11} V_1^+ = Y_1 V_1^+ (1 - S_{11})$$

.So, this is the Y_1 is the admittance of the transmission line to the left.

(Refer Slide Time: 20:16)

Current is continuous in a series element:

$$-I_2 = I_2^- = I_1 = Y_1 V_1^+ (1 - S_{11}) \checkmark$$

But $I_2^- = Y_2 V_2^- \checkmark$


$$\therefore Y_2 V_2^- = Y_1 V_1^+ (1 - S_{11}) \quad (21)$$

We now get $S_{21} = S_{12} = \frac{\overline{V_2^-}}{\overline{V_1^+}} \checkmark$

$$\overline{V_1^+} = \sqrt{Y_1} V_1^+ \checkmark$$

$$S_{21} = S_{12} = \frac{\sqrt{Y_2} V_2^-}{\sqrt{Y_1} V_1^+}$$
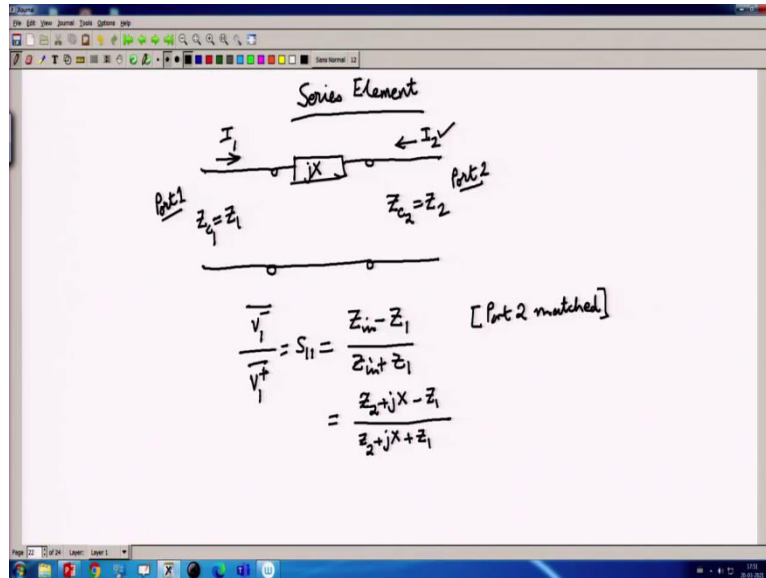
$$= \sqrt{\frac{Y_2}{Y_1}} \frac{Y_1 (1 - S_{11})}{Y_2}$$



Now, we know the current is continuous in a series element. So, let us write that down.

Current is continuous in a series element:

$$-I_2^- = I_2^- = I_1 = Y_1 V_1^+ (1 - S_{11})$$

$$\text{But } I_2^- = Y_2 V_2^-$$

$$\therefore Y_2 V_2^- = Y_1 V_1^+ (1 - S_{11})$$

We just equate the two, we just equate these two. So, we now get

We now get $S_{21} = S_{12} = \frac{\bar{V}_2^-}{V_1^+}$

Now, if I choose a normalized voltage, the normalized voltage is related to the unnormalized voltage


$$\bar{V}_1^+ = \sqrt{Y_1} V_1^+$$

So, we can write:

$$S_{21} = S_{12} = \frac{\sqrt{Y_2}}{\sqrt{Y_1}} \frac{V_2^-}{V_1^+}$$

$$= \sqrt{\frac{Y_2}{Y_1}} \frac{Y_1 (1 - S_{11})}{Y_2}$$

(Refer Slide Time: 27:30)

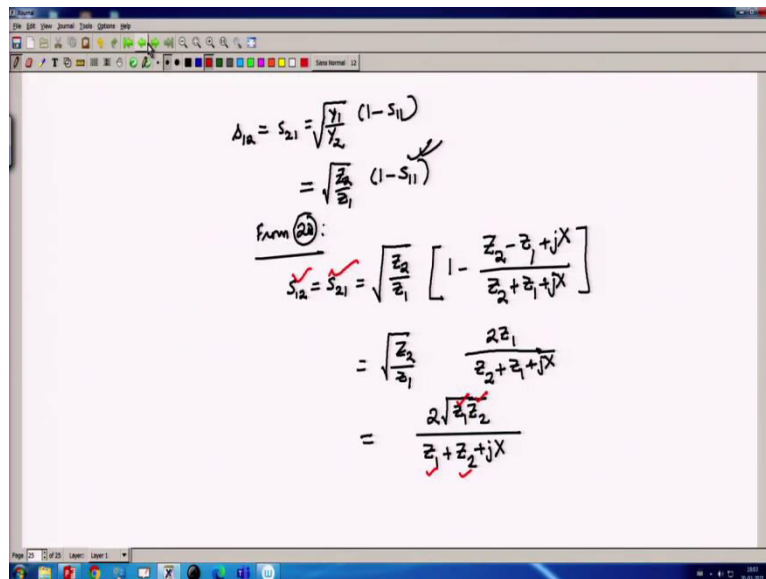

$$S_{21} = S_{12} = \sqrt{\frac{Y_1}{Y_2}} (1 - S_{11})$$


$$= \sqrt{\frac{Z_2}{Z_1}} (1 - S_{11})$$

From (20):

$$S_{11} = S_{21} = \sqrt{\frac{Z_2}{Z_1}} \left[1 - \frac{Z_2 - Z_1 + jX}{Z_2 + Z_1 + jX} \right]$$

$$= \sqrt{\frac{Z_2}{Z_1}} \frac{2Z_1}{Z_2 + Z_1 + jX}$$
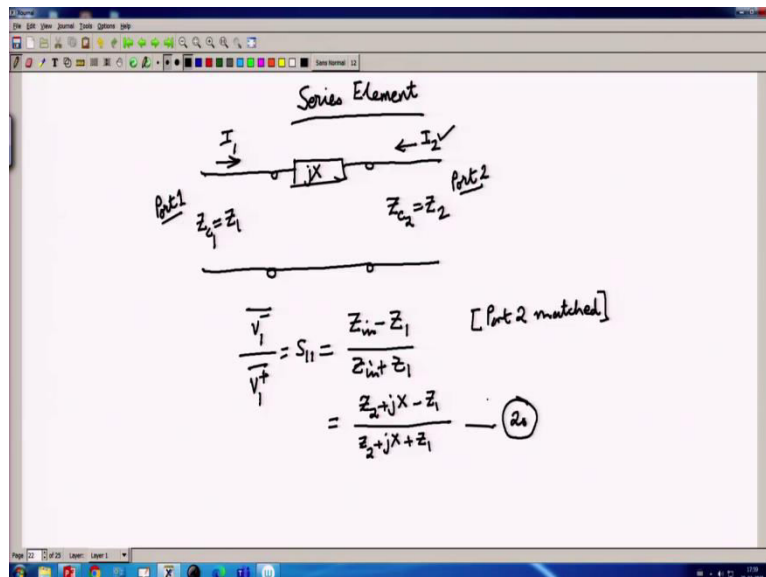
$$= \frac{2\sqrt{Z_1 Z_2}}{Z_2 + Z_1 + jX}$$



And next we can write

$$\begin{aligned}
 A_{12} = S_{21} &= \sqrt{\frac{Y_1}{Y_2}} (1 - S_{11}) \\
 &= \sqrt{\frac{Z_2}{Z_1}} (1 - S_{11}) \\
 \text{From (2a):} \\
 S_{12} = S_{21} &= \sqrt{\frac{Z_2}{Z_1}} \left[1 - \frac{Z_2 - Z_1 + jX}{Z_2 + Z_1 + jX} \right] \\
 &= \sqrt{\frac{Z_2}{Z_1}} \frac{2Z_1}{Z_2 + Z_1 + jX} \\
 &= \frac{2\sqrt{Z_1 Z_2}}{Z_1 + Z_2 + jX}
 \end{aligned}$$

So, the symmetricity of S_{11} , S_{12} and S_{21} appears because of the way the expressions for Z_1 and Z_2 appear in this equation. So, they are symmetric. So, you see that the S_{12} and S_{21} they are symmetric. So, we had used here normalized voltages. So, if unnormalized values are used or if unnormalized voltages are used the same expressions will be obtained for S_{11} and S_{22} which we had obtained now, but the expressions for S_{12} and S_{21} would get changed.

(Refer Slide Time: 32:46)

If unnormalized voltages are used.
 S_{11} & S_{22} will remain unchanged

$$S_{21} = \frac{2Z_2}{Z_1 + Z_2 + jX} \quad S_{12} = \frac{2Z_1}{Z_1 + Z_2 + jX}$$

$$S_{21} = \frac{V_2^-}{V_1^+} \Big|_{V_2^+ = 0} = \frac{Y_1(1-S_{11})}{Y_2} = \frac{Z_2(1-S_{11})}{Z_1}$$

$$= \frac{Z_2}{Z_1} \left[1 - \frac{Z_2 + jX - Z_1}{Z_2 + jX + Z_1} \right]$$

$$= \frac{Z_2}{Z_1} \frac{2Z_1}{Z_2 + Z_1 + jX} = \frac{2Z_2}{Z_1 + Z_2 + jX}$$

In fact, in that case if unnormalized voltages are used S_{11} and S_{22} will remain unchanged. But, S_{21} will be equal

If unnormalized voltages are used.
 S_{11} & S_{22} will remain unchanged

$$S_{21} = \frac{2Z_2}{Z_1 + Z_2 + jX} \quad S_{12} = \frac{2Z_1}{Z_1 + Z_2 + jX}$$

So, in that case if unnormalized voltages are used, we can find S_{21}

$$S_{21} = \frac{V_2^-}{V_1^+} \Big|_{V_2^+ = 0} = \frac{Y_1(1-S_{11})}{Y_2} = \frac{Z_2(1-S_{11})}{Z_1}$$

$$= \frac{Z_2}{Z_1} \left[1 - \frac{Z_2 + jX - Z_1}{Z_2 + jX + Z_1} \right]$$

$$= \frac{Z_2}{Z_1} \frac{2Z_1}{Z_2 + Z_1 + jX} = \frac{2Z_2}{Z_1 + Z_2 + jX}$$

(Refer Slide Time: 36:47)

$$S_{12} = \left. \frac{V_1^-}{V_2^+} \right|_{V_1^+ = 0}$$

Port 1 matched

$$V_2 = V_2^+ + V_2^- = V_2^+ + S_{22} V_2^+ = V_2^+ (1 + S_{22})$$

$$I_2 = Y_2 (V_2^+ - V_2^-) = Y_2 V_2^+ - Y_2 S_{22} V_2^+$$

$$= Y_2 V_2^+ (1 - S_{22})$$

∴ the current is continuous through a series element:

$$I_2 = I_1^-$$

$$\therefore Y_2 V_2^+ (1 - S_{22}) = Y_1 V_1^-$$

In order to find S_{12} , it is nothing but

$$S_{12} = \left. \frac{V_1^-}{V_2^+} \right|_{V_1^+ = 0}$$

Port 1 matched

$$V_2 = V_2^+ + V_2^- = V_2^+ + S_{22} V_2^+ = V_2^+ (1 + S_{22})$$

$$I_2 = Y_2 (V_2^+ - V_2^-) = Y_2 V_2^+ - Y_2 S_{22} V_2^+$$

$$= Y_2 V_2^+ (1 - S_{22})$$

Now since, the current is continuous through a series element,

$$S_{12} = \left. \frac{V_1^-}{V_2^+} \right|_{V_1^+ = 0}$$

Port 1 matched

$$V_2 = V_2^+ + V_2^- = V_2^+ + S_{22} V_2^+ = V_2^+ (1 + S_{22})$$

$$I_2 = Y_2 (V_2^+ - V_2^-) = Y_2 V_2^+ - Y_2 S_{22} V_2^+$$

$$= Y_2 V_2^+ (1 - S_{22})$$

(Refer Slide Time: 40:28)

$$\begin{aligned}
 S_{12} &= \frac{Y_2 (1 - S_{22})}{Y_1} \\
 &= \frac{Z_1 (1 - S_{22})}{Z_2} \\
 &= \frac{Z_1}{Z_2} \left[1 - \frac{Z_1 + jX - Z_2}{Z_1 + jX + Z_2} \right] \\
 &= \frac{Z_1}{Z_2} \frac{2Z_2}{Z_1 + Z_2 + jX} = \frac{2Z_1}{Z_1 + Z_2 + jX} \quad \checkmark
 \end{aligned}$$

And from here, I can write down, S_{12} is

$$\begin{aligned}
 S_{12} &= \frac{Y_2 (1 - S_{22})}{Y_1} \\
 &= \frac{Z_1 (1 - S_{22})}{Z_2} \\
 &= \frac{Z_1}{Z_2} \left[1 - \frac{Z_1 + jX - Z_2}{Z_1 + jX + Z_2} \right] \\
 &= \frac{Z_1}{Z_2} \frac{2Z_2}{Z_1 + Z_2 + jX} = \frac{2Z_1}{Z_1 + Z_2 + jX}
 \end{aligned}$$

So, this completes the derivation of S_{12} for the unnormalized voltage case. So, this ends the section on the concept of scattering matrix. Thank you.