
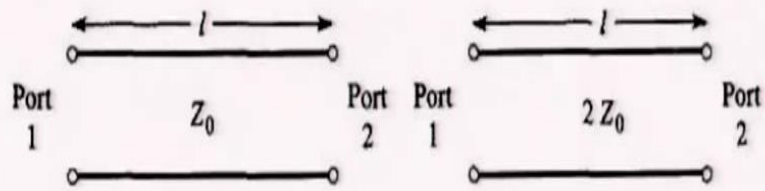


Advanced Microwave Guided-Structure and Analysis
Professor Bratin Ghosh
Department of Electronics and Electrical Communication Engineering
Indian Institute of Technology, Kharagpur
Lecture No. 06
Scattering Matrix Concepts Tutorials (Contd.)

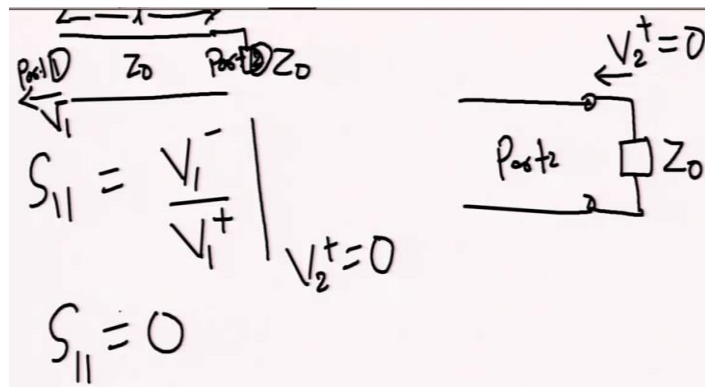3. Derive the scattering matrix for each of the lossless transmission lines shown below, relative to a system impedance of Z_0 . Verify that each matrix is unitary.






$$S_{22} = \frac{V_2^-}{V_2^+} \Big|_{V_1^+ = 0}$$

$$V_2^- = 0 \quad S_{22} = 0$$


$$S_{12} = \frac{V_1^-}{V_2^+} \Big|_{V_1^+ = 0}$$

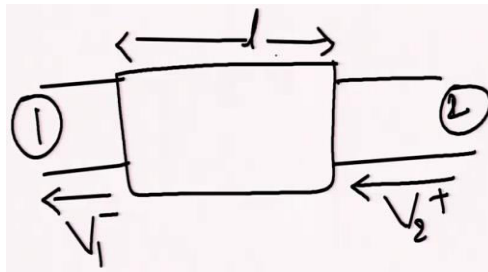

$$S_{12} = e^{-j\beta l}$$

$$S_{21} = \frac{V_2^-}{V_1^+} \Big|_{V_2^+ = 0}$$

$$= e^{-j\beta l}$$

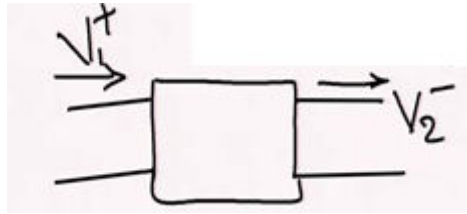


So, we have got $S_{11} = S_{22} = 0$ and $S_{12} = S_{21} = e^{-j\beta l}$.

Scattering Matrix can be written as,

$$[S] = \begin{bmatrix} 0 & e^{-j\beta l} \\ e^{-j\beta l} & 0 \end{bmatrix}$$

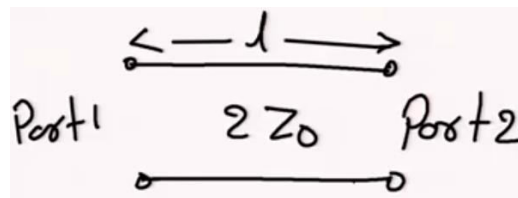After this we can go to the second configuration



$$S_{11} = \frac{V_1^-}{V_1^+} \bigg|_{V_2^+ = 0} = \Gamma_{in} = S_{22}$$

$$\Gamma(0) = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_0 - 2Z_0}{Z_0 + 2Z_0} = \frac{-Z_0}{3Z_0} = -\frac{1}{3}$$

$$Z_{in} = Z_0 \frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$

$$Z_{in} = 2Z_0 \frac{1 + \Gamma(0) e^{-2j\beta l}}{1 - \Gamma(0) e^{-2j\beta l}}$$


$$= 2Z_0 \frac{1 - \frac{1}{3} e^{-2j\beta l}}{1 + \frac{1}{3} e^{-2j\beta l}}$$

And from this Z_{in} we can find out Γ_{in}

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$= \frac{2\left(1 - \frac{1}{3} e^{-2j\beta l}\right) - \left(1 + \frac{1}{3} e^{-2j\beta l}\right)}{2\left(1 - \frac{1}{3} e^{-2j\beta l}\right) + \left(1 + \frac{1}{3} e^{-2j\beta l}\right)}$$
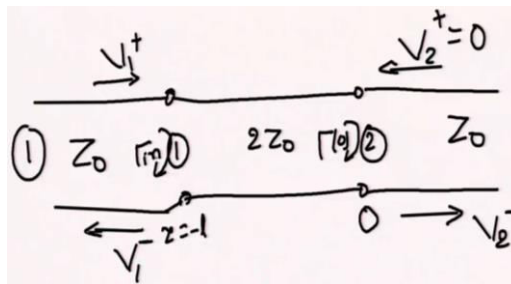
$$\Gamma_{in} = \frac{1 - e^{-2j\beta l}}{3 - \frac{1}{3} e^{-2j\beta l}} = S_{11} = S_{22}$$



Now, we have to find out S_{21} and S_{12} .

$$S_{21} = \frac{V_2^-}{V_1^+} \Big|_{V_2^+ = 0}$$

$$V_1^+ + V_1^- = V_1^+ (1 + \Gamma_{in}) = V_1^+ e^{j\beta l} - \frac{1}{3} V_1^+ e^{-j\beta l}$$

$$V_2 = V_2^+ + V_2^- = V_2^- = V_1^+ \left(1 - \frac{1}{3}\right)$$

we are finding out for S_{21} ,

$$S_{21} = \frac{V_2^-}{V_1^+} \text{ when } V_2^+ = 0$$

$$V_2^- = \frac{2}{3} V_1^+ = \frac{2}{3} \frac{V_1^+ (1 + \Gamma_{in})}{e^{j\beta l} - \frac{1}{3} e^{-j\beta l}}$$

We have

$$\Gamma_{in} = \frac{1 - e^{-2j\beta l}}{3 - \frac{1}{3} e^{-2j\beta l}}$$

$$\frac{V_2^-}{V_1^+} = \frac{\frac{2}{3} \left(1 + \frac{1 - e^{-2j\beta l}}{3 - \frac{1}{3} e^{-2j\beta l}} \right)}{e^{j\beta l} - \frac{1}{3} e^{-j\beta l}}$$

$$= \frac{8}{3} \frac{e^{-j\beta l}}{3 - \frac{1}{3} e^{-2j\beta l}} = S_{21} = S_{12}$$

Now, to satisfy the unitary condition,

$$|S_{11}|^2 + |S_{21}|^2 = \left| \frac{1 - e^{-2j\beta l}}{3 - \frac{1}{3} e^{-2j\beta l}} \right|^2 + \frac{64}{9} \left| \frac{1}{3 - \frac{1}{3} e^{-2j\beta l}} \right|^2$$

$$= \frac{|1 - e^{-2j\beta l}|^2 + \frac{64}{9}}{\left| 3 - \frac{1}{3} e^{-2j\beta l} \right|^2}$$

$$= \frac{(1 - e^{-2j\beta l}) / (1 - e^{2j\beta l}) + \frac{64}{9}}{\left(3 - \frac{1}{3}e^{-2j\beta l}\right) \left(3 - \frac{1}{3}e^{2j\beta l}\right)}$$

$$= \frac{1 - e^{-2j\beta l} - e^{2j\beta l} + 1 + \frac{64}{9}}{9 - e^{2j\beta l} - e^{-2j\beta l} + \frac{1}{9}}$$

= 1 Unitary /