

Analog Integrated Circuits
Prof. S. Aniruddhan
Department of Electrical Engineering
Indian Institute of Technology, Madras

Lecture – 29
Telescopic OpAmp – 5

(Refer Slide Time: 00:16)

In this lecture we are going to look at the noise and offset of the telescopic opamp. Now before we do that it is a good idea to review the noise of a cascode amplifier of a simple cascode amplifier. So, the way we are going to do this is we are going to find out the effective input referred noise, because as we have studied before the input referred noise tells you how much noise is contributed by each particularly each set of components of these circuit.

So, to do this we are going to refer we are going to look at the short circuit noise of the circuit. So, since that is an easier way to do this I am going to redraw the small signal equivalent circuit with the output short circuited. So, we want to find out the short circuit noise, and in this particular case I will use this polarity for the very specific reason we will find out $i_{sc,n}^2$, and if I divide $i_{sc,n}^2$ by the square of the transconductance of the cascode amplifier, this will give me the input referred noise voltage squared which I shall call e_n^2 .

So, to refer this back to the input of the amplifier I will divide by the square of the transconductance, and as we have seen the transconductance of the cascode amplifier is nothing, but g_{m1} . So, this is $s^2 c_n$ over g_m^2 . Now let us take each the noise from each transistor and look at how much of it flows to the output. We will first start off with the noise from noise from M1. So, now, the noise from everyone is i_{dn1}^2 and this noise splits between transistors M1 and M2.

Now, if you look at the way it splits the current will split in the order of the impedances the impedance looking down which I call r_{down} is nothing, but the r_{ds} of M1 the impedance looking up which I will call r_{up} is nothing, but $1/g_{m2}$ because I have a short circuit at the drain of M2. So, this means since g_{m2} is much larger than g_{d1} $1/g_{m2}$ is much smaller than r_{ds1} and this means that almost all of i_{dn1}^2 flows into M2.

The complete current flows for M2 and flows into the a short circuit therefore, the first component of the noise I call that i_{scn1}^2 is equal to i_{dn1}^2 . Now let us look any noise from M two.

(Refer Slide Time: 04:22)

Telescopc opamp - 5 - Windows Journal

File Edit View Insert Actions Tools Help

$i_{scn2} = i_1 - i_2 = 0$

Noise from cascode does not appear at the output

lower impedance

$$e_n^2 = \frac{i_{scn2}^2}{g_{m1}^2} = \frac{i_{dn1}^2}{g_{m1}^2} = \frac{8kT}{3g_{m1}} \Delta f$$

So, if you look at the noise from M2, that can be represented by a current source across the drain source M2 we do and we want to find out how much of this current flows through the short circuit. So, we want to find out the component flowing through the short circuit. So, to do this we will use a small trick that we have used before so, we

know that a current source between 2 nodes can be represented by a series combination of the same currents also all that I can replace that with 2 correct sources i with no change in the circuit, and again this can be changed as 2 current sources i with a short circuit at the at the common mode point.

So, and there is no current through the short circuit therefore, the circuit does not change, it all we are going to do the same thing here. So, we are going to change this circuit to the following I am going to show that show the 2 current sources in red and blue. So, we are going to split this current source the only difference being these 2 sources red, and blue sources are going to be correlated my sources and I call that i_1 squared, and the red i_1 sorry i_1 , and the current in red is flowing into the source of M_2 and that will be called i_2 .

And remember this is equal to and I am interested in finding the overall short circuit current. So, if you look at i_2 or rather if you look at i_1 let us look at i_1 first. So, i_1 has the option of flowing down into the drain of M_2 or up into the short circuit of course, i_1 will prefer to flow into the short circuit directly, because it is the path of least impedance. So, there is a current i_1 flowing in this direction through the circuit.


Now, what about i_2 if you look at i_2 , i_2 also has the option of flowing through 2 paths in the circuit it either has the option of going upwards or flowing downwards as we have seen the impedance looking downwards is r_{ds1} whereas, the impedance looking upwards is $1/g_{m2}$ which is much smaller and therefore, this current is much larger the impedance is much smaller. So, I just point out that this is a low impedance.

Therefore I have seen in red i_2 flows in this direction therefore, i_{scn2} is equal to i_1 minus i_2 is equal to 0. Since i_1 and i_2 have the same impedance, this means that the noise from the cascode does not appear at the appear at the inside the short circuit. So, the noise from even though the cascode produces noise, its noise does not appear at the short circuit node it keeps circulating inside the device. And eventually if you measure the input referred noise you will find that the cascade does not produce any noise at all.

So, therefore e_n squared is nothing, but i_{dn1} squared. So, i_{sc} squared g_1 square this is nothing, but i_{dn1} square over g_{m1} square, and please remember that i_{dn1} is $8kT/3$ $8kT$ by 3 into $g_{m\Delta f}$. So, this is $8kT/3$ g_{m1} square f . So, the power spectral density is $8kT/3$ g_m as you can see the input referred noise of the cascode amplifier

consists only of the noise of M 1, that even though you have added cascode the noise of the cascode does not affect the noise of the amplifiers. Now, we are going to use this to figure out the noise of the telescopic opamp.

(Refer Slide Time: 10:37)

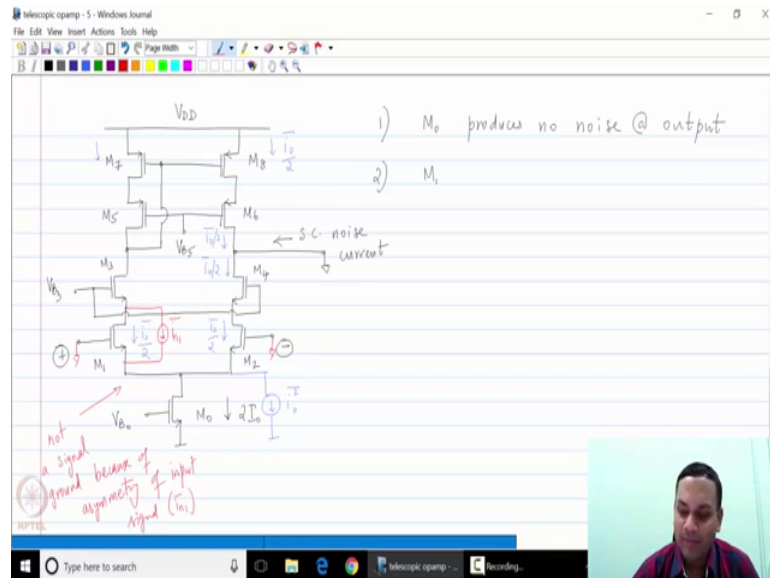

So, now, let us now take the telescopic opamp you can see, now that there are 9 sources of noise in the circuit we will go through these transistors 1 by 1 and figure out how much of this current flows into the output, to do that again we will short circuit the output node and figure out a short circuit noise current. And we can refer that back to the input to figure out what the input referred noise of the telescopic opamps.


As you might imagine the noise of M 0 is in parallel with which I call i_0 is it parallel with M 0 the impedance looking up through both sides is almost the same, because it is 1 over g_{m1} versus 1 over g_{m2} . So, I will see equal and opposite currents are almost equal and opposite currents i_0 by 2 and i_0 by 2 , and this current gets mirrored as i_0 by 2 through M 8 M 6 and therefore, since the 2 these 2 currents are correlated there is no short circuit current noise at the output due to M 0.

So, there is a current i_0 by 2 entering this node, and that is a current i_0 by 2 leaving this node. So, M 0 produces no noise at the opamp, now what about M 1 and M 2 as far as noise of M 1 as concerned you will find that this current has 2 parts to split. So, we will now use the same method as we did for the cascode device, the reason we cannot use

symmetry is because as far as noise is concerned this is not a virtual ground is not signal ground, because of asymmetry of input signal.

So, in this case the input signal of interest is what is I should call i_{n1} we are going to ground the gates of M_1 and M_2 , as you can see as far as the signal is concerned i_{n1} which is i_{n1} . In this case the circuit is no longer no longer has a line of symmetry and therefore, you cannot consider the circuit to be symmetric on both sides. The way we shall approach this problem is to change is the same as before we will add 2 current sources in series and ground the intermediate path, and we shall see how the signal travels through this circuit.

(Refer Slide Time: 14:20)

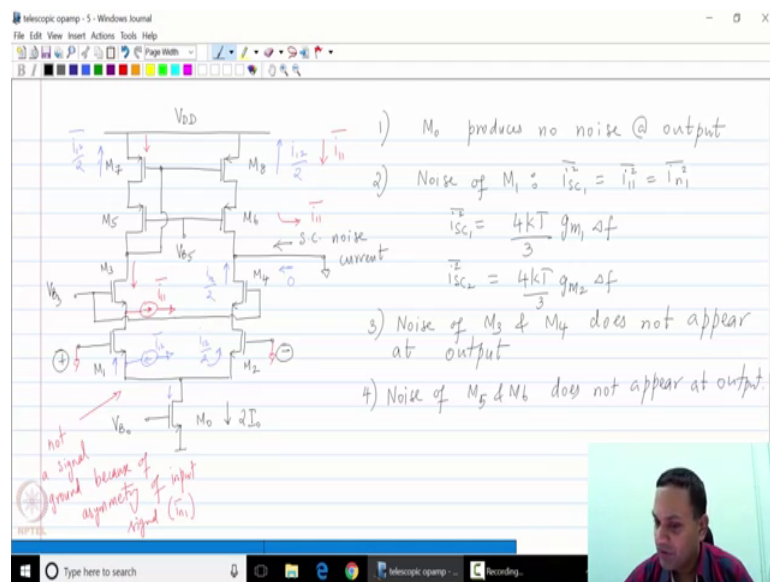

So, I will show that in red and blue as usual so, I recall that i_{n1} and a current source i_{n2} which are both correlated. If you look at i_{n2} seize the impedance of M_0 looking downwards which is extremely large, and the impedance looking up into the source of M_1 which is of the order of $1/g_{m1}$ and therefore, and the other surface by side which is $1/g_{m2}$.

So, these are the 3 parts of the circuit looks, and it turns out that the current i_{n2} is split equally between M_1 and M_2 these 2 paths are of course, a symmetric now. So, now, this current flows into M_7 . So, this is $i_{n2}/2$ and therefore, there is a current $i_{n2}/2$ flowing into the into M_8 what happens to the current flowing here, there is a current flowing in the M_2 of value $i_{n2}/2$ and that current flows into this and therefore, this

current is 0 because by applying case here at the output node. So, there is no current through the short circuit.


Now, what about the current source in the red, you will find that this current has 2 paths to flow at this node it can flow upwards looking up into the source of M 3, which happens to be a very low impedance versus flowing down where it has a very high impedance which is that looking down impedance at the drain of M 1 therefore, what happens is that most of this current flows from M 3, and this current flows down through M 7 and gets reflected to M 8.

So, this current is i_{n1} that is very little current flowing through M 1 M 0 M 2 and M 4, and this current flows through the short circuit therefore, if you look at the noise of M 1 the short circuit noise current is i_{sc1} which is equal to i_{n1} the plane thermal noise of M one. So, therefore, i_{sc1}^2 is this this is. So, i_{sc1}^2 is $4 k T g m_1 \Delta f$. So, all of the noise of M 1 appears through the output short circuit.

You can do a similar analysis for M 2 and show that i_{sc2} is also $4 k T g m_2 \Delta f$ this is the squared noise at the output due to M 2. Now what about M 3 and M 4 you will find that noise of M 3 and M 4 does not appear at the output, this is because of the cascode action of M 3 and M 4, because M 3 and M 4 are cascode transistors that noise does not appear at the output.

Now, what about M 5 and M 6 it turns out that same is true for M 5 and M 6 noise of M 5 and M 6 does not appear finally, we need to look at the noise of M 7 and M 8.

(Refer Slide Time: 18:58)

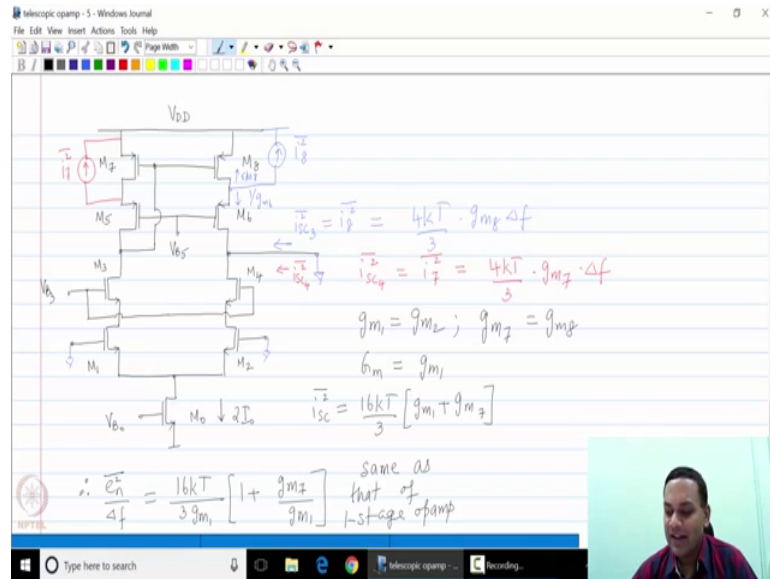

So, let us take the noise of M 8 itself we will show that in blue, the noise of M 8 is the current source which is i_8 squared in parallel with M 8, and as you can imagine i_8 squared has 2 parts to flow the impedance looking downwards as r_{ds8} , but as the impedance looking down this is $1/g_{m8}$.

So, most of i_8 tends to flow through M 6 and eventually through the output short circuit therefore, I will say that i_{sc3} is equal to i_{sc3}^2 is equal to i_8 squared and this is nothing, but $4kT/3$ into g_{m8} delta f. Similarly you will find that noise of M 7 which is i_7 squared also appears at the output, and if all that i_{sc4} squared this is i_7 squared this is $4kT/3$ into g_{m7} delta f.

Finally we will we know that g_{m1} is equal to g_{m2} , g_{m7} is equal to g_{m8} , and we also know that the overall transconductance of the opamp is nothing, but g_{m1} therefore, you can say that e_n squared over delta f. This is the input referred squared voltage noise density this is nothing, but the total short circuit noise current divided by g_{m1} so, maybe firstly, we will write down the total short circuit noise current. The total short circuit noise current this $16kT/3$ into g_{m1} plus g_{m7} .

Therefore the total input referred noise quite voltage density is $16kT/3$ into g_{m1} plus g_{m7} over g_{m1} please note that this is very similar to the noise of the input referred noise of the 1 stage opamp. So, even though the telescopic opamp has much larger d c gain it has very similar noise performance especially at low frequencies. Now,

finally, we will write down the expression for the offset without deriving it directly I just point out that the behavior of an offset voltage or current is similar to that of noise.

(Refer Slide Time: 22:36)

Offset (only V_T mismatches)

- + V_T mismatch of M_3, M_4, M_5, M_6 does not appear in input-referred offset voltage
- + V_T mismatch of M_1 & M_2 appears directly at input
- + V_T mismatch of M_7 & M_8 is scaled by relative g_m s

$$\sigma_{V_{OS,ref}} = \sigma_{V_{T,1,2}} + \left(\frac{g_{m7}}{g_{m1}} \right)^2 \sigma_{V_{T,7,8}}$$

same as that of 1-stage opamp

So, I just point out that as far as offset is concerned we are going to consider only V_T mismatches, you will find that V_T mismatch of M_3 and M_4 does not appear as an input referred offset, just as the noise was did not appear when referred back to their input the V_T mismatch of M_3 and M_4 , these also reduced and does not appear at the input of the at the input of the overall opamp and the same can be said for M_5 and M_6 .

So, (Refer Time: 23:54) write in blue. So, you say that M_3 M_4 M_5 and M_6 , this is similar to the that formulas now what about V_T mismatch of M_1 and M_2 it turns out that V_T mismatch of M_1 and M_2 appears directly at the input of the opamp. And finally, V_T mismatch of M_7 and M_8 is scaled down scaled by the relative g_m , then you refer back to the input. So, the input referred offset voltage which is ah represented by its standard deviation and say sigma squared over s in has 2 components, the first component is the V_T mismatch of 1 and 2, and the p p mismatch of 7 and 8 a scale by the ratio of $g_m 7$ to $g_m 1$ whole square this is also same as that of 1 stage opamp. So, there are some parameters that are different for the telescopic opamp, and some that at the same when compared to the 1 stage opamp.