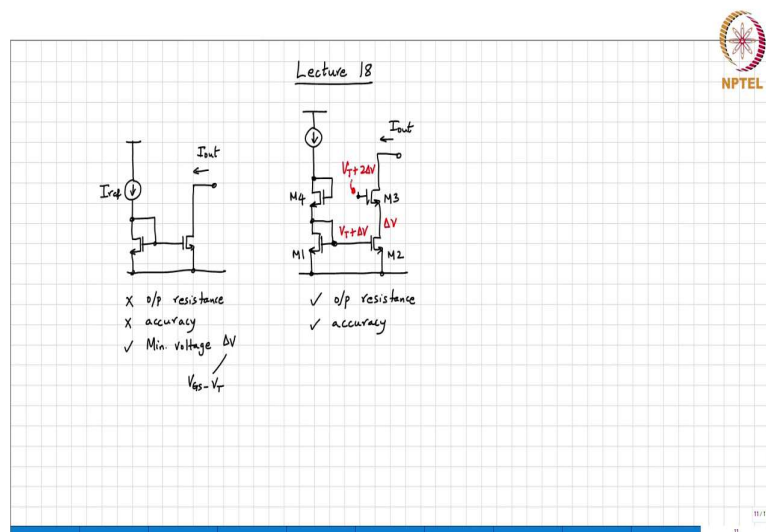


**Analog Electronic Circuits**  
**Prof. Shanthi Pavan**  
**Department of Electrical Engineering**  
**Indian Institute of Technology, Madras**

**Lecture - 37**  
**Comparison of Current Mirrors, The High-Swing Cascode**

(Refer Slide Time: 00:19)



Good morning, everybody and welcome to Analog Electronic Circuits. This is lecture 18. In the last class we were looking at Current Mirrors and this is the Basic Mirror. The output current and what are the problems with this? Yeah, basically output resistance is 4 and accuracy is 4 therefore, accuracy meaning the ratio of  $I_{out}/I_{ref}$ , but what is the good point?

The minimum voltage needed is just.

Student:  $\Delta V$ .

$\Delta V$  where  $\Delta V$  let me remind you is again  $V_{GS} - V_T$ , right. So, to fix this problem what did we do? We said the root cause is that this is the bad current source. We want to make it a better current source. So, what do you do? How do you make a bad current source? A better current source you make that the input to a current controlled current source. And the simplest single transistor current controlled current source that you can think of is the common gate amplifier. And so that led us to the cascode current source. And we discussed how this came about yesterday. This is  $I_{out}$  and what are the good things about this?

So, the output resistance is larger by a factor of  $g_m R_o$  and therefore, also turns out that as we saw yesterday the accuracy is also very good. Why? We discussed this yesterday. Why does this have very good accuracy? Yes, Choudhry.

Student: Means for the gate voltage  $T\Delta$ . So, the gate voltage will be twice of  $\Delta V$  + twice of  $V$ . So, the same current, we need a simply similar to the biasing. No hold down the gate of M3, at this I mean in this picture what is the potential of the gate of M3?

Student:  $2 V_T + \Delta V$ .

Is that necessary to keep you know M2 in the saturation region?

Student: Yes.

If you want to get high output impedance. M3 and M2 must be in what region of operation? How did we come up with the gate bias of M3? The gate bias of M3 is what? What is the bias voltage at what is the voltage of the gate of M3? What is the meaning of it should be at the edge of overdrive voltage? This sentence does not even make any sense. What is it? No, I do not understand what you are writing man I do not understand. Yes, Abhishek Choudhry. How do you get that?

Student:  $V_{GS} - V_T$  is  $\Delta s_o$ .

Why?

Student: same current.

Yeah. So, M3 and M2 are the same size. They are carrying the same current so the gate source voltage of M3 will be  $V_T + \Delta V$ . So, what must be the gate voltage of  $V_G$ ?

Or the gate voltage of M3 must be  $V_T + 2\Delta V$ , right? So, what is therefore, the minimum gate voltage needed to keep M2 in saturation is? I am asking you the same question and I still see you know blank faces. What is the minimum potential needed at the gate of M3 to keep M2 in saturation?

Student:  $V_T + 2 \Delta V$ .

So, why don't I just put  $V$ ? If so, therefore, if I put  $V_T + 2 \Delta V$  here, ok. What comment can you make about the output resistance? Assuming M3 is in saturation.

Student: remains the same.

Remains the same as?


Student:  $g_m R_1 R_2$ .

So, if I connect the gate to  $V_T + 2 \Delta V$ , right? That is enough to keep both M3 and M2 in?

Student: Saturation.

Saturation and the output resistance will be?  $g_m R_o R_o$  which is  $g_m R_o^2$ , alright? Ok.

(Refer Slide Time: 08:07)

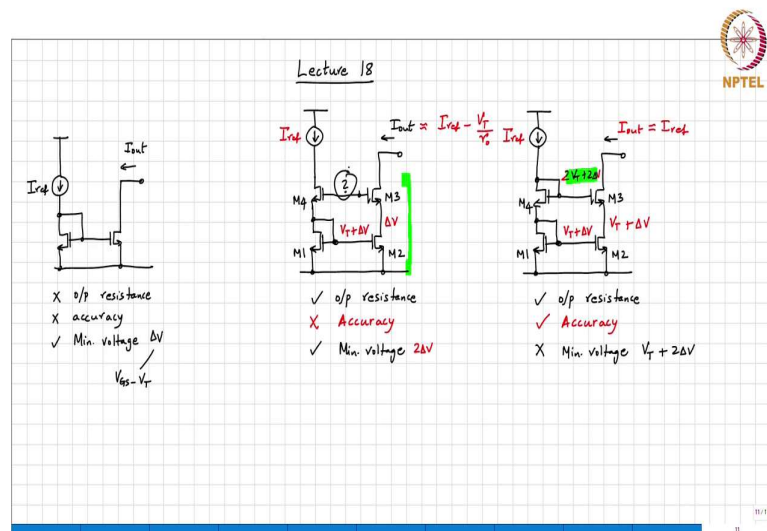

But then why did we connect it to  $V_T + 2 \Delta V$ ? Why did we connect it? The gate of course, is I mean only the  $V_{GS}$  and the  $V_{DS}$  s are Identical, right? So, the gates of course, are identical because they are sorted together.

Student: Yes.

Its  $V_T + \Delta V$  whereas the drain potential of M2 is  $\Delta V$ . So, what comment can you make about the approximately? What comment can you make about  $I_{out}$ ? I know it is less than  $I_{ref}$ , right? But how much less is it? Can we estimate it? So, in other words, if this voltage  $V_G$  is tied to  $V_T + 2 \Delta V$ , what comment can you make about the current  $I_{out}$ ? Yes, Pavan Kumar.

Student: Sir.

It will be smaller, but smaller by how much?

Student:  $V_T$  by half.

How did you get that?

Student:  $V_{GS}$ .

So, the difference in drain currents is basically the difference in drain voltage divided by?

Student:  $R_o$ .

$R_o$ . So, what is so difficult about that? We did this in the last class.

Student: Yes sir.

Alright? So, what I mean the whole discussion started because this gentleman here said that the accuracy is good if the output resistance is high, but they are two fundamentally different things, right, ok? In this case if we tied this gate to  $V_T + 2 \Delta V$ , right? What comment can we make about the output resistance?

It is  $g_m R_o R_o$  which is an order of magnitude better than the basic current mirror. Is this clear to everybody?

Student: Yes sir.

Alright. However, what comment can you make about accuracy? What is  $I_{out}$ ?  $(I_{ref} - V_T)/R_o$  or  $g_m R_o^2$ ?

Student: R.

Why?

Student: R is the current in the M2,  $\Delta V$  is  $V_T / R_o$ ?

So, basically the accuracy is governed by the ratio of current between the transistors M1 and M2, right? And the  $V_{DS}$  difference is  $V_T$  and therefore, it is  $V_T / R_o$ , alright? Ok. So, what comment can you make about accuracy here now, is it good or bad?

Student: Bad.

Bad. So, basically, alright. So, accuracy has got nothing to do with output resistance, right? I mean you can as you can see in this mirror, I mean it is one, it is another matter where we generate  $V_T + 2 \Delta V$ , but what do you call it? What comment can we make about the minimum voltage though? What is the minimum voltage needed to keep to make this behave like a current source? How did you get  $2 \Delta V$ ? The drain potential can go one threshold below the gate and the gate of M3 is at  $V_T + 2 \Delta V$ . So the minimum drain potential is  $2 \Delta$ , right. So, the minimum voltage is not, I mean it is of course, better than, but you had to expect that in order to get this high output resistance, you had to expect to pay something.

Student: Yes sir.

And what you are paying is?

Student: Loss.

Is loss of headroom and that is by only by  $\Delta V$ . And that makes sense because if you want, if you have, if you stack 2 transistors one above the other, but the remember that the minimum drain source voltage needed to keep a transistor in saturation is the minimum potential needed to keep a transistor in saturation, the minimum drain source potential is what we have a transistor.

Student: Normal is what is needed.

That is all I am asking, like we have done here, what is the minimum voltage needed to keep the stack of both transistors in saturation, it is  $2\Delta$ , right? So, you cannot do better than  $2 \Delta$ . Is this clear? Ok. Now, what do you call it? So, for the not to, but if you want to fix the accuracy problem, what did we do yesterday? We recognize that the root cause was what is the root cause? What is the root cause for poor accuracy?

Student: Differentiate potential.

Ok. So, what did we do? So, what should the gate be tied to? Gate of M3, how will we fix the problem? If we want to fix the accuracy problem, what will we do? Go step by step, what should we do? What is the root cause of the problem?

The drain of M2 is basically  $\Delta V$ , but it should be  $\Delta V + V_T$ . So, what should the gate of M3 be tied to? What should be the potential at the gate of M3? Yes, you, in the last bench? Yeah. If


the source of the M3 is at  $V_T + \Delta V$ , what should the gate be at? It should be  $2V_T + 2\Delta$ , correct? Now, so the minimum voltage is  $\Delta V$  in this case,  $2\Delta V$  in this case, alright. So, now what comment can you make about accuracy?

Yeah. So, basically  $I_{out}$  is simply. No, do you, all of you see why this, you know, just putting an M4 there and forcing current into its drain does not result in a magically a gate voltage? Yes, no.

Student: Yes.

Ok, alright. So, that does not work, ok.

(Refer Slide Time: 16:32)

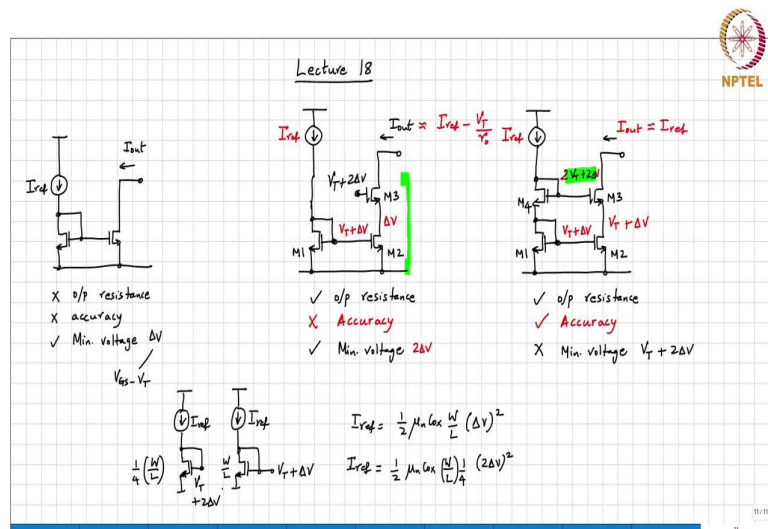

So, what voltage do we need here? We need  $V_T + 2\Delta$ . The question is how do we get  $V_T + 2\Delta$ ? Alright, if I want to get  $V_T + \Delta V$ , what will you do?

I mean, if you want to generate a voltage which is  $V_T + \Delta V$ , what do you do? You will take  $I_{ref}$  and connect it into a diode connected transistor, right? So, this is giving me  $V_T + \Delta V$ , ok? Now, if I want  $V_T + 2\Delta V$ , what do you think I should do? Ok, let me lead you to the answer. What does this say? This is if you write the equations, basically its saying  $I_{ref}$  is nothing but  $\frac{1}{2} \mu_n C_{ox} W/L \Delta V^2$ . If you are, now if we want to generate  $\Delta V$  by 2,  $V_T + \Delta V$  by 2, what do you think we should do?

Student:  $I_{ref} / 4$ .

Yeah, you can either do  $I_{ref} / 4$  or you push,  $I_{ref} / 4$  is definitely something you can do. Alternatively, you can basically say you choose a transistor which is?

One fourth the size. And then the overdrive needed to basically support. If you reduce the size of the device by a factor of 4, but still pump in the same current into the diode connected device, what will the gate voltage be?

This is  $W / L$ , ok? This is  $W / L$  times one fourth. What is this gate potential?

Student:  $\Delta V + V_T$ .


This is  $V_T + 2\Delta$ . Does it make sense?

Student: Yes sir.

Ok. So, now can you tell me how to generate  $V_T + 2\Delta$ ? What will we do?

Student: (Refer Time: 19:16).

(Refer Slide Time: 19:25)

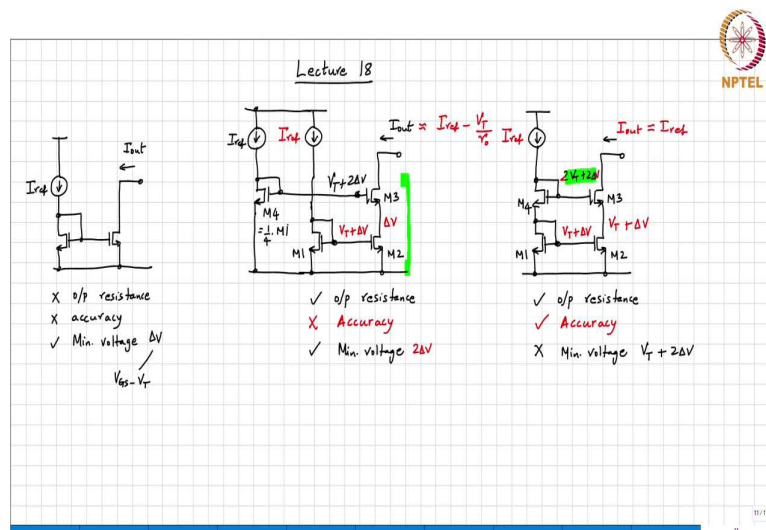


So, basically what you need to do is take. Another current source which is  $I_{ref}$  and uses a device which is? This is all this is M4 which is one fourth of?

Student: M1.

M1. In other words, if all these devices are  $W / L$ , this is one fourth  $W / L$ , ok?

(Refer Slide Time: 20:03)

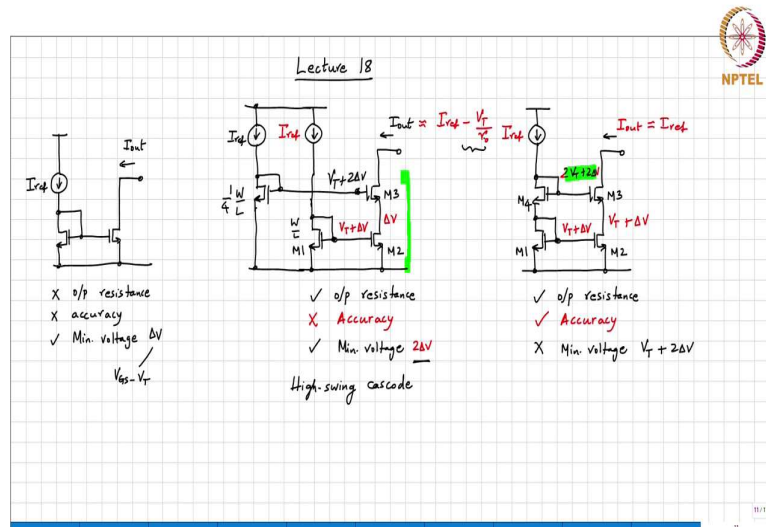

Alright, and you know as we just discussed, the output resistance of this is what is called the high swing cascode. It is called the high swing cascode and, like the regular cascode, it has very high output resistance, but the accuracy is poor because of the drain source potentials of M2 and.

Student: M1.

So, the last thing to do is what would we ideally like to do? We like to have a current mirror where the output resistance is high. The accuracy is good and minimum voltage is I mean what can it be a you know what is the smallest that we can have?

If you want  $g_m R_o^2$ , the minimum headroom that you need is  $2 \Delta V$ , if you want  $g_m R_o^2$ , you are stacking 2 devices.

Student: Yes.

And the minimum voltage needed to keep each of those devices in saturation is  $\Delta V$ . So, you cannot presumably get away with the minimum voltage which is smaller than  $2\Delta$ , right. So, basically what we need to do therefore, is to make sure that the, I mean what we would ideally like to do is to basically see if we can not only get the high output resistance of  $g_m R_o^2$ , we also avoid this error in the output current by I mean which is fundamentally due to the different  $V_{DS}$  s of the of M1 and M.