

Advance Power Electronics and Control
Prof. Avik Bhattacharya
Department of Electrical Engineering
Indian Institute of Technology – Roorkee

Lecture - 35
Matrix Converter III and Power Quality Mitigation Devices


Welcome to our advance power electronics and control courses in NPTEL. We shall continue with your matrix converter and therefore we shall see that different kind of power quality issues briefly. So let us discuss what we have left, we are discussing with the indirect matrix converter. We have discussed different topologies. These are the recapitulations of the previous class.

(Refer Slide Time: 00:50)

Indirect Matrix Converter (IMC) cont.

➤ In case of VSMC as middle switch is absent only 2 control signal is required for each leg of rectifier. While in case of USMC, as the number of switches reduced to one, the number of control signal for each leg of inverter also remains one.

Converter Types	Number of Transistors	No Of Diodes	Isolated Driver Potentials
CMC	18	18	6(CC),9(CE)
IMC	18	18	8
SMC	15	18	7
VSMC	12	30	10
USMC	9	18	7

 NPTEL ONLINE CERTIFICATION COURSE

You know there are different kind of topology has been discussed and the switching count is also been discussed.

(Refer Slide Time: 00:55)

control Strategy: Indirect Matrix Converter (IMC) cont.

$$u_a = \hat{U}_i \cos \omega t$$

$$u_b = \hat{U}_i \cos(\omega t - \frac{2\pi}{3})$$

$$u_c = \hat{U}_i \cos(\omega t + \frac{2\pi}{3})$$

Where

$\hat{U}_a, \hat{U}_b, \hat{U}_c$ = Three phase voltages of input
 = Amplitude of input voltage
 ω = Angular frequency

Let for $\omega t = 0$

$$u_a = 1, u_b = -0.5, u_c = -0.5$$

Hence

$$U_{ab} = u_a - u_b = 1.5$$

$$U_{bc} = u_b - u_c = 1.5$$

Formation of Dc link voltage in SMC

3

And now come to this point actually how actually it has been controlled. So generally you know inverter part is essentially a generally two-level inverter or the three-level inverter depending on the actual rating of the switches but you can consider a sparse matrix here with the reduced switches. So we will consider actually u_a is actually instead of sin cos, so actually that is the most positive phase at the zero instant.

And accordingly u_b will be 120 degree phase shifted and u_c will be 240 degree phase shifted. So at the beginning at the instant you now you can see that this is basically this dotted line you know actually this dotted line is essentially is the u_a and you will be switching in such a manner that maximum DC will be coming to this fictitious Dc bus voltage. So what will happen you know and you can see that and at that time C is the most negative phase.


And thus what will happen you know you will get a ripple that so you will and you will actually conduct the phase A, upper leg of the phase A of these switches and lower leg of the phase C so that you get the voltage u_{ac} . Similarly, you can see that this is basically after this interval after 30 degree interval after 60 degree interval at this point; B will be the most positive phase.

C continued to be the most negative phase, then you will be switching B and C, positive part of the B switches and negative part of the C switches. So you will get u_{bc} , accordingly all the switching sequence will become ac, bc like that you are continued to get. So u_a, u_b, u_c are the three-phase input voltages at the amplitude of having these are the amplitude and angular frequency ω and $\omega t = 0$.

You can see that actually it is a balanced (0) (03:26) system so actually summation of this three instantaneous voltage will give you zero and actually $u_a=1$ and $u_b=-0.5$ and $u_c=+0.5$ and so you are here, basically this is 0.5- for b and 0.5- for c and a here will be 1. So essentially if you subtract -0.5 and 1 so you are going to get essentially the maximum voltage 1.5 time of the line voltages.

Then, C continued to be actually down and thus your voltage will increase and it will change at the point of actually 60 degree from actually zero crossing but here zero crossing start at a instant of $\pi/2$.

(Refer Slide Time: 04:27)

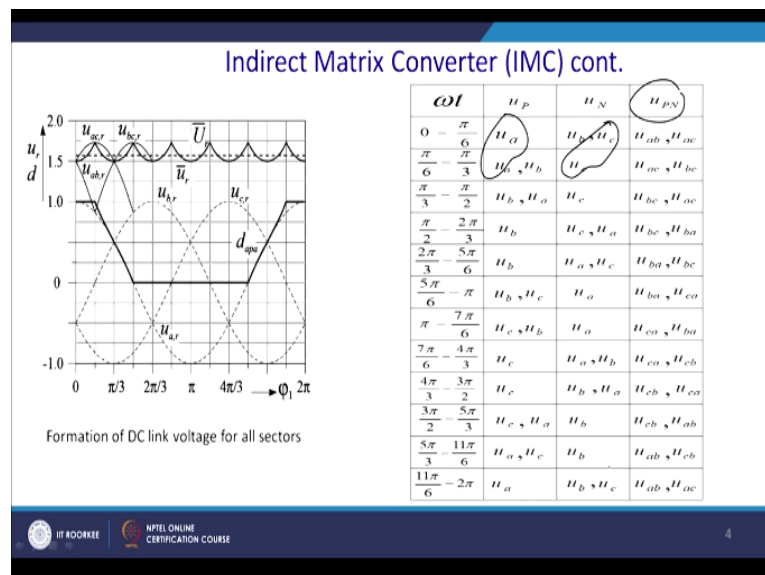


So these are the sequence you know how you will switch it on, you can see that so this is the upper leg and this is the lower leg. So at 0 to 60 degree you know upper leg u_a will be switched on and there will be a changeover at 30 degree to b to c and thus actually PN voltage that is this the pole to neutral voltage will be ab and ac. Similarly, $\pi/6$ to actually $\pi/3$ you will have this sequence u_a, u_b and $u_N=uc$ and this will be the voltage.

So these are the sequential curve with the 30 degree interval of time. So it will be changeover every 60 degree. So u_a will be there for the period of 60 degree. Similarly, u_c will be there for the period of 60 degree. So automatically this switching pattern will take place. So and thus you get a maximum DC link voltage, fictitious DC link voltage in that manner.

(Refer Slide Time: 05:43)

Indirect Matrix Converter (IMC) cont.

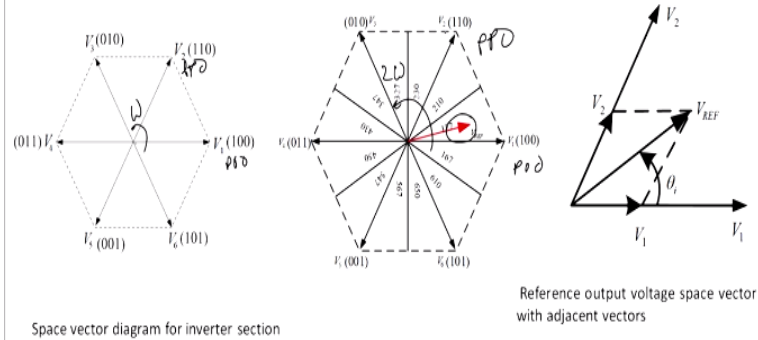


Now how you will generate? Let us consider that you have, we have discussed already that you are changing the frequency 25 hertz to 50 hertz or your actually 50 hertz to 100 hertz. So this is your input space vectors and where 110 what we discuss about POO or similarly to be POO. So this is basically PPO, similarly you have a two-level space vector and this will be mapped to the actually space vector which is rotating maybe the 2 omega or 3 omega.

If it is rotating at a speed omega, so what we required to do, we have to actually split these vectors in between and we are sure that basically if you want to generate some voltage here in this sector, same voltage will be actually generating here at the input at the output of this indirect matrix converter. So it will be the combination of the 1, 2, 7 where 1 is actually 100, 2 is 110 or in terms of the (()) (07:21) actually book actually it is POO, it is PPO.

So this and you will have this V_1 and V_2 and thus you got a V_{REF} here. So let us see how you will generate this.

(Refer Slide Time: 07:58)

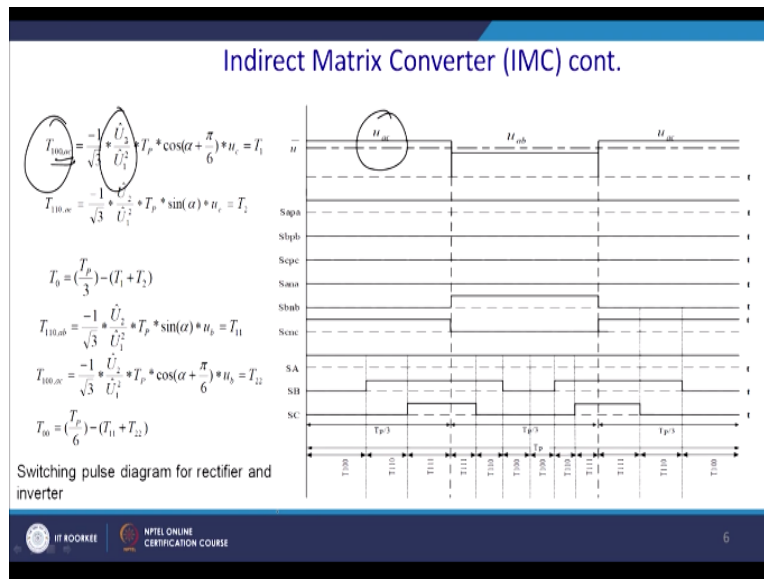


Now this is the switching logic and you have to calculate the same way you have calculated actually the time for the action of voltage vector V1, so that is for a1 that is $-1/\sqrt{3} U_2$ this is basically the unit vector $\cdot T_p$ is the processing sign $\cos(\omega t + \alpha)$ and this time essentially will be equal to T_1 . Basically why, you know this voltage applied here is AC and it is for the duration for 60 degree, for actually $\alpha + \pi/6$.

So for this reason, this is T_1 . Similarly, for T_2 we will have to have a sin component and this should be $-1/\sqrt{3}$ this term $T_p \sin(\alpha) u_c = T_2$. So you subtract T_1 and T_2 and you get the T_0 . First, of course you start with the voltage vector T110 thereafter actually it will be 100, thereafter you will have of course you have to apply the null vector at T_0 that will be basically 111 that again you will apply 111, that again will apply 110, then 100, then 110, then again 111.


Again this sequence will be repeated, so here if you see that this is basically that u_{ac} so this will be the sequence to be followed for these three switches and thus you can generate these voltages in this configuration.

(Refer Slide Time: 09:49)

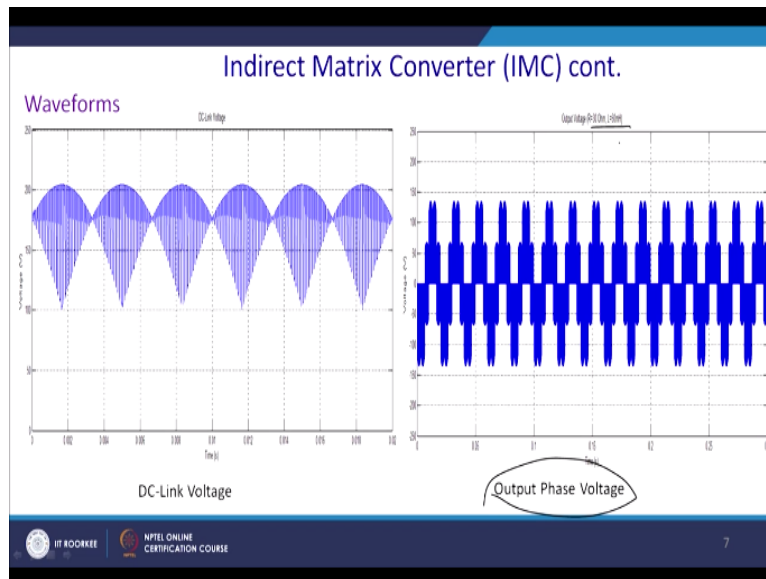

Now this is the DC link voltage you will get, the ripple DC you will get since there is no output voltage, no capacitor to filter it out or smooth out, you will get a ripple voltage every 60 degree interval. Ultimately, you can see that this interval so it will be around 60 degree and similarly this will be the phase output voltages which will be converted for actually for, this is basically the output simulation results, practical results can be shown later that is for the 30 ohm with the 50 hertz applications.

(Refer Slide Time: 10:33)

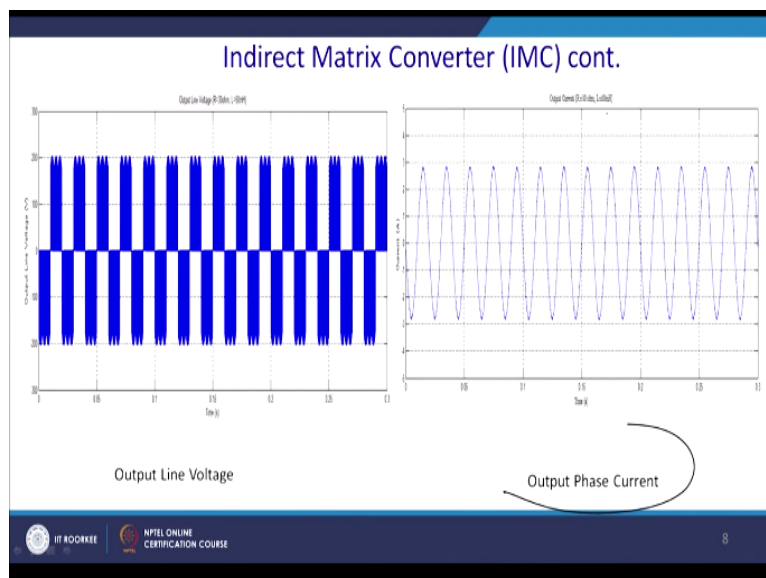


Now here this is the output line voltages and this is the output phase current and which you will find to be sinusoidal and ultimately it gives better results than the sine triangle PWM and THD is quite low for this actually filters.

(Refer Slide Time: 10:57)

Indirect Matrix Converter (IMC) cont.

Practical Circuit:

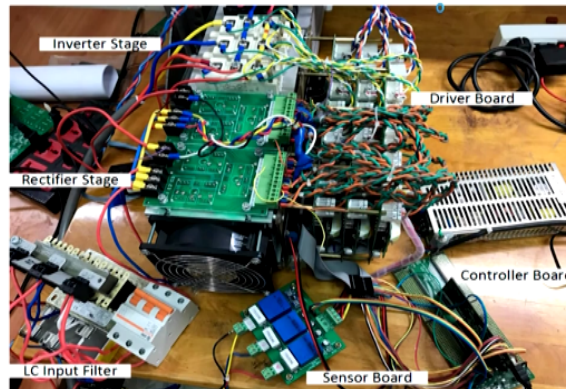

Now this is the hardware setup. We are making the practical hardwares on it and we shall show these results later. Now let us come to the one main challenge of this actually inverter topologies or AC to AC direct conversion. Problem is that your voltage, output voltage is reduced than your input voltage. So this is one of the biggest disadvantages to direct AC to AC conversion and to mitigate this problem you know for this reason we required to have some kind of boosting stage to boost up the voltage.


And this can be done and this can be incorporated into the directly AC to AC conversion. We have already discussed about that Z-source inverter and here in the Z-source inverter we have discussed in our class few classes ago.

(Refer Slide Time: 12:11)

Z-Source Inverter

Quasi Z-source Inverter (QZSI)

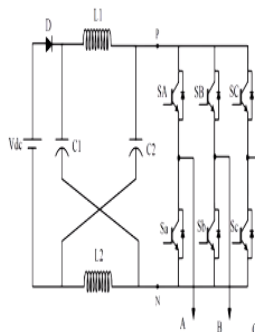- CZSI was 1st introduced by Fang Zheng Peng in the year 2003.
- It consists of 2 inductors and two capacitors.
- It generally performs two mode of operation:-one is shoot through mode and other is non-shoot through mode.
- In case of shoot through mode diode remains off, inductor gets charged by capacitor and input voltage and one leg of inverter gets shorted.




So it is introduced by the F. Z. Peng and this is once actually shorted, these two capacitors comes into the series, ultimately voltage becomes basically $V_{C1}+V_{C2}$ and you get a higher boosting effect. Can we have a same kind of concept incorporated in direct AC to AC conversion? So that is the challenge we can see.

So we know that actually it consists of the two inductor and the two capacitor and it generally performs two mode of operation, one is the shoot through mode that means when you actually shot the switches. Please refer to my lectures of the Z-source inverter and in case of the shoot through mode diode remains off and inductor gets charged by the capacitor and the input voltage and the one leg up of the inverter get shorted and thus boosting operation is achieved.


(Refer Slide Time: 13:15)

Z-Source Inverter cont.

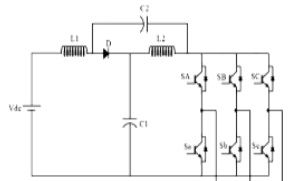

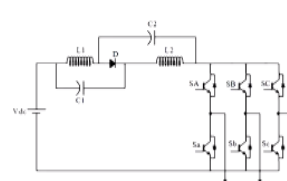- In case of non-shoot through mode diode remains ON, inductor discharges and output voltage gets boosted. In this condition inverter part acts as current source.
- Here boosting factor is calculated by considering average voltage across inductor over a cycle is zero. Boosting factor for CZSI is $1/(1-2D_s)$.
- Two types of Quasi Z-source Inverter topologies have been given below.



Continuous current QZSI



Dis-continuous current QZSI



11

Now in case of the non-shoot through stage, the diode remains on and inductor discharges and the output voltage get boosted up and in this condition inverter part acts as a current source. Here boosting factor is calculated by considering the average voltage across the inductor over a cycle zero and boosting factor of actually this Z-source inverter is $1/1-2 D_s$. So you can maximum actually give the 50% duty cycle, so otherwise there will be a instability.

So two types of Quasi Z-source inverters has been given below. This is one of the case of the Quasi Z-source inverter we had. Please refer to our discussions of the Z-source inverter. It is just the recapitulations, so there is a continuous mode of actually the Z-source inverter and

Quasi Z-source inverter and this is a discontinuous mode of Quasi Z-source inverter where inductor current is quite low.

And we prefer to actually have a discontinuous mode of Quasi Z-source inverter. Now this is the extension of the Quasi Z-source inverter that is called extended boost Z-source inverter. After Quasi Z-source inverter such as where actually focused on increasing the boosting factor further. So how can we actually boost this actually ratio.

(Refer Slide Time: 14:54)

Z-Source Inverter cont.

Extended Boost Z-source Inverter (EBZSI)

- After quasi z-source inverter researchers were focused to increase the boosting factor further.
- For this some passive impedance network blocks were added to QZSI.
- Finally in 2010 a new z-source DC-AC converter was proposed known as Extended Boost Z-source Inverter.
- EBZSI consists of 3 inductors, 3 capacitors and 3 diodes as shown in Fig. During shoot through condition diode D1, D2 remains OFF, but D3 is ON.

1
(1-2D)

A B C

V_{dc}

IT KOOKEE NPTEL ONLINE CERTIFICATION COURSE 12

That is actually $1/1-2D$, so it is limited to actually the some value. So this value is basically 0.5 and can we actually get it actually at a reduced value. For this some passive impedance network were added and you can see that instead of actually two inductors you have a three inductors and finally we can have another boosting effect and finally in 2010 a new DC to DC converters was proposed knows as extended Z-source inverter.

This extended Z-source inverter consist of the 3 inductors and the 3 capacitor and the 3 diodes and during shot through condition diode D1, D2 remains off but the diode D3 is forward biased and it is on and thus it pumps the continuous energy.

(Refer Slide Time: 15:48)

Z-Source Inverter cont.

- In shoot through state, all three inductors get charged by capacitor voltage and input voltage.
- During non-shoot through state D1, D2 remains ON, D1 remains OFF and inductor gets discharged to boost up the output voltage.
- Here also boosting factor is calculated by averaging inductor voltage over a cycle to zero.
- The boosting factor for EBZSI is $1 / (1 - D_s) (1 - 2D_s)$.

In shoot through state all the three inductors gets charged by the capacitors and during on no shoot through state, the diode D1, D2 remains on and D1 remains off and the inductor gets discharged to the boost out the output voltage and so overall boosting stage is been achieved is $1/(1-D)*1-2D$. So huge boosting can be achieved with the help of this actually enhance boosting capacity.

(Refer Slide Time: 16:23)

Z-Source Sparse Matrix Converter (ZSMC)


Introduction

- In spite of many advantages, MC also has some disadvantages.
 - (1) Voltage gain of matrix converter is limited to 0.866 and
 - (2) Output voltage may be affected by grid voltage changes, e.g. when there is decrease in grid voltage, it affects output voltage as matrix converter doesn't perform any boosting action.
- Though by changing modulation index, output voltage can be controlled, but it is up to some range.

So let us incorporate that Z-source concept into the sparse matrix. So in spite of many advantages that is what I was saying this matrix converter also has some disadvantages. Voltage gain of the matrix converter is limited to 0.866, output voltage may be affected by the grid voltage changes when there is a decrease in the grid voltage and it affects the output voltage and the matrix converter does not perform the boosting action.

Though by changing the modulation index, output voltage can be controlled but it is up to some range and voltage gain of the matrix converter direct matrix converter is limited to 0.866. So that is the limitations of it.

(Refer Slide Time: 17:23)

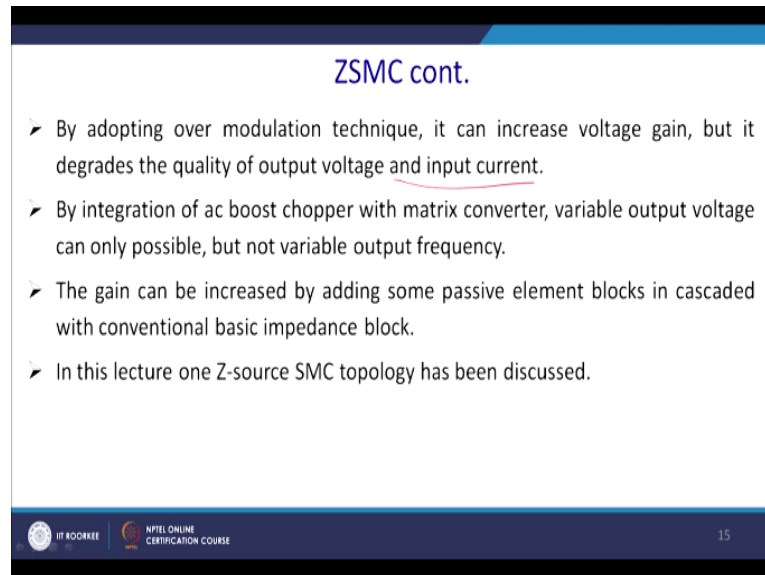

ZSMC cont.

- By adopting over modulation technique, it can increase voltage gain, but it degrades the quality of output voltage and input current.
- By integration of ac boost chopper with matrix converter, variable output voltage can only be possible, but not variable output frequency.
- The gain can be increased by adding some passive element blocks in cascade with conventional basic impedance block.
- In this lecture one Z-source SMC topology has been discussed.

IT KOOKEE NPTEL ONLINE CERTIFICATION COURSE 15

By adopting over modulation technique but it can increase the voltage gain like you know third harmonic injection and all those techniques can be applied here but it degrades the quality of the output voltage and the input current. So THD will be the causality there and also you do not get much of the boosting. By integration of the AC boost chopper with the matrix converter, variable output voltage can only be possible but not variable frequency operation.

So it not allows the variable frequency operation, it can allow only actual fixed voltage operation. The gain is increased by adding some passive elements block in cascade with the conventional basic impedance network. In this lecture, one of the Z-source SMC topology has been discussed for the lack of time.

(Refer Slide Time: 18:35)

Quasi Z-source SMC (QZSMC)

- Here a quasi z-source network is incorporated between rectifier and inverter section as in Fig.
- Quasi z-source network consists of 2 inductors L_1, L_2 and 2 capacitors C_1, C_2 .
- Mainly the inductors play vital role in boosting the voltage. It also consists of a bi-directional switch for bidirectional power flow.

IIT ROORKEE
 NPEL ONLINE CERTIFICATION COURSE

16


So this is actually a topology, it is actually this part is already we have discussed, this is the DC part, this is the converter part and this is the inverter part. In between, you have added this actually the boosting network and here you can see that with this not only you can actually control the frequency but also can control, of course you can actually buck it by changing the modulation index.

And this part of the circuit can help you also boost it thus it is a basically an idealized solid state transformer. So it is fine it will be highly used in future with a penetration of the silicon carbide based device, we shall use this device, this topology and the variant topology as actually solid phase transformer, it will be compact, it will be a very useful thing and it will be less bulky and you have a lot of other advantages.

Let us see how does it work. It is a Quasi Z-source network is incorporated between the rectifier and the inverter as shown in the figure. The Quasi Z-source network consists of the two inductors L_1, L_2 and the two capacitors C_1, C_2 , in between there will be a shoot through state. Mainly, the inductor plays a vital role in boosting the voltage. It also consists of a bidirectional switch and the bidirectional power flow.

So sometime we may not actually but you can use for regenerative braking also, it is not that power flow is this, it can be also in this way. So here we require sometime for bidirectional flow. So this is the configuration, so you have a input state intact as working to generate the DC link voltage and you will apply the shoot through into your actually inversion stage.

(Refer Slide Time: 20:48)

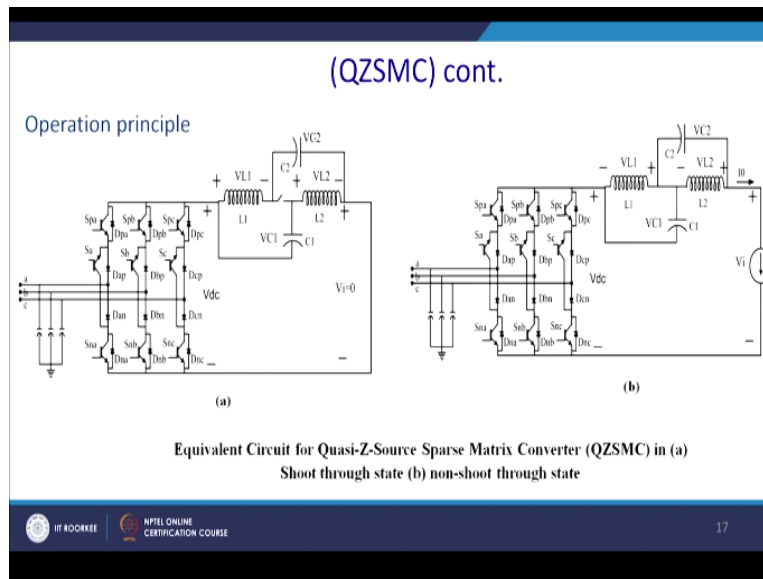

And thus what will happen, you will be boosting a voltage $VC1$ and $VC2$ above your V_{dc} and thus what will happen, $VC1$ and $VC2$ will come and it will add up this DC link voltage and you will get the extra DC link voltage to be converted into the extra AC side line voltages. This is basically the shoot through state and this is a non-shoot through state. We will consider that once CSI is connected.

(Refer Slide Time: 21:23)

(QZSMC) cont.

- It performs two mode of operation:-shoot through mode and non-shoot through mode. To maintain symmetry, condition should be-

$$V_{c1} = V_{c2}$$

$$V_{L1} = V_{L2}$$
- In shoot through mode, the bidirectional switch remains off and any one leg of inverter is shorted. Here inductors get charged by rectifier output voltage and corresponding capacitor voltage. Applying KVL-

$$-V_{dc} - V_{c1} + V_{L2} = 0$$

$$-V_{dc} - V_{c2} + V_{L1} = 0$$
- In non-shoot through mode, the bidirectional switch remains on and inductors discharge through capacitors to boost up the voltage. Applying KVL-

IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 18

So it performs the two mode of operation, shoot through mode and the non-shoot through mode to maintain the symmetrical condition $VC1=VC2$ and $VL1$ will be $VL2$. In shoot-through mode, the bidirectional switch remains of and any one leg of the inverter is shorted. Here inductor gets charged by the rectifier output voltage and corresponding the capacitor voltage and if we apply KVL- $V_{dc}-VC1+VL2=0$ or $-V_{dc}-VC2+VL1=0$.

In non-shoot through mode, this bidirectional switch remains on and the inductor discharges to the capacitor to boost up the voltage.

(Refer Slide Time: 22:12)

(QZSMC) cont.

$$V_{L1} = V_{C1}$$

$$V_{L2} = V_{C2}$$

➤ Now applying volt-sec balance to inductor voltages

$$(V_{dc} + V_{C1})T_s - V_{C1}(T - T_s) = 0$$




$$V_{C1} = V_{dc} \left(\frac{T_s}{T - T_s} \right)$$

Where

T_s = Shoot through time

T = Total time

D_s = Shoot through duty ratio




19

And by applying KVL what essentially will get, $V_{L1}=V_{C1}$ and $V_{L2}=V_{C2}$ and thus what happen you know so you can equate this two equations. $V_{dc}+V_{C1}*T_s-V_{C1} T-T_s=0$ and thus $V_{C1}=V_{dc} T_s/T-T_s$ where T_s is the shoot through state and T is the total time and D_s the shoot through ratio. In that way, you can boost up the V_{C1} .

(Refer Slide Time: 22:49)




(QZSMC) cont.

Again applying KVL in fig-b

$$-V_{dc} - V_{C1} + V_{C2} + V_i = 0$$

$$V_i = V_{dc} \left(\frac{1}{1 - D_s} \right)$$

$$B = \left(\frac{1}{1 - D_s} \right)$$




20

So again applying KVL so you can find it out that basically the overall gain is just in case of a simple boost simple Z-source network that is $1/1-D_s$ where D_s stands for the shoot through ratio that is shoot through by the total time period. Now let us switch over the topic, so it require little conclusion. Actually, we have discussed the direct AC to AC conversion, we

have started with the bulky cycloconverters that are gradually move to a sleek devices like matrix converter and we have seen the problem of the matrix converter.

Then, from this matrix converter we have come down to the actually direct matrix converter to indirect matrix converter and from the indirect matrix converter we have actually derived different topologies and also actually made the challenge of the actually boosting of the voltage. Gradually actually these days are not far behind when we will see that instead of this actually all these copper transformer these are replaced by the silicon carbide based transformer.

And will see that very sleek and bulky instead of this bulky, heavy transformer, will see that a very compact sleek transformer and it is quite useful where weight is a major concern like aircraft, etc. Now let us switch over to another important topic that is basically the power quality. Power quality is actually issue popped up due to the advancement of this power electronics.

Because as long as voltage and current was sinusoidal with the linear load there was no problem and there is a problem with the power factor and that can be minimized with the reverse kind of load by a wall compensator. Now due to the advent of the power electronics and its rampant uses like adjustable speed drive and other applications power what we get it is being virtually is polluted.

Now I as a consumer I want actually a clean power from the utility but unfortunately due to penetration of the power electronics, power quality get degraded. So our now discussions will be focused on the power quality. So let us define power quality, what is it.

(Refer Slide Time: 26:05)

Introduction to Power Quality

- The term electric power quality (PQ) is generally used to assess and to maintain the good quality of power at the level of generation, transmission, distribution, and utilization of AC electrical power.
- Modern distribution systems quality is vulgarized due to large amount of power electronic devices (programmable logic devices and adjustable speed drives), lightning, flashover, equipment failure, faults, voltage distortions and notches.

Power quality problems is an occurrence manifested in non-standard voltage, current or frequency deviation that results in the failure or miss-operation of end equipment.

The term electric power quality is generally used to assess and to maintain the good quality power at the level of generation, transmission, distributions and utilizations of AC electrical power. Modern distribution system, the power quality is vulgarized due to the large amount of the power electronics devices but unfortunately we wanted to have a actually the solution through the power electronics only.


The programmable logic drives, adjustable speed drive, lightning, flashover, equipment failure, faults, voltage, distortion and notches, these are basically spoils or decreases the power quality. Power quality problem is an occurrence manifested in nonstandard voltage and current and frequency. If there is sudden swell and sag or voltage, current and the frequency deviation, that results in failure of the missed operation of the main equipments.

So this is a major challenge nowadays, you can see the different kind of waveforms. All of a sudden, notches has come. This is basically a transient phenomena.

(Refer Slide Time: 27:40)

Power quality problems

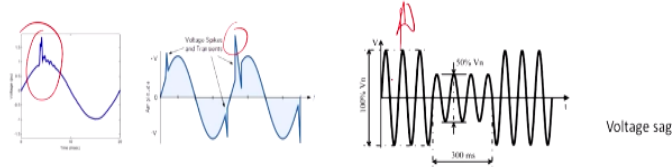- Power quality problems may be classified on the basis of events such as **transient** and **steady state**.
- **Transient** types of power quality problems include the phenomena occurring in transient nature (e.g., impulsive or oscillatory in nature) such as voltage sag (dip), voltage swell, short-duration voltage variations, power frequency variations, and voltage fluctuations.




If notches continue in cycles then we have to consider the spikes. Now all of a sudden, voltages has sagged half of the voltage almost. So this is only basically the voltage sag. So power quality problem may be classified on the basis of the events such as transient, occurrence is all of a sudden thereafter it is okay or in a steady state. This transient type power quality problem includes the phenomena occurring in the transient nature are impulsive and oscillatory nature such as voltage dip, voltage swell.

Voltage swell means actually voltage will go off, short duration voltage variations, power frequency variations and the voltage fluctuations.

(Refer Slide Time: 28:28)

Power quality problems (Cont...)

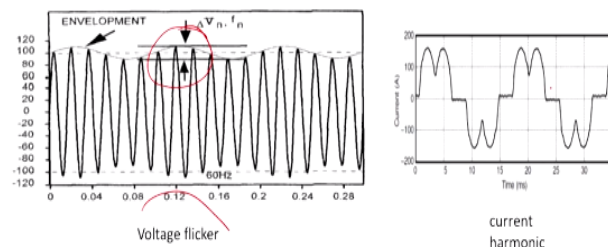- **Steady-state** types of power quality problems include long-duration voltage variations, waveform distortions, unbalanced voltages, notches, DC offset, flicker, poor power factor, unbalanced load currents, load harmonic currents, and excessive neutral current.



So this is the voltage flicker. Now steady state, the types of the power quality problems include the long duration voltage variation, waveform distortion, unbalanced voltages,

notches, DC offset, flickers, poor power factor, unbalanced load current, load harmonics currents and excess neutral current. So you will get all and this is basically the voltage flickers, all of a sudden it will flicker and we can see that with these 50 years, there has been a low frequency is being superimposed.

And due to that it may actually cause lot of damage into the power system. It is very difficult to mitigate this current harmonics and this is actually a typical case of three-phase direct bridge rectifier fitting in RL load and you can see that voltage is far from sinusoid and you get a distorted current. This is a current harmonics.

(Refer Slide Time: 29:48)

Power quality problems (Cont...)

- The classification may be on the basis of quantity such as **current**, **voltage**, and **frequency**, or the **load** and **supply** systems.
- **Voltage quality problems** : Voltage distortions, **flicker**, notches, noise, sag, swell, unbalance, under voltage, and overvoltage.
- **Current quality problems** : Reactive power component of current, harmonic currents, unbalanced currents, and excessive neutral current.

The slide contains two graphs. The left graph, labeled 'Voltage swell', shows a sinusoidal wave with a peak amplitude of 500 on the y-axis and time from 0 to 0.3 on the x-axis. A red line indicates a sudden increase in the amplitude of the wave. The right graph, labeled 'Three phase Current Unbalance', shows three sinusoidal waves (red, green, and blue) on a y-axis ranging from -100% to 100% and a time axis. The waves are out of phase and have different amplitudes, indicating unbalance.

74

Now this is the voltage swell all of a sudden time and this is the unbalanced where one of the phases is basically having more current than two of the other phases. The classification maybe on the basis of the current voltage and the frequency or the load and supply system. Voltage quality problem that is voltage distortion, flickers we have shown it, notches, noise, sag, swell, unbalance, under voltage, overvoltage.

These are the categories of the power quality and current quality problem, the reactive power components of current harmonics, unbalanced current and excessive neutral current. These are power quality problems related to current.

(Refer Slide Time: 30:39)

Power quality problems (Cont...)

- **Frequency-related power quality problems** : Frequency variation above or below the desired base value.
- **Power quality problems due to nature of the load:** Load current consisting of harmonics, reactive power component of current, unbalanced currents, neutral current, DC offset, and so on.
- **Power quality problems due to the supply system:** Voltage and frequency related issues such as notches, voltage distortion, unbalance, sag, swell, flicker, and noise.



Now frequency related problem that is the power quality problem, frequency variation above or below the desired base value. We have a shifting and the power quality problem due to the nature of the load that is from if it is the nonlinear load, this problem arises. Load current consisting of the harmonics and the reactive component of the current, unbalanced current, neutral current and DC offset and so on.

And power quality problems due to the supply of the system, voltage and frequency related issues such as notches, voltage distortion, unbalance, sag, swell, flickers, noise all those things we have discussed. Now thank you for your attention. We shall continue to power quality in our next class. Thank you.