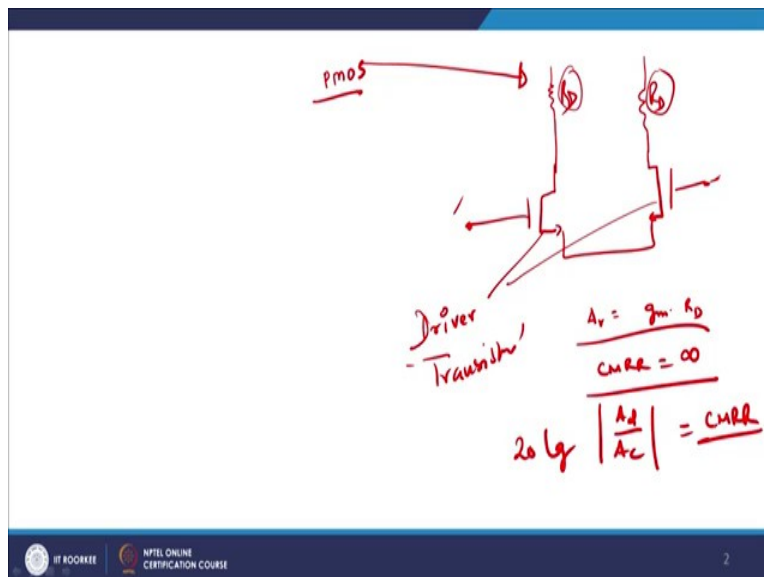


**Microelectronics: Devices to circuits**  
**Professor Sudeb Dasgupta**  
**Department of Electronics & Communication Engineering**  
**Indian Institute of Technology, Roorkee**  
**Lecture 36: MOS Differential Amplifiers**

Hello everybody and welcome to the NPTEL online certification course on Microelectronics Devices to Circuits. We start from where we left in the previous module. We had initially done the work on MOS differential amplifier and we saw that the overall gain of an amplifier depends on the value of your transconductance of the driver transistor and the drain resistance.

(Refer Slide Time: 00:52)




So if we, if we discuss the previous term what we saw was that if you, wherever you are giving the input, please understand, wherever you are giving the input voltages this is the input voltage right this one, this one, these transistors are known as driver transistors, right. Further if you remember we had  $R_D$  here which is the drain resistance right  $R_D$ , this is the  $R_D$  value.

But in reality when you do it on IC or on a chip when you want to fabricate it this resistance is will be performed by MOS devices. Typically if we use a PMOS device here you have a larger resistance being offered at this particular point. So we will see as we move along a lot of how it works out, but typically you have learnt 2 things as the gain is given as  $g_m$  times  $R_D$  by  $CMRR$  is infinitely high because of the fact that you are  $A_d$  it is basically defined as the  $A_d$  by  $A_c$  right.

If you take in db then it will be  $20 \log$  of  $A_d$  by  $A_c$  and this is equals to your CMRR, right and this is typically very high quantity which you get, approximately 10 to the power 5 or 6, ideally this should be infinitely large. What we will do today is we will actually look into MOS differential amplifier part 2 where we will be actually replacing those  $R_D$  the drain resistances by the typical PMOS.

(Refer Slide Time: 02:20)

 

Before we go there let me just do one more amplifier design. That is known as MOS CASCODE design, please understand it is not cascade it is CASCODE, right, so you have a O here, CASCODE design, right, you have a MOS CASCODE design. So, let me draw for you how, this is but please understand this is we are slightly moving away from differential amplifiers. Differential amplifiers, you are feeding signals in a differential fashion to both the inputs of the gate.

Here, it is single stage amplifier it is not a differential stage, so, but, we will see what the advantage of it is as far as designing is concerned. So we apply at voltage source or current source here and then there is (03:03)  $V_{DD}$ , right and then, what we do is, this is quite interesting, that this is Q1 this is Q2 and this is plus minus  $V_{in}$  we apply the voltage here  $V_{in}$  and we apply a fixed bias here  $V_b$ , this Q2 is known as the CASCODED device and this is your input device, you are feeding the input to this and you are taking the output from here, right.

Now, you see this is if you look very carefully this Q1 is basically a common source a design, so this is a Common Source (CS) amplifier, whereas this one if you look very carefully is basically a Common Gate (CG) amplifier, so when common source amplifier and common gate amplifier are stuck together or they are made together, then we defined that to be as a CASCODED amplifier, right.

So what is a CASCODED amplifier you have a common source amplifier you have a common gate amplifier and when they are, when they are, when they are attached like this such a manner that the source of one is connected to the drain of the common source and then we define that as to be a CASCODED, CASCODED case. Now, if I, if I try to plot the  $V_{out}$  versus the  $V_{in}$  to get the transfer characteristics curve here. Right let us suppose this point is  $x$ , right, then if I this is  $V_{out}$ , then I get something like this.

This is your  $V_{th1}$ , this is  $V_{dd}$ , right, and this is  $V_b$  minus I will explain to you,  $V_{th2}$ . If you see as my  $V_{in}$  happens to be very low, right, when my  $V_{in}$  is very, very low I can safely say that my Q1 is cut off, right. So, I am just finding out the voltage at this particular point. Then if this is cut off, which is in the off state, if this is the  $V_{in}$  is very, very low in the off state then you automatically get what that, this is for, this is for, sorry this is for, this is for  $V_{out}$  here and this is  $V_x$ , so  $V_x$  is plotted in this manner and  $V_{out}$ .

So let us look at  $V_{out}$  first, when  $V_{in}$  is very very low, right, as I discussed with you, you can safely assume that Q1 will be cut off and therefore even whatever be the case  $V_{out}$  will be lashed to  $V_{dd}$ , because you do not have any current flowing through the system and therefore  $V_{out}$  will be latched to  $V_{dd}$ . As you start to increase your  $V_{in}$ , as you start to increase your  $V_{in}$  you draw current from Q1, because this is the threshold voltage of the device.

Till  $V_{th1}$  the output will be latched to  $V_b$  minus  $V_{th2}$  what is  $V_b$ ,  $V_b$  is this much,  $V_{th2}$  is the threshold voltage of this device. So remember your  $V_{GS}$  minus  $V_{th}$  was the overdrive, right. So, so this if you look very carefully, this potential here will be nothing but  $V_b$  minus  $V_{th2}$ , right. So this is your, this is your  $V_{GS2}$ , right. So if you look very carefully  $V_x$  will be nothing but  $V_b$  minus  $V_{GS2}$ .

But, for the device to be on  $V_{GS2}$  will be typically equals to  $V_{th}$ , so  $V_b$  minus  $V_{th2}$  will be the value of  $V_x$ , and that is what you are getting here. Till a point, till what point, till the point when the input voltage is just crosses the threshold voltage of the device, which device the common source device which is the Q1 value. As it just crosses the device which is on and

both the currents, and the currents starts to flow through Q1 and Q2 because they are in series. And as it starts to flow the voltage at output starts to fall because  $V_{out}$  will be referred to as  $V_{DD}$  minus  $I_{DRD}$ , say it is the resistance is also here available with you.

So when  $I_D$ , so initially what was happening  $I_D$  was 0, so you had what this was 0 and therefore  $V_{out}$  was equals to  $V_{DD}$ . Now, when the  $I_D$  starts to flow the  $V_{out}$  starts to fall down and that is what is falling down here, right. Similarly, your  $V_x$  will also since your  $V_{out}$  is falling, your  $V_x$  has to also fall, so that  $V_{DS}$  between this and this of Q2,  $V_{DS}$  of Q2 is almost constant. And therefore you see it is almost the same drop is there between the two initially, initially when the  $V_{in}$  is relatively just larger then  $V_{th1}$ , right.

I will just explain to you once again what I just not talked about it, what I talked about it is initially when your  $V_{in}$  is very low less than threshold voltage device, Q1 is in the cut off mode, when Q1 is cut off mode no current is flowing through this CASCODE structure as a result what will happen is your  $I_D$  will be equals to 0, therefore your  $V_{out}$  will be latched out to  $V_{DD}$ , standard case and your  $V_x$  will be equals to  $V_b$  minus  $V_{th2}$ . And we explained why it should be like that, it should be  $V_b$  minus  $V_{GS2}$ , but  $V_{GS2}$  equals to  $V_{th2}$  because that is the on state of the device and therefore that is the overall voltage which you will get here.


Now, as the input voltage crosses threshold voltage of the first device, the device gets on current starts to flow and when the current starts to flow through Q1 it the same current flows through Q2, and therefore the  $V_{out}$  starts to fall down, right, and therefore the  $V_{out}$  starts to fall down, as I discussed with you just now, the  $V_{out}$  starts to fall down, so  $V_{out}$  will fall down as you can see.

But as the  $V_{out}$  falls down you, you have to ensure that Q2 is in saturation and therefore  $V_x$  also starts to fall down and the difference almost remains the same till few values of  $Q_h$ . As  $V_{in}$  further goes on increasing,  $V_{in}$  further goes on increasing this value goes on still further increasing, right, as it goes on increasing, this is, this is basically a gate and source, right. And this is always grounded.

So,  $V_{GS}$  is becoming very, very large which primarily means its over drive is increasing, current is increasing, as a current increases then it forces this voltage to further go down, so that is the reason it is going down and down, right. Ensure it at one point of time it might also happen that  $V_{DS}$  of 1 might be even smaller then  $V_{GS}$  of 1 minus  $V_{th}$  of 1 and forcing the Q1 to enter into triode region, fine.

So, so what I wanted to tell you from this whole, whole, whole idea is that by doing so there is a problem here that common source if you remember was very good amplifier and common gate was a very good a impedance matching purposes. So CASCODE structure helps you to do both of them together that it helps you to match the impedances as well as gives you a improved gain with the with much better gain available to you.

(Refer Slide Time: 10:30)

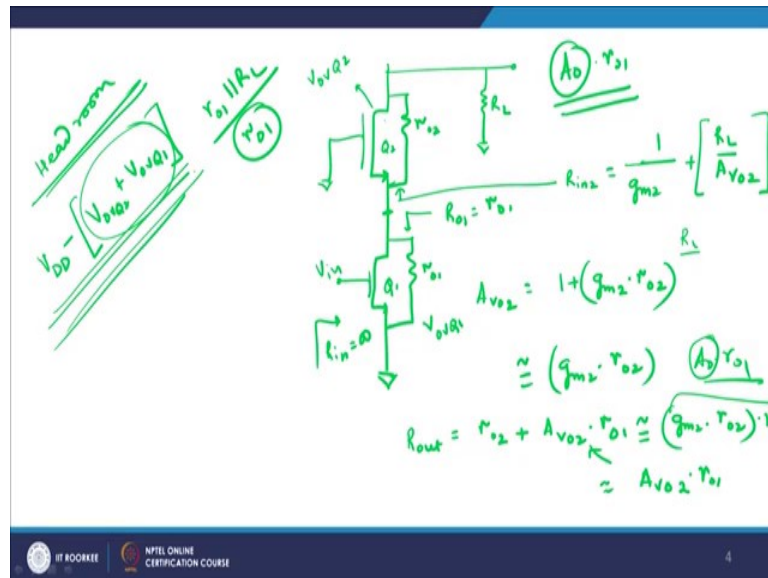

So if I draw the impedance diagram here or if we draw the small signal diagram here and external load is  $R_L$  and let us suppose  $Q_2$  is the input current and  $Q_1$  is the driver CASCODED current, then  $R_{01}$  and  $R_{02}$  are basically the, the resistances offered by those devices, if I assume this is  $Q_2$ , if I assume this is  $Q_1$  and then I am giving a voltage here  $V_{in}$ . So if you look from this side,  $R_{in}$  will obviously be equal to infinity, fine. And, and if you from therefore if you look from this side affectively value of  $R_{01}$  will be equals to  $R_{01}$ . So from this point if you want to look inside affective resistance offered will be equals to  $R_{01}$ . I think I need not to explain it to you why is it like that.

Similarly, if you look from this side, right, and that is quite interesting then  $R_{in2}$  resistance, input resistance of this one will be from source side, is  $1/g_{m2}$ , right plus  $R_L$  by  $A_{V02}$  I will explain to you what do I mean by that. If you remember the whole discussion was that even by inspection also you can predict the value of input impedance, how did you do that just look from the source side and from the source side if a the input impedance will be  $1/g_{m2}$  by transconductance of the device, so that is what we have written here  $1/g_{m2}$  and if you why do you add this  $R_L$  plus  $A_{V0}$  because  $A_{V0}$  is basically the voltage gain right.



Now, so if you divide  $R_L$  by the effective voltage gain I get the input impedance at particular point because  $R_L$  is the external load resistance which you see, which you see here, right.  $A_{V02}$ ,  $A_{V02}$  which is the open circuit voltage gain of the second transistor the common gate one is given as the 1 plus  $g_{m2}$  multiplied by  $r_{02}$ , right. Now, of course this could be approximately return as  $g_{m2}$  into  $r_{02}$ , the reason being that a  $g_{m2}$  into  $r_{02}$  is much larger then 1 and therefore  $A_{V0}$  is equal to  $g_{m2}$  into  $r_{02}$ . Why  $g_{m2}$  into  $r_{02}$  very straightforward  $g_m r_d$ , so  $r_d$  is the resistance offered by the device  $g_m$  is the transconductance of the device.

Now, if you find out  $R_{out}$  and I am not deriving it, it here lot of scope it will be given as  $r_{02}$  plus  $A_{V02}$  into  $r_{01}$  and if you find out this will come out to be  $g_{m2}$  into  $r_{02}$ , right, into  $r_{01}$  and this is nothing but  $A_{V02}$  into  $r_{01}$  which we just found out here, right,  $A_0$  into  $r_{01}$ . So if you look very carefully on this profile here what does it tell me that the output impedance is raised by a factor of  $A_0$ , so suppose, suppose you did not have any CASCODE, you did not have any CASCODE device Q2 was not there, then I would have seen  $r_{01}$  parallel to  $R_L$  now since  $R_L$  is very very large as compared to  $r_{01}$  the output impedance would have been  $r_{01}$ .

Now, when you place a transistor Q2 CASCODED over Q1 you actually increase the impedance by a factor of  $A_0$ , where  $A_0$  is the gain of my Q2, so you multiply this with  $r_{01}$  to get the overall gain  $R_{out}$ . So CASCODE structures, so CASCODE structures improves the gain by a factor of  $A_0$  into  $r_{01}$  and, and gives you a very large value of your output gain, right. So this is a, a brief introduction or a structure of, of CASCODED structures, right, and we will revisit this maybe at a later stage, when we come back. Two things to take away from this discussion on CASCODED important for impedance matching as well as for high gain.


The cost we pay for it is that now you have 2 transistors in CASCODE therefore if you look at this very carefully this will be  $V_{overlap}$ , overlap, sorry  $V_{overlap}$  Q2, and this will be  $V_{overlap}$  Q1. So the available headroom for me will be, will be affectively equals to if you look very carefully will be  $V_{DD}$  minus right,  $V_{overlap}$  Q2 plus  $V_{overlap}$  Q1, right. So this is the available headroom to you in the, in the output side. Which means that if you want the gain to be high for the CASCODED structure you end up having a reduced headroom, so this is basically the headroom, headroom associated with this, right.

(Refer Slide Time: 15:14)

 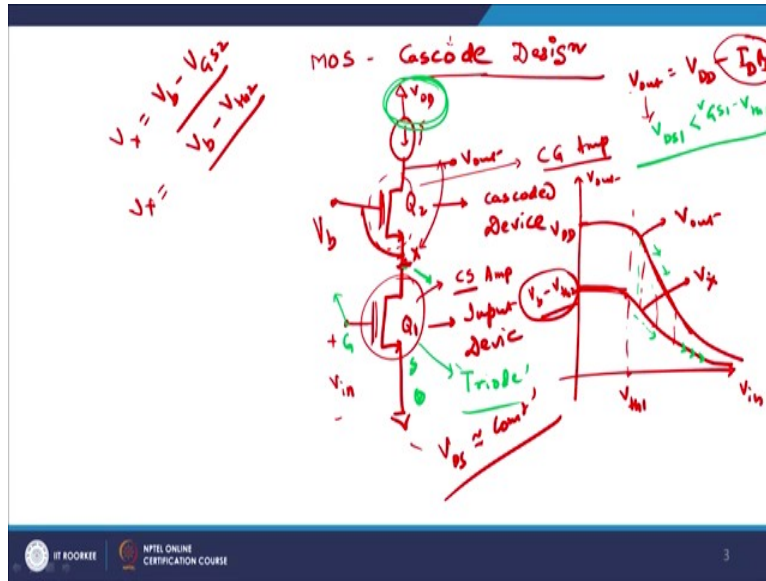

Which means that, so this is connected to so if you look very carefully, if you look at the, this was connected to the  $V_{DD}$  remember, connected to  $V_{DD}$ , which means that it is  $V_{DD}$  minus the sum of the over drives which you see. While looking at this point you please see that the while, while deriving this all quantity you please see that the base of the gate of  $Q_2$  has been grounded, right, whereas, I am giving an input signal to  $Q_1$ , right, please find out why is it like that, why have we grounded  $Q_2$  and why we have taken out the signal through  $Q_1$  here in this case, right. This, this is to rather extent explains the overall features of CASCODED structures using MOS devices.

(Refer Slide Time: 15:50)

 


Let me come to the differential amplifier and let me see how can we change because till now we were what we are looking we were looking in the fact that we had a differential we had a differential 2 differential output. So, I have a differential input and I have a differential output and then what I was doing was I was subtracting  $V_{o1}$  from  $V_{o2}$  or vice-versa. And this is this was  $\Delta V_{out}$  right and already I had  $\Delta V_{in}$  and this was your overall gain which I solved. This is what we are doing till now, we also require to sometimes have a differential to single ended conversion.

So this is the diagram for that, that you apply signals here  $v_{id}$  by 2 so the difference divided by 2 plus and then the difference divide by 2 minus we already know what is  $v_{id}$ . So  $v_{id}$  is basically  $v_{in1}$  minus  $v_{in2}$ , let us suppose, so it is basically this by 2 on this side and then you apply  $v_{in1}$  minus  $v_{in2}$  by 2 with the negative sign on this side perfectly differential signals. As you may, as you mean infinitely high impedance. Then we find put the output impedance at this particular point  $V_o$ , right, and a straightforward way of saying that conversion of a high from a, from differential to single ended input.



(Refer Slide Time: 17:40)

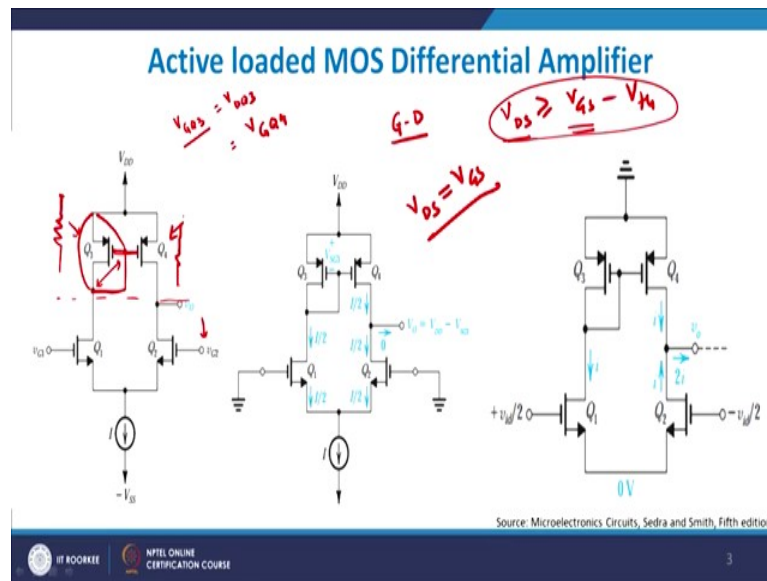

As I discussed with you in the previous turn, what we were doing was that we were, we need not to replace the  $R_D$ , the drain resistance by load, actual PMOS load. So what people thought was that let us apply PMOS load in place of  $R_D$ , the reason was PMOS is effectively having giving you a larger resistance because of lower mobility of holes, for the same dimensions of  $W$  by  $L$ . For the same aspect ratio the resistance offered PMOS will be 3 to 4 times larger as compared to NMOS of the same dimensions. So, if you look, this is exactly the same this below side is exactly the same if you look at the top,  $R_D$  is replaced by  $Q_3$  and  $Q_4$ , right, and these are PMOSs.


And quite interesting what we have done one thing is that we have connected the gate of  $Q_3$  to the drain of  $Q_3$ . So, now if you say  $V_{GQ3}$  right is exactly equals to  $V_{DQ3}$ , right. So gate of, gate of  $Q_3$  and drain of  $Q_3$  are exactly the same which is also equals to  $V_{gate}$  of  $Q_4$  ( $V_{GQ4}$ ), which means that now, gate to source of  $Q_3$  and gate to source of  $Q_4$  is exactly the same. If I join these 2 then it ensures that gate to source of  $Q_3$  and gate to source of  $Q_4$  are exactly same which means that, which means that if I assume that  $Q_3$  and  $Q_4$  are perfectly symmetrical their over drives and resistance will also be equal to each other.

What happens when we join the drain to the gate side of it, right? When you join drain to gate you ensure that the device is basically moving in to a saturation mode and behaving like a resistor, right. If you, if you short gate and drain this is the reason the reason being, remember what was the reason  $V_{DS}$  should be greater than equal to  $V_{GS}$  minus  $V_{th}$ , right. Now,  $V_{DS}$  is this

much,  $V_{DS}$  is this difference and  $V_{GS}$  is this difference. Now, if these 2 are equal then  $V_{DS}$  is always equal to  $V_{GS}$ .

$V_{DS}$  drain to source will always be equal to  $V_{GS}$  gate to source, agree, so drain to source will always be equal to gate to source because your gate and drain have been shorted with respect to each other. Which ensures that which, which is quite interesting that which means that this condition can never be applicable which means that my device can never go into saturated region at all, right, but in triode region behaving like a resistor. So this can be replaced by a simple resistor. If you look back since this is a symmetrical Q4 will also look like a resistor.

(Refer Slide Time: 19:59)

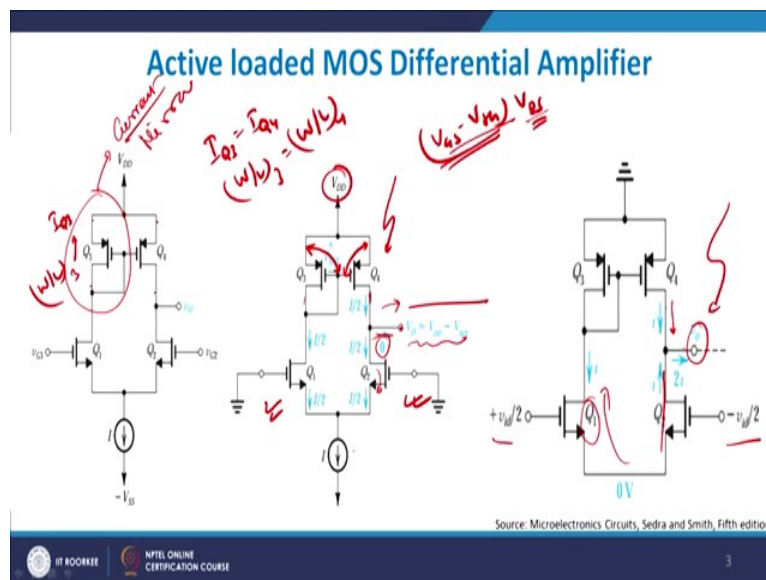

This action is basically known as current mirroring, this, this is known as current mirroring, because this, I will explain it to you later on maybe current mirror. The reason being that the current flowing through Q3 will be exact if the W by L ratios of Q3 and Q4 are same the current flowing through Q3, suppose this is  $I_{Q3}$  will be exactly equals to  $I_{Q4}$  provided W by L of Q3 is exactly equals to W by L of Q3 is exactly equals to W by L of Q4.

The same current will flow, why because remember current is depending on  $V_{GS}$  minus  $V_{th}$  whole square, right, it also depends upon the value of  $V_{DS}$ , if you, if you find out, in the triode region, if you are trying to find out, it depends on the value of  $V_{DS}$  is  $V_{GS}$  minus  $V_{th}$  multiplied by  $V_{DS}$ .

So if I am able to ensure over drive to be equal and  $V_{DS}$  to be equal and everything else taken care of my current will also equal, right. So if you look very closely this difference between


this point and this point will also be equal to the difference between this point and this point. And therefore  $V_{DS}$  will be also equal my over drive will be equal and therefore they will behave like exactly symmetrical structures.

With this knowledge let me say we have this structure available here, so I have, so I, so as I discussed with I have a current source I, it divides into I by 2 here, I by 2 here, so this is I by 2 here, since this is I by 2 as I discussed with you, you will obviously have I by 2 flowing here because it is a current mirroring action here. As a result the current flowing through these will approximately equals to 0 because all I by 2 have has to be routed through Q2, so the net current flowing here will be 0, so that is what is written here.

And therefore  $V_{out}$  will be equals to  $V_{dd}$  minus  $V_{GS3}$ , why,  $V_{dd}$  this voltage minus gate to source, source to gate this to this. So if you subtract this voltage or even if subtract this voltage I get the voltage available at this particular point (())(21:55) Kirchhoff's law. And as a result you will see this. This is for the case when both your Q1 and Q2 are either shorted or having equal dc bias.

Let us come to this point you will have differential voltage given, so I will have I, so this is minus  $V_d$ , minus  $V_d$  by 2 and this is plus  $V_d$  by 2 all current will be routed here. So this is the current flow here, so the other current flowing is here, so net current flow was I plus I 2I and therefore  $V_{out}$  will be having 2I available to you, right. So this is what you get from the, this active load.

(Refer Slide Time: 22:29)

 

Now, therefore if you look here which is what I have done here is I have broken the Q3 Q4 Q1 & Q2 with the effective transient resistance. Where  $r_{o1}$  is the drain to source resistance of Q1,  $r_{o2}$  is the drain to source resistance of Q2, so are and so forth. And I have sort of grounded so 0 voltage is given to the input side to the source side, right. So I will assume that since it is 0 grounded any voltage above them with the threshold voltage of the device give to you gate side will switch on the device, right, switch on the device.

Now this is  $r_{o3}$  and this is  $r_{o4}$  and so on and so forth. So, if you look from if you look from this side towards this side the effective resistance offered will be  $r_{o3}$  is parallel to Q3. And Q3 as I discussed with you if you look from the drain and source side the amount of is given by this, this is the resistance offered. So this resistance is in parallel to  $r_{o3}$  and that is what I have written here. So this is replaced by this quantity, right. Whereas if you look where carefully at this one this is basically again a Q4 is basically a  $V_{CCS}$  a voltage control current source.

And therefore  $g_{m4}$  multiplied by  $V_{G3}$  is the value and  $R4$  is therefore the, the resistance offered between the two, between the two. Assuming that this is the perfect current source I am assuming that there will be no current flowing through  $r_{o4}$  as such, right. So what I see is, if  $v_{id}$  by 2 is the voltage given to the left arm and right arm and I can safely write down  $g_{m2}$  into  $v_{id}$  by 2 as the current flowing here, and  $g_m$  by  $v_{id2}$  opposite direction current will be flowing here, right, and this is what we get.


(Refer Slide Time: 24:16)

$$v_{x1} = -g_{m1} \left( \frac{v_{id}}{2} \right) \left( \frac{1}{g_{m3}} \parallel r_{o3} \parallel r_{o1} \right) \quad r_{o1} \text{ and } r_{o3} \gg \frac{1}{g_{m3}} \quad v_{x1} = - \left( \frac{g_{m1}}{g_{m3}} \right) \left( \frac{v_{id}}{2} \right)$$

$$i_o = -g_{m1} v_{x1} + g_{m2} \left( \frac{v_{id}}{2} \right) \quad i_o = g_{m1} \left( \frac{g_{m1}}{g_{m3}} \right) \left( \frac{v_{id}}{2} \right) + g_{m2} \left( \frac{v_{id}}{2} \right) \quad G_m = \frac{i_o}{v_{id}} = g_m$$

$$\underline{g_{m1} = g_{m2} = g_m} \quad \underline{g_{m3} = g_{m1}} \quad \underline{i_o = g_m v_{id}} \quad G_m = \frac{i_o}{v_{id}}$$

 Source: Microelectronics Circuits, Sedra and Smith, Fifth edition



Now, let me come to the mathematics of it, so if you look very carefully  $V_{G3}$  and this will require some amount of flipping of the power point presentation,  $V_{G3}$  is minus  $g_m$  times  $v_{id2}$  into the sole quantity. What is  $V_{G3}$ ,  $V_{G3}$  is, let me rub this to make it clear,  $V_{G3}$  is nothing but the voltage at the gate of third transistor, right it is nothing but  $g_{m1}$  into  $v_{id}$  by 2, why it is  $g_{m1}$  into  $v_{id}$  by 2 see  $g_{m1}$  is the transconductance of  $Q_1$  into  $v_{id2}$  is the current which the transistor will allow it to flow, so the same current will flow to  $Q_3$ , so that is the, sorry, so that is the  $Q_3$  current here right, I am sorry.

So I get  $g_{m1}$  into  $v_{id}$  by 2 is the current this if you multiply with the impedance that will give you the voltage, what is the impedance, impedance is nothing but  $1/g_{m3}$  because of this one and  $r_{o3}$  this one as well as  $r_{o1}$  because you see this, this and this these 3 will be in parallel to each other. As well as you will get  $g_{m1}$  into  $v_{id2}$  into  $1/g_{m3}$  in parallel to  $r_{o3}$ . Now  $r_{o1}$  and  $r_{o3}$  is much, much larger as compared to  $1/g_{m3}$ . So, what I can safely write now  $g_{m1}$  by  $g_m$ ,  $g_{m1}$  by much larger than  $g_{m3}$ , sorry this will be  $g_{m3}$  I think, this will be  $g_{m3}$  so I will make a correction.

So  $g_{m1}$  by  $g_{m3}$  into  $v_{id}$  by 2, right, now  $i_o$ ,  $i_o$  is the output current right, output current in  $g_{m4}$ , if you look very closely  $g_{m4}$  into  $V_{G3}$ , why,  $V_{G3}$  is the same voltage you are applying on to the fourth transistor  $Q_4$  right. So  $V_{G3}$  multiplied by  $g_{m4}$  is one component of the current and another component of the current is coming from this transistor  $g_{m2}$  multiplied by  $v_{id}$  by 2. So one current component is coming from here another is this one.

This one is  $g_m$  multiplied by  $v_{id}$  by 2 and this one is basically yours, sorry, this one is basically yours  $g_{m4}$  into  $V_{GS}$  by 3 with a negative sign, right. So if you do a small manipulation I get  $i_o$  equals to  $g_{m1}$  into  $g_{m4}$  by  $g_{m3}$  into  $v_{id}$  by 2 plus  $g_{m2}$   $v_{id}$  by 2, as you mean that  $g_{m1}$  and  $g_{m2}$  is equal to  $g_m$  and  $g_{m3}$  and  $g_{m4}$  are equal I can say  $i_o$  is equal to  $g_m$  times  $v_{id}$ .

And therefore capital  $G_m$  is equal to  $i_o$  by  $V_{id}$ , what is  $i_o$ , it is the output current,  $V_{id}$  is the input differential voltage and therefore I use a capital  $G_m$ , capital  $G_m$  is therefore the effective transconductance for the differential pair, fine, so capital  $G_m$  is the effective transconductance of the differential pair (27:04), whereas small  $g_m$  is the transistor level transconductance, fine, so this is the difference between the two.

(Refer Slide Time: 27:17)

**Input and Output Resistance and Differential gain**

$$R_{in1} = \frac{1}{g_{m1}}$$

$$R_{o2} = 2r_{o2}$$

$$R_o = (r_{o2} \parallel r_{o4})$$

$$A_d = g_m (r_{o2} \parallel r_{o4})$$

$$r_{o2} = r_{o3} = r_o$$

$$A_d = \frac{1}{2} g_m r_o$$

The diagram shows a differential pair of NMOS transistors  $Q_1$  and  $Q_2$  with a common source resistor  $r_{cs}$ . The input is a differential voltage  $v_{id}$  applied to the gates. The output is a differential current  $i_o$  taken from the drains. Annotations include:  $r_{in}$  at the input,  $r_{o2}$  and  $r_{o4}$  at the output nodes, and  $R_{in}$  and  $R_{out}$  at the differential input and output ports. Arrows indicate the direction of current flow and voltage drops.


Source: Microelectronics Circuits, Sedra and Smith, Fifth edition

Let us look at the input and output resistance of the differential pair if you look input resistance will be given as  $1/g_{m1}$  we have already looked into the fact that, that input resistance given by here is  $g_{m1}$ ,  $R_{o2}$  will be 2 times  $r_{o2}$  the reason being that if you look from this side, if you look from this side you have  $r_{o1}$  coming from here, one resistance is coming from here and another one is basically coming from here, so they are equal and therefore assuming to be true.

And therefore,  $R_o$  though effective resistance seen at this particular point these two are in parallel, these two are in parallel and therefore I get  $r_{o2}$  parallel to  $r_{o3}$ , right. We will explain to you this why  $R_{o2}$  is actually equals to  $2r_{o2}$ ,  $r_{o2}$  which is looking from this side you will have 2 times  $r_{o2}$  right, and looking from this side you will have this these 2 in parallel that is what

you get here, and therefore the differential gain will be nothing but  $g_m$  times  $r_{o2}$  multiplied by  $r_{o4}$  assuming  $r_{o2}$  equals to  $r_{o4}$  equals to  $r_o$ . I can safely write down  $A_d$  to be equals to  $1$  by  $2 g_m r_o$ , fine, because they are in parallel, write so this is what you get parallel.


(Refer Slide Time: 28:20)

 

Now, we will look into common mode and differential gain so common mode gain if you remember what we did we inserted  $V_{icm}$  as the input mode voltage and I replace my current source by  $R_{SS}$ ,  $R_{SS}$  is of the very large value of your resistances being offered here. It is a quite a large value of resistance because output impedance of the, of the current source will be typically very high. And then what we do, we do a half circuit realization and we divided into 2 parts and we give  $V_{cm}$  here,  $V_{cm}$  here and then this is parallel so  $1$  by  $2 R_{SS}$  plus  $1$  by  $2 R_{SS}$  will give you  $R_{SS}$  and that is the reason we divided into 2 parts and we just separate it out, right, for calculation purposes.



(Refer Slide Time: 28:59)

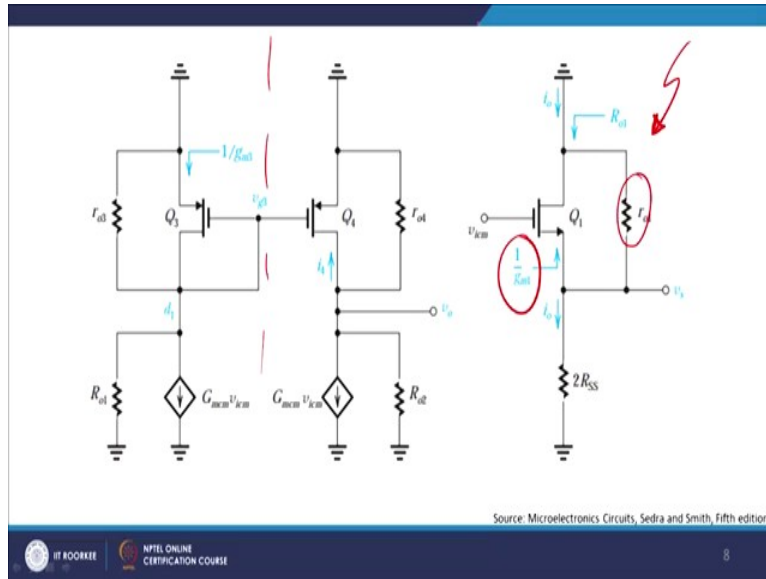

Similarly, when we look in to the, the overall transconductance features here so, so this basically one of the half circuits. This is one of the basically the half circuits. So if you look at the half circuit it is Q1 with  $2 R_{SS}$  here and  $r_{o1}$  as the drain to source resistance offered by this thing and therefore looking from the source side is 1 by  $G_{m1}$  is the effective resistance offered, offered by the device, right. So what we have done is that we have just broken up in to half circuit and explain it to you this basic idea.

(Refer Slide Time: 29:29)

$$i_o = \frac{v_{icm}}{2R_{SS}} \quad G_{mcm} = \frac{1}{2R_{SS}} \quad i_i = -g_{m1} G_{mcm} v_{icm} \left( R_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}} \right)$$

$$R_{o2} = 2R_{SS} + r_{o2} + (g_{m2} r_{o2}) (2R_{SS}) \quad G_{mcm} v_{icm} + i_i + \frac{v_o}{R_{o2}} + \frac{v_o}{r_{o4}}$$


$$R_{o1} = 2R_{SS} + r_{o1} + (g_{m1} r_{o1}) (2R_{SS}) \quad v_o = -v_{icm} \frac{r_{o1} \parallel R_{o2}}{2R_{SS}} \left[ 1 - g_{m1} \left( R_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}} \right) \right]$$

$$v_{o3} = -G_{mcm} v_{icm} \left( R_{o1} \parallel r_{o3} \parallel \frac{1}{g_m} \right) \quad A_{cm} = -\frac{r_{o4}}{2R_{SS}} \frac{1}{1 + g_{m3} r_{o3}}$$

$$i_i = g_{m1} v_{e3} = g_{m1} v_{e3}$$

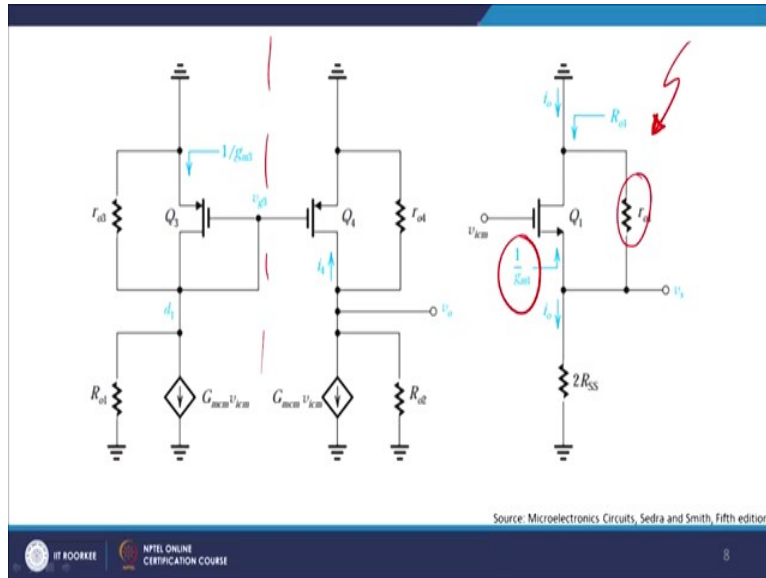Source: Microelectronics Circuits, Sedra and Smith, fifth edition





So, let me come to you and explain to you each one of them individually, so  $i_0$  will be equals to  $v$ , so  $i_0$  will be the output current is  $V_{icm}$ , why it is  $V_{icm}$ ,  $V_{icm}$  is,  $V_{icm}$  is basically this  $V_{icm}$ , this divided by 2 at twice  $R_{ss}$  because twice  $R_{ss}$  is the resistance offered by it, whereas,  $G_m$ , therefore  $G_m$  cm will be  $1$  by  $2 R_{ss}$ , right because current is equals to  $G$  into so if you remember current will be equals to, therefore voltage into  $G$ ,  $G$  is the transconductance.

And therefore, I can safely write down  $G_{2b}$  equals to  $1$  by  $2 R_{ss}$ .  $R_{02}$  is given by this formula,  $R_{02}$  is the,  $R_{02}$  is basically the resistance at this particular point at  $Q_2$ , this is  $r_{o2}$ . Looking from this side this is  $R_{02}$ , right,  $R_{02}$  if you look at this is  $2R_{ss}$  why  $2R_{ss}$  because you will always have  $2R_{ss}$  here, right you will have  $r_{o2}$ , the resistance plus  $g_{m2} r_{o2}$  into  $2R_{ss}$ , what is this quantity  $g_{m2}$  into  $r_{o2}$  into  $2R_{ss}$  into  $2R_{ss}$  will give you the overall resistance offered by the device, right.

Similarly,  $R_{01}$  by symmetricity you will get this, similarly if you (multi) therefore,  $R_{01}$  and  $R_{02}$  are known to you, you can predict the value of  $i_4$  and  $V_{g3}$  and from here, I will get common mode signal value to be equal to  $A_{cm}$  to be equals to this much. Please do it yourself these internal I am not doing it in the lecture module, but, please solve these yourselves to get these values and you will get  $r_{04}$  by by  $2R_{ss}$  by  $1$ .

So if you want your  $A_{cm}$  to be really, really small, right, keep your  $R_{ss}$  infinitely large and that is the reason why we require a almost an ideal current source here to make my  $R_{ss}$  as large as possible, right. That makes my  $A_{cm}$  very small and therefore by  $CMRR$  will also be very large.

(Refer Slide Time: 31:28)

## Recapitulation

- The CMRR for the MOSFETs diff-amp is also a strong function of output resistance of the constant current source.
- The CMRR can be increased by increasing the output resistance of the current source.
- The CMRR can be increased by using the casocde current mirror.
- single-ended, the active-loaded MOS differential amplifier has a low common-mode gain and, correspondingly, a high CMRR.
- The differential transmission of the signal on the chip also minimizes its susceptibility to corruption with noise and interference.

Source: Microelectronics Circuits, Sedra and Smith, Fifth edition

So, let me recapitulate what we did today in this, in this thing, the CMRR MOSFET is a strong function of output resistance we have seen that, and therefore, we have to ensure that it is a constant source or an ideal current source. How can you increase a CMRR by increasing the  $R_0$  value that we have also seen in the previous discussion. If you use a CASCODED current mirror your CMRR will increase because your  $A_{cm}$  will decrease and  $A_d$  will increase.

We discussed that point today also that the differential voltage gain will be much higher in a CASCODED current mirror design. Then, the single ended active loaded MOS differential amplifier as a low common mode gain, and correspondingly high CMRR and the differential transmission of single on the chip also minimises the susceptible corruption with noise and interference. This is quite interesting the last one which take me that if you do have a chip in which you have got large impedances  $R_{out}$  is typically very large, it is actually a very good rejecter of noise also.

So noise resistance capabilities of differential amplifier is typically very high, we have already discussed this point, but not only because differential operation but because also of high impedance nodes in those devices, right. So with this we finish of this module and from next module we will take up another subject, right. Thank you very much.