

Course Name: Design of Electric Motors

Professor Name: Dr. Prathap Reddy B

Department Name: Electronic Systems Engineering

Institute Name: Indian Institute of Science Bengaluru

Week: 09

Lecture: 50

Title: Equivalent Circuit Parameters of Induction Machine

Greetings to all in the last lecture we have discussed the resistance leakage inductances of stator as well as rotor with respect to the various leakage flux components and magnetizing inductance as well as magnetizing current. In this lecture we will discuss the equivalent circuit analysis of an induction machine. If we will consider the three phase balanced machine where the mechanical displacement of the windings as well as electrical current displacement of the windings is 120 degree. In that case the equivalent circuit for an induction machine with respect to per phase is like this we can see in this slide. This is the per phase equivalent circuit of an induction machine. R_s represents the stator side resistance, X_{ls} represents the stator side leakage reactance component and jX_m represents the magnetizing reactance and R_c represents the core loss component and respective currents I_c and I_m with respect to the magnetizing and core loss component and I_{s1} is the stator side current and V phase RMS is the applied voltage and the current referred to the stator side we can see I_r dash the rotor current referred to the stator side is I_r dash and the induced voltage at the stator side as well as rotor side is E_1 and E_2 and rotor side resistance, rotor side leakage reactance component and mechanical load as well as loss components we can see in this equivalent circuit.

If the system or three phase machine is balanced the equivalent circuit is same for all three phases. If the three phase machine is not balanced either it is mechanical displacement or electrical current thing we have to consider the different equivalent circuits per phase. If we will refer the rotor side variables to the stator side the referred rotor resistance will be R_r dash that is the resistance which is referred from rotor side to stator side with some transformation ratio that transformation ratio we will discuss in the coming slides and X_{lr} dash is nothing, but reactance referred to the stator side and R_r dash into $1/s$ minus 1 is nothing, but mechanical load and loss component and if we will neglect the core loss component the equivalent circuit will be in this fashion this is the equivalent circuit with respect to the IEEE standards. Why we have to study the equivalent circuit means to analyze the performance behavior of a machine with respect

to the copper loss in stator as well as rotor maximum and full load torques and output power calculation with respect to the copper losses and power factor at full load as well as no load condition.

After knowing all these parameters like resistances inductances or reactances and resistance and reactances at the rotor side we can analyze all these performance parameters that we will see 1 by 1. First we will discuss the stator resistance per phase the general equation for a to calculate the resistance of an ah winding that is ρl by A we have discussed the equations related to the stator resistance per phase already this is the final equation. Our phase is equals to ρl length of the total coil divided by a_c is nothing, but area of cross section of each conductor we can see right side here the single turn or 1 coil consist of N number of turns and if all coils placed inside the machine we can see the image at the bottom side. How to calculate the length of a coil means the length of coil is nothing, but 2 times the core length if we will place this coil in a machine core the length of the core is nothing, but l_e . So, 2 times the length of core we have to consider and then the end winding length 2 times the end winding length.

So, this end winding length we have to calculate depends upon the arc length like $\pi D I_s$ by P. So, number of poles is nothing, but P and $D I_s$ is the inner diameter of stator this is the pole pitch $\pi D I_s$ by P is nothing, but pole pitch into short pitch factor for a full pitch this short pitch factor will be 1 for full pitch winding for short pitch winding depends upon the short pitch angle let us say the coil is short pitched by 1 slot. So, slot angle equals to 30 degrees means for an example. So, substitute that 30 degrees here and find the short pitch factor and substitute in the length of the coil equation and the additional 20 to 30 percent of core length why we have to consider means we can see here some straight portion of the coil and this is the portion where the end winding is sitting the arc length and this is some portion of conductor straight portion of the conductor which is coming out of the core we can see here with respect to the machine some coil length is coming out of the core the useful conductor length sitting inside the core will be l_e the remaining straight portion of the coil length will be 20 to 30 percent of the machine we have to consider for a large mission we can consider 20 to 30 percent, but for small missions we have to consider slightly higher up to 30 percent we can consider. In order to meet the current rating let us say each coil is carrying 5 ampere to meet the 10 ampere rating we have to connect 2 wires in parallel.

So, this winding is carrying 5 ampere and this winding also carrying 5 ampere. So, total we can see 10 ampere. So, effective resistance if you have to calculate then 1 by parallel number of circuits into actual resistance of a phase that is 1 by c into ρl by a will give the effective resistance of a phase with respect to the parallel connected windings or parallel connected circuits.

Then how with respect to the material we have to choose the resistivity of the material for stator side windings most of the cases we will utilize the copper the copper resistivity value is 1.68×10^{-8} ohm meter and for rotor bars squirrel cage rotor machine we can see here the rotor squirrel cage rotor the resistivity for aluminum bars will be 2.65×10^{-8} ohm meter. So, other materials also we can see conductor semiconductors and insulators, but most of the electrical machines we will see the copper windings. Then the leakage inductance or leakage reactance with respect to the stator the leakage reactance is equals to $2\pi f s$ into L_l , here L_l is the stator side leakage inductance and $f s$ is the stator frequency. The leakage inductance of the stator consist of 5 components first one is with respect to the slot leakage component and second one is with respect to the end winding third one is harmonic or belt leakage inductance fourth component is the zigzag leakage inductance component and fifth one is the skewing effect based inductance. So, by considering all this 5 leakage inductances we have to calculate the stator leakage reactance.

The equations associated with this 5 leakage components we have discussed already in the previous lectures. Same equations we have to apply here to find this leakage components. Then magnetizing inductance depends upon the stator mmf and area flux density. So, the magnetizing inductance L_m is equals to $\frac{3}{2} \times \frac{4}{\pi}$ that is constants and number of turns square by number of poles and k_1 is nothing, but winding factor that is the product of different factors like pitch factor, distribution factor, skew factor and slot opening factors and πD by P is nothing, but pole pitch l_e is the length of the stator core and $\frac{2}{\pi} \times B_g$ is nothing, but average area flux density F_s is nothing, but stator peak fundamental mmf.

Then rotor resistance per mesh that is R_r the rotor resistance with respect to one particular mesh is equals to this one that is 2 into rotor resistance with respect to a single bar rotor resistance with respect to one end ring divided by $2 \sin^2$ into $2 \sin^2$ of slot angle with respect to rotor πP into P by Q r is the slot angle α by 2 we have to consider here.

Then rotor resistance with respect to single bar based upon the conventional resistance equation ρl by a we can see here that is R_b is equals to resistivity of the bar material and length of the each bar and area of cross section of the bar length of the bar how to calculate if without skewing is there then length of the bar is equals to l_e . If we will skew the bar the bar length will increase right that is skewing angle is nothing, but π into P by Q s . So, based upon the skewing angle α skew we have to find the new length of the bar. So, that is l_e by \cos skew angle and area of the area of cross section of the bar is equals to I_{bar} current rms value divided by current density of the bar. So, with respect to the aluminum we can consider the current density and bar current also we know then area of cross section of the bar we can calculate it.

Similarly, the rotor resistance with respect to each end ring this is the end ring portion each end ring like the two end rings are there right. So, based upon these two end rings we have to calculate the end ring resistance again the same formula ρl by a the length of end ring we have to calculate the mean length the inner diameter of the end ring as well as outer diameter of the end ring we have to consider. Then the perimeter with respect to these two diameters will be $\pi D_{out} - 2d_e$ by 2 is nothing, but perimeter with respect to the inner diameter of the end ring and πD_{in} is nothing, but perimeter with respect to the outer diameter by 2 will give the mean length of the end ring that is final equation will be π into outer diameter of the rotor minus depth of the each end ring that is d_e value and cross sectional area of each end ring we can calculate it by I by J.

Then rotor leakage inductance per rotor mesh we can calculate similar to the resistance thing that is 2 into bar leakage inductance and bar harmonic leakage inductance. So, L_{be} is nothing, but effective bar inductance that consist of two components one is bar inductance other is end ring inductance and L_{bh} harmonic is nothing, but harmonic leakage inductance.

So, we have to calculate the bar leakage inductance depends upon the n^2 into permeance equation and here permeance with respect to the each bar will be in this manner depends upon the slot dimensions like d_3 d_1 r b s r and d_{naught} r are the slot dimensions we have discussed already in the earlier lecture and length of the bar we can calculate it with respect to the skewing angle.

And the reference for this equation we can go through this text book and end ring leakage inductance we can calculate it by utilizing this formula and here d_b is nothing, but rotor inner diameter measured at the middle of the end ring. So, that is nothing, but D_{naught} r is the outer diameter of the rotor minus $2d_s$ r that is slot depth into depth of the each end ring mean depth I can say d_e . So, based upon that thing we have to calculate the diameter and we have to substitute d_b value in the end ring leakage inductance that is equals to μ_{naught} into rotor inner diameter measured from the middle of end ring divided by 2 into number of rotor slots into the remaining equations we can see here.

And then rotor harmonic leakage inductance is nothing, but L_{bh} harmonic we have to calculate based upon the permeability and pole pitch with respect to the rotor and length of the core and then number of slots at the rotor side and number of poles.

So, this is the harmonic sum that is 2 into N into number of slots by P plus 1. So, how it will vary this term with respect to the different harmonics we have seen the curve already based upon that thing we can calculate the harmonic leakage inductance at the rotor side. Once we have calculated the rotor resistance and rotor leakage inductance how to transform the these variables to stator side. So, we have to consider the

transformation ratio or turns ratio right. So, the turns ratio for multiple winding based ideal magnetic system will be like this N_2 by N_1 . N_2 is the number of turns at the secondary side N_1 is number of turns at the stator side voltage and currents voltage at the secondary side will be V_2 voltage at the primary side will be V_1 .

So, the MMF turn $N_2 I_2$ is equals to $N_1 I_1$. So, by utilizing this MMF equation we will derive the turns ratio first then transformation ratio to transfer the rotor side resistance and reactance to the stator side. First MMF term we can consider. So, the stator side MMF that is m_s is the number of phases at the stator side, N_s is the number of turns per phase at stator side and k_{1s} is nothing, but winding factor with respect to stator winding and I_r dash is the rotor current referred to the stator side. Secondary side we have m_r is the number of phases at the rotor side and number of turns per phase at the rotor side that is number of turns per phase will be 1 right if I will consider 1 bar per phase.

If I will consider N_r by 3 per phase then number of phases at the rotor side you have to consider 3. If you are considering number of phases at the rotor side that is Q_r equals to N_r then here number of turns per phase should be 1. In both cases you will see N_r only the product of m_r into N_r will give the N_r value only and then rotor current is I_r and winding factor with respect to the rotor is k_{1r} . So, here k_{1r} depends upon the skewing the winding factor at the rotor side the winding factor at the stator side depends upon the pitch factor distribution factor and skewing factor and slot opening factor. From this equation we can see the transformation ratio or turns ratio I_r by I_r dash is equals to m_s number of phases at the stator side N_s and k_{1s} divided by m_r into N_r into k_{1r} .

So, the final equation with respect to the turns ratio we will get this one. Now, if we will see the equivalent circuit of the induction machine before transferring the rotor side variables or parameters to the stator side and after transferring the rotor side variable to the stator side the loss with respect to the rotor resistance before and after referring the with respect to the transformation terms should match. So, that ratio we have to maintain. So, the loss with respect to the resistance before referring and after referring has to be match. So, based upon that analogy we can see here with respect to the single bar resistance here R_b is the single bar resistance I_r is the rotor current and m_r is the number of phases at the rotor side and m_s is nothing, but stator side number of phases and I_r dash is nothing, but rotor current referred to the stator side and R_b dash is nothing, but rotor resistance bar resistance referred to the stator side.

So, the copper loss equations we have to match. So, based on this equation R_b dash rotor resistance referred to the stator side divided by rotor resistance of the bar is equals to Q_r into I_r square. Q_r is the number of bars or number of slots at the rotor side divided by number of phases at the stator side into I_r dash square. So, from this equation if we will substitute I_r divided by I_r dash terms ratio term here square means 2 times we have to substitute this is 1 and this is 2 substitute those things here I_r by I_r dash term 2 times here

then we will get the R_b dash rotor bar resistance referred to the stator side. The turns ratio or transformation ratio will be this one that is 4 into m_s is the number of phases at the stator side and N phase is nothing, but number of turns per phase square into winding factor with respect to the stator square divided by number of slots or number of bars at the rotor side into winding factor at the rotor side square.

Now, if we will consider the complete resistance per mesh, R_r is the resistance per mesh, right rotor mesh. So, if I will consider complete mesh, so we have to multiply the I square R loss with respect to the how many number of meshes are there, right. So, m is m mesh is nothing, but number of meshes at the rotor side that into I_r square into R_r the resistance of the each mesh that should be equals to the number of phases at the stator side that is 3 if number of phases are 3 then $3 I_r$ square that is reflected referred to the stator side current into rotor resistance referred to the stator side.

So, based on this equation also we will get we will arrive at the same transformation ratio R_r dash divided by R_r is equals to 4 into m_s is the number of phases at the stator side and turns per phase and winding factor at the stator side divided by rotor number of slots or rotor number of bars into winding factor at the rotor side square. So, this transformation ratio will not change whether you are transferring one bar resistance or complete rotor bar resistance that ratio will not change that same ratio will be applicable to refer the leakage reactance component to the stator side that we can see here the bar resistance and rotor resistance per mesh both are having the same transformation ratio.

And this ρ TR is nothing, but transformation ratio this transformation ratio term will be applicable for reactance also. So, the leakage reactance of the rotor referred to the stator side will be this thing L_{lr} dash divided by L_{lr} is equals to the ρ TR that is the transformation ratio this one X_{lr} is nothing, but reactance of the rotor referred to the stator side here the frequency is the stator side frequency f_s into L_{lr} dash.

So, the final equivalent circuit parameters we have we know how to calculate the resistance at the stator side reactances and resistance of the rotor resistance of the sorry reactance of the rotor referred to the stator side and magnetizing inductance and mechanical load component if you know the slip then we have calculated the all impedance terms of this equivalent circuit then we can analyze the stator current equations and power factor equations right. So, the impedance with respect to the rotor side is nothing, but R_r dash by S plus J into X_{lr} dash just addition of these two impedances and then Z_f is nothing, but parallel or equivalent impedance seen at these two terminals J_{xm} parallel to the R_r plus JX_{lr} dash that is the Z_f . So, equivalent impedance with respect to these two terminals A and B is nothing, but this one then total impedance seen with respect to the supply terminals will be Z_s that is sorry Z_s is the stator impedance the total impedance seen at the stator input terminals is nothing, but Z equivalent Z is equivalent is equals to impedance with respect to the stator that is Z_s plus

the impedance with respect to the points A and B that is Z_f then we can calculate the stator side current is nothing, but voltage divided by impedance then magnitude and angle both we will get it from this equation that angle is nothing, but power factor angle.

So, \cos of that particular angle will give the power factor of the machine under the loaded condition then the rotor equivalent equations as per this equivalent circuit we can calculate based upon the current division rule the stator current we know that is the I_s into opposite impedance divided by total impedance Z opposite plus Z same thing. So, here Z opposite is nothing, but magnetizing reactance and Z_r is nothing, but R_r dash plus $j X_{lr}$ dash based upon that thing we can calculate the rotor current referred to the stator side.

Then how to find the rotor short circuit current equations under blocked rotor condition generally the blocked rotor test we will perform with the reduced voltage and reduced frequency if we will operate at the rated voltage because of the lesser resistance as well as impedance huge currents will flow because slip is equals to 0 because of that reason we have to reduce the phase voltage as well as frequency with a factor X_{sc} voltage per phase reduced value and frequency reduced value we can get it the factor of reduction with respect to the short circuit condition into the phase voltage and factor of reduction into frequency. So, with respect to this reduced phase voltage and equivalent impedance we can calculate it based upon the equivalent impedance then the short circuit current under the blocked rotor condition is equals to V divided by Z equivalent and that equation with respect to the resistances and inductance term we can see in this equation this one. So, this is the rotor short circuit current equation.

So, with this I am concluding this lecture. In this lecture we have discussed the summary of the equivalent circuit parameters like resistances, inductances or leakage reactance components and how to find the power factor and how to find the different currents with respect to the equivalent circuit analysis we have discussed. Thank you.