

**Microwave Integrated Circuits**  
**Professor Jayanta Mukherjee**  
**Department of Electrical Engineering**  
**Indian Institute of Technology Bombay**


**Module 1**

**Lecture No 2**

**Reflection Coefficient, VSWR, Smith Chart.**

Hello welcome to another module of this course, microwave integrated circuits. In the previous module, we saw the properties of microwave circuits, the wave nature and the distributed and then we also found the solution of transmission lines equation is for dealing with distributed circuit elements. In this lecture let us continue with the discussion. So the 1<sup>st</sup> so one more concept that is associated with microwave circuits is the concept of impedance.

(Refer Slide Time: 0:55)

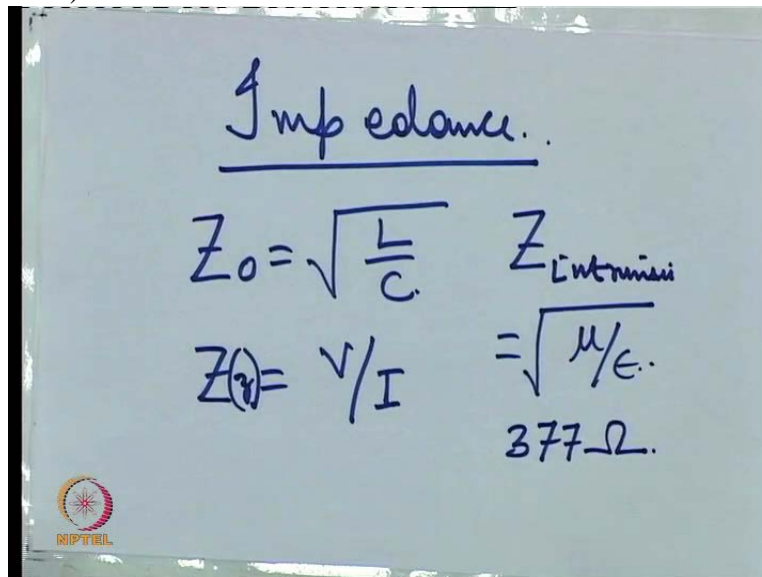


Impedance.

$$Z_0 = \sqrt{\frac{L}{C}}$$
$$Z(z) = V/I$$
$$Z_{\text{intrinsic}} = \sqrt{\frac{\mu}{\epsilon}} = 377 \Omega$$

The impedance can be defined in various ways. One is that characteristic impedance associated with distributed circuits that which we found out to be L and C. Then Z also is defined as V and I as we saw in the case of distributed circuits. We can have V and I solutions so then we can also have Z. Z of course is a function of z the small z the distance from the source. Then there is also another kind of impedance that is defined which is called Z intrinsic which is related to the properties of the material. For example for air this ratio comes out to be 377 ohms. So this has nothing to do, this definition of impedance has nothing to do with voltages and currents. Still this holds.


In fact for microwave engineering as we saw for single conductor waveguide. You know that in a single conductor waveguide we cannot have a unique definition of voltage and current. But we can have a definition of impedance. Either from this relationship that is we have an electromagnetic wave passing through some media. Then you can find out  $Z$  intrinsic from this relation.

(Refer Slide Time: 2:34)

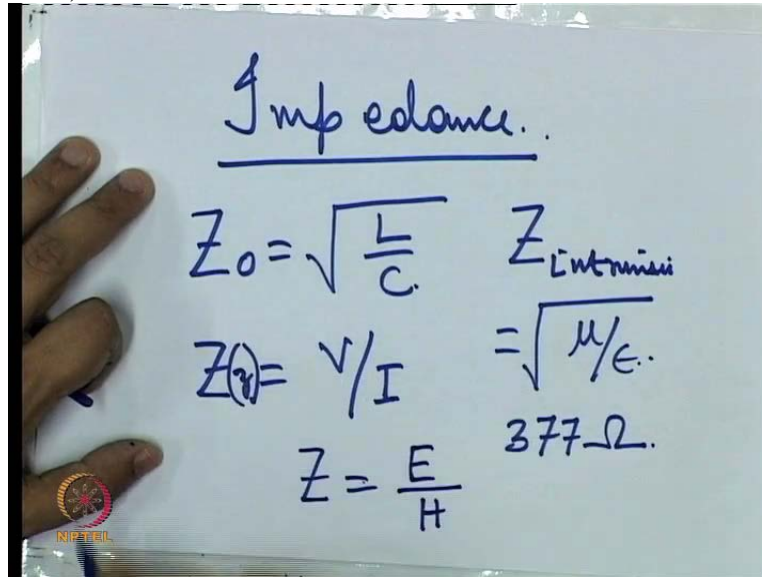

Or  $Z$  is also yet another definition of  $Z$  is ratio of electric to magnetic field. So these are the various definitions of impedance.

(Refer Slide Time: 2:57)

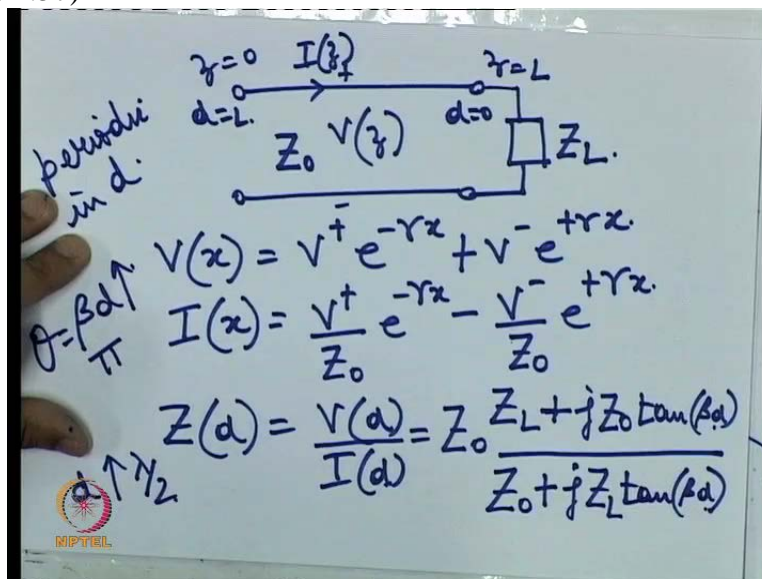


Now let us see let us come back to our definition come back to our transmission lines where we had found out the solution for  $V_x$  or  $Z$ . This is  $Z$  equal to 0 this is  $Z$  equal to  $L$ . Where  $V$  at a particular  $Z$  and  $I$  at a particular  $Z$ .  $Z_0$  is the characteristic impedance.

Now solving this equation you can obtain the solution for  $Z_d$  given by  $V_d/I_d$  where  $d$  is the distance from the load end that is here  $d$  is equal to 0 and here  $d$  is equal to  $L$ . And this comes out to be equal to  $Z_0(Z_L + jZ_0)$ .

We see that this definition of  $Z_d$  means  $Z_d$  is periodic in  $d$  i.e. when every time  $d$  increases by  $\lambda/2$  we get the same value of  $Z_d$ . Or when  $\theta$  given by  $\beta d$  increases by  $\pi$  we also get the same value of  $Z_d$ . In fact from this we can derive the expressions of input impedance i.e.  $Z_d$  for some special types of transmission lines.


So we have obtained solution for the input reflection coefficient of input impedance. I beg your pardon. We have not come across the concept of reflection coefficient yet. We have found that the input impedance of transmission line loaded with an impedance  $Z$ . Now let us see what happens if we consider some special cases. So the special cases are:

(Refer Slide Time: 6:29)

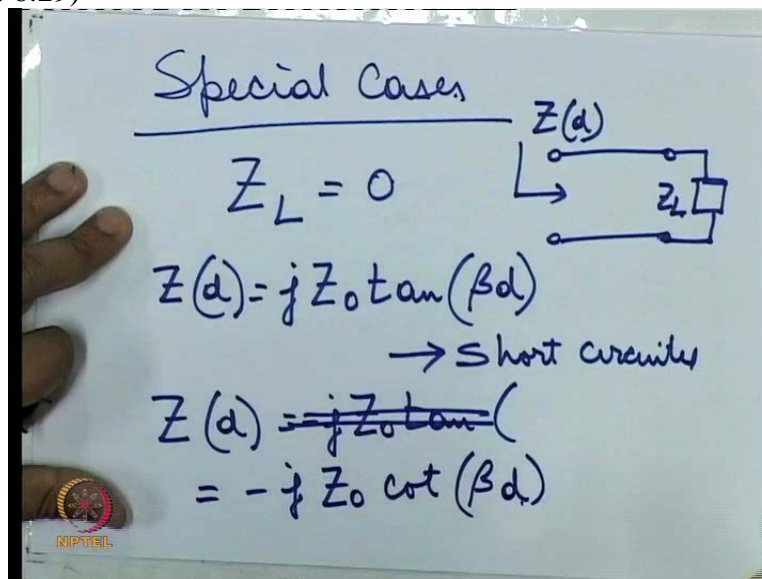


1<sup>st</sup> is when  $Z_L$  is equal to 0. So when  $Z_L$  equal to 0. So this is our transmission line once again,  $Z_L$  the load. Then,  $Z_d$  this is for a short-circuited line. So short-circuited line will have this kind of an input impedance. For an open circuited line this will be sorry this will be  $-jZ_0 \cot$  of  $\beta d$ .

(Refer Slide Time: 7:46)

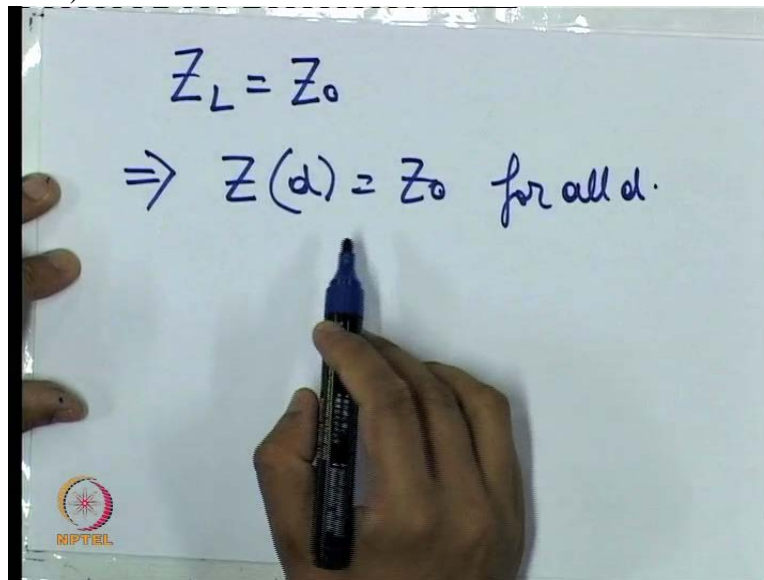

And for the case when  $Z_L$  is equal to  $Z_0$ ,  $Z_d$  will be simply equal to  $Z_0$  for all  $d$ . Means as if the transmission line is never present. If we plot a curve the value of  $Z_d$  for the shorted transmission line, it appears to be something like this.


(Refer Slide Time:8:16)

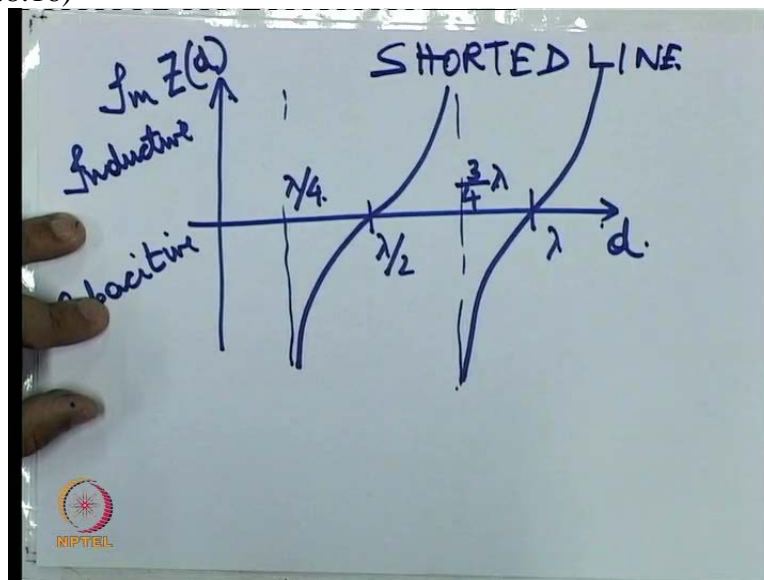

So we can see a shorted transmission line can take on both positive values as well as negative values for different values of  $d$ . For example, when  $d$  is equal to 0, it has a 0. So it is like a short. When  $d$  is between  $\lambda/2$  and  $3\lambda/4$ , it is positive.  $Z_d$  is positive for a shorted line. So this is for a shorted line.  $Z_d$  is positive. So it acts as an inductor. When  $d$  is between  $\lambda/4$  and  $\lambda/2$ ,  $Z_d$  is negative and hence the shorted transmission line acts as capacitor. A special


type of transmission line which is very commonly used is what is called as a quarter wave Transformer.

(Refer Slide Time: 10:08)

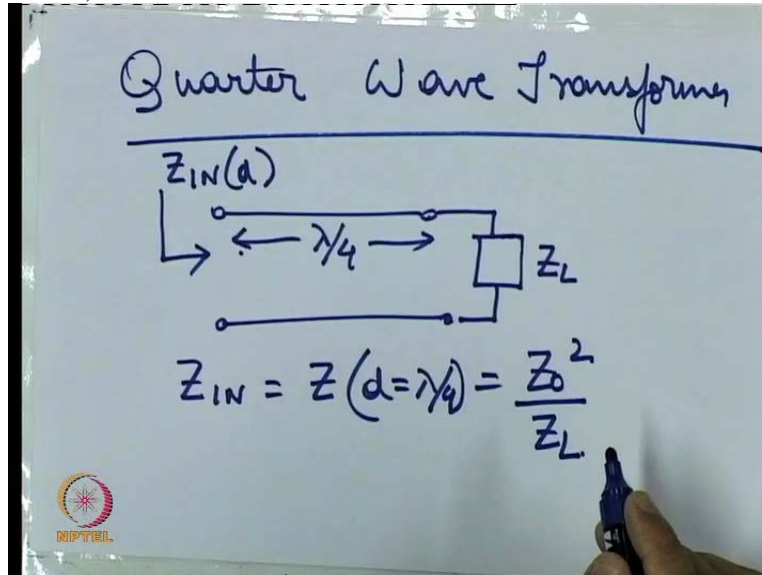


For quarter wave Transformer is a transmission line which is quarter wavelength long i.e.  $\lambda/4$  long. It is also terminated by a load  $Z_L$ . Now, in place of  $Z_d$  I can also write this as  $Z_{in}$ . So  $Z_{in}$  will be equal to  $Z_d$  equal to  $\lambda/4$  and this comes out to using the equation that I just gave if we put in the equation that I had previously stated that if this equation

(Refer Slide Time: 11:07)

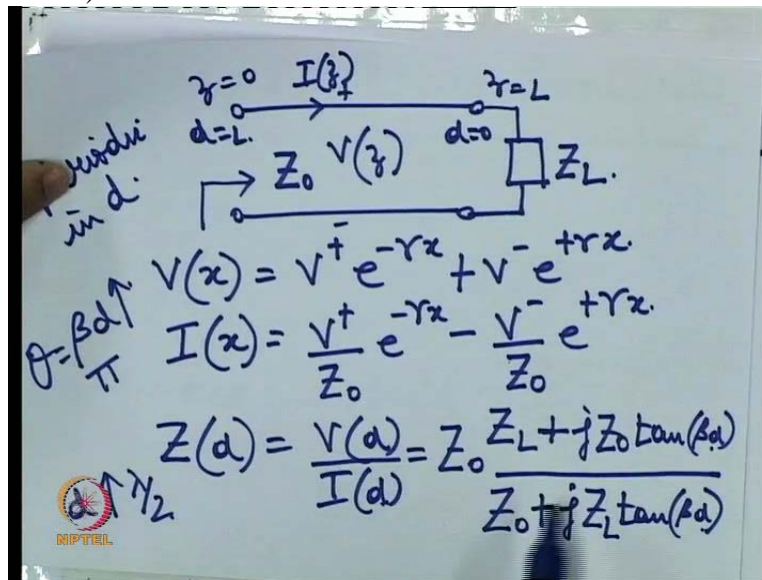


this equation if we substitute in place of  $d$  as  $\lambda/4$  and  $\beta$  as  $2\pi/\lambda$  then we get this particular relationship.

(Refer Slide Time: 11:21)

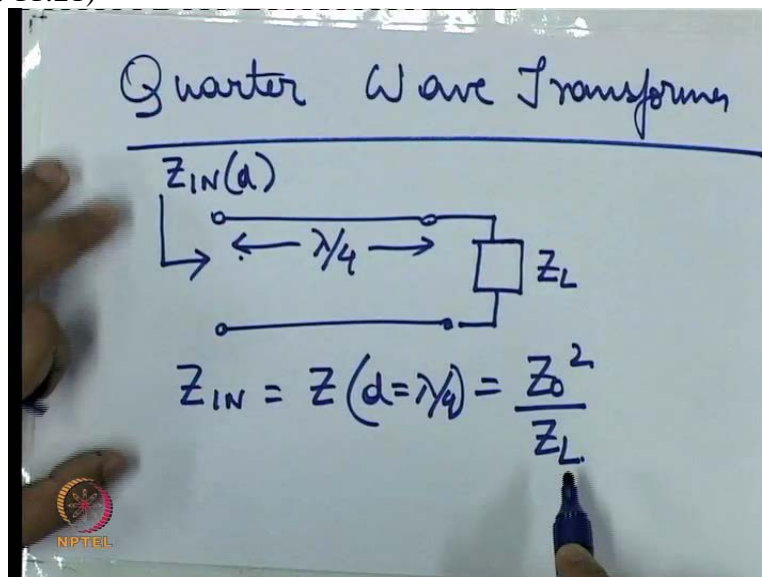


So what we see is that the input impedance is proportional to the inverse of the load impedance. If the load impedance  $Z_L$  is shorted, input impedance will appear to be open. If the load is open, the input will appear to be shorted.

(Refer Slide Time: 11:46)

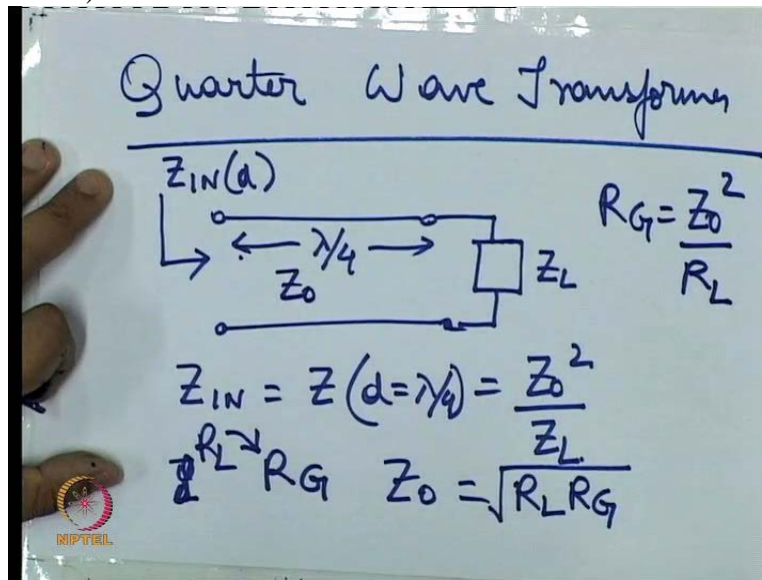

Conversely, if you want to convert any impedance say you want to convert resistance  $R_G$  sorry resistance  $R_L$  connected at the load to some value  $R_G$  then you choose a transmission line which a characteristic impedance square root of  $R_L R_G$  and using this, you will get  $R_G$  is equal to  $Z_0$  square upon  $R_L$ . So we see, by connecting our  $R_L$  this is converted to  $R_G$  when we have this transmission line with a  $Z_0$  given by this value. This is one of the that is why it is called a Transformer. A transfer from one value of load impedance to another value of source impedance. Now coming to yet another important concept that is frequently associate it with transmission lines that is called as the reflection coefficient.

(Refer Slide Time: 12:43)

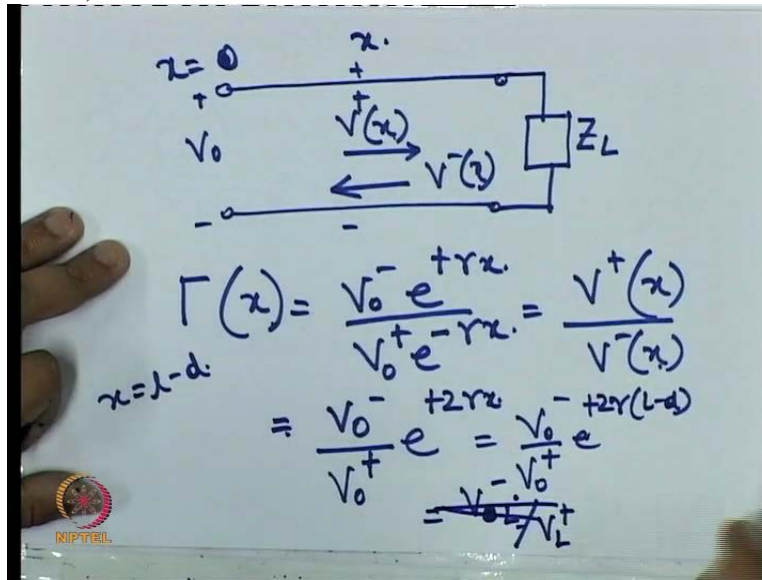


So once again if we have our transmission line with a load  $Z_L$  connected like this and suppose the voltage as I said there are 2 concepts, one is  $V^+$  and  $V^-$  then the reflection coefficient at a particular length  $x$  is given by  $V^-$  or  $E^+$  gamma into upon  $(V^+ - \text{gamma } x)$ .

Now this actually, the reflection coefficient is given as simply  $V^+x$  upon  $V^-x$ . We know we can write  $V^+x$  in terms of the voltage at the source,  $V_0$  like this. So from here we get this is nothing but  $V_0^-$  the reflected wave at the source upon  $V_0^+ e^{+2\gamma x}$ . If we do a coordinate transformation where we write  $X$  is equal to  $L-d$  then this becomes so then now if you take out this  $E$  raise to  $+2\gamma L$  then this  $V_0^-$  upon  $V_0^+$  is converted to  $V_L^-$  upon  $V_L^+$ . Let me write it on a different sheet.




(Refer Slide Time: 14:52)

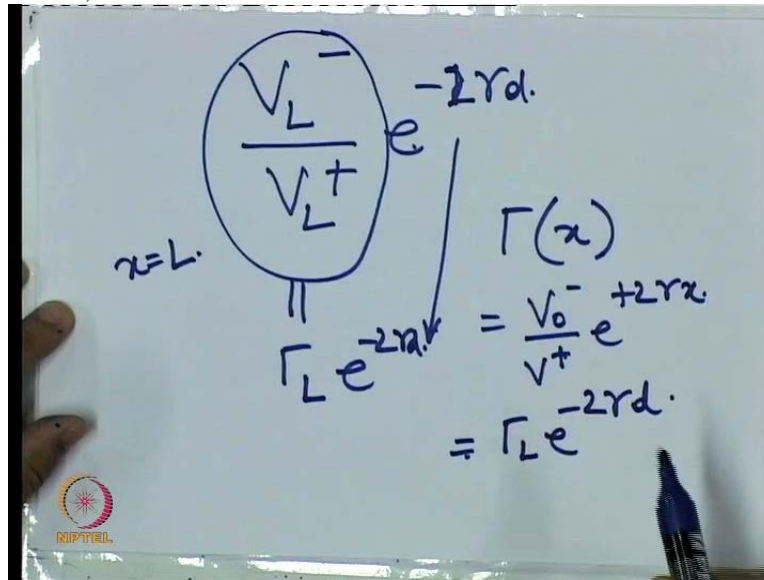

This is converted to  $V_L^- / V_L^+ e^{-2\gamma d}$ . This is nothing but the ratio of the reflected wave to the incident wave at the load end. That is at  $x$  equal to  $L$  and this is nothing but the reflection coefficient at the load end and this is simply  $\Gamma_L$ .  $\Gamma$  at a particular point  $x$  in terms of the source voltages, reflected and incident voltages is given by this and in terms of the load parameters, it is given by this. So we have both key, you can express  $\Gamma$  at any point in terms of both the source parameters as well as the load parameters.

(Refer Slide Time: 16:13)

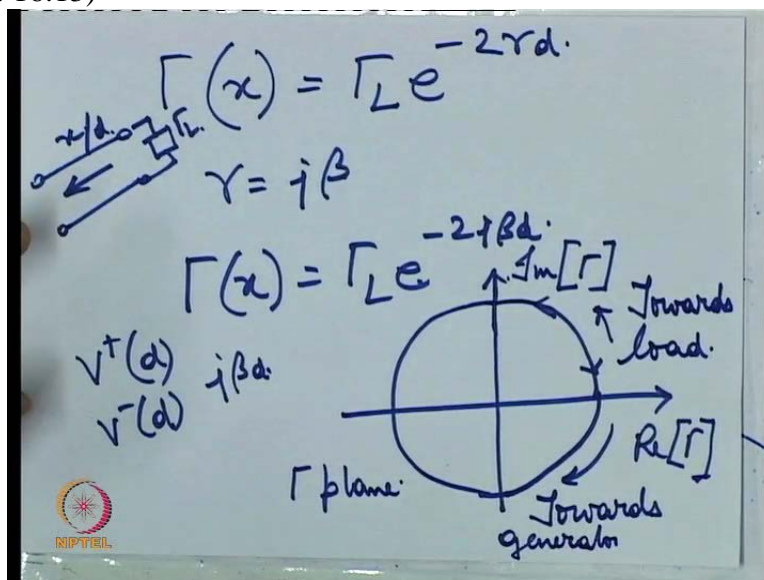

Now one interesting thing that we observed if I write the gamma X value now assuming this is a non-dispersive media gamma is equal to jbeta then we can write gamma X is equal to gamma L raised to -2jbeta d. Now what we see is that we had our transmission line at a particular point X or d. So d is away from the load. This is our gamma L and this is we are going away from the load. Now as we go away from the load, the phase of V+d or V-d changes by jbeta d only. Plus or minus jbeta d. But the phase of this reflection coefficient changes twice. So if we can draw this, as d increases or we are going away from the load, our phase angle keeps on decreasing and phase angle decreasing means we are moving in a clockwise direction.

The other thing that we note is that the magnitude of the reflection coefficient as we go away from the load remains constant and if we are going towards the load, then we move in an anticlockwise direction. If we are moving in a clockwise direction if we are moving towards the load, if we are going away from the load, we are moving in a clockwise direction. If we are moving towards the load, we are going in an anticlockwise direction. And the phase transit is twice the phase transit of as of that what we encountered while going along the transmission line. So this is one important concept associated with transmission lines. The reflection coefficient is changes twice faced change for the voltage for the incident and reflected waves.

(Refer Slide Time: 19:31)

$$P_L = \frac{|V^+|^2}{Z_0} - \frac{|V^-|^2}{Z_0}$$

incident power.      reflected power.  
||  $P^+$

$$P_L = P^+ - P^- = P^+ (1 - |\Gamma_L|^2)$$

$$\Gamma_L = 0$$

Now we had already come across this formula for the total real power that is delivered to the load and that was discussed in the previous module like this. Where say, V+ and V- are the

voltages are the incident and reflected voltages at the load. Now, if we represent this incident power so this I can call incident power and this I can call the reflected power.

If I call denote it by the term  $P_+$  then  $P_L$  can be written as  $P_+ - P_-$  which in turn can be written as  $P_+$  if I take this  $V_+$  square upon  $Z_0$  common  $1 - \Gamma_L$  whole square. Because  $V_-$  upon  $V_+$  is nothing but  $\Gamma_L$ . And so, we see that for total power transmission that if we want the entire incident power to go to the load  $\Gamma_L$  should be equal to 0. Because for any other values of this  $\Gamma_L$  some component of power will be reflected back and only when  $\Gamma_L$  is equal to 0 we have complete transmission of the incident power to the load.

No see one thing about this  $\Gamma_L$  is that this is a constant quantity.  $\Gamma_L$  does not change. It only depends on the load. Whereas the other components are not fixed. For example, what is the input reflection coefficient or what is the reflection coefficient at any other point along the transmission line,  $\Gamma_L$  is a quantity that depends purely on the load property. So can we then derive a formula of  $\Gamma_L$  in terms of the load impedance?

(Refer Slide Time: 21:57)

$$\begin{aligned}
 Z(z) &= \frac{V(z)}{I(z)} \\
 &= \frac{V^+ e^{-\gamma z} + V^- e^{+\gamma z}}{\frac{V^+}{Z_0} e^{-\gamma z} - \frac{V^-}{Z_0} e^{+\gamma z}}
 \end{aligned}$$

The impedance at any point Z or X's whatever. We can take X also in place of Z is given  $Z$  of small is equal to  $V$  of Z upon  $I$  of Z. If I write the voltage and current relationship at Z, that is...now this can be simplified to this relationship.

(Refer Slide Time: 22:51)

$$Z(z) = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$
$$Z(z=L) = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L}$$
$$Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L}$$
$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

So then the impedance or the input impedance at  $Z$  equal to  $L$  is nothing but  $Z_0$  upon  $1 + \text{gamma}$   $L$  upon  $1 - \text{gamma}$   $L$ . So then  $Z_L$  is nothing but  $Z_0$  upon  $1 + \text{gamma}$   $L$  upon  $1 - \text{gamma}$   $L$ . From here, we can write if we want to find  $\text{gamma}$   $L$  in terms of  $Z_L$  that will come out to... So this is the value of load reflection coefficient.

(Refer Slide Time: 24:17)

$$Z(z) = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$
$$Z(z=L) = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L}$$
$$Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L}$$
$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \Rightarrow Z_L = Z_0$$


*impedance matching*

Now for total power transmission, we saw that  $\text{gamma}$   $L$  should be 0 which also implies  $Z_L$  should be equal to  $Z_0$ . And such a condition where the entire incident power is transmitted to the

load is called matching, impedance matching. So impedance matching is that condition where the entire incident power is transmitted to the load and that happens when my load impedance is equal to the characteristic impedance. Now this concept of load impedance this reflection coefficient, we saw the relationship that relates the  $\Gamma_L$  and  $Z_L$ . The relationship is nothing but a bilinear transformation from one coordinate to another.

So once again if I write the question for  $\Gamma_L$ ...

(Refer Slide Time: 25:07)

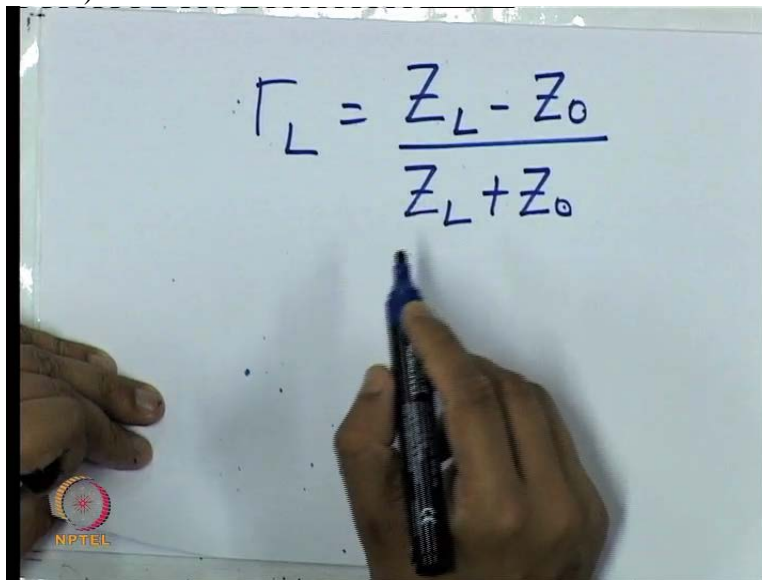

The image shows a whiteboard with the following equation written in blue marker:


$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

A hand is visible on the left side of the whiteboard, and another hand is holding a blue marker on the right side, pointing towards the equation. In the bottom left corner of the whiteboard, there is a small logo for NPTEL.

This is a bilinear transformation of  $Z$ . A special chart which does this transformation for all impedances is what is known as a Smith chart.


(Refer Slide Time: 25:36)

Smith Chart

$$\Gamma = \frac{Z - Z_0}{Z + Z_0} = \frac{\gamma - 1}{\gamma + 1}$$
$$\gamma = \frac{Z}{Z_0} = r + jx.$$


So if we want to draw 1<sup>st</sup> of all the definition of Smith chart is like this or this can also be written as this small Z where this small Z is equal to the normalised what you call as normalised impedance. This is in terms of the normalised resistance and reactance. Small Z can be written like this.

(Refer Slide Time: 26:36)

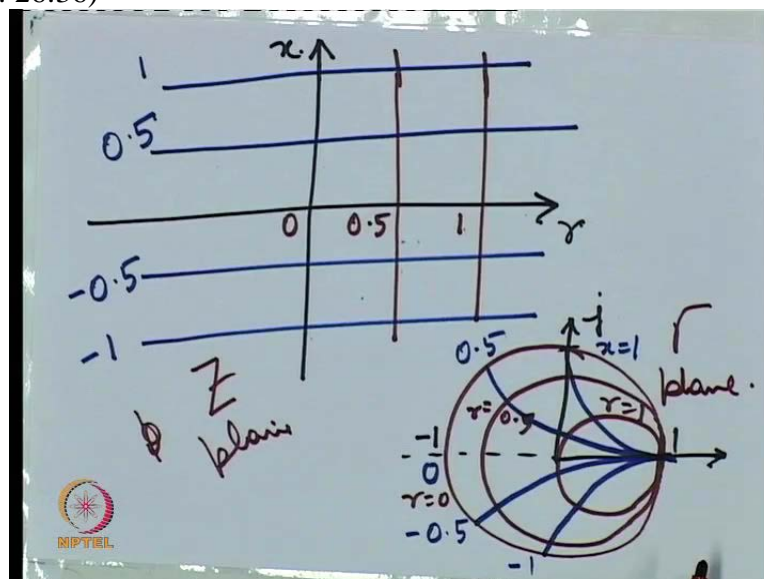


Now, if we plot this transformation, this particular transformation for various values of Z, the curve that we get is something like this. Now this line as you can see, this red and blue line is what is called as a constant resistance and constant a constant reactance line and upon doing this

bilinear transformation, they are transformed to these circles. So is the  $R$  equal to 0 line, this is the  $R$  equal to 0.5 line. Sorry, this is  $X$  equal to 0 line, this is  $X$  equal to +0.5 line, this is  $X$  equal to -0.5 line: this is  $X$  equal to -1 line, this is  $X$  equal to 1 line. These lines are like the  $R$  equal to one line,  $R$  equal to 0.5 line. And this is the  $R$  equal to 0 line. This is the way conversion is done.


Now 1<sup>st</sup> thing we have to know is why do we do this conversion? We do this conversion because the entire right half of the  $Z$  plane this is our  $Z$  plane and this is our gamma plane. The entire right half of our  $Z$  plane is now confined within this entire circle. The circle has a radius 1. This helps us to visualise all passive devices because for all passive devices,  $R$  is greater than 0 and that is a convenient way of expressing it.

(Refer Slide Time: 30:10)

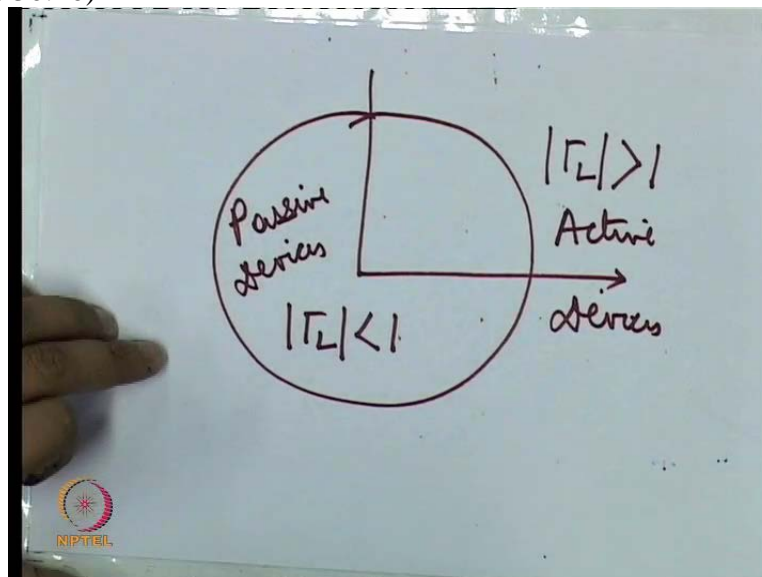


So we can write this as suppose this is a unit circle, the circle has been unit radius and within the circle, we have gamma L modulus lesser than 1 and outside the circle, we have gamma L modulus greater than 1. So this corresponds to all active devices and this corresponds to all passive devices. In the same way that we obtained the curve from  $Z$  value, we should also be able to get the curve, Smith chart from the  $Y$  values and such a Smith chart is called as  $Y$  Smith chart.

(Refer Slide Time: 30:52)

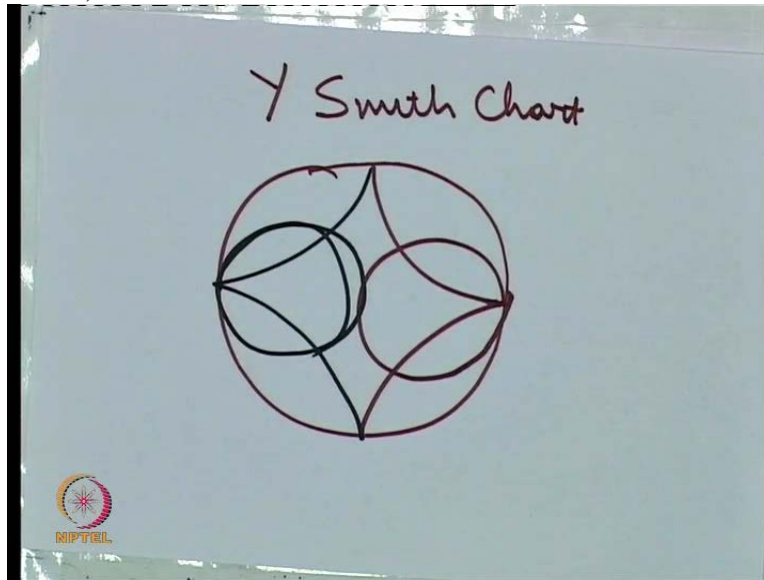

Now suppose this is our Z Smith chart, then the Y Smith chart will be  $180^\circ$  oriented from the Z Smith chart and like this. This will join.

(Refer Slide Time: 31:32)

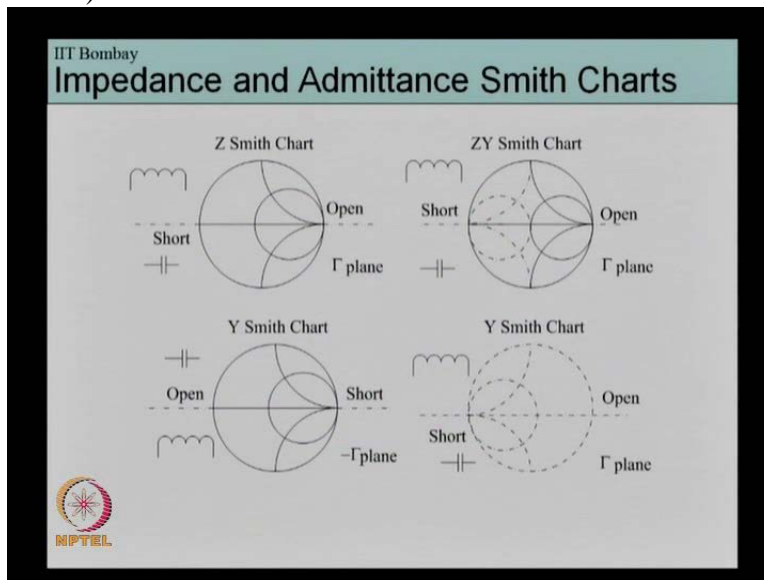

So if we can go back to the slides the monitor for a moment, these are the various configurations of the impedance and admittance Smith charts. Say this is our impedance Smith chart, then the top half we will have inductive i.e for the top half, the reactance X will be positive and for the bottom half, reactance X will be negative.



For the Y Smith chart, it is just the opposite. Top half is capacitive, bottom half is inductive. For the Z Smith chart, the right-hand side is open. Open means infinite impedance. And the left hand side is short or 0 impedance. Now, a combination of the 2 means Z-Y Smith chart as we were discussing as shown here. And a point that is plotted for the Z Smith chart, will have the same sense for the Y Smith chart. That particular point on this Z-Y Smith chart will have the same sense for the Y Smith chart. Now one final concept that I want to introduce is what is called as the voltage standing wave ratio.

(Refer Slide Time: 32:44)

IIT Bombay  
**Voltage Standing Wave Ratio (VSWR)**

The voltage wave inside a transmission line can be written using

$$\Gamma = \frac{V^-}{V^+}$$

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z} = V^+ e^{-j\beta z} (1 + \Gamma e^{j2\beta z})$$

The voltage varies between

$$|V|_{\max} = |V^+| (1 + |\Gamma|)$$

$$|V|_{\min} = |V^+| (1 - |\Gamma|)$$

The voltage standing wave ratio (VSWR) is defined as:

$$\text{VSWR} = \frac{|V|_{\max}}{|V|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

NPTEL

Maybe we can go to the slides on the monitor itself. So we saw that the voltage at any point in a transmission line is given by this relationship which in turn is also related to the reflection coefficient. The maximum voltage at any point and the minimum voltage at any point, maximum means the maximum that can be achieved over time, minimum also means minimum that can be achieved over time is given by this ratio and by this relationship the ratio of these 2 values is what you called as the voltage standing wave ratio.

Now, VSWR was a very important concept in the olden days when we could not directly measure the reflection coefficient. It is something that can be directly measured with a meter because it is the ratio of the maximum to the minimum voltages. So, usually for good microwave matching, we require VSWR of less than 2. VSWR less than 2 is considered a good matching or as we saw from the concept of impedance matching that when most of the incident power is

transmitted to the load. So in terms of reflection coefficient, that translates is to  $\Gamma_L$  equal to 0. In terms of VSWR that translates to VSWR lesser than 2.

So in this course, in this module, we covered some of the more standard parameters associated with microwave circuits. In the next module we shall be further covering the more advanced concepts. Thank you