

Design of Power Electronic Converters
Professor Shabari Nath
Department of Electronics and Electrical Engineering
Indian Institute of Technology, Guwahati
Module Snubber Design
Lecture – 37

RCD Snubbers - II

Welcome to the course on Design of Power Electronic Converters. We had been discussing the module snubber design and we had seen the snubber designs for RC snubbers, then we started with the analysis of RCD snubbers. And in that we saw that we can divide it into three types, one is normal snubber, large snubber and small snubber. We had derived equations for normal snubber in last lecture. Now, this lecture we will be continuing for the analysis for large snubber and small snubber.

(Refer Slide Time: 01:04)

Switch voltage and current

Switch current

$$i_{sw} = I_L \left(1 - \frac{t}{t_s} \right) \quad (1)$$


Capacitor current

$$i_c = I_L - i_{sw} \quad (2)$$

Voltage across switch

$$\begin{aligned}
 e &= \frac{1}{C_s} \int_0^t i_c dt = \frac{1}{C_s} \int_0^t (I_L - i_{sw}) dt \\
 &= \frac{1}{C_s} \int_0^t \left(I_L - I_L \left(1 - \frac{t}{t_s} \right) \right) dt = \frac{I_L}{C_s} \int_0^t \frac{t}{t_s} dt \\
 &= \frac{I_L t^2}{2C_s t_s} \quad (3)
 \end{aligned}$$

The slide also includes a circuit diagram of an RCD snubber connected in parallel with a switch. The circuit consists of a DC source ϵ , a diode, a switch, an inductor L , a resistor R_s , and a capacitor C_s . The capacitor C_s is connected in parallel with the resistor R_s and the switch. The inductor L is in series with the switch. The diode is connected in parallel with the switch and the snubber network.

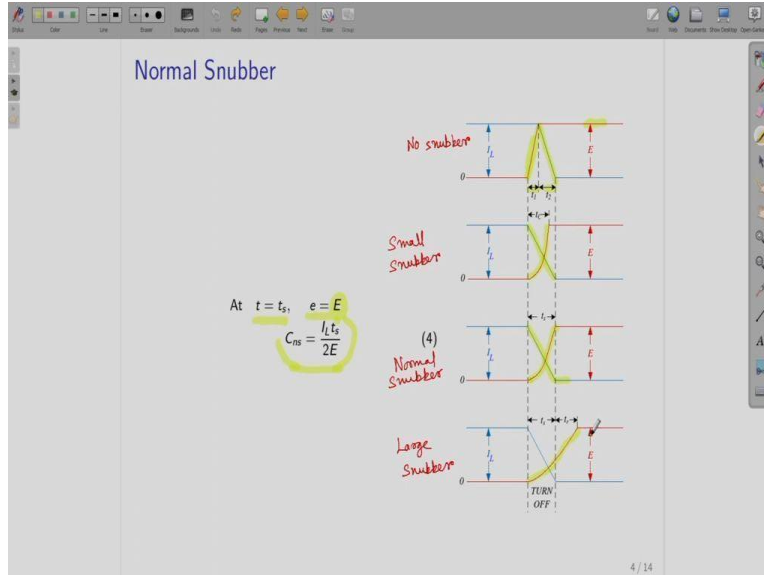

So, to do the analysis, so we first wrote down these simple equations for currents and voltages. For this device, voltage e which is basically the voltage across this capacitor C_s , and then we had also written expression for this switch current. Then, we divided it into three parts, small snubber, normal snubber, and large snubber. And for normal snubber case, we had noted down that this snubber can be the capacitance can be calculated as this

$$C_{ns} = \frac{I_L t_s}{2E}$$

where I_L is the load current, t_s is the turn off time, and E is the blocking voltage.

(Refer Slide Time: 01:46)

Large Snubber $C_s > C_{ns}$

At $t = t_s$:


$$e = E_s = \frac{I_L t_s}{2C_s} = E \frac{C_{ns}}{C_s} \quad (5)$$

For $t > t_s$, switch current is zero and all the current flows through capacitor.

$$\therefore \frac{de}{dt} = \frac{I_L}{C_s}$$

Time t_r to complete commutation can be obtained as shown:
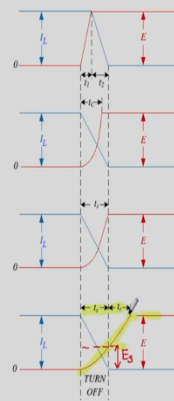
$$\begin{aligned} C_s \frac{de}{dt} &= C_s \frac{E - E_s}{t_r} \\ \Rightarrow t_r &= \frac{E - E_s}{de/dt} = \frac{\frac{I_L t_s}{2C_s} - \frac{I_L t_s}{2C_s}}{I_L / C_s} \\ &= \left(\frac{C_s}{C_{ns}} - 1 \right) \frac{t_s}{2} \quad (6) \end{aligned}$$



Switch voltage and current

Switch current

$$i_{sw} = I_L \left(1 - \frac{t}{t_s}\right) \quad (1)$$

Capacitor current

$$i_c = I_L - i_{sw} \quad (2)$$

Voltage across switch

$$e = \frac{1}{C_s} \int_0^t i_c dt = \frac{1}{C_s} \int_0^t (I_L - i_{sw}) dt$$

$$= \frac{1}{C_s} \int_0^t \left(I_L - I_L \left(1 - \frac{t}{t_s}\right) \right) dt = \frac{I_L}{C_s} \int_0^t \frac{t}{t_s} dt$$

$$= \frac{I_L t^2}{2C_s t_s} \quad (3)$$

Now, let us do further and do the analysis for large snubber. Large snubber means this case where your capacitor voltage builds up slowly that means it is large enough, and it reaches to this blocking voltage at a time later than this turn off time t_s . And let us say it reaches later by that time by an additional time of t_r .

So, at the time t_s , let us say that this voltage is equal to E_s . So, now when you want to write equations using the previous equation, so you can write this E_s at time t_s

$$e = E_s = \frac{I_L t_s}{2C_s}$$

$$= E \frac{C_{ns}}{C_s} \quad (5)$$

C_{ns} is the normal snubber capacitance.

And for this time interval which is t greater than t_s , what will happen is that the switch current has become 0 in that case. So, what we are telling is that after the time period t is this current your i_{sw} , this is gone from your I_L to the value 0. So, your this switch current is 0 now, and so all this current is going to flow through the capacitor C_s .

So, in that case your de by dt the rate of change of the voltage will be equal to

$$\frac{de}{dt} = \frac{I_L}{C_s}$$

And the time t_r to complete this commutation process can be obtained as

$$C_s \frac{de}{dt} = C_s \frac{E - E_s}{t_r}$$

Now t_r is equal to,

$$C_s \frac{de}{dt} = C_s \frac{E - E_s}{t_r}$$

and you substitute for ease, you substitute for E_s using the previously derived equations. And then when you reduce it,

$$\Rightarrow t_r = \frac{E - E_s}{de/dt} = \frac{\frac{I_L t_s}{2C_{ns}} - \frac{I_L t_s}{2C_s}}{I_L / C_s}$$

$$t_r = \left(\frac{C_s}{C_{ns}} - 1 \right) \frac{t_s}{2}$$

(6)

this is what you are going to get. And C_s by C_{ns} minus 1 into t_s by 2 is the the extra time it needs to complete the commutation.

(Refer Slide Time: 04:38)

Cont..

Total commutation time:

$$t_c = t_s + t_r = t_s + \left(\frac{C_s}{C_{ns}} - 1\right) \frac{t_s}{2} = \left(\frac{C_s}{C_{ns}} + 1\right) \frac{t_s}{2} \quad (7)$$

Turn OFF switching loss during $0 < t < t_s$

power

$$p = ei_{sw} = \frac{I_L^2}{2C_s t_s} I_L \left(1 - \frac{t}{t_s}\right) = \frac{I_L^2}{2C_s} \left(1 - \frac{t}{t_s}\right) \frac{t^2}{t_s} \quad (8)$$

To obtain peak power,

$$\begin{aligned} \frac{dp}{dt} &= \frac{I_L^2}{2C_s} \left(\frac{-1}{t_s}\right) \frac{t^2}{t_s} + \frac{I_L^2}{2C_s} \left(1 - \frac{t}{t_s}\right) \frac{2t}{t_s} = 0 \\ &\Rightarrow \frac{I_L^2}{2C_s} \left[\frac{-t^2}{t_s^2} + 2\frac{t}{t_s} - 2\frac{t^2}{t_s^2}\right] = 0 \\ &\Rightarrow \frac{2t}{t_s} - \frac{3t^2}{t_s^2} = \frac{t}{t_s} \left(2 - 3\frac{t}{t_s}\right) = 0 \\ &\Rightarrow \frac{t}{t_s} = \frac{2}{3} \quad (9) \end{aligned}$$

6 / 14

So, the total commutation time will be

$$t_c = t_s + t_r = t_s + \left(\frac{C_s}{C_{ns}} - 1\right) \frac{t_s}{2} = \left(\frac{C_s}{C_{ns}} + 1\right) \frac{t_s}{2} \quad (7)$$

Now, the switching power loss you can say that during this time period 0 to t_s .

So, this is your p equal

$$p = ei_{sw} = \frac{I_L^2}{2C_s t_s} I_L \left(1 - \frac{t}{t_s}\right) = \frac{I_L^2}{2C_s} \left(1 - \frac{t}{t_s}\right) \frac{t^2}{t_s} \quad (8)$$

And now we want to obtain the peak power. So, if you want to obtain the peak power that means you have to differentiate it, you have to obtain the maxima, and you differentiate and equate it to 0. So, we do that exercise and we obtain,

$$\begin{aligned} \frac{dp}{dt} &= \frac{I_L^2}{2C_s} \left(\frac{-1}{t_s}\right) \frac{t^2}{t_s} + \frac{I_L^2}{2C_s} \left(1 - \frac{t}{t_s}\right) \frac{2t}{t_s} = 0 \\ &\Rightarrow \frac{t}{t_s} = \frac{2}{3} \quad (9) \end{aligned}$$

So, at this time t by t s equal to $2/3$ is your this power, this switching power is going to become maximum. Now, you whether it is a maxima or minima, you can check it for yourself, do the double differentiation and then you can check it.

(Refer Slide Time: 06:22)

Cont..

Peak power P_m at $\frac{t}{t_s} = \frac{2}{3}$ is

$$P_m = \frac{I_L^2}{2C_s} \left(1 - \frac{2}{3}\right) \frac{4}{9} t_s = \frac{2 I_L^2 t_s}{27 C_s}$$

$$= \frac{2}{27} \frac{2C_{ns} E I_L}{C_s} = \frac{4 C_{ns} E I_L}{27 C_s} \quad \because C_{ns} = \frac{I_L t_s}{2E} \quad (10)$$

Switch turn OFF energy loss

$$W_p = \int_0^{t_s} p dt = \frac{I_L^2}{2C_s} \int_0^{t_s} \left(1 - \frac{t}{t_s}\right) \frac{t^2}{t_s} dt$$

$$= \frac{I_L^2}{2C_s} \int_0^{t_s} \left(\frac{t^2}{t_s} - \frac{t^3}{t_s^2}\right) dt = \frac{I_L^2}{2C_s} \left(\frac{t^3}{3t_s} - \frac{t^4}{4t_s^2}\right) \Big|_0^{t_s}$$

$$= \frac{I_L^2}{2C_s} \left[\frac{t_s^2}{3} - \frac{t_s^2}{4}\right] = \frac{I_L^2 t_s^2}{24C_s} \quad (11)$$

$$= \frac{2C_{ns} E I_L t_s}{24C_s} = \frac{E I_L t_s C_{ns}}{12 C_s} \quad (12)$$

7 / 14

Further, if you substitute this t by t_s equal to 2 by 3 in the power expression. So, if you do it and then reduce it, so, this is what you will be getting

$$P_m = \frac{2}{27} \frac{I_L^2 t_s}{2E}$$

Now, we want to reduce everything in terms of that normal snubber capacitance value. So, you substitute for these I_L square t_s from the previously derived equation for C_{ns} , and then when you reduce it, this is what you will be getting

$$P_m = \frac{4}{27} \frac{C_{ns}}{C_s} E I_L$$

(10)

So, now if we want to turn off energy loss in the switch that means in only in the device. So, then that will be integration of this power from this time 0 to t_s , during the turn off time 0 to t_s .

So, you write down the expression for p that we just derived and then you integrate it, and you solve it. So, and further when you reduce this is what you will be getting

$$W = \int_0^{t_s} p dt = \frac{I_L^2 t_s^2}{24C_s} \quad (11)$$

Again, we do not like this term, so, we want to give get everything in terms of this normal capacitance C_{ns} . So, you do those adjustments and substitutions. This is what you will be getting

$$W = \frac{EI_{L_s} t_s}{12} \frac{C_{ns}}{C_s}$$

(12)

this is the device loss that is taking place during the time t_s .

(Refer Slide Time: 08:04)

Cont..

Snubber energy loss

$$W_S = \frac{C_s E^2}{2} = \frac{C_s E}{2} \frac{l_s t_s}{2 C_{ns}} \quad \therefore E = \frac{l_s t_s}{2 C_{ns}}$$


$$= \frac{E l_s t_s C_s}{4 C_{ns}} \quad (13)$$

Total energy loss

$$W_T = W + W_S = \frac{E l_s t_s C_{ns}}{12 C_s} + \frac{E l_s t_s C_s}{4 C_{ns}}$$

$$= \frac{E l_s t_s}{2} \left(\frac{1}{6} \frac{C_{ns}}{C_s} + \frac{1}{2} \frac{C_s}{C_{ns}} \right) \quad (14)$$

$\frac{C_s}{C_{ns}} = \alpha$ $W_T(\alpha) = K \left(\frac{1}{6\alpha} + \frac{\alpha}{2} \right)$
 $k = \frac{E l_s t_s}{2}$



8 / 14

Cont..

Snubber energy loss

$$W_S = \frac{C_s E^2}{2} = \frac{C_s E}{2} \frac{l_s t_s}{2 C_{ns}} \quad \therefore E = \frac{l_s t_s}{2 C_{ns}}$$


$$= \frac{E l_s t_s C_s}{4 C_{ns}} \quad (13)$$

Total energy loss

$$W_T = W + W_S = \frac{E l_s t_s C_{ns}}{12 C_s} + \frac{E l_s t_s C_s}{4 C_{ns}}$$

$$= \frac{E l_s t_s}{2} \left(\frac{1}{6} \frac{C_{ns}}{C_s} + \frac{1}{2} \frac{C_s}{C_{ns}} \right) \quad (14)$$

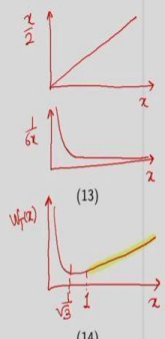$\frac{C_s}{C_{ns}} = \alpha > 1$ $W_T(\alpha) = K \left(\frac{1}{6\alpha} + \frac{\alpha}{2} \right)$
 $k = \frac{E l_s t_s}{2}$
 $\frac{1}{6\alpha} = \frac{\alpha}{2}$
 $\alpha^2 = \frac{1}{3}$
 $\alpha = \frac{1}{\sqrt{3}} < 1$



8 / 14

Now, we obtain the device loss. Now, what about this snubber loss? In this snubber loss, there is some loss going to take place. Now, what do we mean by snubber loss here? So, this is your device and then this is the RC and with that this diode is connected. So, whatever is the energy that gets stored in this capacitor that same energy is going to get dissipated in the resistor R_s later on. So, whatever is the stored energy that is actually a loss. So, we just can obtain this snubber energy loss as half of C_s into E square, so you substitute for E as equal to $IL T_s$ by $2 C_{ns}$.

And then what you obtain is this expression

$$W_s = \frac{EI_L t_s C_s}{4 C_{ns}} \quad (13)$$

Now, the total energy loss will be the sum of the device loss means your switch loss plus this snubber loss. So, you write down the two expressions that we just obtained. And we can write that in this term

$$W_T = W + W_s = \frac{EI_L t_s C_{ns}}{12 C_s} + \frac{EI_L t_s C_s}{4 C_{ns}}$$

$$W_T = \frac{EI_L t_s}{4} \left(\frac{1 C_s}{6 C_{ns}} + \frac{1 C_s}{2 C_{ns}} \right)$$

Now, this let us say that your this is C_s by C_{ns} , let us say with this is equal to x . So, this then this W_T can be written as a function of x ,

$$\frac{C_s}{C_{ns}} = x, \quad K = \frac{EI_L t_s}{2}, \quad W_T(x) = K \left(\frac{1}{6x} + \frac{x}{2} \right)$$

Now, let us see what would be the nature of the graph of this equation.

So, if you plot the first one, that is x by 2 , so x by 2 graph will be something like this with respect to x . And the nature of the graph of a 1 by $6x$ with respect to x will be something like this. And so, if we have to then plot this W_T x total loss with respect to x , then this nature of the graph will be that initially it will be dominated.

The graph will be dominated for lower values of x by this 1 by $6x$. And then later on as x increases, this is what is going to dominate the W_T x value, this x by 2 curve, so accordingly, you expect the nature of the graph to be something like this. And then what point is the minimum going to occur? That is going to occur basically, if you want you can differentiate and equate to 0 and also find out.

You can see that when these two are actually equal, so when

$$\frac{1}{6x} = \frac{x}{2}, \quad x^2 = \frac{1}{3}$$

so x will be equal to

$$x = \frac{1}{\sqrt{3}} < 1$$

Now, this x is something less than 1, so, that means this minima occurs at $1/\sqrt{3}$. And here what we are interested in, since this is a large number, we our values of x which for which we are doing the analysis is x is greater than 1.

So, for x greater than 1, what happens is what you see is that this is just an increasing function. So, even if you search for a minima, you are not going to get a minima for x greater than 1, it is continuously increasing function. So, that is why we are not going to search for this large number of minimum value for your WT.

(Refer Slide Time: 12:37)

Small Snubber $C_s < C_{ns}$

At $t = t_c$

$$e = E = \frac{I_L t_c^2}{2C_s t_s} \quad (15)$$

$$\Rightarrow t_c = \sqrt{\frac{2C_s E t_s}{I_L}} \quad (16)$$

$$= \sqrt{\frac{C_s}{C_{ns}} t_s^2} = \sqrt{\frac{C_s}{C_{ns}}} t_s \quad \therefore C_{ns} = \frac{I_L t_s}{2E} \quad (16)$$

Turn OFF switch power during $0 < t < t_c$

$$p = e i_{sw} = \frac{I_L t^2}{2C_s t_s} I_L \left(1 - \frac{t}{t_s}\right) = \frac{I_L^2}{2C_s} \left(1 - \frac{t}{t_s}\right) \frac{t^2}{t_s} \quad (17)$$

Turn OFF switch power during $t_c < t < t_s$

$$p = e i_{sw} = E I_L \left(1 - \frac{t}{t_s}\right) \quad (18)$$

Now, let us do the analysis for small snubber. So, small snubber means your C_s , the snubber capacitance is less than your normal snubber capacitance. So, this is the graph that we are going to take up, then that it gets charged the capacitor gets charged before this turn off period is over. So, before the current reaches to 0, before that the voltage has already built up to the blocking voltage.

So, let us say that happens at the time which we call it as the t_c time time for your voltage to build up. So, that is there at that time this is the equation that you will be obtaining

$$e = E = \frac{I_L t_c^2}{2C_s t_s}$$

So, from here if you want to write down the expression for t_c , t_c could be written as

$$t_c = \sqrt{\frac{2C_s E t_s}{I_L}} \quad (15)$$

Now, we want to get rid of some of the terms here in terms of C_{ns} , normal snubber capacitance.

$$t_c = \sqrt{\frac{C_s}{C_{ns}}} t_s \quad (16)$$

So, the turn off switch power during the interval 0 to t_c that will be

$$p = ei_{sw} = \frac{I_L t_c^2}{2C_s t_s} I_L \left(1 - \frac{t}{t_s}\right) = \frac{I_L}{2C_s t_s} \left(1 - \frac{t}{t_s}\right) \frac{t^2}{t_s}$$

(17)

multiplication of E into i_{sw} . So, write down the expression for E, write down expression for i_{sw} , and from there this is what we get. And this is the same as that we had expression that we had obtained for your large snubber, for this time interval 0 to t_c .

Then, for your Turn OFF switch power during this time interval t_c to t_s , so we are now further when we go down to this interval, so here this is between t_c to t_s . What we see is that the current is reducing and it is becoming 0, while the voltage is a capital E. So, then you can write down the equation.

$$p = ei_{sw} = EI_L \left(1 - \frac{t}{t_s}\right)$$

(18)

that is what will be the expression for power.

(Refer Slide Time: 14:56)

Cont..

If $\frac{t_c}{t_s} > \frac{2}{3}$, peak power P_m is given by (10).

$$P_m = \frac{4}{27} \frac{C_{ns}}{C_s} E I_L$$

Else

$$P_m = E I_L \left(1 - \frac{t_c}{t_s}\right)$$

$$= E I_L \left(1 - \sqrt{\frac{C_s}{C_{ns}}}\right) \quad (19)$$

Note,

For normal snubber, $C_{ns} = \frac{I_L t_s}{2E} \Rightarrow E = \frac{I_L t_s}{2C_{ns}}$

For small snubber, $E = \frac{I_L t_c^2}{2C_s t_s}$

$$\therefore \frac{C_s}{C_{ns}} = \left(\frac{t_c}{t_s}\right)^2 \quad (20)$$

Small Snubber $C_s < C_{ns}$

At $t = t_c$

$$e = E = \frac{I_L t_c^2}{2C_s t_s}$$

$$\Rightarrow t_c = \sqrt{\frac{2C_s E t_s}{I_L}} \quad (15)$$

$$= \sqrt{\frac{C_s}{C_{ns}}} t_s = \sqrt{\frac{C_s}{C_{ns}}} \frac{I_L t_s}{2E} \quad \therefore C_{ns} = \frac{I_L t_s}{2E} \quad (16)$$

Turn OFF switch power during $0 < t < t_c$

$$p = e i_{sw} = \frac{I_L t^2}{2C_s t_s} I_L \left(1 - \frac{t}{t_s}\right) = \frac{I_L^2}{2C_s} \left(1 - \frac{t}{t_s}\right) \frac{t^2}{t_s} \quad (17)$$

Turn OFF switch power during $t_c < t < t_s$

$$p = e i_{sw} = E I_L \left(1 - \frac{t}{t_s}\right) \quad (18)$$

So, if we want to obtain the peak power P_m , then if t_c by t_s is greater than 2 by 3, so it will be the same expression that we have obtained for your large snubber case. Because, what we found there for large snubber case that the peak occurs at t by t_s equal to 2 by 3, and here we have the same expression is the large snubber. So, if t_c by t_s is greater than 2 by 3. So, if this expression has its peak at a before that, so the peak power expression will be the same as the large snubber. So, that is what it will be part of this is not so. If let us say this is less than 2 by 3, then this peak will occur at time t_c .

Now, why is it going to occur at time t_c ? Because this is your voltage E which is building up at time your t_c . And this is the current to which falls down like this and that happens for this time

period t_s . So, from here to here, your this voltage is fixed, now the current is reducing. So, your multiplication will be maximum over at this t_c point only, beyond that the current value decreases, so the p value is also going to decrease. So, P_m will be equal to

$$P_m = EI_L \left(1 - \frac{t_c}{t_s} \right)$$

So, you can substitute for t_c by t_s in terms of C_s by C_{ns} . And how do we get it? You can note down this that C_{ns} is equal to this, we have previously derived. And for small snubber this also we have previously written. You equate these two terms, this is what you will be getting C_s by C_{ns} equal to t_c by t_s whole square (see the screenshot). So, from there you can write down this

$$P_m = EI_L \left(1 - \sqrt{\frac{C_s}{C_{ns}}} \right) \quad (19)$$

(Refer Slide Time: 17:11)

Cont..

Switch turn OFF energy loss from $t = 0$ to $t = t_c$

$$W_1 = \int_0^{t_c} p dt = \frac{I_L^2}{2C_s} \int_0^{t_c} \left(1 - \frac{t}{t_s} \right) \frac{t^2}{t_s} dt$$

$$= \frac{I_L^2}{2C_s} \int_0^{t_c} \left(\frac{t^2}{t_s} - \frac{t^3}{t_s^2} \right) dt = \frac{I_L^2}{2C_s} \left(\frac{t^3}{3t_s} - \frac{t^4}{4t_s^2} \right) \Big|_0^{t_c}$$

$$= \frac{I_L^2}{2C_s} \left[\frac{t_c^3}{3t_s} - \frac{t_c^4}{4t_s^2} \right] = \frac{I_L^2}{2C_s} t_c^2 \left[\frac{t_c}{3t_s} - \frac{t_c^2}{4t_s^2} \right]$$

$$= El t_s \left[\frac{t_c}{3t_s} - \frac{t_c^2}{4t_s^2} \right] \quad \because \text{At } t_c, E = \frac{I_L t_c^2}{2C_s t_s} \quad (21)$$

Switch turn OFF energy loss from $t = t_c$ to $t = t_s$

$$W_2 = \int_{t_c}^{t_s} p dt = El \int_{t_c}^{t_s} \left(1 - \frac{t}{t_s} \right) dt$$

$$= \frac{El t_s}{2} \left[1 - \frac{t_c}{t_s} \left(2 - \frac{t_c}{t_s} \right) \right] \quad (22)$$

11 / 14

So, now if we want to find out the energy loss, you integrate that power expression from time 0 to t_c . This is for the switch turn OFF energy loss. Because, this time period your capacitor voltage is building up, so, the equation is different, then, from the time period t_c to t_s . So, we have to find out the switch loss in two parts. So, first part from 0 to t_c interval, you just simply

write down the power expression, and then you have to basically integrate and solve it, so, this is what finally you are going to get.

$$W_1 = EI_L t_s \left[\frac{t_c}{3t_s} - \frac{t_c^2}{4t_s^2} \right]$$

(21)

And switch turn OFF energy loss from t_c to t_s , so the equation is different there. So, you then you have to solve that equation, you integrate it. And if you solve it this is what you will be getting.

$$W_2 = \frac{EI_L t_s}{2} \left[1 - \frac{t_c}{t_s} \left(2 - \frac{t_c}{t_s} \right) \right]$$

(22)

So, we obtain the switch loss in two parts for the time interval 0 to t_c , and t_c to t_s , so, to total switch loss will be the sum of these two.

(Refer Slide Time: 18:26)

Cont..

Total switch turn OFF energy loss from $t = 0$ to $t = t_s$

$$W = W_1 + W_2 = EI_L t_s \left[\frac{t_c}{3t_s} - \frac{t_c^2}{4t_s^2} \right] + \frac{EI_L t_s}{2} \left[1 - \frac{t_c}{t_s} \left(2 - \frac{t_c}{t_s} \right) \right]$$

$$= \frac{EI_L t_s}{2} \left[1 - \frac{4}{3} \frac{t_c}{t_s} + \frac{1}{2} \left(\frac{t_c}{t_s} \right)^2 \right] \quad (23)$$

$$= \frac{EI_L t_s}{2} \left[1 - \frac{4}{3} \sqrt{\frac{C_s}{C_{ns}}} + \frac{1}{2} \frac{C_s}{C_{ns}} \right] \quad \text{using (20)} \quad (24)$$

Total energy loss

$$W_T = W + W_S = \frac{EI_L t_s}{2} \left[1 - \frac{4}{3} \sqrt{\frac{C_s}{C_{ns}}} + \frac{1}{2} \frac{C_s}{C_{ns}} \right] + \frac{EI_L t_s}{4} \frac{C_s}{C_{ns}}$$

$$= \frac{EI_L t_s}{2} \left[1 - \frac{4}{3} \sqrt{\frac{C_s}{C_{ns}}} + \frac{C_s}{C_{ns}} \right] \quad (25)$$

12 / 14

So, W equal two W_1 plus W_2 , you add these two expressions, and you solve it. So, this is what you will be getting

$$W = W_1 + W_2 = EI_L t_s \left[\frac{t_c}{3t_s} - \frac{t_c^2}{4t_s^2} \right] + \frac{EI_L t_s}{2} \left[1 - \frac{t_c}{t_s} \left(2 - \frac{t_c}{t_s} \right) \right]$$

$$W = \frac{EI_L t_s}{2} \left[1 - \frac{4}{3} \frac{t_c}{t_s} + \frac{1}{2} \left(\frac{t_c}{t_s} \right)^2 \right]$$

(25)

$$W = \frac{EI_L t_s}{2} \left[1 - \frac{4}{3} \sqrt{\frac{C_s}{C_{ns}}} + \frac{1}{2} \frac{C_s}{C_{ns}} \right]$$

(24)

Now, total energy loss will be switch loss plus snubber loss, snubber loss expression remains the same as before that what we saw in large snubber case. So, you write down both of them and you reduce it, this is what you will be getting

$$W_T = W + W_S = \frac{EI_L t_s}{2} \left[1 - \frac{4}{3} \sqrt{\frac{C_s}{C_{ns}}} + \frac{C_s}{C_{ns}} \right]$$

(25)

So, now let us see the summary of this analysis what we obtained. But before that, let us look into the minima for this total energy loss.

(Refer Slide Time: 19:39)

Cont..

To obtain minimum total energy loss

$$\frac{dW_T}{d\left(\frac{C_s}{C_{ns}}\right)} = \frac{EI_L t_s}{2} \left[-\frac{4}{3} \left(\frac{C_s}{C_{ns}}\right)^{-\frac{5}{2}} + 1 \right] = 0$$

$$\Rightarrow \frac{C_s}{C_{ns}} = \frac{4}{9} < 1 \quad (26)$$

Minimum total energy loss

$$W_{T \min} = \frac{5 EI_L t_s}{9 \cdot 2} \quad (27)$$

$$= W + W_s \quad (28)$$

$$= \frac{1}{3} \frac{EI_L t_s}{2} + \frac{2}{9} \frac{EI_L t_s}{2}$$

No snubber
 $\frac{EI_L t_s}{2}$

13 / 14

So, you differentiate this total energy loss with respect to C_s by C_{ns} . And when you differentiate that and you equate it to 0, after solving this is what you will be getting.

$$\frac{C_s}{C_{ns}} = \frac{4}{9}$$

(26)

Now, this is less than 1 and this is small snubber case analysis is also for these values to be less than 1, so, this is valid. So, minimum total energy loss will take place for this value(4/9) of snubber.

So, minimum total energy loss, then if you substitute for this C_s by C_{ns} in this expression(25). Then, what you will be obtaining that this minimum total energy loss is

$$W_{T \min} = \frac{5 EI_L t_s}{9 \cdot 2} \quad (27)$$

$$= W + W_s$$

$$= \frac{1}{3} \frac{EI_L t_s}{2} + \frac{2}{9} \frac{EI_L t_s}{2}$$

which is equal to W plus W_s , means your device loss plus snubber loss. And you can substitute this $\frac{4}{9}$ in the expressions that you obtain for device losses as well as for snubber losses.

So, what you will be seeing is that one third of this is the device loss, and $\frac{2}{9}$ of that is the rest of it is the snubber loss. Now, if you recall with the case of no snubber, we had obtained the power loss expression. So, for no snubber case what it was? It was equal to EIL t_s by 2. So, what we observe here is that that your device losses have decreased from the case of no snubber. So, by adding snubber, we affected the turn off trajectories, means how the voltage builds up and that affects the device losses. And if we design this snubber properly, it will so happen that although there are some snubber losses, the total loss will be lesser than the case when there was no snubber. So, you reduce the stress on the device.

(Refer Slide Time: 21:57)

Summary of Analysis			
$\frac{C_s}{C_{ns}}$	>1	<1	$\frac{4}{9}$
Switch turn OFF loss	$\frac{E I_L t_s C_{ns}}{12 C_s}$	$\frac{E I_L t_s}{2} \left[1 - \frac{4}{3} \sqrt{\frac{C_s}{C_{ns}}} + \frac{1}{2} \frac{C_s}{C_{ns}} \right]$	$\frac{1 E I_L t_s}{3 \cdot 2}$
Snubber loss	$\frac{E I_L t_s C_s}{4 C_{ns}}$	$\frac{E I_L t_s C_s}{4 C_{ns}}$	$\frac{2 E I_L t_s}{9 \cdot 2}$
Total loss	$\frac{E I_L t_s}{2} \left(\frac{1 C_{ns}}{6 C_s} + \frac{1 C_s}{2 C_{ns}} \right)$	$\frac{E I_L t_s}{2} \left[1 - \frac{4}{3} \sqrt{\frac{C_s}{C_{ns}}} + \frac{C_s}{C_{ns}} \right]$	$\frac{5 E I_L t_s}{9 \cdot 2}$
Peak power	$\frac{4 C_{ns}}{27 C_s} E I_L$	$\frac{4 C_{ns}}{27 C_s} E I_L$ or $E I_L \left(1 - \sqrt{\frac{C_s}{C_{ns}}} \right)$	

Switching Loss when No Snubber

$$W_T = \int_0^{t_s} e^{i_{sw}} dt = \int_0^{t_1} I_L E \frac{t}{t_1} dt + \int_{t_1}^{t_s} E I_L \left(1 - \frac{t-t_1}{t_s-t_1} \right) dt$$

$$= E I_L \left[\frac{t^2}{2 t_1} \Big|_0^{t_1} + \left(t - \frac{t^2}{2(t_s-t_1)} + \frac{t_1 t}{t_s-t_1} \right) \Big|_{t_1}^{t_s} \right]$$

$$\stackrel{\bullet}{=} \frac{E I_L t_s}{2}$$

This is the summary of the analysis that we performed. So, the important equations that we obtain was is your the switch turn OFF loss, and this is for large snubber case this

$$\frac{E I_L t_s C_{ns}}{12 C_s}$$

is what we obtained for small snubber case,

$$\frac{E I_L t_s}{2} \left[1 - \frac{4}{3} \sqrt{\frac{C_s}{C_{ns}}} + \frac{1}{2} \frac{C_s}{C_{ns}} \right]$$

this is the expression. And then this is

$$\frac{1}{3} \frac{EI_{L's} t_s}{2}$$

what we obtained for the minimum loss where the total loss is minimum at for that your when your C_s by C_{ns} is equal to 4 by 9. So, for that case, we obtained this expressions(see the table in screenshot).

Further, your snubber loss that actually remains the same in these two cases,

$$\text{For } > 1, \frac{EI_{L's} t_s}{4} \frac{C_s}{C_{ns}} \quad \text{for } < 1, \frac{EI_{L's} t_s}{4} \frac{C_s}{C_{ns}}$$

it is not affected by your large snubber or small snubber. I mean the expression is not affected by that, of course your values are going to get affected. And if you substitute for that C_s by C_{ns} , this is what you will be obtaining

$$\frac{2}{9} \frac{EI_{L's} t_s}{2}$$

And the sum of these two, the total loss expression. So, total loss in terms of the snubber values, this

$$\frac{EI_{L's} t_s}{2} \left(\frac{1}{6} \frac{C_{ns}}{C_s} + \frac{1}{2} \frac{C_s}{C_{ns}} \right)$$

is what you obtain for large snubber. And this one

$$\frac{EI_{L's} t_s}{2} \left[1 - \frac{4}{3} \sqrt{\frac{C_s}{C_{ns}}} + \frac{C_s}{C_{ns}} \right]$$

is for the small snubber number, and then this is where you have the minimum total loss, this

$$\frac{5}{9} \frac{EI_{L's} t_s}{2}$$

is the expression that you obtain. And then the peak power expressions that also we had obtained for large snubber, this

$$\frac{4}{27} \frac{C_{ns}}{C_s} EI_L$$

is the expression. For small snubber, we saw that if your the commutation time is actually greater than 2 by 3 of the turn OFF time. Then this

$$\frac{4}{27} \frac{C_{ns}}{C_s} EI_L$$


is the same as the large snubber, else it is given by this.

$$\frac{4}{27} \frac{C_{ns}}{C_s} EI_L \text{ or } EI_L \left(1 - \sqrt{\frac{C_s}{C_{ns}}} \right)$$

So, these are the important expressions that we had obtained. Now, if we look into it, what we observe is that that the way these derivations are done, all the expressions are in terms of this snubber size, snubber size with respect to your normal snubber. So, C_s by C_{ns} is the ratio in which all the expressions are obtained. And there are other terms which are your EI_L ts by 2, this is also a factor. You can call it as like as a multiplication factor, which is also present in almost all the cases. So, now, if we see, previously we had obtained this switching loss when no snubber is present, that is in terms of this EI_L ts by 2.

So, if we normalize this expression with respect to the case when there is no snubber. So, your EI_L ts by 2 will disappear, so, it will be a normalized loss expressions that you will be obtaining. And so, those will be just in terms of some ratios, and then the whole thing can be like a generalized expression, which you can use it for any design of your converter, irrespective of your values of EI_L ts. So, that is what then is done. And these are then plotted as normalized with respect to the case when there is no snubber.

(Refer Slide Time: 25:30)

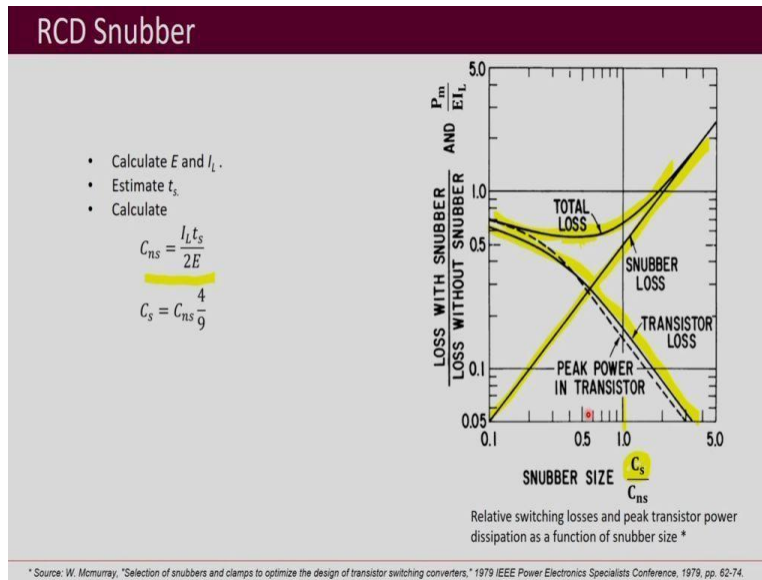

Summary of Analysis

$\frac{C_s}{C_{ns}}$	>1	<1	$\frac{4}{9}$
Switch turn OFF loss	$\frac{E I_L t_s C_{ns}}{12 C_s}$	$\frac{E I_L t_s}{2} \left[1 - \frac{4}{3} \sqrt{\frac{C_s}{C_{ns}} + \frac{1}{2} \frac{C_s}{C_{ns}}} \right]$	$\frac{1 E I_L t_s}{3 \cdot 2}$
Snubber loss	$\frac{E I_L t_s C_s}{4 C_{ns}}$	$\frac{E I_L t_s C_s}{4 C_{ns}}$	$\frac{2 E I_L t_s}{9 \cdot 2}$
Total loss	$\frac{E I_L t_s}{2} \left(\frac{1}{6} \frac{C_{ns}}{C_s} + \frac{1}{2} \frac{C_s}{C_{ns}} \right)$	$\frac{E I_L t_s}{2} \left[1 - \frac{4}{3} \sqrt{\frac{C_s}{C_{ns}} + \frac{C_s}{C_{ns}}} \right]$	$\frac{5 E I_L t_s}{9 \cdot 2}$
Peak power	$\frac{4}{27} \frac{C_{ns}}{C_s} E I_L$	$\frac{4}{27} \frac{C_{ns}}{C_s} E I_L$ or $E I_L \left(1 - \sqrt{\frac{C_s}{C_{ns}}} \right)$	

So, this with respect to this snubber size that means this ratio C_s by C_{ns} , and the plot of loss of width snubber by loss without snubber. So, basically it is a normalized thing, you get rid of that $E I_L t_s$ by 2 term. And also, this power is also plotted, your peak power expression and that is divided by $E I_L$. Because you can see here if you want to normalize this peak power, you have to divide it by $E I_L$, because that is the term which actually is specific to the converter. And this ratio is not specific to any converter when we are doing this analysis. So, then if you, when you plot it, this one is the snubber loss plot.

You can see it is continuously increasing with your snubber size see C_s by C_{ns} . Then this one is your transistor loss, so, that is decreasing with the size of the snubber. And this is in the total loss, the snubber loss plus the device loss. So, what we see is that this minimum occurs before one and somewhere around here it is occurring, so, that is your 4 by 9 what we had obtained is the total loss where it becomes minimum. So, and around this value actually the minima, you can see that it is relatively insensitive, it is not varying too much. So, around this value you can actually play around, you adjust the values a little bit, it does not change the total loss much.

And one more thing that you observe here is that that as you increase this C_s value, as you keep on increasing your device loss, your transistor loss is decreasing. So, you are reducing the device's stress, your device losses are increasing. But, the cost then you pay is that you use to store energy is increasing and that is what will become the snubber loss, so that is going to increase. So that is what you can observe here. And so, we would like to reduce device stress, we would like to minimize the losses, and then that becomes the optimum snubber design your RCDs snubbers. So, those values of your C_s is what we are supposed to choose.


So, how can we do the snubber design? So, you calculate your E and IL for your converter, which we are designing, this something you will be knowing when you design the converter and you estimate your t_s that is your turn OFF time. Now, this is something you have to estimate, turn OFF time is not fixed. We did the assumption that in all these cases, your large snubber, small snubber, normal snubber t_s is fixed. It is not getting affected by the choice of this snubber value, but in reality, it does get affected. It gets affected by many things. It gets affected by what kinds of parasitics are present in your converter, how good your layout is, your device, so many things, your turn OFF time and turn on time they get affected.

So, you try to have an estimate of your t_s , which is definitely you can estimate, you can start with the datasheet values also, you can do some preliminary experiments to observe the t_s value. So, estimate your t_s and then you have this expression for obtaining the normal snubber capacitance IL t_s by $2E$. And then from there you can start for your starting design, you can choose this number value C_s as C_{ns} 4 by 9. That is what you can choose the value of capacitance to start your design with. And then further as I said, you can fine tune with the experimental results. And how do you choose your R_s value?

So, this whole of C_s energy that gets dissipated in R_s , you can use that expression also to obtain your value for R_s . And one more thing that you can observe here this peak power P_m , this normalized peak power P_m with respect to EIL is also plotted here, and this is that dotted line that that is shown here. Now, this is also something you should pay attention to, because when we do the snubber design, we would like to keep the device within the SOA limits. So, you can observe that with respect to your snubber size, what is the peak power that is expected, and if it is well within the SOA the safe operating area or not?

And if it is not, then you can adjust the snubber value, so that it goes within your SOA limits. So, you may not always design it for the minimum total loss as you might have to modify it also. And finally, the values as I said gets adjusted and modified based on your experimental results, what waveforms do you observe. So, this is the way you can do your RCD snubber design.

(Refer Slide Time: 31:16)

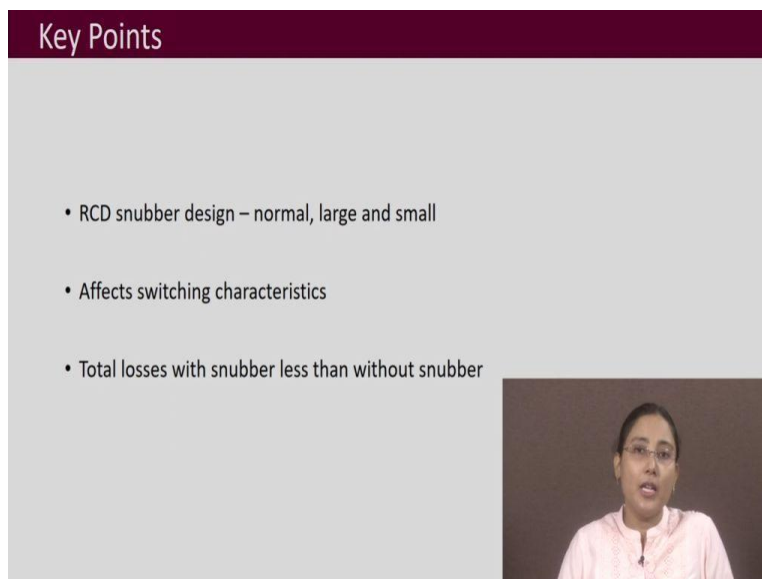

The slide is titled "Key Points" in a dark red header. It contains three bullet points on a light gray background. In the bottom right corner, there is a small video inset showing a woman with glasses and a pink shirt speaking.

- RCD snubber design – normal, large and small
- Affects switching characteristics
- Total losses with snubber less than without snubber

So, the key points of this lecture are that your RCD snubber design analysis is done by dividing into three parts: normal snubber, small snubber, and large snubber. And what we saw is that choice of snubber affects your switching characteristics, and we can reduce the device stress by properly choosing the values of these snubbers. And we can also try to keep it within the SOA limits by proper choice of your snubber design.

And also, what we observed is that that your device losses are getting affected in, and it can be lesser than what it is when there is no snubber. So, your total loss of your converter basically the

switching loss need not increase, because you are adding a snubber resistance. It may reduce also if you have chosen proper values of snubbers. Thank you.