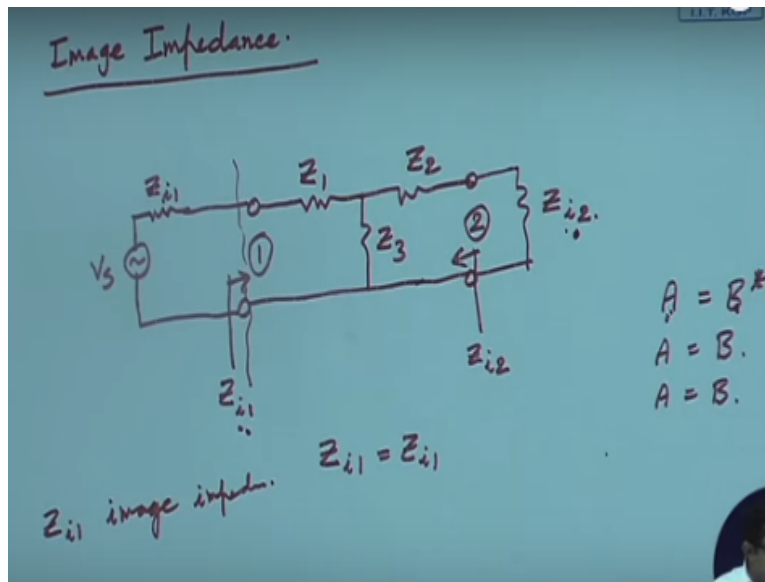


**Design Principles of RF and Microwave Filters and Amplifiers**  
**Prof. Amitabha Bhattacharya**  
**Department of Electronics and EC Engineering**  
**Indian Institute of Technology - Kharagpur**

**Module No # 01**  
**Lecture No # 02**  
**Concept of Image Impedance and propagation constant**

Welcome to this second lecture on concept of image impedance. Now, I hope you agree with me that any 2 port network can always be represented by either a T section or a PIE section without losing a generality I take that my 2 port network that means transmission matrix characterization is ABCD that is a T section the same analysis hold for PIE section. So now I have that T section, this is  $Z_1$ , this is  $Z_2$ , this is  $Z_3$  all this are impedances, complex impedances.

**(Refer Slide Time: 01:04)**



So this is many port 2, this is my port 1, this is the internal description of the network. Now, I want when will I excide the port 1 with that voltage BS and I have some internal impedance let us call that internal impedance  $Z_{i1}$  last time I called it  $Z_S$  this time I am calling it  $Z_{i1}$  is simply change of number this is my port 1 this is my port 2.

Now you see all of you are familiar with maximum power transfer theorem says that if the load impedance complex is a complex conjugate of the source impedance then maximum power gets transferred. I think that you have noticed that in low frequency particularly this VLSI people etc.,

when they work upto gigahertz range they do not give any consideration to these maximum power transfer theorem.

Because in baseband unless you go upto radio frequency and transmit it you have plenty of power so you are more concerned with your voltage maximization that is why you design a good C amplifier with very high voltage gain but voltage gain is not necessarily mean a maximum power gain but we when we go to radio frequency we know power microwave power is very precious to produce microwave power lots of complete complicated circuits are required.

So also when power is received by a receiver in radio frequency it is very small amount so its life and death for RF engineer or RF circuits to maximize power. So maximum power transfer theorem always is the design of RF circuits always we try to pay regard to the maximum power transfer theorem. So can I have this whole thing suppose this I will terminate by some load impedance let the load impedance is called  $Z_{I2}$  this one I called  $Z_{I1}$  source impedance is  $Z_{I2}$ .

Now the idea of image impedance at this point obviously if I look at I will get some impedance. Now if this impedance is equal to  $Z_{I1}$  then I can from the source I can have maximum power transfer ok. Now according to maximum power transfer I suppose these I am looking at some  $Z_{in}$  or something  $Z_{in}$  now  $Z_i$  is complex conjugated  $Z_{I1}$  star then I know that maximum power transfer will takes place.

But as I said that our consideration now is filter which is lossless network so this  $Z_1, Z_2, Z_3$  there is no R involved ideally. So they are complex, but they are generally they will be either real or not real either all of them will be pure imaginary term there will be pure reactance. So in that case I say that now I say that I will look into here  $Z_{I1}$  then  $Z_{I1}$  is equal to  $Z_{I1}$  suppose any complex conjugate for pure imaginary things it is equal.

As you know that suppose I have to complex two number A is equal to B star suppose a is a complex number B is a complex number if A is pure real and B is pure real then I can say A is equal to B. Similarly, if A is pure imaginary and B is pure imaginary then on low I can say A is

equal to  $B$ . Since we know that this will be my all these are pure reactances this may be a pure resistance so that is why I can call that my demand is  $Z_{I1}$  here should be equal to  $Z_{I1}$  here.

That means source impedance and these input impedance looking at this port should be equal but you see this  $Z_{I1}$  is a function of this load resistance  $Z_{I2}$ . But now so why it is called this  $Z_{I1}$  is called image impedance if I can find an impedance load impedance  $Z_{i2}$  so that if I terminate this network this is already given network and I look at here and see that the input impedance is  $Z_{I1}$  then I know that I can transfer maximum power from the source to this network this to this port one of this network.

now why  $Z_{I1}$  is called an image impedance because if at this plane I look so I looking at this side I am getting to the right side and getting and  $Z_{I1}$  looking at left side I am seeing the impedance  $Z_{I1}$ . So this side is image of these that is why this is an image impedance it so  $Z_{I1}$  is an image impedance. Same thing here and here I want that if I look at here I should look at some output impedance that should be equal to  $Z_{i2}$ .

So at port 2 if I look to this side I am getting  $Z_{I2}$  if I look this side I should get  $Z_{I2}$ . So if I can find PR to  $Z_{I1}$   $Z_{I2}$  so if I terminate by  $Z_{I2}$  then I get here  $Z_{I1}$  impedance similarly here if I terminate by  $Z_{I1}$  and excite here I should see here is  $Z_{I2}$  these two pairs are called image impedance. Since this is an a symmetrical network because  $Z_{I1}$  is not equal to  $Z_{I2}$  I will have two impedance  $Z_{I1}$  and  $Z_{I2}$ . Let us see that whether this image impedance can be represented in terms of this impedance of this network.

**(Refer Slide Time: 08:50)**

$Z_{in}$

$$Z_{i1} = \sqrt{\frac{(Z_1 + Z_3)(Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1)}{Z_2 + Z_3}}$$

$$Z_{i2} = \sqrt{\frac{(Z_2 + Z_3)(Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1)}{Z_1 + Z_3}}$$

..

$$\left\{ \begin{array}{l} Z_{i1} = Z_1 + (Z_3 \parallel (Z_2 + Z_{i2})) \\ Z_{i2} = Z_2 + (Z_3 \parallel (Z_1 + Z_{i1})) \end{array} \right.$$

So the same diagram I can write that  $Z_{i1}$  or do like this so this  $Z_{i1}$  I can write as what is  $Z_{i1}$  obviously it is  $Z_1$  plus you see  $Z_3$  parallel to  $Z_2$  plus  $Z_{i2}$ . Likewise what is  $Z_{i2}$  it is  $Z_2$  plus  $Z_3$  parallel to  $Z_1$  plus  $Z_{i1}$ . Now these two equations you see  $Z_{i1}$  here I have  $Z_{i2}$  I have  $Z_{i2}$  here. I have  $Z_{i1}$  I have two equations so I can solve for  $Z_{i1}$  and  $Z_{i2}$  in terms of  $Z_1, Z_2, Z_3$ .

If I do that upon solving this I get  $Z_{i1}$  is equal to root over  $Z_1 + Z_3$  into  $Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1$  by  $Z_2 + Z_3$  and  $Z_{i2}$  is  $Z_2 + Z_3$  into  $Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1$ . So you see that this image impedance can be represented in terms of the component impedances of the T section. Now always we won't be knowing  $Z_1, Z_2, Z_3$  as I said that let us consider two port network as a black box. But we can do measurements and always find these image impedances.

How, you know that any measurement requires either an open circuit or short circuit of the one of the port. So for any impedance measurement you look to do this also you have seen that if you want to find any 2 port parameter you need some port condition either short or open etc etc., So if we measure measurement of image impedance, let us say that port one we measure impedance when port 2 open.

**(Refer Slide Time: 11:52)**

Measurement of  $Z_{i1}$  &  $Z_{i2}$

port 1 → measure input. when port 2 open:

$$Z_{1OC} = Z_1 + Z_3.$$

port → measure input. when port 2 short:


$$Z_{1SC} = Z_1 + (Z_2 \parallel Z_3) = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2 + Z_3}.$$

$$Z_{i1} = \sqrt{Z_{1OC} \times Z_{1SC}}.$$

We call that measurement as  $Z_1$  since we are doing at port 1 open circuit  $Z_{1OC}$  means I am measuring the impedance input impedance at port 1 with port 2 open. So if we look at the circuit if I open circuit this what will be  $Z_{1OC}$  it will be simply  $Z_1 + Z_3$ . Similarly if we measure impedance with port 2 with sorry again port 1 measure impedance when port 2 is short it now let me short this port. So I call  $Z_{1SC}$  second port is shortened you look at the circuit If I short it, it will be  $Z_1 + Z_2 \parallel Z_3$ .

So  $Z_1 + Z_2 \parallel Z_3$  Ok now what is this, this is  $Z_1 \frac{Z_2 + Z_3}{Z_2 + Z_3} + \frac{Z_2 Z_3}{Z_2 + Z_3}$ . Now you observe the image impedance terms already I have solved  $Z_{i1}$  can I just compare can I say that  $Z_{i1}$  is equal to  $Z_{1OC}$  into  $Z_{1SC}$ . So by measurement I can always find  $Z_{1OC}$  I can find  $Z_{1SC}$ . I know what image impedance is immediately I can calculate from these.

**(Refer Slide Time: 14:50)**

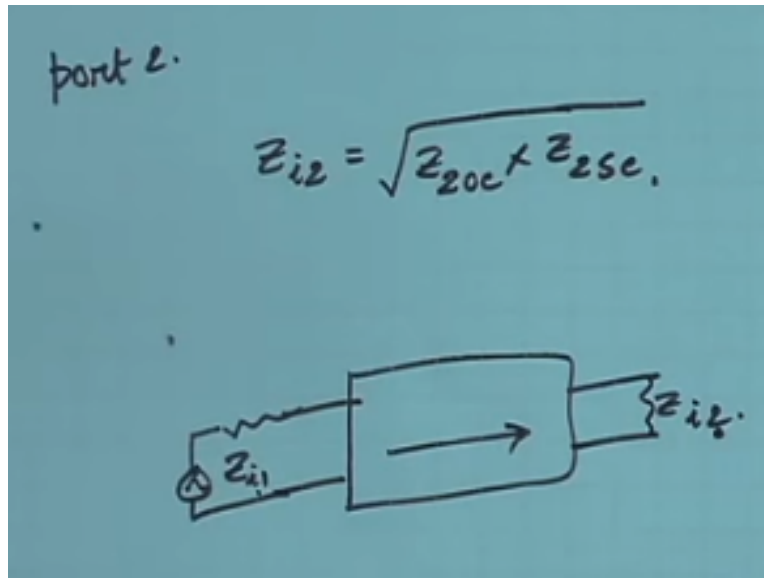

Similarly instead of port 1 if I measure in port 2 by once open circuiting port 1 find the input impedance at port 2 and then again you short the port 1 and measure the input impedance and port 2. So port 2 things if we do you will see the same thing that  $Z_{i2}$  can be expressed as  $Z_{2OC}$  into  $Z_{2SC}$ . So this shows that in image impedances can be always obtained from short or open circuit measurements on any network.


So we can easily do this suppose I am given a network I can always find this  $Z_{1OC}$   $Z_{1SC}$   $Z_{2OC}$   $Z_{2SC}$  and find out this  $Z_{i1}$   $Z_{i2}$  and then I choose a source with that internal impedance that I want and terminate or choose the load as  $Z_{i2}$  I know I can achieve maximum power transfer. Already I said so that means I can have maximum power transfer is guaranteed if I use image impedance as the terminating impedance at both the ports.

Now we know we have said that we will be using the two port network as only lossless components, that means you do not use any hard so their own many internal loss there. So, by terminating with image impedances I assume maximum power transfer no loss in the circuit lossless. So image impedance is an important thing performance measure of the power transport power transmission that is taking place to a network so you see that we can specify something on it later when we will design a filter.

So instead of ABCD we can specify image impedances and that will solve one many of our problems but think one point that I have image impedance here I have image impedance here also you see with this I require to know that ok by this  $Z_{i1}$  and  $Z_{i2}$  terminations  $Z_{i1}$  here and  $Z_{i2}$  here I have to ensure that I am giving maximum power am delivering to this load.

But I am assuming that here there is no loss but the power is flowing in this direction it may so happen since I am using reactive elements power may be locally confined that is not flowing there. So I need to also see how propagation is taking place inside this 2 port network. So we need to have the transmission of power to the network also that we will next see that this is called propagation of power.

**(Refer Slide Time: 18:28)**

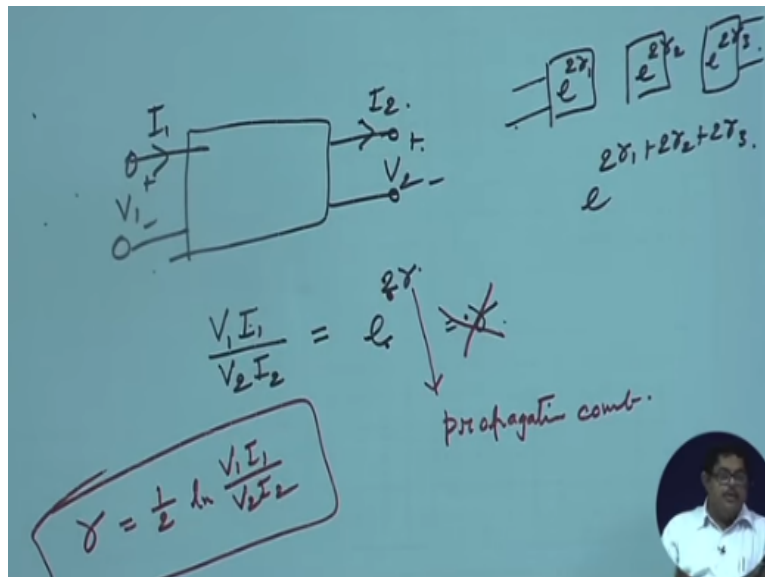

So what we define that again to two network I have this  $V_1$ , I have  $V_2$ , I have  $I_1$ , I have  $I_2$  as before now let me define  $V_1 I_1$  by  $V_2 I_2$  is volt ampere the concept you have learnt in you electrical circuit class. So input volte ampere these are complex quantities input volte ampere and output volt ampere. What is this ratio that will be something now I want to ensure that is fully making the power transmission possible.

So we call this I can name it any number this will be some number you see input by output volt ampere but we have certain advantage if we instead of defining any number here we write it as some exponential factor  $e$  to the power two gamma why because you see when I will cascade

many such networks this one will have some this ratio  $e$  to the power  $2\gamma_1$  this will have  $E$  to the power  $2\gamma_2$  another will have  $E$  to the power  $2\gamma_3$  etc.,

Now from this input to this input if I want to find what is this transmission ratio of all the volt-ampere if I express it exponential factor the final thing will  $E$  to the power  $2\gamma_1 + 2\gamma_2 + 2\gamma_3$  but if I do not use this exponential factor. If I just write it as  $\gamma$  suppose then I will have to work out and I will have to work out and I will have to find out what is the magnitude and phase all these things here.

But exponential factor makes simply be an addition in if it is an absolute value it would have been some multiplication. We always prefer addition to multiplication that is why it initially people did like that they put this as propagation constant. But now with after some learning people understood that if we represent this ratio is it exponential factors and also you see I have taken a factor two here why because many times will be interested to see what is the voltage ratio what is the current ratio.

But this is actually a volt-ampere ratio which is for that it is actually product of voltage and current. So I have taken two  $\gamma$ , this  $\gamma$  is called propagation constant. So what is the definition of propagation constant you see  $\gamma$  is equal to  $\frac{1}{2} \ln \frac{V_1 I_1}{V_2 I_2}$  a very important definition propagation constant you see it shows that how input power is propagating through the network inside the 2 port network.

So my job is now to find out what is this  $e$  to the power  $2\gamma$  ratio is equal to  $\frac{V_1 I_1}{V_2 I_2}$  is equal to in terms of ABCD parameters  $AV_2 + BI_2$  into  $CV_2 + DI_2$  by  $V_2 I_2$  also I know  $V_2$  is equal to  $Z_I I_2$  image impedance it is terminated with image impedance so if you do that finally you can solve that this ratio will turn out to be this simple manipulation put thus and you know the value of  $Z_{i1}$   $Z_{i2}$ . So you will get this will be simply this or  $e$  to the power  $\gamma$  is equal to  $\sqrt{\frac{AD}{BC}}$ .

**(Refer Slide Time: 22:11)**



$$e^{2\gamma} = \frac{V_1 I_1}{V_2 I_2} = \frac{(AV_2 + BI_2)(CV_2 + DI_2)}{V_2 I_2}$$


$$V_2 = Z_{i2} I_2$$

$$= (\sqrt{AD} + \sqrt{BC})^2$$

$$e^{\gamma} = \sqrt{AD} + \sqrt{BC}$$

Now here you see this propagation constant I have expressed in terms of ABCD parameters. One more thing is remaining I have already said about characteristic impedances is characteristic impedances also expressible in terms of ABCD parameters. Let us see I have the same 2 port network I have  $I_1$  here, I have  $V_1$  here, and I want this should be  $Z_{i1}$  and here this should be terminated by  $Z_{i2}$  and this is  $V_2$  this is my  $I_2$ .


(Refer Slide Time: 23:29)

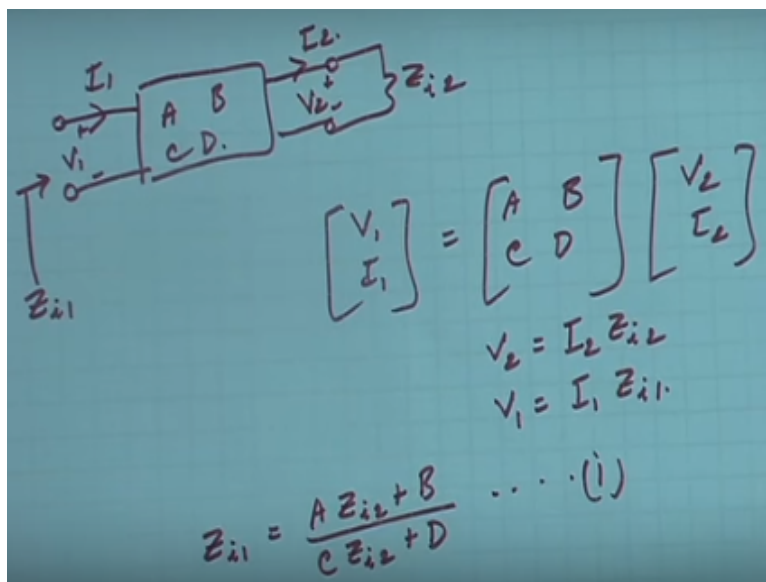

So I can write I know this is ABCD so  $V_1 I_1$  is equal to ABCD the definition of transmission parameters also I have  $V_2$  is equal to  $I_2 Z_{i2}$  and  $V_1$  is equal to  $I_1 Z_{i1}$ . So put these equations and find out what the  $Z_{i1}$  you will see you will get  $AZ_{i2} + B$  by  $CZ_{i2} + D$  let me call this for

timing equation 1. Now reverse the picture that same transmission line this time I am putting the excitation here.

(Refer Slide Time: 24:50)

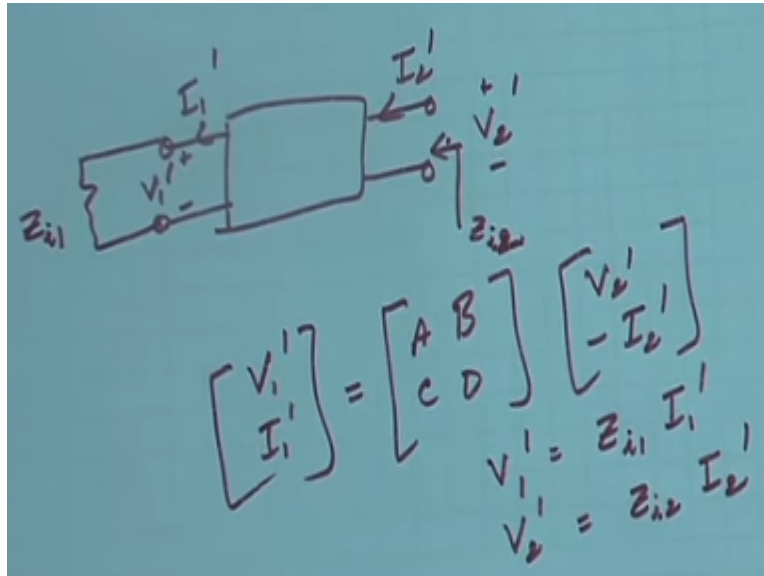

Equations showing the derivation of the input impedance  $Z_{i1}$ :

$$\begin{bmatrix} V_1' \\ I_1' \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix}$$

$$V_1' = Z_{i1} I_1'$$

$$V_2' = Z_{i2} I_2'$$

$$Z_{i1} = \frac{V_1'}{I_1'} = \frac{A Z_{i2} - B}{-C Z_{i2} + D} \dots (ii)$$

So I am looking at it here I will get  $Z_{i2}$  and this is my  $V_2'$  as before this is my  $I_2'$  as before and from here I am taking terminating you to  $Z_{i1}$  this is my  $V_1'$  this is my  $I_1'$  dashed so here again I can write that  $V_1'$   $I_1'$  dashed is equal to  $ABCD$   $V_2'$  dashed minus  $I_2'$  dashed and what about the ports  $V_1'$  dashed is equal to  $Z_{i1}$   $I_1'$  dashed  $V_2'$  dashed is equal to  $Z_{i2}$   $I_2'$  dashed. Then find out that what is your  $Z_{i2}$ .


So or you find what is your  $Z_{I1}$  which is nothing but  $V_1$  dash by  $I_1$  dash that will turn out to be  $AZ_{I2} - B$  by  $-C Z_{I2} + D$ . So this let me call equation 2, you have equation 1, you have equation 2 to solve for  $Z_{I1}$ . If you solve even so from 1 & 2 you can solve for  $Z_{I1}$  and that will be equal to or  $Z_{I1}$  will be equal to  $AB$  by  $CD$  and  $Z_{I2}$  will be equal to root over  $BD$  by  $AC$ .

Now I am happy because I know that  $Z_{I1}$ , one of the image impedance can be expressed in terms of four ABCD parameters  $Z_{I2}$  also I can express in terms of ABCD parameters and I have already seen that propagation constant,  $\gamma$  you see this propagation constant that also I can express in terms of ABCD parameters. ABCD parameters completely characterization 2 port network I say equivalently I can say two image impedance  $Z_{I1}$   $Z_{I2}$  and  $e$  to the and  $\gamma$  these three also characterizes a network.

But what is the beauty if I have  $Z_{I1}$   $Z_{I2}$  I know what is impedance level of the excitations of the network that means what is the source impedance what is the load impedance they are according to the power matching. So that no maximum power sorry they are according to the maximum power will flow and by putting conditions and  $\gamma$  I will be able to say whether these frequency will pass or not. So instead of ABCD parameters this is a better description of a 2 port network if I want to design a filter.

And already I have seen that I can do the measurement of image impedances that time I said in terms of the by opening and shorting the port. I will also have to prove that I can do this for propagation constant also because this is a new thing that time I didn't say these. So that I will do now that measurement of image impedance and propagation constant. So what we will do the same network this is port 2 this is open circuit and I am looking here at let me call this  $Z_{O1}$ .

**(Refer Slide Time: 29:45)**

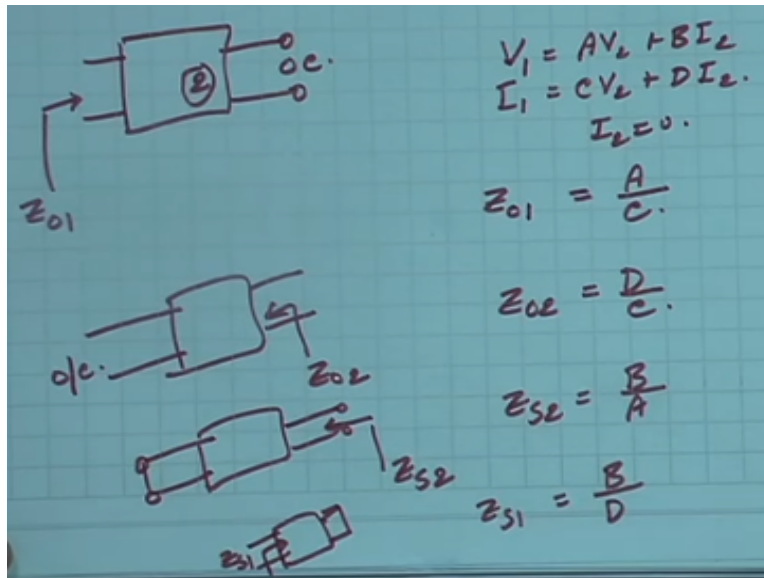

So I know  $V_1$  equal to  $AV_2$  plus  $BI_2$   $I_1$  is equal to  $CV_2$  plus  $DI_2$  etc and open circuit means  $I_2$  is equal to 0. So if you enforce that is  $Z_{01}$  that will be  $A$  by  $C$  then you short circuit so or open circuit this port purpose you open circuit and measure here  $Z_{02}$  so  $Z_{02}$  that will be turn out to be  $D$  by  $C$  then you do that short circuit port one and measure the from this port you measure  $Z_{s2}$ , you will see  $Z_{s2}$  will turn out to be  $B$  by  $A$ .

**(Refer Slide Time: 31:31)**

$Z_{i1} = \sqrt{\frac{AB}{CD}} = \sqrt{Z_{01} Z_{s1}}$

$Z_{i2} = \sqrt{\frac{BD}{AC}} = \sqrt{\frac{D}{C} \frac{B}{A}} = \sqrt{Z_{02} Z_{s2}}$

$\tanh \gamma = \frac{\sinh \gamma}{\cosh \gamma} = \frac{e^{\gamma} - e^{-\gamma}}{e^{\gamma} + e^{-\gamma}} = \sqrt{\frac{BC}{AD}} = \sqrt{\frac{Z_{s1}}{Z_{01}}} = \sqrt{\frac{Z_{s2}}{Z_{02}}}$

$\gamma = \tanh^{-1} \sqrt{\frac{Z_{s2}}{Z_{02}}}$

And which one I missed 2,  $Z_{s1}$  this, so you short circuit this port and measure here  $Z_{s1}$   $Z_{s1}$  will be  $B$  by  $D$ . Once you have that you can immediately write because already we have seen  $Z_{i1}$  is equal to the  $Z_{01}$  into  $Z_{02}$  etc., So you will get that is equal to  $AB$  by  $CD$  and that is nothing but  $Z_{01}$  similar  $Z_{i2}$  is equal to root over  $BD$  by  $AC$  and that is  $D$  by  $C$  into  $B$  by  $A$  that is nothing

but  $Z_{O2}$   $Z_{S2}$ . And you see what is  $\tan \gamma$ ,  $\tan \text{hyperbolic } \gamma$  all of you are familiar with hyperbolic functions.

So this is  $E$  to the power  $\gamma$  minus  $E$  to the power minus  $\gamma$  by  $E$  to the power  $\gamma$  plus and that is nothing but  $BC$  by  $AD$  that is  $Z_{S1}$  by  $Z_{O1}$  and or  $Z_{S2}$  by  $Z_{O2}$ . So you see that  $\gamma$  can be expressed completely in terms of short circuit and open circuit measurement. So I can measure image impedance by open circuit, short circuit measurements. I can also measure  $\gamma$  by open circuit short circuit measurements.

Previously I showed that  $Z_{I1}$   $Z_{I2}$   $\gamma$  the completely characterizes the network reciprocal 2 port network. Now I have now I have shown that they also can be measured so you do not have a difficulty any 2 port network, lossless network you can represent like this. So an alternate description for characterization of 2 port network is in terms of  $Z_{I1}$  and  $Z_{I2}$  and  $\gamma$  I think in the next class will introduce another criteria all symmetrical network and we will simplify this procedure. Thank you