

Power System Analysis
Prof. Debapriya Das
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture - 27
Load Flow Studies (Contd.)

(Refer Slide Time: 00:19)

(75)

$$\therefore I_R = \frac{|V_S|}{|B|} \angle \delta_S - \delta_B - \frac{|A| \cdot |V_R|}{|B|} \angle \delta_A - \delta_B \dots (77)$$

The receiving end complex power,

$$S_{R(3\phi)} = P_{R(3\phi)} + jQ_{R(3\phi)} = 3V_R I_R^* \dots (78)$$

Using eqn. (78) and (77), we get

$$S_{R(3\phi)} = 3 \cdot \frac{|V_S| |V_R|}{|B|} \angle \delta_B - \delta_S - 3 \cdot \frac{|A| \cdot |V_R|^2}{|B|} \angle \delta_B - \delta_A$$

or in terms of line-to-line voltage,

$$S_{R(3\phi)} = \frac{|V_{S,L-L}| |V_{R,L-L}|}{|B|} \angle \delta_B - \delta_S - \frac{|A| |V_{R,L-L}|^2}{|B|} \angle \delta_B - \delta_A \dots (79)$$

So, we will come back to this thing. Therefore, you will this thing, just hold on. So, this is that expression for receiving end 3 phase power, right. This is equation 79 right.

Next what you do? This one this angle delta B minus delta S, you can write this term cosine delta B minus delta S plus j sin delta B minus delta S. Here also this one cosine delta B minus delta A plus j sin delta B minus delta A. So, multiply and then you separate real and imaginary part right.

(Refer Slide Time: 00:57)

Separating real and imaginary parts of eqn. (70). (74)

$$P_{R(3\phi)} = \frac{|V_{s,L-L}| |V_{r,L-L}|}{|B|} \cos(\delta_B - \delta_S) - \frac{|A| |V_{r,L-L}|^2}{|B|} \cos(\delta_B - \delta_A) \dots (80)$$

$$Q_{R(3\phi)} = \frac{|V_{s,L-L}| |V_{r,L-L}|}{|B|} \sin(\delta_B - \delta_S) - \frac{|A| |V_{r,L-L}|^2}{|B|} \sin(\delta_B - \delta_A) \dots (81)$$

Similarly we can obtain

$$P_{S(3\phi)} = \frac{|A| |V_{s,L-L}|^2}{|B|} \cos(\delta_B - \delta_A) - \frac{|V_{s,L-L}| |V_{r,L-L}|}{|B|} \cos(\delta_B - \delta_S)$$

$$Q_{S(3\phi)} = \frac{|A| |V_{s,L-L}|^2}{|B|} \sin(\delta_B - \delta_A) - \frac{|V_{s,L-L}| |V_{r,L-L}|}{|B|} \sin(\delta_B - \delta_S)$$

and Reactive power losses are

So, if you do So then, your then it will be receiving end 3 phase power it will be mode V S L-L in to V R L-L that is line to line voltage by mode B magnitude. Cosine delta B minus delta S minus A mode A V R line to line square by mode B cos delta B minus delta A. This is equation 80.

And similarly, this one you are reactive one V S L-L, V R L-L upon B sin delta B minus delta S minus mode A V R L-L, magnitude square up on B sin delta B minus delta A this is equation 81, right. This is receiving end. So, this is an exercise for you find out for the sending end side, but I am giving you the final expression.

(Refer Slide Time: 01:42)

$$Q_{R(3\phi)} = \frac{|V_{s,L-L}| |V_{r,L-L}|}{|B|} \sin(\delta_B - \delta_A) - \frac{|A| |V_{r,L-L}|^2}{|B|} \sin(\delta_B - \delta_A) \dots (81)$$

Similarly we can obtain

$$P_{S(3\phi)} = \frac{|A| |V_{s,L-L}|^2}{|B|} \cos(\delta_B - \delta_A) - \frac{|V_{s,L-L}| |V_{r,L-L}|}{|B|} \cos(\delta_B + \delta_S) \dots (82)$$

$$Q_{S(3\phi)} = \frac{|A| |V_{s,L-L}|^2}{|B|} \sin(\delta_B - \delta_A) - \frac{|V_{s,L-L}| |V_{r,L-L}|}{|B|} \sin(\delta_B + \delta_S) \dots (83)$$

Real and Reactive power losses are

$$P_{Loss(3\phi)} = P_{S(3\phi)} - P_{R(3\phi)} \text{ and } Q_{Loss(3\phi)} = Q_{S(3\phi)} - Q_{R(3\phi)}$$


Similarly, we can obtain sending end one right. So, it is P S your sending end 3 phase power it is a V S L-L square up on mode B cosine delta B minus delta A, right. And this is V S L-L, V R minus V S L-L V R L-L upon mode B cos delta B plus delta S, this is equation 82. And similarly Q S is equal to that is 3 phase a V S L-L square up on mode B sin delta B minus delta A minus, V S line to line V R your line to line all magnitude by B magnitude sin delta B plus delta S this is equation 83. So, real and reactive power losses easily you can find; sending end real power, minus receiving end real power that will give you 3 phase real power loss.

So, P loss 3 phase P S 3 phase minus P R 3 phase, and Q loss 3 phase will be Q S 3 phase minus Q R 3 phase, right. This way you can calculate the loss this is another way of calculating there are many ways. So, this is another way of calculating. So, so this performance and characteristic of transmission line this particular topic will be, I think here we will stop, right. And as far as possible we have tried to understand the things of characteristics of transmission line, right. And whatever possible things are available this things are I mean important we have try to discuss right.

So, this characteristic of transmission line this thing is over next one is that most important one is that your power flow or load flow studies right. So, in this case for next one, next one and half hour or so or above that, what will do I have retained your rather

horizontal it will be vertically right. So, load flow this thing you have to you know, you have to try to understand little bit right.

(Refer Slide Time: 03:45)

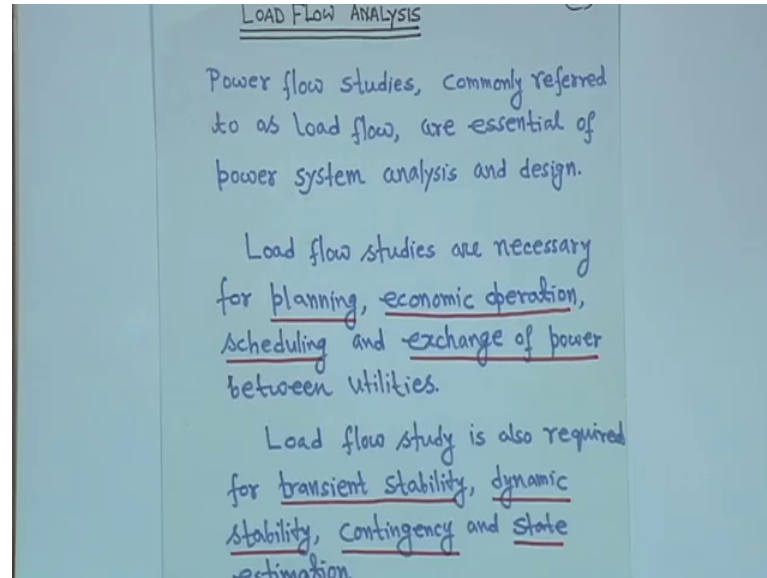


And that particularly this topic actually involves as you know, that involves huge mathematics and when this transmission line load flow will be your load flow or power flow analysis will be covered at the end, I will I will give you one latest thing that is that P bus and P Q V bus that is at the end how to form the Jacobean matrix.

But here in the classroom teaching also we can take we cannot show we can take a small example, because this is a topic where you need computer and you have to write code. Although nowadays So many your what you call your packages or codes are available, but in that case what is happening, that in that code you are giving input and getting the final result that is fine right.


But my question is that if you try to write code of your own then definitely you will learn many things right. So, this load flow analysis will when will go step by step, and what will do that each very step or every line please try to understand for this load flow studies, as much as possible from my side I will try. So, load flow analysis or power flow studies commonly referred to as the load flow, right. Essential for power system analysis and design both right.

(Refer Slide Time: 05:16)

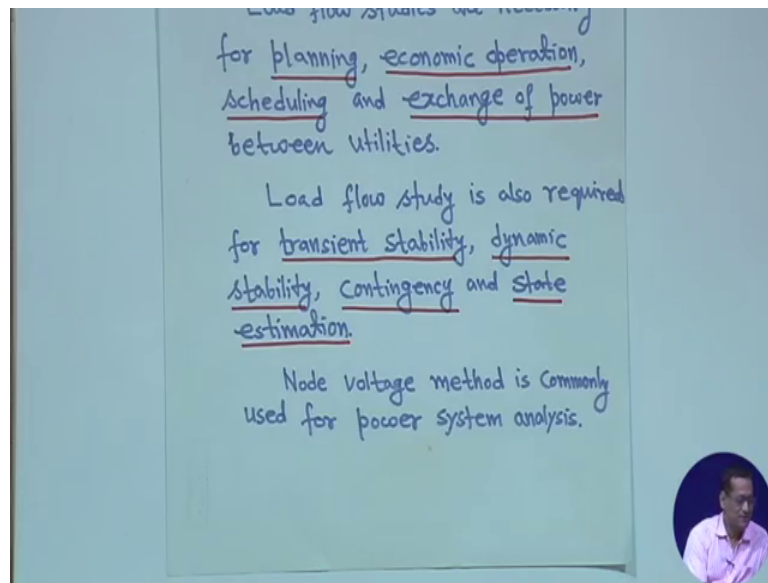


So, basically load flow studies are necessary that planning economic operation scheduling and exchange of power between utilities, you you need that load flow thing, right. Apart from this load flow or power flow is also required for transient stability that small signal stability sometimes will call dynamic stability, contingency and state estimation right. So, everywhere that load flow is requiring, right. And node voltage method is commonly used for power system analysis right.

(Refer Slide Time: 05:52)

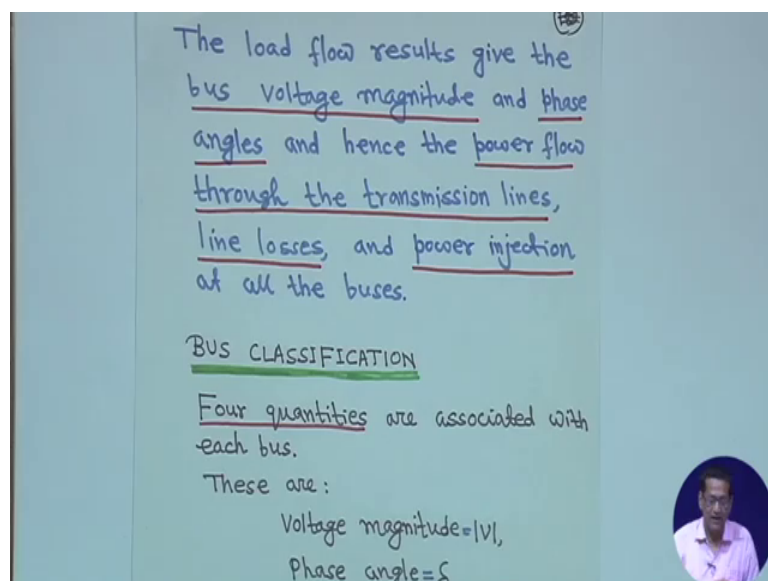

Therefore this load flow results give the, what it will give? It will give you the bus voltage magnitude, right. Then it will give your voltage phase angle that is the voltage angle. And then power flow it will be through the transmission line losses you can compute. And the power injection at every bus bar, right. That also you can compute. So, and whenever we do So we have to, we have to see that how we can make it right; so basically in load flow that you have to first classify the bus the bus classification.

(Refer Slide Time: 06:31)

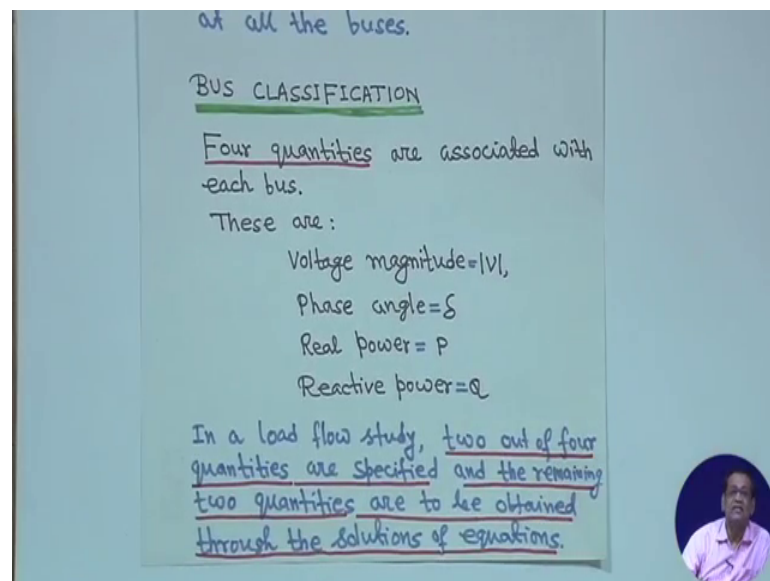

So, basically 4 quantities are associated with each bus right. So, these are actually voltage magnitude, this is voltage magnitude that V then phase angle your δ , and real power is equal to P and reactive power is Q , right. Therefore, in a load flow studies at least 2 out of 4 quantities are specified, right. At least 2 you have to specify and the remaining 2 quantities are to be obtained through the solutions of equations right. But let me tell you, this are the common thing that, we have a slack bus will come to that you have a your what you call P Q bus you have P Q bus, right.


Apart from that nowadays as electrical engineering is changing, right. Because of that smart grid micro grid and renewable energy sources particularly solar you know, and other types of sources, right. That dispatchable diseases and non dispatchable disease all are coming and in your heavy power injection to the power network. So, that is why many cases that apart from this many other type of buses are being introduced right.

P and P Q bus P Q bus is one thing answer other also you can make it, right; as per your requirement. So, for example, if you make if suppose, suppose for although at third year level or even at PG level also this is not this may not be very familiar with you for say, when distribution network, actually working your under eye landed mode. That is it is not connected to the grid right. So, at that time you will find load flow is a different, right. A load flow is completely different and at that time that particularly that dispatchable device like your say biomass device or diesel generator, one has to consider that droop characteristics right.

So, in that case that Jacobean matrix whatever will see in the load flow studies it will become the function of what you call that frequency also, right. That Jacobean matrix and in that case of course, you can follow the same Newton-Raphson method, but with lot of modifications right. So, thing such changing and electrical engineering also changing particular the power system engineering is changing like anything, right. Because of this smart grid and micro grid although those things are beyond the scope of this course, but I am giving you some hint of this one and for distribution power flow although Newton-Raphson method works well couple of your couple Newton-Raphson method it works very well, but at the same time some other types of load flow techniques also available for distribution network.

Because distribution networks actually mostly it operates your radially, right. I mean a and your what you call transmission network move it is actually messed distribution messed network right.

(Refer Slide Time: 09:43)

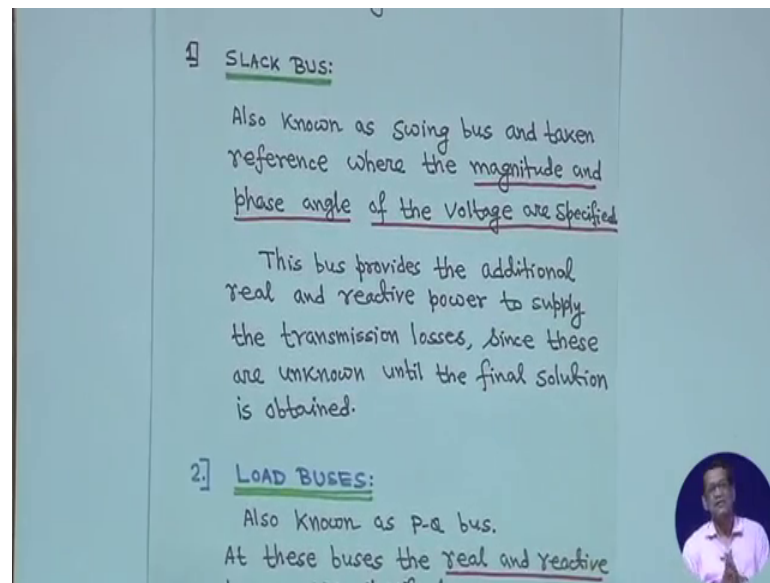


So, 4 volt 4 quantities for load flow studies will basically handle. The system buses or classified one is first one is that that slack bus. This is sometimes also called the swing bus and taken reference, when the magnitude in this bus actually voltage magnitude and phase angle this 2 are specified, right. And I told you, that your what you call that here you are taking slack bus, but when we are coming to your what you call that, sometimes for micro grid, DC micro grid there we can also see that your slack bus free actually, right. Anyway, those are beyond us scope. So, this bus provides the additional real and reactive power to supply the transmission losses. That is the slack bus we have to choose our reference bus and result will come around that your what you call that slack bus, right.

Since these are unknown until the final solution is obtained. Because these slack buses actually provide the additional real and reactive power to supply the transmission losses and these are known until the final solution is obtained because unless and until your solution load flow solution has converted, you cannot do anything, right. You cannot compute a loss also.

(Refer Slide Time: 10:58)

This bus provides the additional real and reactive power to supply the transmission losses, since these are unknown until the final solution is obtained.


2.] LOAD BUSES:
Also known as P-Q bus.
At these buses the real and reactive powers are specified.
The magnitude and phase angle of the bus voltage are unknown until the final solution is obtained.



Now, another thing is load bus, sometimes we call this one as a P Q bus; that means, load bus P Q bus means that at that load that P and Q both are specified right; that means, in that bus you will find that power injection P and Q both are known, right. That that and that and magnitude of the voltage of this bus and its phase angle these 2 are unknown quantity and you will be knowing only when you will solve this load flow this thing in iterative way right. So, unless and until you final solution is not obtain I mean obtained you will never be knowing the magnitude and voltage angle, but P and Q both will be your what you call this thing are this thing specified at the load bus right.

(Refer Slide Time: 11:51)

3.] VOLTAGE CONTROLLED BUSES:
Also known as generator buses or regulated buses or P-V buses.
At these buses, the real power and voltage magnitude are specified.
The phase angles of the voltages and the reactive power are unknown until the final solution is obtained.
The limits on the value of reactive power are also specified.
The following table summarises the



Then another bus is called voltage controlled buses or P V bus, right. Here that real power is known P is known and voltage magnitude is known. That is why we are this called sometime this is called generator buses or regulated buses or simply P V buses, P I put magnitude V buses because P is known and voltage magnitude is also known for this bus then, what is unknown? Q is unknown and what you call that voltage angle it is unknown, right. This 2 are unknown; that means, at P V buses, right.

That what you call that voltage magnitude of that bus you want to maintain, right. As P is known voltage angle is not known, but Q is unknown right; that means, at that bus you have to inject that reactive power such that you can maintain this voltage magnitude V for that bus. So, this is called sometimes we call P V bus, right. Or generator buses or regulated buses right.


So, in that case that as Q at P V buses Q is unknown; so we have to also set the limit on the Q injection that is some minimum value to maximum value. But let me tell you one thing, as it is a classroom exercise. So, taking Q_{min} Q_{max} all sort of things it is difficult to put in the classroom you one need code computer code one has to write, and one should see observe what is happening? But in this case, in this thing it will take it will take I think few hours to explain all sort of thing, but I will try to I will take throughout this load flow studies, I will take only one example and give all sort of your what you call a this thing methodology right. So, Q limit also you have to consider and it has to be specified for P V buses right.

(Refer Slide Time: 13:48)

...ages of the voltages and the reactive power are unknown until the final solution is obtained. The limits on the value of reactive power are also specified.


The following table summarizes the above discussion:

| Bus Type | Specified quantities | Unknown quantities |
|------------------------|----------------------|--------------------|
| Slack bus | V, δ | P, Q |
| Load bus | P, Q | V, δ |
| Voltage controlled bus | P, V | Q, δ |



Therefore the following table summarizes the above discussion right. So, bus type it is slack bus voltage magnitude and delta both are known that is specified unknown quantities are P and Q. For load bus P and Q are specified right, but voltage magnitude and delta these are unknown quantities. And voltage controlled bus that is P V s, right. P and voltage magnitude real power and voltage magnitude are specified, but Q and delta are not known right. So, with this in our mind slack bus P Q bus and P V bus now will move to see that first the bus admittance matrix right.

(Refer Slide Time: 14:36)

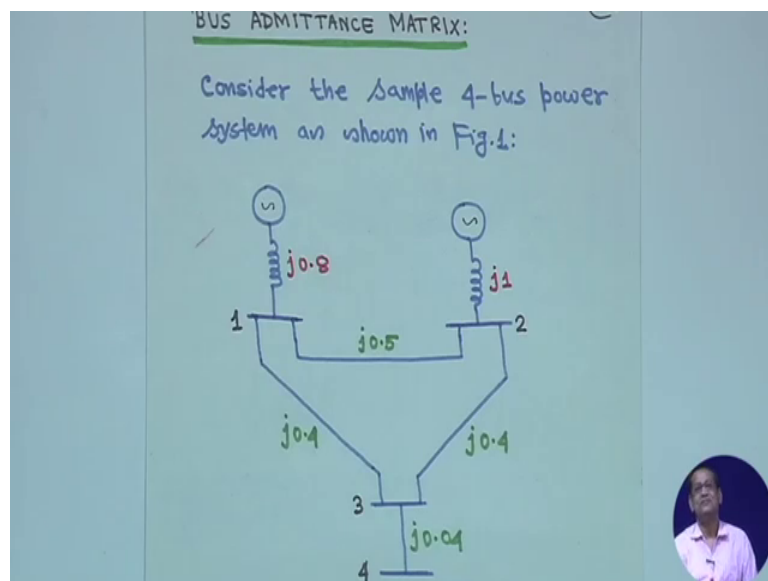


So, in will go for bus admittance matrix I will explain everything, but I put the question to you for load flow studies we use y matrix. But not z matrix that is admission admittance matrix we use, but we do not use your impedance, right; matrix, right. Z we do not do, we make admittance for the full sane. Why we do not use z bus for load flows?

This is a simple question to you and answer also will be simple. So, this should be keep it in your mind, right. Now what will do for bus admittance matrix, we consider this your what you call this sample 4 bus power system. This is a 4 bus power system, right. This is this is one generator this is one generator, right. And for purpose of class classroom exercise what we have done is that R we have not considered, but when will when will consider what you call numerical at that time will take R, but here you do not want to complicate the things.

So, only reactance is what you call consider right. So, this is a this is your suppose generator one, 2 whatever is given and this is your j 0.8 everything you assume it is per unit. So, this j 1, this for line one to j 0.5 j 0.4 j 0.4 and line 3 to 4 j point, I think it is your this thing j point 0 4 right. So, this is the, this is the sample power system 4 bus power system we have taken, and this is the impedance diagram, but we have not considered your what you call that resistance right.


(Refer Slide Time: 16:18)

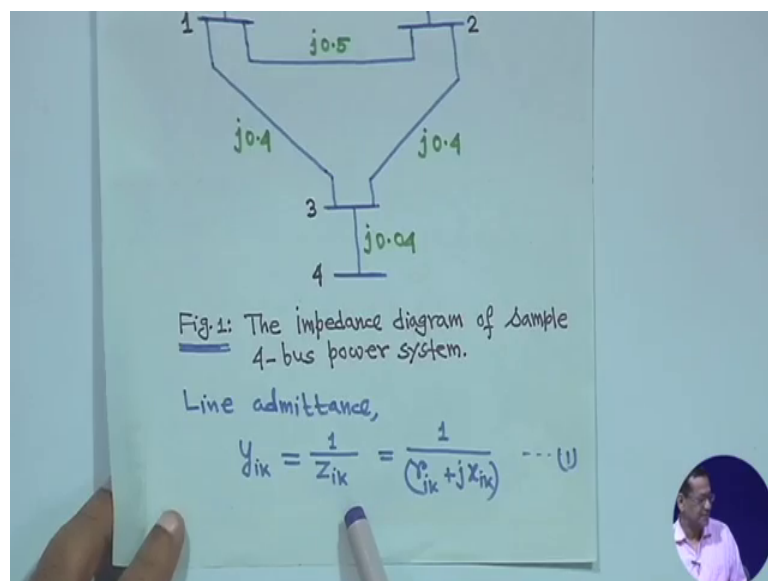


So, generally as you know from your this thing, that line admittance actually for line i 2 k bus i 2 k small y i this is like the small y i k is equal to 1 up on z I. K, right. This small z i k.

Is equal to 1 up on r i z i k is equal to r i k plus j x I k this is equation 1, right. This is the admittance, right. Now what we will do? Why we have taken this everything this 2 sources, right. This 2 1 you transform in to what you call that current source right. So, instead of instead of this 2 generators are given right. So, instead of voltage one you transform in to a current source right. So, if you do so, look at this is the diagram, this is the diagram.

(Refer Slide Time: 17:05)

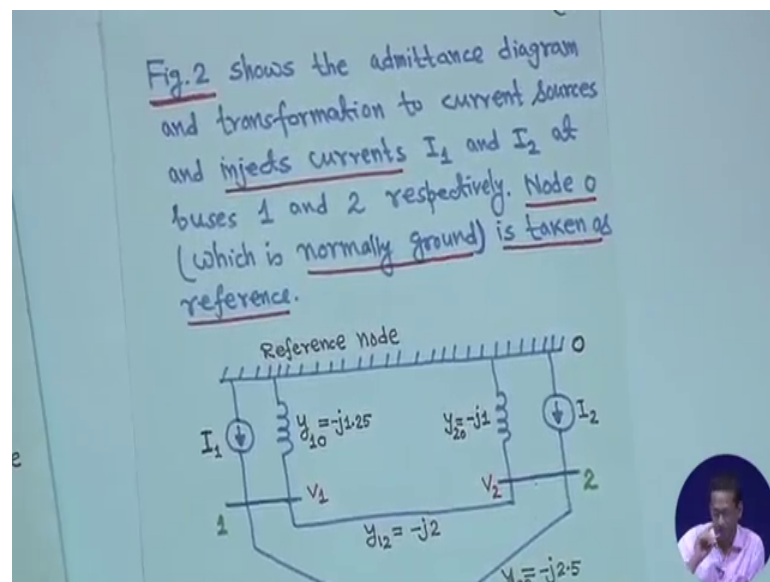

(Refer Slide Time: 17:08)

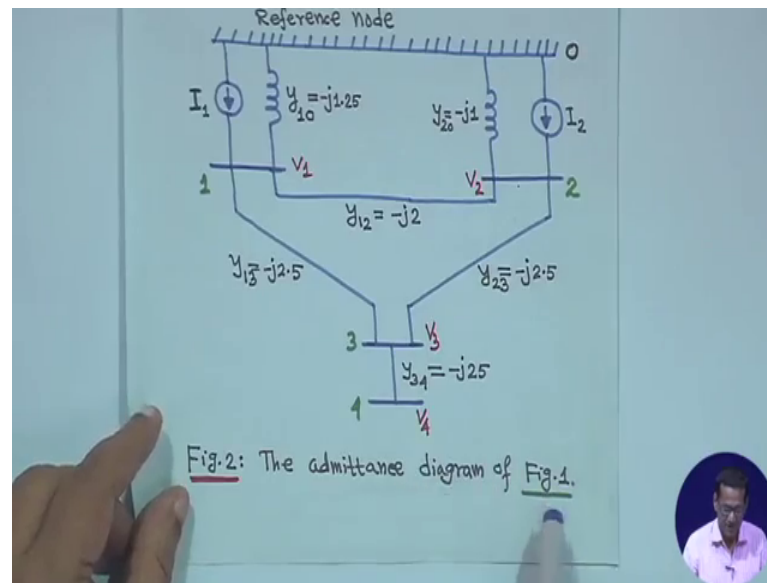

If you look so, though figure 2 look this it shows that your what you call the admittance diagram. In that case what you have to do is that you take a reference node. This node number is given as a 0, and this basically it is a ground and exponential is it is at 0 potential right; that means, and this 2 sources have been converted to current source. So, this is your current I_1 injecting your this current I_1 getting injected here and current I_2 from this side getting injected here and all this all this your reactance thing has been converted to admittance; that means, it was an as it is a current source. So, this will be it is in parallel so; that means, it is $j 0.8$. So, $1 \text{ upon } j 0.8$ is equal to your y it is making as $1 \text{ over } 0 \text{ minus } j 1.25$ this is 0 node this is one node, that is why writing $1 \text{ over } 0 \text{ minus } j 1.25$ right

And this is $j 1$; so $1 \text{ upon } j 1$ that is $\text{minus } j 1$, so, y_{20} that is $2 \text{ to } 0$ $y_{20} \text{ minus } j 1$, right. And this is I_2 this current is getting injected, right. And this line 1 to 2 voltage here 1, 2, 3, 4 voltage are marks at V_1, V_2, V_3, V_4 this are the complex voltage, right. And this is 1 to 2 the reactance is $j 0.5$, right. Or impedance you contain R is neglected, that is $1 \text{ upon } j 0.5$ that is $\text{minus } j 2$. So, admittance y_{12} is equal to $\text{minus } j 2$ is equal to y_{21} , they are same, right. Similarly 1 2 3 is $j 0.4$. So, admittance is $1 \text{ upon } j 0.4$; so $\text{minus } j 2.5$. So, this is $\text{minus } j 2.5$, right.

And similarly here it is also $0.4 \text{ over } 0.4$ it is also $\text{minus } j 2.5$ and here it is $j 0.04$. So, $1 \text{ upon } j 0.04$, that is $\text{minus } j 25$. So, this diagram this one actually, transform this 2 sources transform in to current source and all the impedance diagram I have been transform in to

admittance diagram, right. So; that means, this is an one reference node is required and this is your what you call this is your normally it is a ground and you can take it as a 0 potential, right. And this is the admittance diagram of figure one that is this is figure 2. I hope this is very easy to understand actually not much is there right.

Next is you have to apply KCL to the independent nodes 1 2 3 4 right. So, look this is this current is getting injected here I_1 if you write if you apply KCL, right. At this bus bar I_1 . So, what will be your equation, right? I_1 should be is equal to if this voltage is V say 0 potential. So, if I make V_0 is equal to 0, and this current is getting injected and you take all this current out then, I_1 is equal to your first before my writing I_1 is equal to this take out; so $y_{10} V_1$ plus y_{12} in to V_1 minus V_2 plus y_{13} in to V_1 minus V_3 . But everywhere your y_{ij} or y_{ik} is equal to Y_{ki} I mean it both are same. Y_{13} is equal to y_{31} , small y of course, small y this one, small y_{12} is equal to small y_{21} and small y_{23} is equal to small y_{32} small y_{34} is equal to small y_{43} .

(Refer Slide Time: 20:53)

Applying KCL to the independent nodes 1, 2, 3, 4 we have,

$$I_1 = y_{10}V_1 + y_{12}(V_1 - V_2) + y_{13}(V_1 - V_3)$$

$$I_2 = y_{20}V_2 + y_{12}(V_2 - V_1) + y_{23}(V_2 - V_3)$$

$$0 = y_{23}(V_3 - V_2) + y_{13}(V_3 - V_1) + y_{34}(V_3 - V_4)$$

$$0 = y_{34}(V_4 - V_3)$$

Rearranging the above equations, we get

$$I_1 = (y_{10} + y_{12} + y_{13})V_1 - y_{12}V_2 - y_{13}V_3$$

That means, this current at this one I_1 is equal to $y_{10} V_1$, this thing then you take this one and plus $y_{12} V_1$ minus V_2 $y_{12} V_1$ minus V_2 plus $y_{13} V_1$ minus V_3 $y_{13} V_1$ minus V_3 , right. No equation number. Similarly, for this one I_2 is equal to your $y_{20} V_2$ minus I told you this 0 potential, so basically $y_{20} V_2$ minus 0 basically $y_{20} V_2$. So, it is $y_{20} V_2$ plus your y this current that y_{12} to y_{21} same. So, I will write y_{12}

only y_{12} in to $V_2 - V_1$ because current leaving from this 2 to one. So, $V_2 - V_1$

So, $y_{12} V_2 - V_1$ because $y_{12} = y_{21}$ same. So, I am not writing y_{21} understandable right; so $V_2 - V_1$ plus 2 to 3 so $y_{23} V_2 - V_3$. So, here it is $y_{23} V_2 - V_3$ this is the second equation for the second bus bar, right. Now third bus bar here there is no current injection, this bus bar and this bus bar. Because in this diagram in this diagram it is it is nothing was given. So, no current injection; that means, 0 right; that means, this; that means, 0 is equal to for the bus 3 you take all the outgoing current, right.


For example, your y_{23} in to $V_3 - V_2$ $V_3 - V_2$ $y_{23} V_3 - V_2$ then, $y_{13} V_3 - V_1$, because y_{13} is equal to y_{31} so $V_3 - V_1$. So, it is taken $y_{13} V_3 - V_1$. Then you take this outgoing one that is $y_{34} V_3 - V_4$ plus $y_{34} V_3 - V_4$ and no current injection here. So, it is 0 is equal to this one this is the third equation. Now fourth one when you come here, this bus bar 4, right. Current injection is 0, right. And this is and if you take that $V_4 - V_3$. So, it is $y_{34} V_4 - V_3$. So, 0 is equal to $y_{34} V_4 - V_3$. So, for the all bus 4 1 2 3 4 you have got this 4 equation sets of equation for the time being not putting any equation number. So, this one from this diagram, from this diagram you have got we have got this one this we have understood very easy right.

And from this you write down all this equation in terms of admittance, right. Line admittance, charging capacitance will come later first you understand this.

(Refer Slide Time: 23:33)

$$\begin{aligned}
 0 &= y_{23}(V_3 - V_2) + y_{13}(V_3 - V_1) + y_{34}(V_3 - V_4) \\
 0 &= y_{34}(V_4 - V_3)
 \end{aligned}$$

Rearranging the above equations, we get
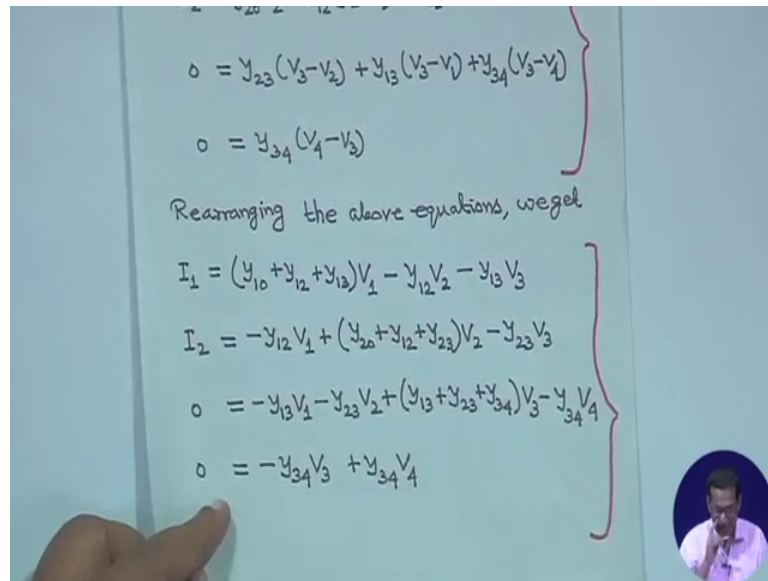
$$\begin{aligned}
 I_1 &= (y_{10} + y_{12} + y_{13})V_1 - y_{12}V_2 - y_{13}V_3 \\
 I_2 &= -y_{12}V_1 + (y_{20} + y_{12} + y_{23})V_2 - y_{23}V_3 \\
 0 &= -y_{13}V_1 - y_{23}V_2 + (y_{13} + y_{23} + y_{34})V_3 - y_{34}V_4 \\
 0 &= -y_{34}V_3 + y_{34}V_4
 \end{aligned}$$


Now, rearrange this all this 4 equation above equation; that means you collect all the terms to V_1 , V_2 and V_3 . So, I_1 you can write y_{10} plus y_{12} plus y_{13} in to V_1 I mean this equation we are rewriting then minus $y_{12}V_2$ minus $y_{13}V_3$. Similarly this one also you can write I_2 is equal to minus $y_{12}V_1$ plus y_{20} plus y_{12} plus $y_{23}V_2$ minus $y_{23}V_3$, right. Then this one you can write the third one, that 0 is equal to minus $y_{13}V_1$ minus $y_{23}V_2$ plus y_{13} plus y_{23} plus $y_{34}V_3$ minus $y_{34}V_4$, right.

And last one 0 is equal to this one minus $y_{34}V_3$ plus $y_{34}V_4$; that means, we are arranging V_1 , V_2 , V_3 , V_4 this way right. So, this is I_1 , I_2 this is 2 current injection 0. So, variant, but no equation number is given, right. Once it is done then you define for example, for example, that you define capital Y_{11} capital Y_{11} is equal to y_{10} plus y_{12} plus y_{13} .

(Refer Slide Time: 24:57)

Let,

$$Y_{11} = (y_{10} + y_{12} + y_{13})$$

$$Y_{22} = (y_{20} + y_{12} + y_{23})$$

$$Y_{33} = (y_{13} + y_{23} + y_{34})$$

$$Y_{44} = y_{34}$$

⇒ Diagonal Elements

$$Y_{12} = Y_{21} = -y_{12}$$

$$Y_{13} = Y_{31} = -y_{13}$$

$$Y_{23} = Y_{32} = -y_{23}$$

⇒ Off-diagonal Elements

So, write capital Y_{11} is equal to y_{10} plus y_{12} plus y_{13} . This was capital Y_{11} , right. Similarly first diagonal elements you define then y_{22} this one. Capital Y_{22} you write y_{20} plus y_{12} plus y_{23} . So, capital Y_{22} is equal to y_{20} plus y_{12} plus y_{23} , these are only diagonal elements we are writing, right. Then third one this y_{33} , this is y_{13} plus y_{23} plus y_{34} the third one. That is your y_{33} is equal to y_{13} plus y_{23} plus y_{34} , right. And this y_{44} is equal to the last one, y_{44} is equal to y_{34} . So, capital Y_{44} is equal to y_{34} these are all diagonal elements right.

Next you make off diagonal elements. Off diagonal elements this one whatever we have from this for this equation that y_{12} , right. This is y_{12} capital Y_{12} , you define and y_{12} is equal to y_{21} you write capital Y_{12} is equal to capital Y_{21} is equal to minus y_{12} .

(Refer Slide Time: 26:00)

The image shows a whiteboard with handwritten mathematical equations. At the top, $Y_{44} = Y_{34}$ is written. Below it, a dashed line separates the equations. The next set of equations is $Y_{12} = Y_{21} = -Y_{12}$, $Y_{13} = Y_{31} = -Y_{13}$, $Y_{23} = Y_{32} = -Y_{23}$, and $Y_{34} = Y_{43} = -Y_{34}$. A bracket on the right side of these equations is labeled "Off-diagonal Elements". Below this, the text "The node equations reduce to," is written. Underneath, three equations are listed: $I_1 = Y_{11}V_1 + Y_{12}V_2 + Y_{13}V_3 + Y_{14}V_4$, $I_2 = Y_{21}V_1 + Y_{22}V_2 + Y_{23}V_3 + Y_{24}V_4$, and $I_3 = Y_{31}V_1 + Y_{32}V_2 + Y_{33}V_3 + Y_{34}V_4$. A hand is visible on the left side of the whiteboard, and a small circular inset in the bottom right corner shows a person's face.

Similarly, this is V_3 . So, it is one 3 right. So, capital Y_{13} is equal to capital Y_{31} is equal to minus small y_{13} . So, capital Y_{13} is equal to capital Y_{31} is equal to minus small y_{13} , right. Similarly you come to the next is the 2 right. So, y_{23} . So, your what you call this is a symmetric matrix.

So, your what you call y_{12} y_{21} will minus y_{12} here also 221 capital Y_{21} will be minus y_{12} symmetry. So, that is why it is what you call this y_{21} is minus y_{12} , right. It is symmetry matrix then 223 capital Y_{23} will be is equal to capital Y_{32} is equal to minus small y_{23} . So, capital Y_{23} is equal to y_{32} is equal to minus y_{23} , right, and then y_{34} , right. You your come to this one this are symmetric matrix. So, directly you will come here y_{34} capital Y_{34} is equal to capital Y_{43} is equal to minus small y_{34} . So, capital Y_{34} is equal to capital Y_{43} is equal to minus small y_{34} . So, this are all our off diagonal elements right.


(Refer Slide Time: 27:23)

The image shows a whiteboard with handwritten mathematical equations. At the top, four pairs of equations are listed, each pair enclosed in a curly brace on the right. These pairs are: $Y_{12} = Y_{21} = -Y_{12}$, $Y_{13} = Y_{31} = -Y_{13}$, $Y_{23} = Y_{32} = -Y_{23}$, and $Y_{34} = Y_{43} = -Y_{34}$. To the right of these four pairs, the text "Off-diagonal Elements" is written with an arrow pointing to the braces. Below this, the text "The node equations reduce to," is written. Underneath, four equations for $I_1, I_2, I_3,$ and I_4 are listed, each enclosed in a curly brace on the right. The equations are: $I_1 = Y_{11}V_1 + Y_{12}V_2 + Y_{13}V_3 + Y_{14}V_4$, $I_2 = Y_{21}V_1 + Y_{22}V_2 + Y_{23}V_3 + Y_{24}V_4$, $I_3 = Y_{31}V_1 + Y_{32}V_2 + Y_{33}V_3 + Y_{34}V_4$, and $I_4 = Y_{41}V_1 + Y_{42}V_2 + Y_{43}V_3 + Y_{44}V_4$. A hand is visible on the left side of the whiteboard, and a small circular inset in the bottom right corner shows a person's face.

Now So, now when you write this equation you write like this, I_1 is equal to capital $Y_{11} V_1$ plus capital $Y_{12} V_2$ plus capital $Y_{13} V_3$ plus capital $Y_{14} V_4$. This way you write some of them why you will become zero, but make it like this, right. I_2 is equal to similarly again and again not again and again, I am not uttering that capital understandable; so $y_{21} V_1$ plus $y_{22} V_2$ plus $y_{23} V_3$ plus $y_{24} V_4$, right. Similarly I_3 I_3 actually 0 I_4 actually 0 some of the voice elements are also zero, but we make it like this first.


So, I_3 is equal to $y_{31} V_1$ plus $y_{32} V_2$ plus $y_{33} V_3$ plus $y_{34} V_4$, right. Similarly I_4 is equal to $y_{41} V_1$ plus $y_{42} V_2$ plus $y_{43} V_3$ plus $y_{44} V_4$ this way first you make right, but now you see the connectivity of the line right.

(Refer Slide Time: 28:33)

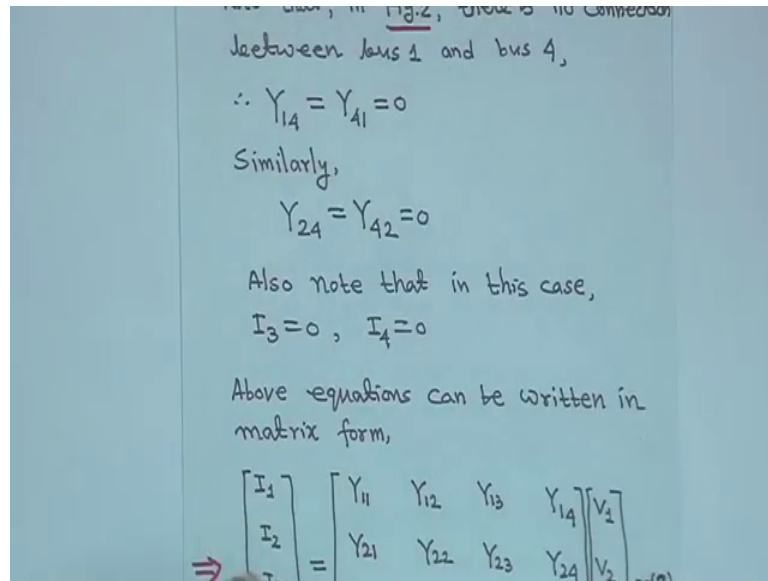

So, but I 3 and I 4 they are zero, but we have to put them in matrix form so; that means, that your just one minute; that means, in that your in figure 2 there is no now there is no connection between bus 1 and bus 4. So, there is no connection between 1 and 4. So, actually y 4 is equal to y 4 1 is 0 similarly there is no connection between 2 and 4, right. That is why 2 y 2 4 actually y 4 2 will be 0 and at this node I 3 and I 4 actually 0. So, also note that in this case I 3 0 I 3 I 4 0. So, in this equation in this equation I 3 I 4 will be 0 and other 2 elements of why I told you that also will be 0, right; so but for the sake of your mathematics and completeness.


(Refer Slide Time: 29:22)

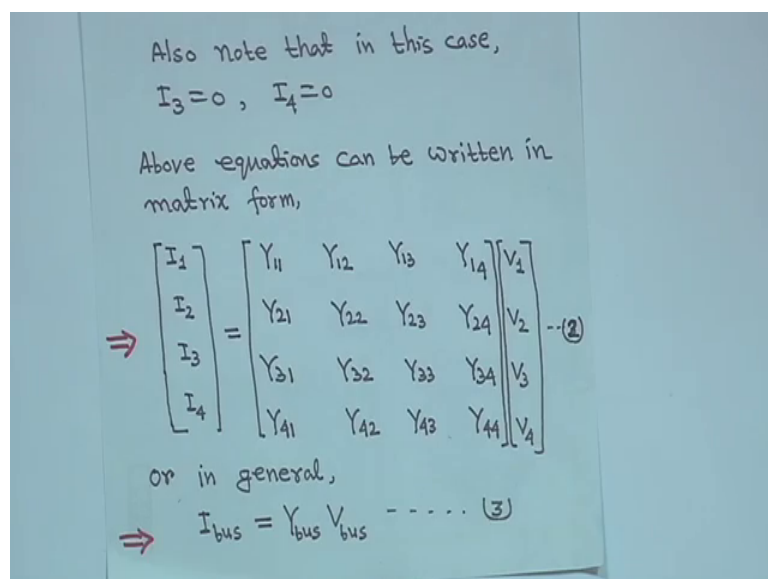

We have to make this equation $I_1 I_2 I_3 I_4$ is equal to this is y matrix $V_1 V_2 V_3 V_4$, right. And this is actually just hold on just one minute this y i k equation actually 1 upon z i k this actually equation 1, right. And this equation your $I_1 I_2 I_3 I_4$ is equal to basically y V this equation actually equation 2 or in general you can write it that I_{bus} , this is the bus current injection I_{bus} is equal to y_{bus} this is that bus admittance matrix y_{bus} in to V_{bus} this is the bus voltage right.

So, this is actually equation 3. So, we represent this equation basic in general I is equal to y V right.

(Refer Slide Time: 30:14)

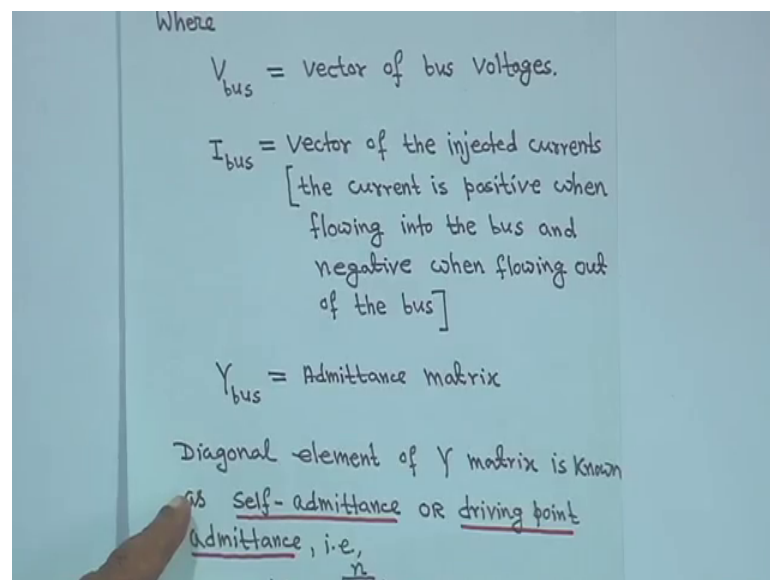

So, V_{bus} now we are giving the nomenclature. V_{bus} is equal to vector of bus voltage $V_1 V_2 V_3$ and up to V_4 , right. And I_{bus} is equal to your vector of the injected currents, right. That is $I_1 I_2 I_3 I_4$, but later will see when you will form the Jacobean that when you choose one bus is slack bus that voltage is known, right. In that case you will see Jacobean matrix and other things will be how it how it we one can form, but this is the preliminary thing. So, y_{bus} that I_{bus} is the vector of injected currents right. So, the current is positive when flowing in to the bus and is negative when flowing out of the bus the convention will follow. And y_{bus} is equal to that bus admittance matrix right.

So, diagonal elements of y matrix actually is not known as self admittance or driving point admittance right.

(Refer Slide Time: 31:06)

of the bus]

Y_{bus} = Admittance matrix

Diagonal element of Y matrix is known as self-admittance OR driving point admittance, i.e.,

$\Rightarrow Y_{ii} = \sum_{k=0}^n Y_{ik}, k \neq i \quad \dots (4)$

Off-diagonal element of Y matrix is known as transfer admittance OR mutual admittance i.e.,

$\Rightarrow Y_{ik} = Y_{ki} = -Y_{ik} \quad \dots (5)$

That diagonal elements that is that y_{11} y_{22} y_{33} and y_{44} , these elements diagonal known as self-admittance or driving point admittance, right, that is in general in general capital Y I is equal to k is equal to 0 2 n you write y_{ik} , but k not is equal to I right; that means, in that case also if you take your what you call that your including the reference bus that is 0 to 4 ; that means, we expand y_{11} y_{22} you will get the same thing right. And off diagonal elements of y matrix is known as transfer admittance or mutual admittance that s i y capital y_{ik} is equal to capital Y_{ki} is equal to minus small y_{ik} , right this minus sign for small one because this is each your branch admittance 1 upon z_{ik} .

So, that is capital y_{ik} is equal to capital Y_{ki} is equal to minus small y_{ik} and this is actually equation 5. And this y_{11} this y_{ii} actually k is equal to 0 2 n is taken and it is y_{ik} , but k not is equal to I such that, and later much detail I will explain when you will take this, right. And in to and when you will if you if you that row wise y matrix later when we will consider charging admittance when you will when you will add the elements of a particular row of y matrix at that time you really something else right. So, from that you can check out whether your y matrix is construction is correct or not. So, this is that general thing.

Thank you, again we are coming.