

Power System Analysis
Prof. Debapriya Das
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture - 54
Symmetrical components (Contd.)

(Refer Slide Time: 00:22)

and

$$V_b = V_c = (I_b + I_c)Z_f = 3Z_f I_{a0} \dots (31)$$

The symmetrical components of voltages are given by

$$\begin{bmatrix} V_{a1} \\ V_{a2} \\ V_{a0} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & \beta & \beta^2 \\ 1 & \beta^2 & \beta \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c = V_b \end{bmatrix} \dots (32)$$

From eqn. (32), we get,

$$V_{a1} = V_{a2} = \frac{1}{3} [V_a + (\beta + \beta^2)V_b] \dots (33)$$

and

$$V_{a0} = \frac{1}{3} (V_a + 2V_b) \dots (34)$$

$$\begin{bmatrix} I_{a1} \\ I_{a2} \\ I_{a0} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & \beta & \beta^2 \\ 1 & \beta^2 & \beta \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

$$\begin{bmatrix} I_{a1} \\ I_{a2} \\ I_{a0} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & \beta & \beta^2 \\ 1 & \beta^2 & \beta \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} 0 \\ I_b \\ I_c \end{bmatrix}$$


$$\therefore I_{a0} = \frac{1}{3} (I_b + I_c)$$

$$\therefore I_b + I_c = 3I_{a0}$$

So, V_b is equal to V_c equal to $I_b + I_c$ into Z_f is equal to $3Z_f I_{a0}$. So, I in this case what you call that this one will come to that; this one why we are writing $3Z_f I_{a0}$. So, here if you see will see that $I_b + I_c$ is equal to $3I_{a0}$; I am making it here on the right hand side here. I_{a1} , I_{a2} , I_{a0} you know one-third $1 \beta \beta^2$, $1 \beta^2 \beta$ and $1 \ 1 \ 1$; $I_a \ I_b \ I_c$ this are known to us.

Therefore, I_{a1} , I_{a2} , I_{a0} is equal to one-third $1 \beta \beta^2$ is the same you know matrix then I_a is equal to 0 and this is I_b and this is I_c .

(Refer Slide Time: 01:10)

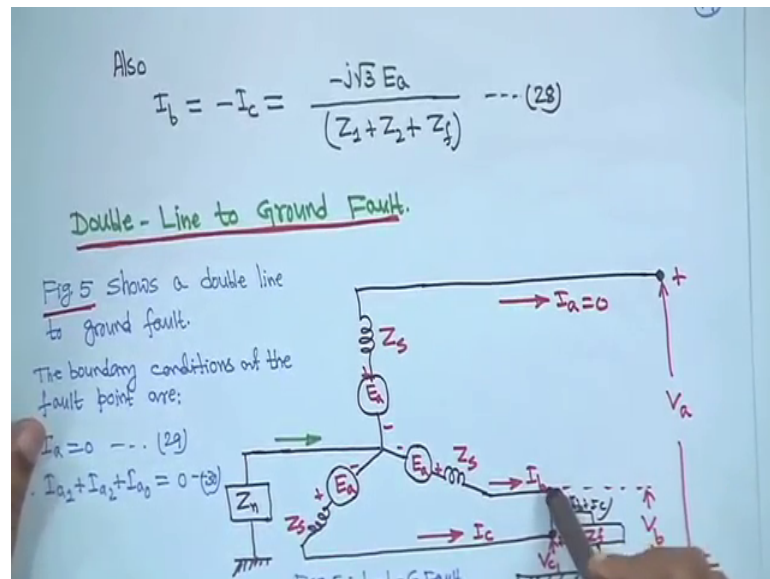

Because that this double line to ground fault, it has happen between phase b and c so I_a is equal to 0. So, here if you put I_a is equal to 0 then it is $I_b = I_c$, therefore I_{a0} is equal to from this equation because I_{a0} is equal to one-third then your I_b plus I_c . That means, I_b plus I_c is equal to $3 I_{a0}$. Therefore, this one I_b plus I_c is replaced by $3 I_{a0}$. That is why V_b is equal to V_c is equal to $3 Z_f I_{a0}$.

Now, the symmetrical components of voltages are given by. These are again known to us. So, V_{a1} , V_{a2} , V_{a0} is equal to one-third $(1 + \beta + \beta^2) V_b$, $(1 + \beta^2 + \beta) V_b$, $(1 + 1 + 1) V_b$. And this is your V_a , V_b and V_c is equal to V_b . Here we are writing V_c is equal to V_b this is equation say 32. Now from equation 32 you can write directly I am writing if you write V_{a1} for example if you write V_{a1} it will be $V_a + \beta V_b + \beta^2 V_b$ again, because V_c is equal to V_b .

If you write V_{a2} that is also one-third you will write $V_a + \beta^2 V_b + \beta V_b$. That means, $\beta^2 + \beta$ both the equation is common. That means, directly we can write that V_{a1} is equal to V_{a2} is equal to one-third in bracket $(V_a + \beta + \beta^2) V_b$. This is equation 33. And the V_{a0} the last one it is $V_a + V_b + V_c$ is equal to V_b ; that means V_{a0} is equal to one-third $(V_a + 2 V_b)$. So, this is equation 34.

So, using equation 33 and 34; that means using this two equation you subtract equation 33 from equation 34.

(Refer Slide Time: 03:28)

Using eqn. (33) and eqn. (34)

$$V_{a0} - V_{a1} = \frac{1}{3} [2 - \beta - \beta^2] V_b$$


$$\therefore V_{a0} - V_{a1} = \frac{1}{3} [3 - (1 + \beta + \beta^2)] V_b$$

$$\therefore V_{a0} - V_{a1} = \frac{3 \times 1}{3} V_b = V_b \quad [\because 1 + \beta + \beta^2 = 0]$$

$$\therefore V_{a0} - V_{a1} = 3Z_f I_{a0} \quad [\because V_b = 3Z_f I_{a0} \text{ from eqn. (31)}]$$

$$\therefore V_{a0} = V_{a1} + 3Z_f I_{a0} \quad \dots (35)$$

From eqn. (33), (35) and (30), we can draw the connection of sequence network as shown in Fig. 6




If you subtract you will get; we want V_{a0} minus V_{a1} . So, subtract equation your 33 from equation 34. If you do so V_{a0} minus V_{a1} will come like this one-third 2 minus beta minus beta square in to V_b . Now V_{a0} minus basically one-third add 1 subtract 1. If you add 1 2 plus 1- 3, then minus you take common it will be 1 plus beta plus beta square into your V_b .

So, in this case we know that this identity 1 plus beta plus beta square is equal to 0. During symmetrical component we have given this so put here it is 0. That means, V_{a0} minus V_{a1} is equal to 3, because of this 3 into one-third V_b . That means, V_{a0} minus V_{a1} actually is equal to V_b . And V_b is equal to V_c , so naturally it will be is equal to V_c . So, V_{a0} minus V_{a1} is equal to $3Z_f I_{a0}$, because V_b is equal to $3Z_f I_{a0}$. Here we have in equation 31 we have shown that V_b is equal to V_c is equal to $3Z_f I_{a0}$: all exercise has been done for you on the right hand side.

So in this case, that means your V_{a0} is equal to V_{a1} plus $3Z_f$ into I_{a0} . This is actually equation 35. That means this equation, the equation 33 35 and 30 this three equation we can draw the connection of the sequence network as shown in figure 6: so 33 35 and 30.

(Refer Slide Time: 05:14)

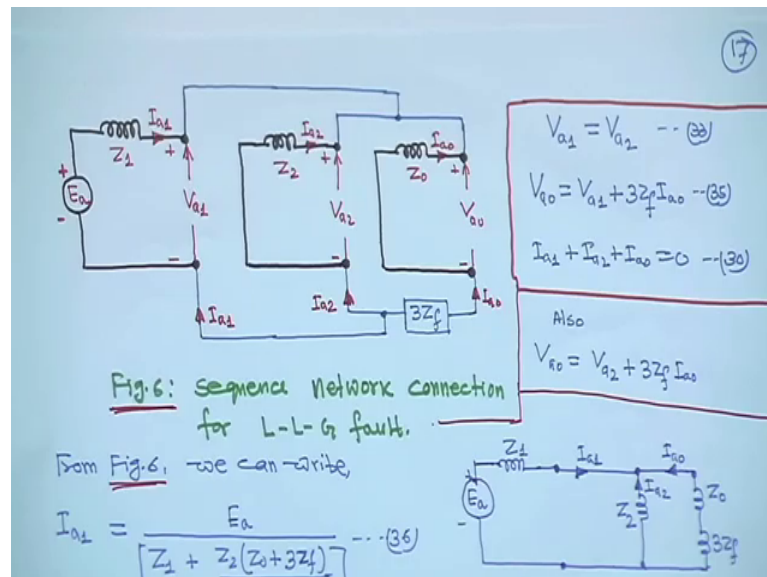

So, equation 33 it is actually V_{a1} is equal to V_{a2} , this is the first thing. Then equation 35 I have written right hand side it is V_{a0} is equal to V_{a1} plus $3Z_f I_{a0}$. And equation 30 actually I am rewriting this equation just for drawing this diagram and it is given $I_{a1} + I_{a2} + I_{a0}$ is equal to 0. That means, these three equations suppose this for example, suppose these three equations are given to you and you please draw the complete your sequence network connection. Suppose some fault has happened these equations are given to you.

For example, say after solving somebody has given that these are the positive negative and zero sequence connection you please make the circuit. So, 33 is V_{a1} is equal to V_{a2} ; that means we suggest that positive and negative your sequence it perhaps to be connected in parallel. And another is $I_{a1} + I_{a2} + I_{a0}$ is equal to 0, this condition also you have to satisfy. And V_{a0} is equal to also you have to satisfy $V_{a1} + 3Z_f I_{a1} + 3Z_f I_{a0}$; how one will make it.

So, the black color is my positive sequence network E_a is there $Z_1 I_{a1}$. This one is my negative sequence one, this is Z_2 , again by there is a black ink I have used right. And this is zero sequence Z_0 . Now first thing is that my V_{a1} is equal to V_{a2} and all this connect connectors $I_{a1} + I_{a2} + I_{a0}$ is equal to 0. So, in this case what you will do that this your V_{a0} this your this negative sequence network: this is I_{a2} is coming here and from zero sequence this I_{a0} is coming here and from positive sequence I_{a1} an come inverse you have to make a junction point such that $I_{a1} + I_{a2} + I_{a0}$ is equal to 0. That means, this I_{a1} is coming here, I_{a2} is coming here, I_{a0} also coming here, at this

point you apply here (Refer Time: 17:17) of first law. So, $I_{a1} + I_{a2} + I_{a0}$ is equal to 0

Similarly this is your plus plus connection, right. Similarly here also that you have to see first outgoing one here also as you have connected here means here also you have to connect, but question is that V_{a0} is equal to $V_{a1} + 3Z_f I_{a0}$. That means, this I_{a0} is this current is flowing to the fault impedance total is coming as a equivalent $3Z_f$. That means, this is I_{a0} ; I_{a0} current is entered and going like this so this is I_{a0} . So, leaving this terminal, but it will be $3Z_f I_{a0}$ will be there because V_{a0} is equal to $V_{a1} + 3Z_f I_{a0}$, so $3Z_f I_{a0}$ will come here. And here also I_{a2} this is the current path for I_{a2} . So, from this I_{a2} also will leave, and this is the current path for I_{a1} it will also leave, but this $3Z_f I_{a0}$ will come. If Z_f is equal to 0 then it will be same as before, only one is incoming and here it is all currents are outgoing.

And this is what you call this is V_{a1} is equal to V_{a2} , because if you make a KVL here this loop will go like this, it will go like this, this is your plus V_{a2} it will come like this minus V_{a1} is equal to 0. Only it will go like this, it will go like this, go like this, it will go like this, it will go like this. So, that is why V_{a1} is equal to V_{a2} . And if you make that V_{a0} is equal to $V_{a1} + 3Z_f I_{a0}$. That in this case if you make loop like this KVL you come here right, so it will be your plus your V_{a0} plus V_{a0} then this current is going so opposing. So, minus I_{a0} in to $3Z_f$ and then your minus V_{a1} is equal to 0. That means, V_{a0} will be is equal to $V_{a1} + 3Z_f I_{a0}$. And at this point or at this point $I_{a1} + I_{a2} + I_{a0}$ is equal to 0.

So, this is the equivalent circuit connection for what you call that your double lines to ground fault. So I mean here, from your intuition only you have to make the circuit connection correct. So from this condition different type of faults will be there, so accordingly you have to make it. Suppose all the conditions you have to make and accordingly you have to this thing. Different places, different way this diagram is given, but I prefer always this way. Make positive negative 0, after that look in to the equation and accordingly you try to make it.

So therefore, this is the sequence network connection for double line to ground fault. I hope this much you have understood. Now this circuit if you make equivalent I mean equivalent is there. Suppose this is this is for you only I have made it figure 6 a, this is

figure 6 a this is E_a and this is Z_1 . So, this current is going I_{a1} , now this is Z_2 the current is going here because all the summation of all this current is 0. So, this is Z_2 and this is your and this is I_{a0} and this is Z_0 and $3Z_f$ they are in series. So, Z_0 $3Z_f$ this current is there. That means, your this two are in parallel that your what you call that negative sequence and zero sequence, but here Z_0 plus $3Z_f$ these two are in parallel.

We suggest also that V_{a0} is equal to your this thing what you call that your this positive sorry this negative sequence and this zero sequence this two are in parallel. So, that means from here this two are in parallel. So, their equivalent will be Z_2 in to Z_0 plus $3Z_f$ divided by Z_2 plus Z_0 plus $3Z_f$. That means, your this equation also I have written that is why that V_{a0} is equal to V_{a2} plus $3Z_f I_{a0}$, this is because V_a earlier this we have we have made it that V_{a1} is equal to your V_{a1} is equal to V_{a2} ; this one we have made it.

That means, V_{a0} instead of V_{a1} we can write also V_{a2} plus $3Z_f I_{a0}$. That means, this suggest that your negative sequence and your zero sequence they are in parallel, but here fault impedance will be there. If Z_f is 0 then $3Z_f$ (Refer Time: 11:54) will not be there. So, here they referring to your equation 33. That means, my I_{a1} is equal to your E_a divided by this Z_1 plus the parallel combination of this Z_2 into Z_0 plus $3Z_f$ divided by Z_2 plus Z_0 plus $3Z_f$. This is equation 36.

Similarly if you apply KVL in this loop this circuit is the simplest version of this one right; equivalent version of this one same circuit but drawn. If you apply KVL in this loop so it will be $Z_1 I_{a1}$ minus your $Z_2 I_{a2}$ minus E_a is equal to 0. That means, I am writing this from this circuit only here for such that you can understand easily.

(Refer Slide Time: 12:53)

(18)

Also,

$$Z_1 I_{a2} - Z_2 I_{a2} - E_a = 0$$

$$\therefore Z_2 I_{a2} = Z_1 I_{a1} - E_a = -(E_a - Z_1 I_{a1})$$

$$\therefore I_{a2} = -\frac{(E_a - Z_1 I_{a1})}{Z_2} \quad \dots (37)$$

Similarly,

$$Z_1 I_{a1} - (Z_0 + 3Z_f) I_{a0} - E_a = 0$$

$$\therefore (Z_0 + 3Z_f) I_{a0} = -(E_a - Z_1 I_{a1})$$

$$\therefore I_{a0} = \frac{-(E_a - Z_1 I_{a1})}{(Z_0 + 3Z_f)} \quad \dots (38)$$

That means your $Z_1 I_{a1} - Z_2 I_{a2} - E_a$ is equal to 0. That means, from simply the simplification I_{a2} is equal to minus in bracket $E_a - Z_1 I_{a1}$ by Z_2 this is equation 37. Similarly, in this circuit again here in this you made this. That means, KVL this second one. $Z_1 I_{a1}$ right minus I_{a0} in bracket in to $Z_0 + 3Z_f$ minus E_a is equal to 0. If you do so then same I am writing $Z_1 I_{a1} - Z_0 + 3Z_f$ in to I_{a0} minus E_a is equal to 0. That means, open simplification I_{a0} will be minus in bracket $E_a - Z_1 I_{a1}$ divided by $Z_0 + 3Z_f$. This is equation 38.

So, this way one has to solve, when data will be given and how things can be solved that through numericals we will see. But only before moving to that I would like to tell that particularly the positive sequence negative sequence and zero sequence component when you consider for a problem and fault has occurred this problems are little bit of; I will say that little bit of complexity is involved and little bit of long I mean lengthy. But will take few examples and will show you how things can be solved.

That means so far we have studied line to line fault, line to ground fault, and what you call double line to ground fault and all the expression. I hope you have understood this, but only if different fault is I mean some different type of fault is created so you have to generate those equations; I mean and accordingly you have to draw the sequence network.

(Refer Slide Time: 14:41)

Open Conductor Faults.

Fig. 7 shows transmission line with one conductor open,

Fig. 7: One conductor open (phase-a)

From Fig. 7,

$$V'_{bb} = V'_{cc} = 0 \quad \dots (39)$$

$$I_a = 0 \quad \dots (40)$$

Next is that open conductor fault. These are although very very rare very rare, but suppose open conductor broken conductor; open conductor is broken conductor. Suppose this is the figure 7: you have a phase a b c, current flowing through this were I_a I_b I_c , but suddenly in phase a suppose conductor is open. So, what we are doing is we are marking F F dash, then b b dash and c c dash. So, one conductor you open that is phase a conductor is open.

So in that case, as this is a continue as this is a there is no broken part here there be b and b dash point is common, c and c dash point common; that means, your V_{bb} dash is equal to V_{cc} dash is equal to 0. This is equation 39, because b and b dash actually common point c c dash common point, so no broken part here in phase b and c. So, V_{bb} dash is equal to V_{cc} dash is equal to 0 this is equation 39. And this phase a conductor is broken, so I_a is equal to 0. So, I_a is equal to 0 these are the boundary conditions.

(Refer Slide Time: 15:56)

(20)

In terms of symmetrical components, these conditions can be expressed as:

$$\begin{bmatrix} V_{aa'1} \\ V_{aa'2} \\ V_{aa'0} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & \beta & \beta^2 \\ 1 & \beta^2 & \beta \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} V_{aa'} \\ V_{bb'} \\ V_{cc'} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & \beta & \beta^2 \\ 1 & \beta^2 & \beta \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} V_{aa'} \\ 0 \\ 0 \end{bmatrix}$$

$$\therefore V_{aa'1} = V_{aa'2} = V_{aa'0} = \frac{1}{3} V_{aa'} \quad \dots (41)$$

and $I_{a1} + I_{a2} + I_{a0} = 0 \quad \dots (42)$

Eqns (41) and (42) suggest a parallel connection of sequence networks


Now this one if you put in symmetrical component we can write like this in terms of this. This equation always known to you, we can write it write down $V_{aa'1}$ positive sequence, $V_{aa'2}$ that is conductor open conductor cases. Then $V_{aa'2}$ then $V_{aa'0}$ positive negative zero sequence component is equal to one-third, because we are we are taking the voltage $V_{aa'}$; $V_{aa'}$ is equal to $V_{aa'1}$ plus $V_{aa'2}$ plus $V_{aa'0}$.

That means, it is equal to one-third, $1 \beta \beta^2$, $1 \beta^2 \beta$ $1 1 1$ this are known to you; into $V_{aa'}$ $V_{bb'}$ $V_{cc'}$. Now we are doing now $V_{aa'1}$ $V_{aa'2}$ $V_{aa'0}$ is equal to this matrix into $V_{aa'}$ $V_{bb'}$ $V_{cc'}$, here also because of open conductor that $V_{aa'}$ $V_{bb'}$ $V_{cc'}$ $V_{cc'}$, but $V_{bb'}$ and $V_{cc'}$ is both are 0, here 0 because of this one $V_{bb'}$ this two are zero from equation 39.

Therefore, we can write this is a zeros we can write then $V_{aa'1}$ is equal to $V_{aa'2}$ is equal to $V_{aa'0}$ is equal to one-third $V_{aa'}$; this is equation 41. The reason is very simple: $V_{aa'1}$ is equal to one-third $V_{aa'}$, $V_{aa'2}$ is equal to one-third again $V_{aa'}$, and $V_{aa'0}$ is equal to one-third again here as because this two are 0. So, this all are equal. This all are equal suggest it is a parallel connection. And $I_{a1} + I_{a2} + I_{a0} = 0$ because phase conductor a has broken or open. That means, I_{a1} is equal to 0 I_{a2} is equal to 0 means your $I_{a1} + I_{a2} + I_{a0} = 0$. This equation 42

From this you have to draw the; that means, this equation 41 and 42 this equation this two suggest a parallel connection of sequence network as shown in figure 8; that means next figure. That means, they are connected parallel and some of this current positive negative and zero sequence is 0. That means, this is your say I make it.

(Refer Slide Time: 18:14)

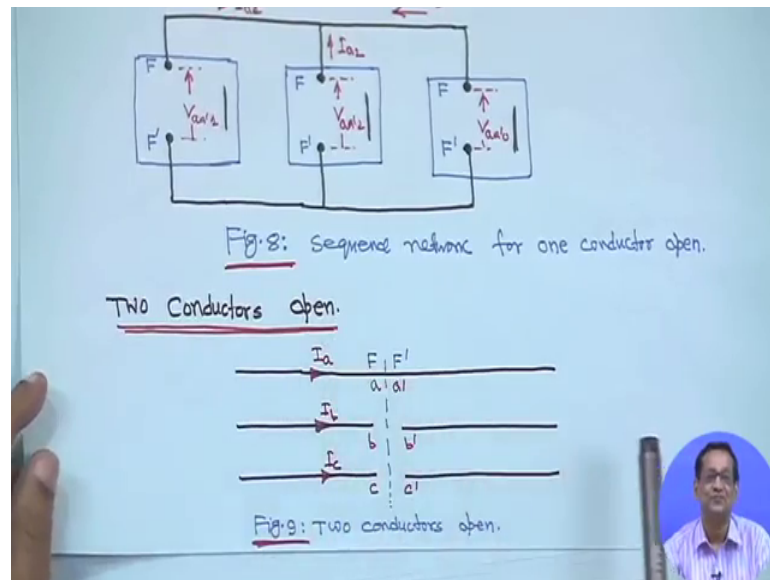

Because the conductor open, open conductor only, so this is suppose F F dash F F dash F F dash right, this is for phase a. Why you are making F F dash, because phase a conductor has open positive negative and zero sequence that is why F F dash. That is why it is your F F dash your. I mean if you want you can make a line like this that conductor open F F dash and here also right. So, in that case this F F dash for positive sequence negative sequence zero sequence all voltage are in all parallel, because all voltages are same right and all the sum. And from here current is I_{a1} from here current is I_{a2} , from here current is I_{a0} because I_a is equal to 0, so at this is the meeting point. So, $I_{a1} + I_{a2} + I_{a0} = 0$ (Refer Time: 19:07) of first law. And this is the sequence network for one conductor open.

So, things are very simple only from that fault condition you have to write those equations boundary conditions. And then you easily you can mathematically you can manipulate and you can easily construct the positive negative and zero sequence cancel. Then one more: that two conductors open. Suppose phase b and phase c both conductors are open. So, it is a a dash, then b b dash and c c dash, but phase b and phase c

conductors are open. That means, I_b is equal to 0 I_c is equal to 0 right and this is a continue this is your V_a dash it will be 0, because there is no broken path here a and a dash common point, so V_a dash is equal to 0. And I_b is equal to 0, I_b is equal to 0; this are actually boundary condition.

(Refer Slide Time: 20:12)

From Fig.9, we can write

$$V_{aa'} = 0 \dots (42)$$

$$I_b = I_c = 0 \dots (43)$$

In terms of symmetrical components, we can write,

$$V_{a1} + V_{a2} + V_{a0} = 0 \dots (45)$$

and

$$I_{a1} = I_{a2} = I_{a0} = \frac{1}{3} I_a \dots (46)$$

Eqns. (45) and (46) suggest a series connection of sequence networks as shown in Fig. 10.

So, from this figure boundary condition we can write that V_a dash is equal to 0 I_b is equal to I_c is equal to 0. So, in terms of symmetrical component you that V_a dash is equal to 0 means V_a dash 1 plus V_a dash 2 plus V_a dash is equal to 0: 45. This is positive negative and zero sequence components. And I_b is equal to I_c is equal to 0 and same way if you go for symmetrical component I_a not putting it here now you have understand everything you will get I_{a1} is equal to I_{a2} is equal to I_{a0} is equal to one-third as it all I_{a1} I_{a2} I_{a0} is equal to one-third I_a all are same.

That means this condition suggest actually a series connection because I_{a1} is equal to I_{a2} is equal to I_{a0} , when currents are same it is suggested series connection. So, if it is a series connection this is your F F dash F F dash: F F dash I have told you earlier also. Series connection means this is your positive, positive to negative, than positive to negative, than positive to negative. And this is your positive sequence, this is your negative sequence, and this is your zero sequence connection. So, it is I_{a1} I_{a2} is equal to I_{a1} I_{a0} is equal to I_{a1} because all are same that is one-third I_{a1} . This is equation 46.

So, this is actually sequence network for two conductors open. So, although this are very rare phenomena, but for the sake of completeness I took this one. And even simultaneous occurrence of I told you suppose line to ground fault that is same time double line to line fault very rare, but will see. I think we have taken one problem later on that will see.

(Refer Slide Time: 22:11)

Ex-1:

Fig. 11 shows a sample power system. Before the occurrence of a solid L-G fault at line (g), the motors were loaded. If the prefault current is neglected, calculate the fault current and subtransient currents in all parts of the system.

Fig. 11

DATA \Rightarrow Same as Ex-4 of the previous topic, Symmetrical Component.

Now what will do that this example actually we have taken from your previous symmetrical component. Because then it will be easy for you to understand right.

(Refer Slide Time: 22:25)

Ex-4

A 50 MVA, 11 kV, synchronous generator has a subtransient reactance of 20%. The generator supplies two motors over a transmission line with transformers at both ends as shown in Fig. 9. The motors have rated inputs of 30 and 15 MVA, both 10 kV, with 25% subtransient reactance. The three phase transformers are both rated 60 MVA, 10.8/11 kV, with leakage reactance of 10% each. Assume zero-sequence reactances for the generator and motors of 6% each. Current limiting reactors of 2.5 Ω each are connected in the neutral of the generator and motor No. 2. The zero sequence reactance of the transmission line is 300 Ω . The series reactance of the line is 100 Ω . Draw the positive, negative and zero sequence networks.

This example actually is the same example four of that your symmetrical component; details have been given there. This is the same problems same problem is taken.

(Refer Slide Time: 22:34)

Assume that the negative sequence reactance of each m/c is equal to its subtransient reactance. (53)

Fig. 9: Circuit diagram of Ex-4

Soln.

Assume base power = 50 MVA, Base Voltage = 11 kV
 Base Voltage of transmission line = $11 \times \frac{121}{10.8} = 123.2 \text{ kV}$
 Motor base Voltage = $123.2 \times \frac{10.8}{121} = 11 \text{ kV}$
 Transformer reactance,
 $X_{T1} = X_{T2} = 0.10 \times \left(\frac{50}{60}\right) \times \left(\frac{10.8}{11}\right)^2 = 0.0805 \text{ pu}$

And same diagram and that same diagram everything all data are also same all the data are available in that in this problem all the data or whatever data we have made it.

(Refer Slide Time: 22:44)

Ex-1: (54)

Line reactance (positive and negative sequence)
 $= \frac{100 \times 50}{(123.2)^2} \text{ pu} = 0.33 \text{ pu}$

Line reactance (zero sequence)
 $= \frac{300 \times 50}{(123.2)^2} = 0.99 \text{ pu}$

Reactance of motor-1 (positive and negative sequence)
 $= 0.25 \times \left(\frac{50}{30}\right) \times \left(\frac{10}{11}\right)^2 = 0.345 \text{ pu}$


Zero sequence reactance of motor-1
 $= 0.06 \times \left(\frac{50}{30}\right) \times \left(\frac{10}{11}\right)^2 = 0.082 \text{ pu}$

For example four of symmetrical component, I have taken the same data all data are same such that it will save time, it will help us to understand this. So, this same problem same diagram we have taken. So, all data remain same of example four of the

symmetrical component. And there is a fault that point g that is solid line to ground fault, when it is telling solid line to ground fault means that fault impedance is 0. Now we have to find out that current supplied by the generator by the motor and how things will happen. So, all the parameters are same. Now when you will see that data of this problem, but still I have brought that previous one that motor terminal voltage was 10 kv.


Now fault actually has happened to the motor side; this motor side. And that is why here it is written data same as example four of the previous topic that is symmetrical component, you have all the data. Now if it is so and fault has occurred here fault has occurred at point g. Now if it is so first I will show you the diagram then the connection. So, this positive: just hold on this positive negative and zero sequence diagram for this network was given was shown to earlier.

(Refer Slide Time: 24:14)

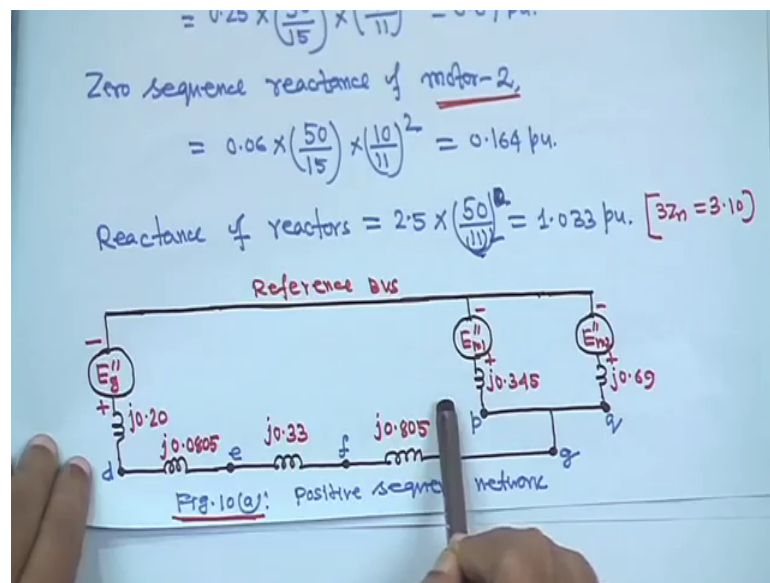


This is your positive sequence one, earlier I told you how to make it with all the voltage sources everything will be there positive it is by and all the positive sequence impedance.

(Refer Slide Time: 24:21)

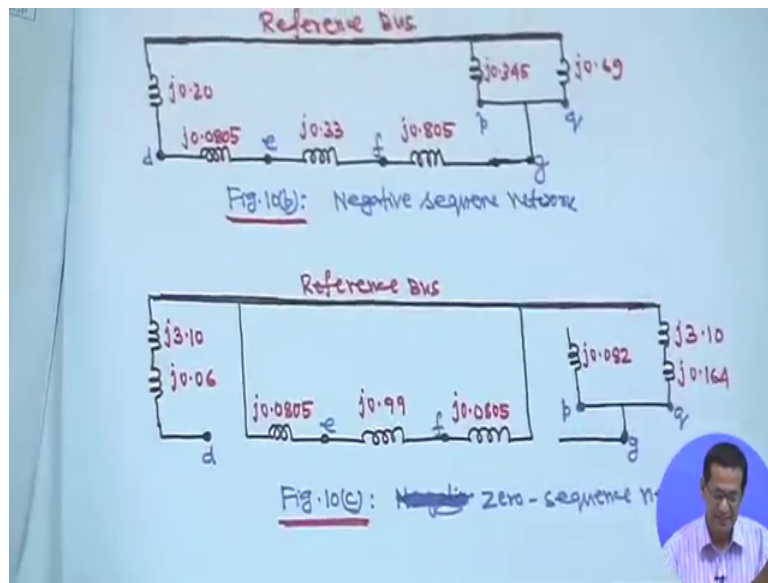

Negative sequence parameters are same, but only there is no voltage source. And all the zero sequence also this has been shown; that how it has been drawn has been explain in detail; so same network and same diagram. Now there is a point that fault has occurred. I mean there is a point here that is your near motor terminal this side there is a point here; suppose this is your g that means in this diagram that is p q and g things are there. So, in this diagram that is there is a point at g this is g at this point fault has occurred. So, in this case that this is the point g say that fault has your occurred fault has occurred line to ground fault solid line to ground fault has occurred.

(Refer Slide Time: 25:19)

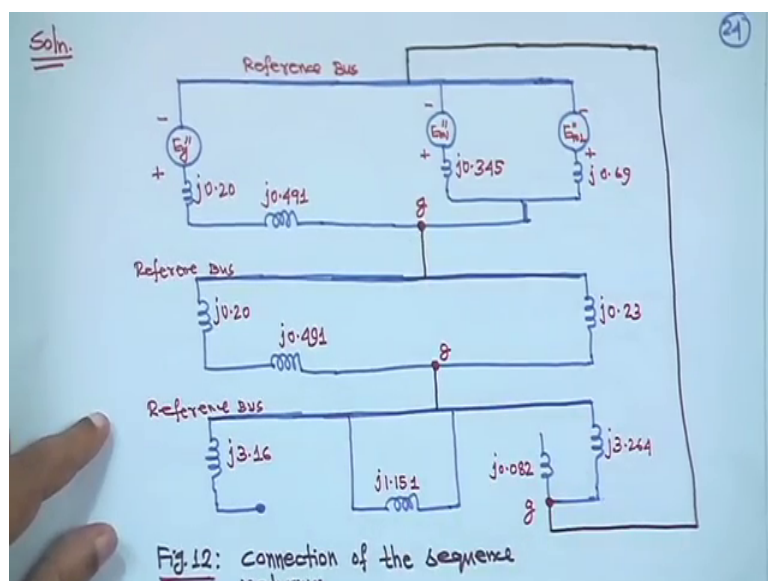

So, in this case what will happen that then how to connect. Now that this is your same positive sequence network of example four, same negative, same zero sequence. So, in this the fault has occurred here, this is reference bus, this is reference bus, this is reference bus. So, fault has occurred here, so make this ground to the reference bus of the that your negative sequence network and here also ground to reference network, and then here also this is this is your g point rather g point; g point to reference network and this is g point and it will go to the your reference bus.

So, this point is a g. That means, in this what you call this point is g; the fault has occurred here line to ground fault has occurred here. That means, this is my point g, they connected to the reference bus, then g connected to the reference bus, and this is also g connected to the reference bus. Before solving this problem that when you solve it using equation per three phase. For three phase fault we have made that pre fault voltage taken out and equivalent Thevenin representation. Three phase fault only our objective was to see that your Z bus will link algorithm, although little bit complicated and some problem few problems for solving this. But more emphasis we have given here symmetrical component and unbalanced fault.

So, in this case if you look at that that you have to find out what is the pre fault voltage because motor side fault has occurred. So, its voltage was 10 kv; that will see later. Now question is that if you look in to that that zero sequence network same network right that your zero sequence current actually will flow up from the motor side, because that this is your there are three motors: one is what you call ungrounded and another this one is your what you call this is better this one. If you take this one this one this is star connected this is star connected and this is through some impedance till grounded. So, here also I have missed that it is star connected, but ungrounded.

So, here that means this zero sequence diagram that it is connected to the reference if you see the circuit is computed, but if you look at the generator side right because of the isolation star is grounded but delta is here, so there is an isolation. That means, from the generator side there be no zero sequence current, but from the motor side there will be what you call there will be zero sequence current right. That means, when you will solve this all the zero sequence current by whatever it is it will flow from the motor side, because you see it is getting a path, it is getting a path, it is getting a path like this, but

this side there is isolation. So, no current will flow from the generator side. This you have to judge looking at the zero sequence network.

That means if you make only your Thevenin equivalent from the for the positive sequence network.

(Refer Slide Time: 28:34)

$$E_g'' = E_{m2}'' = E_{m2}'' = V_f^0 = \frac{10}{11} = 0.909 \text{ pu.}$$

Thevenin equivalent of positive sequence network is shown in Fig. 13.

$$Z_1 = \frac{j(0.491+0.20) \times 0.23}{(0.491+0.20) + 0.23} = j0.172 \text{ pu}$$

$$Z_2 = Z_1 = j0.172 \text{ pu}$$

$$Z_0 = j3.264 \text{ pu}$$

Fig. 13: Thevenin equivalent of positive sequence network of Fig. 12.

So, motor side voltage was 10 kv, so pre fault currents are neglected. So, we can say E_g'' is equal to E_{m1}'' is equal to E_{m2}'' is equal to V_f^0 is equal to 10 by 11 0.909 per unit. But motor side terminal voltage 10 kv base k V we have taken 11, so 0.909. So, this is my your V_f^0 this thing.

And next is this all this thing sum of this two and take the equivalent of this parallel point 0.345 and 0.69 j take this equivalent, its equivalent will be actually j 0.23. And this side is point j 0.20 j 0.491 we have to add this two and take the equivalent. If you take then Z 1 will become j 0.172 per unit and Z 2 is equal to Z 1 will be j 0.172 per unit and Z 0 is equal to j 3.264 this is the j 3.2 this. All this parameters have been computed for example, four in symmetrical component. So, all parameters we are taking. Other this one, this one, this one, will not be equaled for that kind of fault where fault had occurred at your what you call point g. And this is the Thevenin equivalent.

Now that means, similarly this one also this two were and this are there make equivalent parallel and this one in this case only j 3.264 will come. So, if you make that equivalent

circuit. So, this equivalent is coming your Z 2 is equal to Z 1 is equal to this one and this is this one.

(Refer Slide Time: 30:16)

The image shows handwritten calculations and a circuit diagram. The calculations are as follows:

$$\therefore I_{a1} = \frac{V_f^0}{(Z_1 + Z_2 + Z_0)}$$

$$\therefore I_{a1} = \frac{0.909 \angle 0^\circ}{j(0.172 + 0.172 + 3.264)}$$

$$\therefore I_{a1} = \underline{-j0.252 \text{ pu}}$$

$$\therefore I_{a1} = I_{a2} = I_{a0} = \underline{-j0.252 \text{ pu}}$$

Fault current = $3I_{a0} = 3 \times (-j0.252) = \underline{-j0.756 \text{ pu}}$

The circuit diagram shows a series circuit with three reference buses (Ref. Bus) connected by impedances. The top bus is at potential V_f^0 . The impedances are $j0.172$, $j0.172$, and $j3.264$. The current I_{a1} is shown flowing downwards through the circuit. Below the diagram, it is noted that $I_{a1} = I_{a2} = I_{a0}$.

So, equivalent circuit will be this one. This is reference bus, reference bus, this is $j 0.172$ $j 0.172$ and $j 3.264$ and I_{a1} is equal to I_{a2} is equal to I_{a0} . So, in that case I_{a1} will get V_f^0 on Z_1 plus Z_2 plus Z_0 . So, substitute all these. If you substitute all this then you will get I_{a1} is equal to minus $j 0.252$ per unit.

And I_{a1} is equal to I_{a2} is equal to as all are same right; I have not shown here, but this is I_{a1} , this is I_{a2} , this is I_{a0} series circuit all are same; that means, your this will be minus $j 0.252$. Now fault current will be $3 I_{a0}$; that is your 3 into minus j your 0.252 . That means, it is minus $j 0.756$ per unit. So, this way this what you call this way you have to solve that zero sequence your positive sequence negative sequence at zero sequence you have to understand and then only you can apply that how are why fault has occurred. And accordingly you have to see that how all parameters are computed correctly. And then you can easily solve that what will be my fault current.

Thank you, again we will be back.