

Analog Integrated Circuit Design
Prof. Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology, Madras

Lecture - 47

Type I PLL Loop Gain and Transfer Function Reference feed Through

Hello and welcome to lecture forty seven of analog integrated circuit design. In the previous lecture, we looked at how to implement a phase detector, and the kind of non ideal characteristics that appear, that is there will be a periodic error in addition to the measurement of phase that is why in this lecture what we will do just to evaluate the effect of that that will also give us some practice in the kind of analysis that is relevant for a phase lock cube that is to measure the incremental phase error at the output and see what its effect is and then we will see that there are some shortcomings of type one phase lock cube and then we will see how to improve on the structure of the phase lock cube.

(Refer Slide Time: 00:50)

Lecture 47 3 state phase detector:

* Average output = $\frac{V_{pd} \Delta\phi}{2\pi} K_{pd}$


* Periodic error (input referred) = 2π [Diagram showing a square wave with a shaded area representing error]

peak-peak = 2π

duty cycle = $\frac{\Delta\phi}{2\pi}$

We saw that, the phase detector that we implemented. It has an average output which is, proportional to delta five or the difference in the phase between its two inputs in this V p d by 2 pi is nothing but, the gain of the phase detector, but there is also a periodic error, which when referred to the input will have a peak to peak value of 2 pi, and it will have an average value of 0 that is the positive and negative areas are equal, and the duty cycle would be delta five divided by 2 pi. So, this is the periodic error that gets added to, the input of the phase detector just because of the way, the phase detector is implemented.

(Refer Slide Time: 02:29)

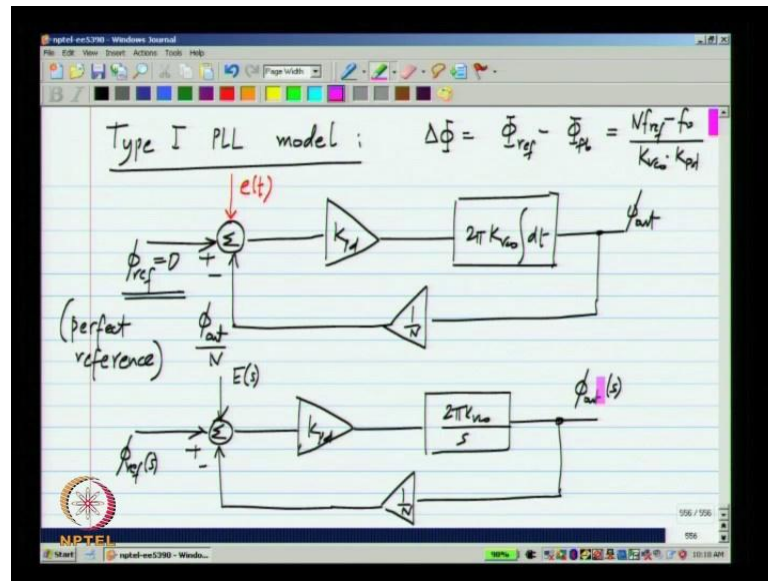

Now, let us put this in the incremental model of the phase lock loop. We have evaluated this, any input phase increment is ϕ_{ref} , and here we have a gain of K_{pd} and the VCO, which basically integrates the control voltage to result in the output phase, and the feedback divider is simply an attenuation of 1 by N . Now the additional thing we have because of the way the phase detector is implemented is a periodic error $e(t)$, which I described as earlier, it has zero average and a duty cycle of $\Delta\phi$ by 2ϕ , where $\Delta\phi$ is the operating point.


Phase difference it is not in the incremental domain there is operating point phase difference between the input and the feedback phases, and that will be equal to the difference between the output frequency and the free running frequency of the VCO divided by the gain of the VCO, and the gain of the phase detector. So, now, what do we do with model such as this we have a periodic error $e(t)$, and what this says is that the output incremental phase ϕ_{out} will not be 0 even if ϕ_{ref} is 0 now, what is the meaning of ϕ_{ref} being 0 ϕ_{ref} this ϕ_{ref} here the lower case ϕ_{ref} refers to the phase error compared to the ideal ramp.

As you know, the phase ref of the periodic signal will be an ideal ramp, if it is perfectly periodic, but in general it will have some error, but in this case if we set ϕ_{ref} is equal to 0, it means that, we are operating using a perfectly periodic input, but ϕ_{out} will not be 0 because $e(t)$ is not 0. So, what does this mean even with a perfectly. Periodic input

the output of the phase lock loop will not be perfectly periodic. So, we have initially done the analysis with this e of t set to 0. So, in that case the output will be periodic at n times f_{rep} now, we will insert e of t and assuming that errors are small.

We can calculate the error from this and add it to our previous result. So, the thing is to calculate ϕ_{out} from v of t and ϕ_{ref} will be set to zero. So, this as I said means a perfect reference. Now, that we have the system diagram, we can calculate the output for any input, but we can do it in a simple way while making some assumptions about e of t . So, if I put down the Laplace domain model, everything will be exactly the same except that the integrator will be replaced by $2\pi K_{pd} K_{vco}$ by s , and this could be some input and this could be some output, and that will be the output. So, we can calculate the transfer function from here to there, and it is exactly the same as the transfer function from ϕ_{ref} to ϕ_{out} .

(Refer Slide Time: 06:58)

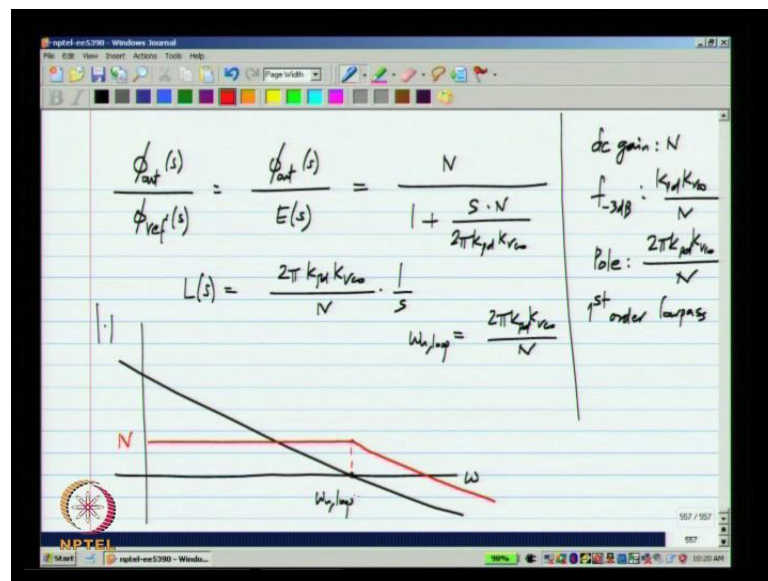

This is of course, assuming that each of this is acting one at a time and that will be equal to, it will be low pass transfer function with a d c gain of n and a three d b frequency in hertz of $K_{pd} K_{vc}$ divided by n . So, the pole is at $2\pi K_{pd} K_{vc}$ by n . So, it is a first order low pass transfer function, and the loop gain of this feedback loop, we have discussed loop gain extensively while talking about op amps and other feedback circuits. So, I will simply assume that you know the results.

So, the loop gain is you break the loop and you go around and see what is the gain, and that will be $2\pi K_p d K_v c o b y n 1 b y s$. So, if I now plot the magnitude response versus ω on a log scale, the magnitude response of the loop gain will be something like this, where this is the unity loop gain frequency, and if I plot ϕ out by ϕ ref it will have a d c gain of n , and after that twenty degree per decade roll off, and the unity loop gain frequency will be the three d b bandwidth of the system.

(Refer Slide Time: 09:38)

The whiteboard content includes the following mathematical expressions and a block diagram:

$$\frac{\phi_{out}(s)}{E(s)} = N \cdot \frac{L}{1+L} = N \cdot \frac{1}{1+1/L}$$

$$\approx N \quad |L| \gg 1$$

$$\approx N \cdot L \quad |L| \ll 1$$

Assuming $f_{cF} > f_{-3dB}$, the feedback is negligible

The block diagram shows a summing junction with a disturbance signal $c(t)$ and a feedback signal $\phi_{out}(t)$. The forward path consists of a gain block K and an integrator block $\frac{2\pi K_{vo}}{s}$.

Now, we have seen earlier that the close loop gain of a feedback system can be expressed as in this particular case n times loop gain by one 1 loop gain or in other words also n times one by $1 + 1$ over L , and we know that, this is approximately equal to n , where the magnitude of the loop gain is very large, and approximately equal to n times L , where the magnitude of the loop gain is very small. We have seen all of these things, what does it mean, if the magnitude of the loop gain is very small, we can simply neglect the feedback for the fit.


We assume that nothing is coming back, and the gain from here to there will be simply the gain of the forward path. It will be the product of E of s $K_p d 2\pi K_v c o b y s$ that will be the output. So, now, this E of s itself, it is a rectangular wave at a frequency of f_{ref} . So, that is what E of t is, now, what does this mean, it will have f_{ref} and its harmonics.

So, now, the calculation becomes very easy, if we assume that f_{ref} is well beyond this unity loop gain frequency or the three dB bandwidth of the system, in that case the feedback is negligible, what I am trying to say here is that $E(t)$ is a periodic signal in the frequency of f_{ref} .

So, that means that it will have f_{ref} in its harmonics, and if f_{ref} is higher than the three dB bandwidth of the system or the unity loop gain frequency of the system, then all the frequency components of the system for $E(t)$ will be beyond the unity loop gain frequency; that means, that for these frequencies there will be negligible feedback, and we can compute the output by simply considering the forward path and completely neglecting the feedback. So, that makes the things a lot easier and that is what we are going to do.

So, approximately, we can calculate the effect of $E(t)$, I am assuming ϕ_{ref} is 0 that is a perfect reference by considering only the forward path. So, this part I will show just to show that I have neglected the feedback. So, I have K_p and $2\pi K_v \int$ versus time. So, all that I need to do is to calculate ϕ_{out} as a result of this path, now, $e(t)$ is a rectangular wave. So, all I have is the integral of the rectangular wave with some proportionality constant, which can be very easily evaluated.

(Refer Slide Time: 13:26)

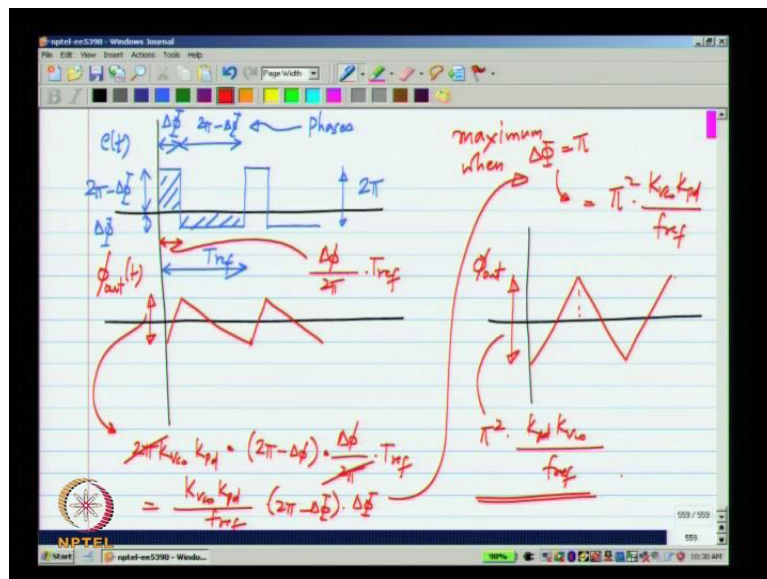

As usual, I suggest that you take it as an exercise and do it yourself, pause the video at this point, and then compare it to the result that I derived. So, here I have shown two

cycles of e of t . Now this is going through an integrator, what does it mean, the output will rise during this part when e of t is positive, and it will fall during that part, when e of t is negative, and also, we know that, this area equals that area. So, the amount of rise equals the amount of fall, this would have to be the case anyway because the system is in steady state, otherwise this quantity ϕ out will be continuously increasing or decreasing.

So, this is what it looks like, this is ϕ out of t and it will be some sort of triangular wave whose peak to peak value equals the area under the positive part of e of t times the proportionality constant $2\pi K_v c_o$ times $K_p d$. Now, for e of t , we know that, the peak to peak value is 2π and the duty cycle is $\Delta\phi$ divided by 2π , and you can calculate it very simply to show that, this has to be 2π minus $\Delta\phi$ and that has to be $\Delta\phi$.

So, here again $\Delta\phi$ refers to the phase difference between the reference and feedback at the operating point. So, you can clearly see that, 2π minus $\Delta\phi$ times $\Delta\phi$ that is the positive area equals $\Delta\phi$ times 2π minus $\Delta\phi$, which is the negative area. So, the peak to peak value here will be simply $2\pi K_v c_o K_p d$, which is the proportionality constant times this height, which is 2π minus $\Delta\phi$ times this width by the way what I have shown here is in terms of phases, but what I need here is width in terms of time, and we know that phase shifted 2π corresponds to t_{ref} .

So, that is t_{ref} . So, this duration is nothing but, $\Delta\phi$ divided by 2π times t_{ref} . So, what I have here will be $\Delta\phi$ divided by 2π times t_{ref} . So, this can in turn be written as this goes away and t_{ref} is one over f_{ref} . So, the phase error and the output due to the periodic error in the phase detector is a triangular wave whose peak to peak value is given by this expression $K_p d$ times $K_v c_o$ divided by f_{ref} times 2π minus $\Delta\phi$ times $\Delta\phi$. So, this clearly depends on $\Delta\phi$ but, we can easily see that, this is maximum, when $\Delta\phi$ equals π .

So, this term is increasing as $\Delta\phi$ decreases, and this term is increasing as $\Delta\phi$ increases, the two will be equal, when $\Delta\phi$ equals π , and at that point for this value this will be equal to $\pi^2 K_v c_o K_p d$ times f_{ref} . So, in that case also the duty cycle of this will be fifty percent, and this ϕ out of t will be a triangular wave, which is symmetrical.

So, now, that we have calculated phi out of t then what, what we need to do is to look at what the output should be in the ideal periodic case, and look at what it will be with the addition of phase error phi out, and see what the effect is. In fact, this kind of calculation will appear repeatedly in phase lock loops and in general wherever you are looking for periodic signals.

(Refer Slide Time: 19:05)

Output signal:

ideal case: $\cos(2\pi N f_{ref} t + \Phi_{out})$ Periodic in t: period of $\frac{1}{N f_{ref}}$

with phase error $\phi(t)$: $\cos(2\pi N f_{ref} t + \Phi_{out} + \phi(t))$ Not periodic in t

$\cos(A+B) = \cos A \cos B - \sin A \sin B$

$\cos(2\pi N f_{ref} t + \Phi_{out}) \cdot \underbrace{\cos(\phi(t))}_{\approx 1} - \sin(2\pi N f_{ref} t + \Phi_{out}) \cdot \underbrace{\sin(\phi(t))}_{\approx \phi(t)}$

If $|\phi(t)| \ll 1 \text{ rad}$

What is the output signal in the ideal case, it is just a periodic signal, again I will show it as cosine, but I will emphasize that the pulse shape can be anything, the wave shape can be anything, cosine plus some arbitrary phase phi out. Now, with the phase error phi of t what you get is. Now, clearly this function is periodic in t with a period of 1 over n f ref, and this is in general not periodic in t, if phi of t is not zero.

So, what we will think of it as an ideal periodic signal plus some error, and that can be got by expanding this, we know that cosine a plus b is cosine a cosine b minus sine a sine b. So, this whole thing will be, and if the magnitude of phi of t is very small compared to 1 radian, what happens for very small values phi of t, this part is approximately equal to 1, and this part is approximately equal to phi of t.

(Refer Slide Time: 21:58)


$$\cos(2\pi N f_{ref} t + \Phi_{out}) \cdot \underbrace{\cos(\phi(t))}_{\approx 1} - \sin(2\pi N f_{ref} t) \cdot \underbrace{\sin(\phi(t))}_{\approx \phi(t)}$$

If $|\phi(t)| \ll 1 \text{ rad}$

$$\approx \underbrace{\cos(2\pi N f_{ref} t + \Phi_{out})}_{\text{ideal periodic output}} - \underbrace{\phi(t) \sin(2\pi N f_{ref} t)}_{\phi(t) \text{ modulating a carrier at } N f_{ref}}$$

So, what we finally get, in presence of a phase error is this, we will get this to be this is the ideal periodic signal that we would have got plus an error, and what is this error this is a signal which is again periodic at frequency n times f_{ref} , and this ϕ of t this phase error modulating that carrier. Now, there are two ways to characterize a signal that is almost periodic, but not exactly. So, and this is just like any other signal, we can do it in time domain or in the frequency domain. So, in the time domain it is characterized simply by this phase error ϕ out of t , ideally this ϕ out of t is 0 in reality, it is not zero, and this leads to the description of aperiodicity in terms of what is known as jitter.

(Refer Slide Time: 23:43)

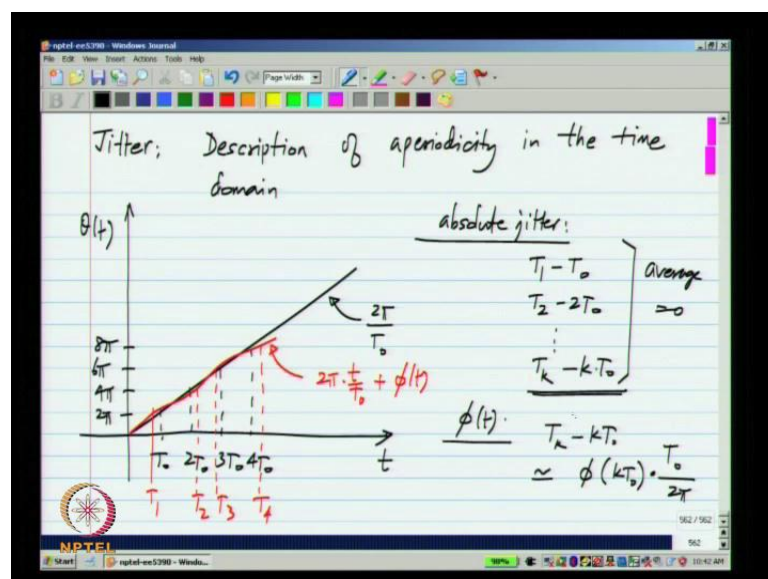


So, let me draw the phase of an ideal periodic signal it will be a ramp, and it will cross integer multiples of 2π at integer multiples of some interval T , which is the period of the periodic wave form. This is phase versus time and this will be a ramp with a slope of 2π by t . In reality, there will be some phase error and the phase may do something of this sort. What happens then, this will cross 2π at sometime T_1 , its crossing 4π at sometime T_2 , and its crossing 6π at sometime T_3 , and 8π at some T_4 and so on.

And now, ideally there is T_1, T_2, T_3 and T_4 will be integer multiples of T . In reality they will be different. The absolute jitter is nothing, but the difference between the ideal crossings of 2π and actual crossings of 2π . So, in general T_k minus K times T , and the average value of this will be 0, because the average slope of this red curve and the black curve are the same. So, the average value of the jitter numbers will be 0, sometimes this jitter will be negative and sometimes it will be positive.

Now, this jitter is directly related to the phase ϕ of t , now, what is this red curve after all, it is 2π times T by T plus 2π times the frequency of the signal times T plus this ϕ of t , and for small values of this error that is small values of jitter here to make it visible I have shown it as exaggerated number, but we can assume this to be relatively small compared to one period.

So, in that case these deviations can be approximated by the value of the phase at K times T divided by 2π . So, this ϕ is in terms of phase in radians now, we have to translate it to times. So, if you want to do that then the scaling factor of T by 2π will appear. So, the jitter values will be approximately ϕ of K times T divided by 2π there will be a minus sign over here.

(Refer Slide Time: 27:45)

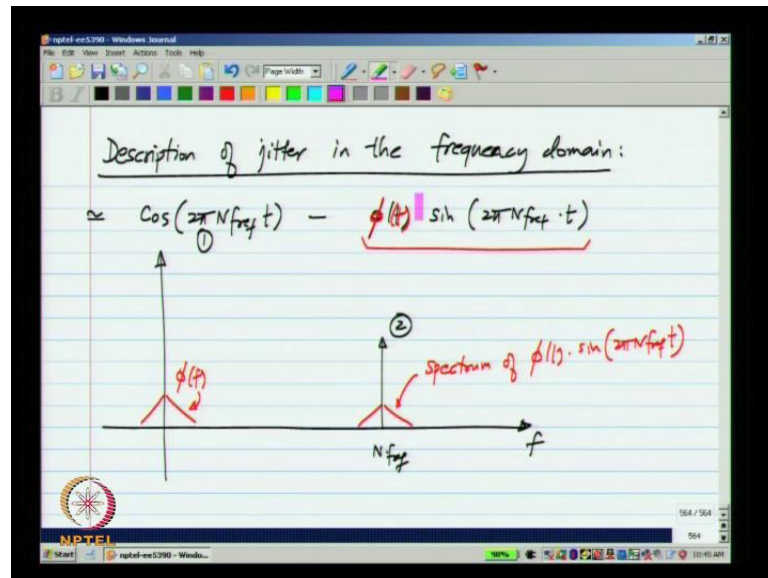

In terms of time, it will be, where this ϕ is basically the phase error that appears and this is the description of aperiodicity in the time domain its commonly used in certain kinds of applications, but in communications applications phase lock loops are used very it is also common to use jitter in the frequency domain, and now in our case we have evaluated the output to be $\cos 2\pi N_{\text{ref}} t$ minus $\phi(t) \sin 2\pi N_{\text{ref}} t$, when $\phi(t)$ is very small.


Now, what is this in the frequency domain, the first $\cos 2\pi N_{\text{ref}} t$ corresponds to an impulse at N_{ref} . So, this is the first part of it, and the second part it is $\phi(t) \sin 2\pi N_{\text{ref}} t$. Now, let me say that, $\phi(t)$ has a spectrum of the sort that is $\phi(f)$. Now, $\phi(t) \sin 2\pi N_{\text{ref}} t$ will have a spectrum that is centered around N_{ref} , because this $\phi(t)$ here is modulated to N_{ref} .

So, what is supposed to have in an impulse as an impulse and something on the side, now exactly what is on the side depends on the spectrum of $\phi(t)$, now, in our particular case, we have evaluated the effect of $\phi(t)$ to be a periodic $\phi(t)$ it is a triangular wave. So, if $\phi(t)$ is periodic; that means, the spectrum of $\phi(t)$ will consist of impulses and those impulses will also get modulated to N_{ref} and now later we will see different kinds of $\phi(t)$.

Let us say, there will be something called the v c o phase noise in which case the spectrum of $\phi(t)$ will not be a set of impulses, but some continuous function and that

continuous stuff will also get translated to n times f_{ref} . Now, this is how we interpret the result from the model of the phase lock loop. The results that you get are in terms of phase, and then you either interpret that in the time domain of the jitter or in the frequency domain as this sidebands or phase noise as the case may be.

(Refer Slide Time: 31:28)

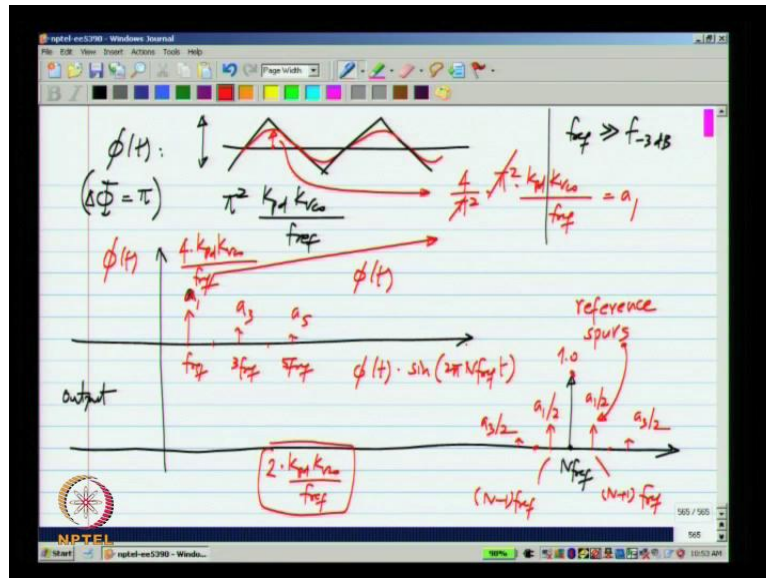

So, in our case what is $\phi(t)$ it is a triangular wave I will take 1 with the highest peak to peak value this is for $\Delta\phi = \pi$, and we know that this peak to peak value happens to be $\pi^2 K_p K_v / f_{ref}$. By the way all of these things are under assumption that f_{ref} is much more than the bandwidth and this is a very reasonable assumption as we will see soon.

Now, what will be the spectrum of the $\phi(t)$, it will consist of impulses at f_{ref} , $3f_{ref}$, $5f_{ref}$ and so on. Now, if the triangular wave is asymmetric, we will also have a component set $2f_{ref}$ and $4f_{ref}$ etc. We have considered the symmetric case or $\Delta\phi = \pi$ it will be symmetrical. Now, what will be the spectrum of the output as I said earlier, it will consist of an impulse corresponding to the $\cos(2\pi N f_{ref} t)$ and all these impulses of $\phi(t)$ will also get modulated to $n f_{ref}$.

So, we will have and so on. This will be at $n + 1$ times f_{ref} , and this will be at $n - 1$ times f_{ref} and so on. So, in general there will be at spacing of integer multiples of f_{ref} from $n f_{ref}$, which is the desired output frequency. So, what happens is if you have a periodic error the output will consist of these other sidebands in the frequency

domain, and the strength of the sideband should be limited to some value. So, that we can still think of the output as sufficiently good periodic signal, and the sidebands are known as reference spurs.

Spurs is a shorthand for spurious components, and these are the spurious components in the output, this is what should have been there, but we also get these things, but if these things are sufficiently small, the output can still be thought of as periodic. So, now, what we should do is calculate the strength of these things, and from there calculate the difference between the strength of the main output, which is supposed to be there and the strength of these spurs which is not supposed to be there, and make them sufficiently large.

And, this is something like making sure that the signal noise ratio of a signal is sufficiently large. So, that is what we have to do and how do we go about doing that we have to calculate the Fourier component triangular wave, and when you modulate it by $\sin 2\pi n_{ref} t$, what happens is half of it goes to the positive side, and half of it goes to the negative side, what I mean is let us say, this is a 1 a 3 a 5 and so on.

And, when you multiply this is the spectrum of $\phi(t)$, and when you take $\phi(t) \sin 2\pi N f_{ref} t$, what happens is you will have a 1 by 2 here a 3 by 2 there, and also a 1 by 2 there and a 3 by 2 there and so on. And, In general for any signal that you have here, you can calculate the spectrum of the modulated signal you would be very familiar with this from communication systems and so on. So, here what I will do is not calculate it exactly for all the components, but do it only for the fundamental components that is the component at f_{ref} , and you know that in general for most signals these components tend to get smaller as you take the higher order harmonics. So, that is not universally true, but in this triangular wave that is true.

Now, what is the value of a 1 you can consult some standard text books on fourier series. So, now, it turns out that the fundamental component of the triangular wave, will have a peak that is slightly less than the peak value of the triangular wave. So, it turns out that the peak value of the fundamental component of the wave will be $\frac{4}{\pi^2}$ times the peak to peak value of the triangular wave.

So, that is the peak value that is the 1. So, this you can get from some standard text book on communications or Fourier series. So, this a 1 will be $\frac{4}{\pi^2} K_p d K_v c o$ divided

by f_{ref} as a 1 by 2 will be naturally 2 times $K_p d K_v c o$ divided by f_{ref} . Now, we want this to be sufficiently small compared to the main one which has a strength of 1, this has a peak value 1, and this will have a peak value that I just now calculated a 1 by 2, and we will look for a relatively modest requirement.

(Refer Slide Time: 37:45)

$$\frac{a_1}{2} = 10^{-2} \quad \left[\text{reference spur} = 40\text{dB below the component at } Nf_{ref} \right]$$

$$2 \cdot \frac{K_p K_v}{f_{ref}} = 10^{-2}$$

$$K_p \cdot K_v = \frac{10^{-2}}{2} \cdot f_{ref} = 5 \cdot 10^{-3} \cdot f_{ref}$$

$$\text{Lock range: } |Nf_{ref} - f_o| < 2\pi \cdot K_p \cdot K_v$$

$$\pi \cdot 10^{-2} \cdot f_{ref} \quad ??$$


We will say that a 1 by 2 is 10 to the minus 2, what this means is the largest reference spur is forty d b below the component at N times f_{ref} . Now, this is a relatively modest requirement usually you like this to be sixty d b or eighty d b below the component at N times f_{ref} . Then all we have to do is plug in the numbers 2 times $K_p d$ times $K_v c o$ divided by f_{ref} should be 10 to the minus 2 or $K_p d$ minus $K_v c o$ is 10 to the minus 2 divided by 2 times f_{ref} or 5 times 10 to the minus 3 times f_{ref} .

So, this is the constraints that we get from this phenomenon, which is also known as reference speed through the output will have reference spurs to make the reference spurs sufficiently small, we need to make sure that this number is smaller than some value, and also you see that the value a 1 should be smaller than some number; that means, that the value of $K_p v$ times $K_v c o$ should be smaller than a certain number. Now, let us go back to what we had for the lock range, and the lock range was related to the product of $K_p g$ times $K_v c o$.

And now, what does this mean what was the lock range that is the difference between the output and the free running frequency was less than 2 pi times $K_p d$ times $K_v c o$. Now

I will plug the value of $K_p d K_v c o$ from here, and that comes out to be π times 10 to minus 2 times f_{ref} .

(Refer Slide Time: 40:44)

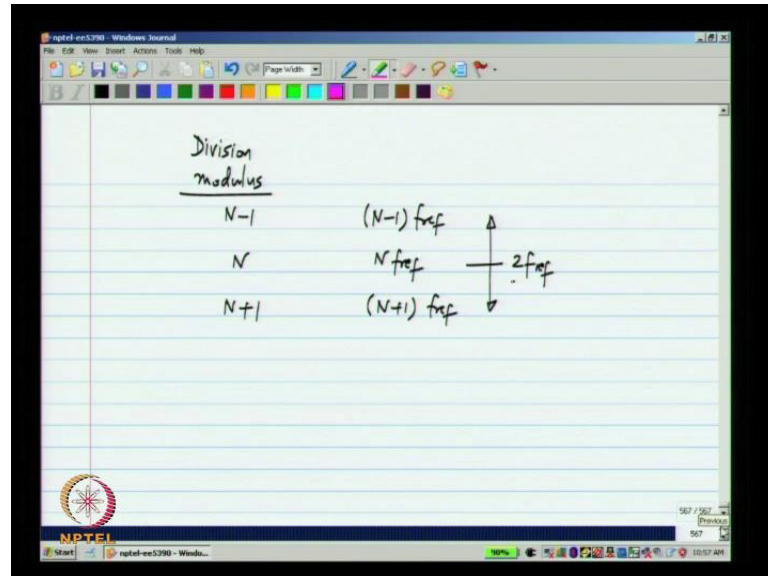

Now, what does this mean one of the things I said was that we would like to change the division module as to change the output frequency. So, if it is N , the output will be N times f_{ref} , and if the module is N plus 1 the output is N plus 1 times f_{ref} , and if this is n minus one it is n minus one times f_{ref} and so on. So, what does it mean let us say I want to move the division modulus by one in each direction.

So, the range has to be at least $2 f_{ref}$. So, between these two we have a range of 2 times f_{ref} . now the range that I am getting is much smaller than f_{ref} . So, what this means is I cannot change the value of n at all. So, let us say that for some particular value of N this $N f_{ref}$ happens to be equal to if not I will not be able to change the value of N because I will not be able to deviate more than a very small frequency so that means, that I cannot really make my frequency synthesizer.

So, I hope the result of the calculation is clear, we went through some detailed calculation where do not get distracted by the details, but you need to do this in order to practice calculations involving phase lock loop in the phase domain in the frequency domain and the time domain and so on. But, what is the summary, we have a lock range that is limited by the periodicity of the phase detector to move the $v c o$ from the pre-running frequency.

We have to apply a non-zero control voltage and to have a non-zero control voltage, there has to be some phase difference between the input and the feedback quantities, and that phase difference can only be a maximum of 2π in either direction, this is because of the periodicity of the phase detector. So, the lock range is limited to $2\pi \text{ time } k_p d$ times $K_v c o$.

On the other hand, the phase detector implementation that we had, has periodic errors and this periodic errors causes periodic fluctuations in the output phase even, when the input is perfectly periodic. So, this means that the output is not exactly periodic what we did was to analyze its spectrum in the frequency domain, and we see that in addition to the components at N times f_{ref} . We also have additional components at integer multiples of f_{ref} away from it.

This phenomenon is known as reference speed through because the references at f_{ref} components related to reference will appear at the output. And the spurious components are reference spurs, and to have a reference spur that is hundred time slower than the fundamental that we want, we find that the lock range is much much smaller than f_{ref} .

So, now, what does it mean for the lock range to be smaller than f_{ref} ; that means, that I cannot build a frequency synthesizer, what is a frequency synthesizer I changed the division module as an and I changed the output frequency in steps of f_{ref} . Now, with my lock range limited to less than f_{ref} , I will not be able to change the value of N at all. In fact, at best I will be able to build this phase lock loop for a particular value of N which makes N times f_{ref} f_{naught} , and that is about it, and this is clearly not a satisfactory situation, and we need to find a way around it, and what is the way around it, the key here is that the periodic error that is injected is proportional to $\Delta\phi$, this we have seen.

So, the periodic error injected will be proportional to $\Delta\phi$, and $\Delta\phi$, if it happens to be 0, there will be no periodic error at all. And now, this makes sense because, if the input and feedback pulses are aligned exactly the output of the phase detector will be continuously 0. It is supposed be 0 and there is no periodic error at all. In that case, there will be no periodic modulation of the $v_{c o}$. So, we will try to exploit this to come up with a better phase lock loop in which case, this tradeoff between the lock range and the reference speed through is broken in summary.

(Refer Slide Time: 45:06)

* Periodicity of phase detection limits the lock range to $2\pi \cdot K_{pd} \cdot K_{vco} \rightarrow$ Make $K_{pd} \cdot K_{vco}$ large

* Periodic errors in the phase detector limit the value of $K_{pd} \cdot K_{vco}$.

-40 dBc reference spur $\Rightarrow K_{pd} \cdot K_{vco} = 5 \cdot 10^{-3} f_{ref}$

\Rightarrow Lock range = $\pi \cdot 10^{-2} f_{ref} \ll f_{ref}$

Cannot change N at all!

So, to have minus 40 d b c this is a unit that is used to show that it is relative to the main component. This means that lock range, which is this basically means that you cannot change N at all. In fact, you may not be able to build the p l l for any value of N. Now, if the free running frequency of the v c o happens to be equal N f ref for some value of N you will be able to build it for that, but then you will not be able to change the N for that in the next lecture, we will see how to get around the state of by introducing some refinements of phase lock loop. Thank you.